

**BUILD A CHANCE/STRATEGY ELECTRONICS GAME**

14278

# Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

NOVEMBER 1976/\$1.25

**Build a  
"Westminster Chime"  
Digital Clock**

**Checking the Sun  
for Home  
Propagation  
Forecasts**



**How to Protect  
Power Supplies  
From Damage**

**The 35-mm  
Slide Syncer**

**AN AUDIO-VISUAL  
PROGRAMMER TO BUILD**

**TEST REPORTS:**

**Spectro-Acoustics**

**Stereo Equalizer**

**Pickering**

**Stereo Cartridge**

**Siltronix CB AM**

**Mobile Transceiver**

## A CB/Ham Selective Calling Project

- **CODED TONE ACTIVATES  
RECEIVER**
- **SILENT CHANNEL  
UNTIL WANTED**





**Experience is the best teacher.** You might settle for any CB first time around. Understandably. A lot of people think they're all pretty much alike. But you'll soon discover that, like everything else, there are exceptions.

**Ask the pros.** America's long distance truckers. These guys talk CB day in and day out. And they demand the best. That's why truckers refer to the Cobra 29 as "The Diesel Mobile."

**Listen to Cobra.** You'll hear a big difference. Because the Cobra 29 gives you features which assure crystal clear reception. Like switchable noise limiting and blanking, to cut out practically all pulse and ignition interference. Add squelch control and RF gain and you've got exceptional—adjustable—receiver clarity. Even in the heaviest CB traffic. You also get Delta Tuning which makes up for the other guy, because even off-frequency transmitters are pulled in. Perfectly.

**Talk to Cobra.** And you know you're punching through. One glance at the

29's over-sized illuminated meter tells you just how much power you're punching out and pulling in. For voice modulation the DynaMike delivers at 100%. Same way with power: The 29 transmits at maximum power levels.

**Sooner or later you'll get a Cobra.** And you'll get engineering and craftsmanship second to none. Performance that will make your first CB seem obsolete. Reliability and durability that have set standards for the industry. Above all, you'll get power. The power to punch through loud and clear like nothing else. Because when it comes to CB radio, nothing punches through loud and clear like a Cobra.



**Punches through loud and clear.**

Cobra Communications Products  
**DYNASCAN CORPORATION**  
6460 W. Cortland St., Chicago, Illinois 60635

# IF YOUR FIRST CB ISN'T A COBRA YOUR SECOND ONE WILL BE.





# If you thought a rugged, professional yet affordable computer didn't exist,


## think IMSAI 8080.

Sure there are other commercial, high-quality computers that can perform like the 8080. But their prices are 5 times as high. There is a rugged, reliable, industrial computer, with high commercial-type performance. The IMSAI 8080. Fully assembled, it's \$931. Unassembled, it's \$599. And ours is available now.

In our case, you can tell a computer by its cabinet. The IMSAI 8080 is made for commercial users. And it looks it. Inside and out! The cabinet is attractive, heavy-gauge aluminum. The heavy-duty lucite front panel has an extra 8 program controlled LED's. It plugs directly into the Mother Board without a wire harness. And rugged commercial grade paddle switches that are backed up by reliable debouncing circuits. But higher aesthetics on the outside is only the beginning. The guts of the IMSAI 8080 is where its true beauty lies.

The 8080 is optionally expandable to a substantial system with 22 card slots in a single printed circuit board. And the durable card cage is made of commercial-grade anodized aluminum.

The IMSAI 8080 power

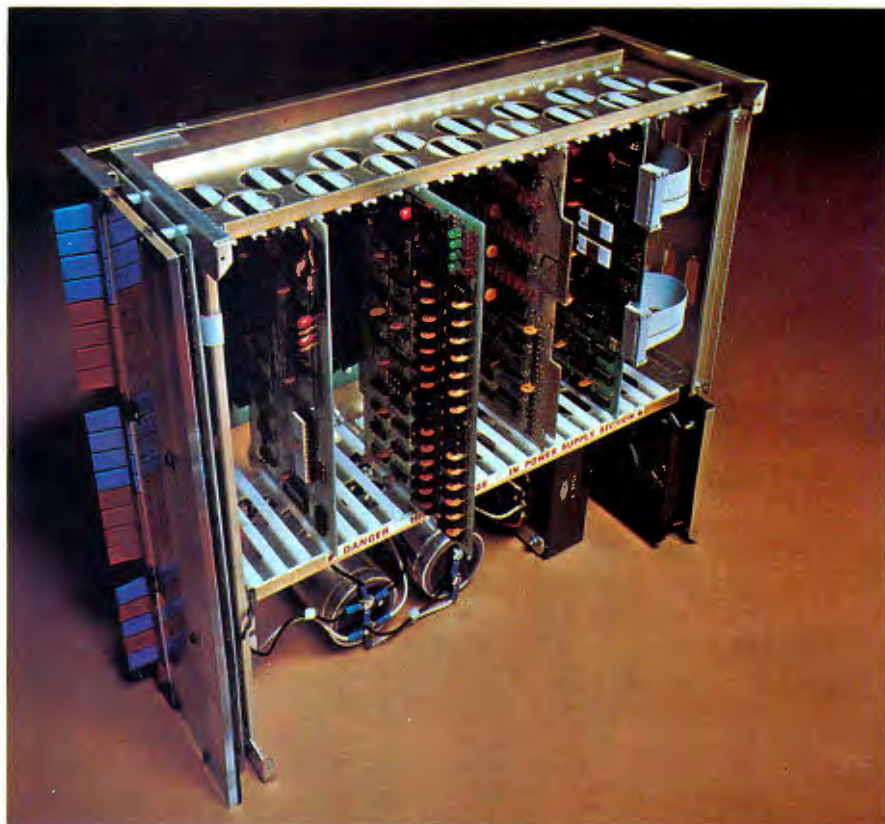

supply produces a true 28 amp current, enough to power a full system.

You can expand to a powerful system with 64K of memory, plus a floppy disk controller, with its own on-board 8080—and a DOS. A floppy disk drive, an audio tape cassette input device, a printer, plus a video terminal and a teleprinter. These peripherals will function with an 8-level priority interrupt system. IMSAI BASIC software is available in 4K, that you can get in PROM. And a new \$139 4K RAM board with software

memory protect. For the ultimate in flexibility, you can design the system for low-cost multiprocessor, shared memory capability.

Find out more about the computer you thought didn't exist. Get a complete illustrated brochure describing the IMSAI 8080, options, peripherals, software, prices and specifications. Send one dollar to cover handling.

Call us for the name of the IMSAI dealer nearest you.

Dealer inquiries invited.

## IMSAI

IMS Associates, Inc.  
14860 Wicks Boulevard  
San Leandro, CA 94577  
(415) 483-2093





# HIT THE ROAD WITH THE AUTOMATIC CB. JOHNSON.

You've got four hundred miles of dotted white line stretched out in front of you. And a couple of dozen tons riding in back.

That's why you keep the automatic CB sitting at your side. No hassle, no gadget controls, just the crisp, clean Johnson sound all day long. Automatically.

Johnson's exclusive voice tailored circuitry automatically drops off unwanted frequencies to give you clear



reception. Our automatic noise limiter keeps reception clean and built-in gain control prevents "blasting" and "fading."

Johnson's unique electronic speech compression automatically selects and compresses the clearest voice frequencies to produce

uniform, high-level modulation and maximum transmit range. All automatically.

When you hit the road, go with Johnson CB. We back every Johnson with a full year parts and labor warranty and walk-in service at more than 850 locations. See a Johnson CB dealer and take off on the great American adventure.



## JOHNSON

E. F. JOHNSON COMPANY, WASECA, MINN. 56093  
In Canada: A. C. Simmonds & Sons, Ltd.

**JOHNSON CB. THE GREAT AMERICAN ADVENTURE.**

CIRCLE NO. 33 ON FREE INFORMATION CARD



# Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

## FEATURE ARTICLES

PROPAGATION FORECASTS FOR RADIO COMMUNICATORS .....	Editorial Staff	34
<i>How to examine the sun and use other sources to determine sunspot activity.</i>		
PROTECTING YOUR POWER SUPPLY .....	Robert C. Arp, Jr.	56
<i>Semiconductor components need protection from shorts, overloads, etc.</i>		
PROFESSIONAL VS. CONSUMER TAPE .....	Larry Zide	66
<i>Would there be an advantage for the home recordist in using studio-type tape?</i>		
ENGLISH-LANGUAGE SHORTWAVE BROADCASTS FOR NOV. THRU FEB .....	Richard E. Wood	102

## CONSTRUCTION ARTICLES

A CB/HAM SELECTIVE CALLING PROJECT .....	Martin Meyer	41
<i>Coded tone activates receiver, with channel silent until wanted.</i>		
TIE INTO HAM REPEATERS WITH THIS LOW-COST AUTOPATCH .....	Joe Jarrett	47
<i>Crystal-controlled unit for initiating telephone calls.</i>		
DIGITAL ELECTRONIC "WESTMINSTER" CLOCK .....	Alan Roehl	57
<i>The famous Big Ben tune played on your own digital clock.</i>		
BUILD ODDS-ON—A GAME OF CHANCE AND STRATEGY .....	David L. Heiserman	64
BUILD THE 35-MM SLIDE SYNCER .....	Harry Lowenstein	74
<i>A low-cost programmer for audio-visual presentations.</i>		

## COLUMNS

STEREO SCENE .....	Ralph Hodges	22
<i>Mods and Modifiers.</i>		
HOBBY SCENE Q & A .....	John McVeigh	32
SOLID STATE .....	Lou Garner	89
<i>Rara Avis.</i>		
CB SCENE .....	Ray Newhall	94
<i>40-channel Expansion and Purac II.</i>		
DX LISTENING .....	Glenn Hauser	96
<i>Change in the Air.</i>		
COMPUTER BITS .....	Hal Chamberlin	106
<i>Mass-Storage Systems.</i>		
EXPERIMENTER'S CORNER .....	Forrest M. Mims	110
<i>The Silicon Solar Cell.</i>		

## PRODUCT TEST REPORTS

SPECTRO ACOUSTICS MODEL 210 GRAPHIC EQUALIZER .....	78
PICKERING MODEL XV-15/625E PHONO CARTRIDGE .....	79
SILTRONIX MOHAWK AM CB MOBILE TRANSCEIVER .....	84
SCHOBER THEATRE ORGAN .....	86

## DEPARTMENTS

EDITORIAL .....	Art Salsberg	4
<i>Majority Rules—The Bitter Pill.</i>		
LETTERS .....		6
NEW PRODUCTS .....		10
NEW LITERATURE .....		20
ADVERTISERS INDEX .....		133

POPULAR ELECTRONICS, November 1976, Volume 10, Number 5. Published monthly at One Park Avenue, New York, NY 10016. One year subscription rate for U.S., \$9.98; U.S. Possessions and Canada, \$12.98; all other countries, \$14.98 (cash orders only, payable in U.S. currency). Second Class postage paid at New York, NY and at additional mailing offices. Authorized as second class mail by the Post Office Department, Ottawa, Canada and for payment of postage in cash.

POPULAR ELECTRONICS including ELECTRONICS WORLD. Trade Mark Registered. Indexed in the Reader's Guide to Periodical Literature. COPYRIGHT © 1976 BY ZIFF-DAVIS PUBLISHING COMPANY. ALL RIGHTS RESERVED.

Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Modern Bride, Popular Photography, Skiing and Stereo Review.

Material in this publication may not be reproduced in any form without permission. Requests for permission should be directed to Jerry Schneider, Rights and Permissions, Ziff-Davis Publishing Co., One Park Ave., New York, NY 10016.

**Editorial correspondence:** POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. Editorial contributions must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of manuscripts, art work, or models.

**Forms 3579 and all subscription correspondence:** POPULAR ELECTRONICS, Circulation Dept., P.O. Box 2774, Boulder, CO 80323. Please allow at least eight weeks for change of address. Include your old address, enclosing, if possible, an address label from a recent issue.



**EDGAR W. HOPPER**  
Publisher

**ARTHUR P. SALSBERG**  
Editorial Director

**LESLIE SOLOMON**  
Technical Editor

**JOHN R. RIGGS**  
Managing Editor

**STEPHEN B. GRAY**  
Senior Editor

**ALEXANDER W. BURAWA**  
Feature Editor

**EDWARD I. BUXBAUM**  
Art Director

**JOHN McVEIGH**  
Associate Editor

**ANDRE DUZANT**  
Technical Illustrator

**PATRICIA GIRRIER-BROWN**  
Production Editor

Contributing Editors  
**HAL CHAMBERLAIN, LOU GARNER**  
**GLENN HAUSER, JULIAN HIRSCH**  
**RALPH HODGES, ART MARGOLIS**  
**FORREST MIMS, RAY NEWHALL**  
**SOL PRENSKY, WILFRED SCHERER**

**JOSEPH E. HALLORAN**  
Advertising Director

**JOHN J. CORTON**  
Advertising Sales

**LINDA BLUM**  
Advertising Service Manager

**PEGI McNEANEY**  
Executive Assistant

**STANLEY NEUFELD**  
Associate Publisher

**ZIFF-DAVIS PUBLISHING COMPANY**  
Popular Electronics  
Editorial and Executive Offices  
One Park Avenue New York, New York 10016  
212-725-3500

Hershel B. Sarbin, President  
Furman Hebb, Executive Vice President  
John R. Emery, Senior Vice President, Finance and  
Treasurer

Phillip T. Heffernan, Senior Vice President, Marketing  
Edward D. Muhlfeld, Senior Vice President, Sports Division  
Philip Sine, Senior Vice President

Frank Pomerantz, Vice President, Creative Services

Arthur W. Butzow, Vice President, Production

Lawrence Sporn, Vice President, Circulation

George Morrissey, Vice President

Sydney H. Rogers, Vice President

Sidney Holtz, Vice President

Al Traina, Vice President

Phillip Korsant, Vice President

Paul H. Chook, Vice President, Market Planning

Charles B. Seton, Secretary

Edgar W. Hopper, Vice President, Electronics Div.

William Ziff, Chairman

W. Bradford Briggs, Vice Chairman

Midwestern Office

The Patis Group, 4761 West Touhy Ave.,  
Lincolnwood, Illinois 60464, 312 679-1100  
GERALD E. WOLFE, THOMAS HOCKNEY

Western Office

9025 Wilshire Boulevard, Beverly Hills, CA 90211

213 273-8050; BRadshaw 2-1161

Western Advertising Manager, **BUD DEAN**

Japan: James Yagi

Oji Palace Aoyama; 6-25, Minami Aoyama  
6 Chome, Minato-Ku, Tokyo 407-1930/6821,  
582-2851



Member Audit Bureau  
of Circulations



The publisher has no knowledge of any proprietary rights which will be violated by the making or using of any items disclosed in this issue.



## Editorial

### MAJORITY RULES—THE BITTER PILL

The attitudes of hams toward CB'ers have been changing. Many radio amateurs, for example, have also become CB'ers, recognizing the value of a two-way radio communication system that can be widely used on all highways throughout the country at most any hour. Conversely, there are CB'ers who, "tasting" two-way radio, have become radio amateurs in order to enjoy the benefits of long-distance communications, video transmissions, etc., as well as the technical camaraderie that exists in hamdom.

However, there exists a hard-core minority of hams who begrudge the easy manner in which citizens can get on the air. This attitude was underlined by letters I received from some hams in response to the favorable viewpoint expressed by our CB columnist toward "Class E" CB allocations. In an effort to defend retention of a small slice of the radio spectrum for hams—and I do not denigrate this view—virtually all the writers focused on one point: The use of the radio spectrum is a privilege that must be earned!

Well, these radio amateurs are spitting into the wind. According to this philosophy, taxicab drivers shouldn't be using two-way radios. Neither should boating enthusiasts. Obviously, personal communications via radio without requiring any technical know-how or passing of an examination is here to stay. So these hams shouldn't rest on this argument. There are certainly enough more cogent reasons that can be used in defense of retaining the present 220-MHz spectrum allocation.

It's doubtful, though, if these arguments will be sufficient to withstand the assaults of a majority group, judging by the way high-quality TV fare is excised owing to relatively low viewer numbers. In any event, this judgement is in the hands of the FCC, which must also consider many other factors.

Hams are an elitist group by any definition. And like elitist groups everywhere, don't look kindly upon "out groups" that infringe on their territory. By maintaining high standards, however, their potential numbers—and "political" punch—are limited. Even today, most hams would prefer to maintain a Morse Code test, based on a 1975 ARRL study among its 100,000 members.

Moreover, proselytizing efforts over the years have been pathetically meager. This extends to top management of amateur radio equipment companies. As evidence, we get very little in the way of press releases on new equipment from these companies. Unlike CB manufacturers, they seem to be content to feed upon themselves by reaching people who are already hams. And that's why the great ham-gear names such as Hallicrafters and Hammarlund, among others, have gone the way of the famous great Auk.

There are some faint signs of regeneration for amateur radio in the matter of expanding their numbers. The American Radio Relay League was represented by an exhibit booth at last year's "Personal Communications" CB show, hoping to pick up some CB'ers. And the ARRL's new "Tune in the World with Ham Radio," with a workbook, cassette tape and call-area wall map for \$7.00, is a nice package for beginners.

My 12-year-old, in fact, is using the above in his quest for a Novice license. I'd like him to become a ham because it is an accomplishment he can be proud of; and it can open the door to a life-long, fruitful hobby. In view of these opportunities for personal growth, I, for one, would look upon the weakening of amateur radio as a tremendous loss. We must make sure there is always room for the good things in life and not subjugate minority groups to the point of extinction.

*Art Salsberg*

POPULAR ELECTRONICS



# Laser Beam Digital Watch

*Never press another button, day or night, with America's first digital watch that glows in the dark.*



*Announcing Sensor's new Laser 220—the first really new innovation in digital watch technology.*



*Would you do this with your solid-state watch? Of course not. Most solid-state watches require care and pampering but not the Sensor. You can dunk it, drop it and abuse it without fear during its unprecedented five-year parts and labor warranty.*

It's ingenious, it's simple and it makes every other digital watch obsolete. Scientists have perfected a digital watch with a self-contained automatic light source—a major scientific breakthrough.

## SELF-CONTAINED LIGHT SOURCE

The Laser 220 uses laser beams and advanced display technology in its manufacture. A glass ampoule charged with tritium and phosphor is hermetically sealed by a laser beam. The ampoule is then placed behind the new Sensor CDR (crystal diffusion reflection) display.

The high-contrast CDR display shows the time constantly—in sunlight or normal room light. But, when the room lights dim, the self-contained tritium light source automatically compensates for the absence of light, glows brightly, and illuminates the display.

No matter when you wear your watch—day or night—just a glance will give you the correct time. There's no button to press, no special viewing angle required, and most important, you don't need two hands to read the time.



*Replace the battery yourself by just opening the battery compartment with a penny. Free batteries are provided whenever you need them during the five-year warranty.*

## A WORRY-FREE WATCH

Solid-state watches pose their own problems. They're fragile, they must be pampered, and they require frequent service. Not the Laser 220. Here are just five common solid-state watch problems you can forget about with this advanced space-age timepiece:

**1. Forget about batteries** The Laser 220 is powered by a single EverReady battery that will actually last years without replacement—even if you keep the 220 in complete darkness. In fact, JS&A will supply you with the batteries you need, free of charge, during the next five years. To change the battery, you simply unscrew the battery compartment at the back with a penny and replace the battery yourself.

**2. Forget about water** Take a shower or go swimming. The Laser 220 is so water-resistant that it withstands depths of up to 100 feet.

**3. Forget about shocks** A three-foot drop onto a solid hardwood floor or a sudden jar. Sensor's solid case construction, dual-strata crystal, and cushioned quartz timing circuit make it one of the most rugged solid-state quartz watches ever produced.

**4. Forget about service** The Laser 220 has an unprecedented five-year parts and labor

warranty. Each watch goes through weeks of aging, testing and quality control before assembly and final inspection. Service should never be required. Even the laser-sealed light source should last more than 25 years with normal use. But if it should require service anytime during the five year warranty period, we will pick up your Sensor, at your door, and send you a loaner watch while yours is repaired—all at our expense.

**5. Forget about changing technology** The Sensor Laser 220 is so far ahead of every other watch in durability and technology that the watch you buy today, will still be years ahead of all others.

## THE ULTIMATE ACHIEVEMENT

Other manufacturers have devised unique ways to produce a watch you can read at a glance. The new \$300 LED Pulsar requires a snap of the wrist to turn on the display, but the Pulsar cannot be read in sunlight. The new \$400 Longine's Gemini combines both an LED and liquid crystal display. (Press a button at night for the LED display, and view it easily in sunlight with the liquid crystal display.) But you must still press a button to read the time. All these applications of existing technology still fail to produce the ultimate digital watch: one you can read under all light conditions without using two hands. Until the introduction of the Sensor.

## PLENTY OF ADVANCED FUNCTIONS

Sensor's five time functions give you everything you really need in a solid-state watch. Your watch displays the hours and minutes constantly, with no button to press. But depress the function button and the month and the date appear. Depress the button again and the seconds appear. To quickly set the time, insert a ball-point pen into the recessed time-control switch on the side. It's just that easy.

Sensor's accuracy is unparalleled. All solid-state digitals use a quartz crystal. So does the Sensor. But crystals change frequency from aging and shock. And to reset them, the watch case must be opened and an airtight seal broken which may affect the performance. In the Sensor, the crystal is first aged before it is installed, and secondly, it is actually cushioned in the case to absorb tremendous shock. The quartz crystal can also be adjusted through the battery compartment.



*The new exclusive laser-sealed tritium and phosphor light source is a thin solid-state tube that automatically illuminates the display when the lights dim.*

ment without opening the case. In short, your watch should be accurate to within 5 seconds per month and maintain that accuracy for years without adjustment and without ever opening the watch case.

## STANDING BEHIND A PRODUCT

JS&A is America's largest single source of digital watches and other space-age products. We have selected the Sensor Laser 220 as the most advanced American-made, solid-state timepiece ever produced. And we put our company and its full resources behind that selection. JS&A will warranty the Sensor (even the batteries) for five full years. We'll even send you a loaner watch to use while your watch is being repaired should it ever require repair. And Sensor's advanced technology guarantees that your digital watch will be years ahead of any other watch at any price.

Wear the Laser 220 for one full month. If you are not convinced that it is the most rugged, precise, dependable and the finest quality solid-state digital watch in the world, return it for a prompt and courteous refund. We're just that proud of it.

To order your Sensor, credit card buyers may simply call our toll-free number below or mail us a check in the amount indicated below plus \$2.50 for postage, insurance and handling. (Illinois residents add 5% sales tax.) We urge you, however, to act promptly and reserve your Laser 220 today.

Stainless steel w/leather strap . . . . . \$129.95  
(Add \$10 for matching metal band)

Gold tone w/leather strap . . . . . \$149.95  
(Add \$10 for matching metal band)

**JS&A** NATIONAL  
SALES  
GROUP

Dept. PE JS&A Plaza  
Northbrook, Illinois 60062  
CALL TOLL-FREE . . 800 323-6400  
In Illinois call . . . (312) 498-6900  
© JS&A Group, Inc., 1976



The Best  
Way To Show  
You What  
You'll Get  
Out Of An  
Empire  
Phono  
Cartridge  
Is To  
Show You  
What Goes  
Into One.

At Empire we make a complete line of phono cartridges. Each one has slightly different performance characteristics which allow you to choose the cartridge most compatible to your turntable.

There are, however, certain advantages, provided by Empire's unique design, that apply to all our cartridges.

One is less wear on your records. Unlike other magnetic cartridges, Empire's moving iron design allows the diamond stylus to float free of its magnets and coils, imposing much less weight on your record's surface and insuring longer record life.

Another advantage is the better channel separation you get with Empire cartridges. We use a small, hollow iron armature which allows for a tighter fit in its positioning among the poles. So, even the most minute movement is accurately reproduced to give you the space and depth of the original recording.

Finally, Empire uses 4 coils, 4 poles, and 3 magnets (more than any other cartridge) for better balance and hum rejection.

The end result is great listening. Audition one for yourself or write for our free brochure, "How To Get The Most Out Of Your Records". After you compare our performance specifications we think you'll agree that, for the money, you can't do better than Empire.

Empire Scientific Corp.  
Garden City, New York 11530

**EMPIRE**

Already your system  
sounds better.

# Letters

## WHERE CREDIT IS DUE

In "Buyer's Guide to Antenna Rotators" (August 1976), the interesting photograph that illustrates the corrosive effect on antenna rotators should have been credited to Channel Master.—*Daniel S. Roher, New York, NY*

## ANOTHER TIM VIEW

I enjoyed reading Ralph Hodges' comments on the never-ending tubes-versus-transistors debate in the July "Stereo Scene." His sober observations were very refreshing. However, I must disagree with his comments regarding transient intermodulation distortion (TIM); an amplifier's ability to "keep up with the music signal" is adequately specified by its frequency response (for small signals) and its slew rate (for large signals). The technical papers written so far on TIM consist of little more than a rediscovery of slew-rate limiting and the consequences of this form of overloading. Many U.S. designers of high-quality amplifiers have routinely provided more than adequate slew rates in their products, which may explain why there is a lack of excitement over TIM here.

The argument that an amplifier is without feedback for a "moment" following the application of a signal is dubious. This "moment" is roughly equal to the excess phase delay (not to be confused with the open-loop time constant), which is generally 150 ns. An audio input signal limited to a 20,000-Hz bandwidth cannot rise fast enough in this time to overload an input stage. Finally, the amount of feedback used, when properly compensated, has little to do with susceptibility to TIM if adequate slew rate is maintained.—*Robert R. Cordell, Tinton Falls, NJ*

## MIXING APPLES AND ORANGES

I built the "Improved Gas and Fume Detector" described in the August issue and am happy to state that it not only detects carbon monoxide and carbohydrates, but that it also detects the fats and proteins that my car produces. Seriously, though, I believe that the sentence on page 47 should read: "The major problem with . . . carbon monoxide and hydrocarbons." The last word should not be "carbohydrates" as in the article.—*Michael J. Di Julio, WB2BWJ, Maplewood, NJ*

The author meant to imply the equivalent of "apples and oranges" to indicate dissimilarity.

## A ROUND OF CHEERS

Three cheers for "DX Programs and DX Clubs on Shortwave" in the August issue. I hope you will continue to cover the SWL/DX field in the future.—*Paul E. Kotke, St. Paul, MN*

## FIREFIGHTER SPEAKS OUT

I enjoyed reading the informative article "Lightning and the Radio Amateur" ("Amateur Radio," August 1976) but the last sentence of the second paragraph was in poor taste and a disservice to firefighters. What many people do not realize is that there are times when walls and wiring must be cut open to check for the extension of fire. If we did not do this where indicated, chances are that a "hidden" fire would burn a home or shack down after we left.—*N. Nicastro, Jr., KMD1175, WDX2HHS, KNJ2AQ, Spotswood, NJ*

The author meant no disservice to the dedicated force of firefighters. All he was pointing out was that it's better to protect against the possibility of lightning-induced fire than to suffer the damage that can result without taking the proper precautions.

## PICO NOT MICRO

There are two errors in "Learning Electronic Theory With Hand Calculators, Part Two." In the center of page 64, the second sentence in the paragraph that begins: "Finally, in a series RC circuit . . ." the X, in the next sentence should be changed to Z. The second error was in converting the displayed quantity 2.780659563 - 11 to conventional capacitance notation; the correct answer should be 27.8 pF—not 0.0278  $\mu$ F.—*Ken Gentile, West Palm Beach, FL*

## TUNING IN PHYSICIANS RADIO

In the May 1976 "Letters" column, you turned aside an inquiry about the Physicians Radio Network, stating that it was confidential and available only to physicians. In New York, dedicated hypochondriacs can receive the net on the SCA subcarrier of WEVD-FM. But believe me, for non-pro's it wins the Emmy for the "World's Dullest Program."—*Edward M. Roberts, Glen Head, NY*

In my area at least, PRN is broadcast as a standard SCA subcarrier on WIOQ (102.1 MHz). An SCA subcarrier can hardly be called "confidential."—*L.S. Huntsinger, Audubon, NJ*

## PROGRAMMABLE CALCULATORS

I was pleased with the article "Here Are  
POPULAR ELECTRONICS



# SAVE UP TO 50% ON PARTS.

Hobbyist or professional, there are probably a lot of circuits you build just for the fun of it. And a lot you'd like to build, but never get around to.

One reason is the cost of parts. Parts you buy for one project, but can't re-use... because you haven't time to take them carefully apart. Or because of heat and mechanical damage that occur when you do.

Now, there's an easier way that can save you big money on parts *and hours on every project*, as well: *Proto-Board® Solderless Breadboards*.

Now, assembling, testing and modifying circuits is as easy as pushing in—or pulling out—a lead. IC's, LED's, transistors, resistors, capacitors... virtually every kind of component... connect and inter-connect instantly via long-life, nickel-silver contacts. No special patch

MODEL	NO. OF TIE-POINTS	14-PIN DIP CAPACITY	SUGG LIST *	OTHER FEATURES
PB-6	630	6	\$15.95	Kit — 10-minute assembly
PB-100	760	10	19.95	Kit — with larger capacity
PB-101	940	10	29.95	8 distribution buses, higher capacity
PB-102	1240	12	39.95	Large capacity, moderate price
PB-103	2250	24	59.95	Even larger capacity, only 2.7¢ per tie-point
PB-104	3060	32	79.95	Largest capacity, lowest price per tie-point
PB-203	2250	24	75.00	Built-in 1% regulated 5V, 1A low ripple power supply
PB-203A	2250	24	120.00	As above plus separate 7-amp +15V and -15V internally adjustable regulated outputs


\*Manufacturer's suggested list  
Prices and specifications subject to change without notice

cords or jumpers needed—just lengths of ordinary #22-30 AWG solid hookup wire.

Circuits go together as quickly as you can think them up. And parts are re-usable, so as your "junk box" builds, you build more and more projects for less and less money.

Before you invest in your next project, invest in a CSC breadboard. See your dealer or order by phone: 203-624-3103 (East Coast) or 415-421-8872 (West Coast)—major charge cards accepted. You've got nothing to lose... and a lot to gain.

CONTINENTAL SPECIALTIES CORPORATION

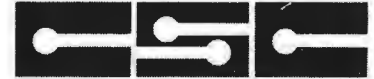

44 Kendall Street.  
Box 1942 • New Haven, CT 06509  
203-624-3103 TWX 710-465-1227  
West Coast office Box 7809, San Francisco, CA  
94119 • 415-421-8872 TWX 910-372-7992

© 1976, Continental Specialties Corporation





the New Programmable Calculators" in the May 1976 issue of POPULAR ELECTRONICS. It is the first article that I have seen in any major consumer magazine dedicated to programmables.—Philip Earnhardt, Burlington, NC

## FREE SCHEMATIC WOES

POPULAR ELECTRONICS has left it entirely up to project kit suppliers to provide free schematics and pc etching and drilling guides [when they're too large for magazine pages]. But the May 1976 Editorial states that it is not unreasonable for a supplier to drop the free patterns after a period of time. (The period mentioned was something over a year.) I agree with him.

However, this means that your major construction articles have a built-in "destruct" feature.—Andrew Oldroyd, Norman, OK

Our new policy for future articles is to supply directly any artwork that is too large to appear in the magazine. We will keep such artwork on file for a number of years, thus obviating the problem of project obsolescence.

## "MUSIC MODULE" PARTS SOURCES

The Top Octave Generator integrated circuit, IC4, called for in the "Music Modules" (June 1976) is a Mostek device that is also available from AMI. Suitable sources

for crystals include Crystek, International Crystal, and CTS Knight. The optional Molex connectors are available from Tracy Design Corp. and Force Electronics; alternatively, any standard 0.153" edge connector can be substituted.—Don Lancaster, Author

## GIANT STEP FOR UN-GENIUSES

At last! An article on 7400 series TTL IC's that explains the basic logic, with experimenter circuits. We, the un-geniuses of the IC world, took a giant step, thanks to the June 1976 "Experimenter's Corner." We would like to learn more and be shown more experiments with TTL devices.—F. Arthur Byington, Birmingham, MI

## EUROPEAN TV QUALITY

The July 1976 Editorial titled "Who Killed TV Picture Quality?" struck me as being rather incomplete in that it made no mention of the SECAM (Sequential Couleur a Memoire) TV system used in some 20 countries nor of PAL (Phase Alternation Line) used in 22 other countries, including all of Australia. As of the end of 1974, there were 162-million NTSC, 74-million SECAM, and 70-million PAL TV receivers in use worldwide. Surely, the higher color stability of SECAM and PAL should have been mentioned.

Because of its superior color rendition and stability, SECAM 60 equipment was carried by Pioneer X for its color-TV pictures of Jupiter.—J.M. Lagerwerff, Palo Alto, CA

Having been involved with color TV in England, I endorse your Editorial comments about the very poor quality here in the U.S. Principally, the English system uses PAL transmission, which eliminates the "Purple Plague." Drift is cancelled by integration of adjacent lines by the eye. Thus, flesh tones are always correct and no need exists to distort the receiver's characteristics, which permits pure deep saturated tones to be displayed. In addition, the quality of electron optics seems to be much better. British engineers demand pin-sharp convergence, even at the corners of the screen.

I have the Independent Broadcast Authority Technical Reference Book that gives Codes of Practice for TV studio and broadcasting standards for Commercial (note that this is not BBC) television in the U.K. The standards call for very elaborate and complete specifications for every parameter of audio and video performance and include very detailed rules for assessing and reporting transmission quality. I doubt such standards exist in the U.S.

It has been my impression that a well-adjusted receiver in the U.K. gives a picture as good as a Technicolor movie. I think most Americans are completely unaware that their TV quality is lousy because nobody has exposed them to what can be done.—R.J. Best, Miami, FL

## Checklist of Books for the Libraries of Technicians, Hobbyists & Students

BRAND NEW BOOKS—JUST PUBLISHED!	
<input type="checkbox"/> Transistor Ignition Systems 252 p., 162 il.	\$5.95
<input type="checkbox"/> How to Repair Home Kitchen Appliances 294 p., 205 il.	\$5.95
<input type="checkbox"/> Fun With Electronics 140 p., 88 il.	\$3.95
<input type="checkbox"/> How to Hear & Speak CB in a Short-Short 172 p., 85 il.	\$3.50
<input type="checkbox"/> The Complete Handbook of Model Railroad 350 p., 238 il.	\$6.95
<input type="checkbox"/> Talk-Back TV: Two-Way Cable Television 238 p., 64 il.	\$5.95
<input type="checkbox"/> Understand Use Modern Sig. Generators 294 p., 145 il.	\$6.95
<input type="checkbox"/> Numbers: Shortcuts & Pastimes 336 p., 80 il.	\$6.95
<input type="checkbox"/> 106 Easy Electr. Projs.: Beyond Transistors 224 p., 136 il.	\$5.95
<input type="checkbox"/> Using Modern Elect. Servicing Test Eqp't 252 p., 177 il.	\$5.95
<input type="checkbox"/> Mathematics Unraveled—Building Block Approach 280 p.	\$6.95
<input type="checkbox"/> Master Tube Substitution Handbook 322 p.	\$4.95
<input type="checkbox"/> Modern Guide to Digital Logic 294 p., 222 il.	\$6.95
<input type="checkbox"/> VHF/UHF Fire, Police, Ham Scanners 250 p., 114 il.	\$6.95
<input type="checkbox"/> OP AMP Circuit Design & Applications 280 p., 239 il.	\$6.95
<input type="checkbox"/> Master Handbook of Digital Logic Applications 392 p., 287 il.	\$7.95
<input type="checkbox"/> CET License Handbook 2nd ed. 448 p., 381 il.	\$8.95
<input type="checkbox"/> The Electronic Musical Instrument Manual 210 p., 385 il.	\$6.95
<input type="checkbox"/> Microprocessor Microprogramming Handbook 294 p., 176 il.	\$6.95
<input type="checkbox"/> Sourcebook of Electronic Organ Circuits 168 p., 101 il.	\$5.95
<input type="checkbox"/> Build Your Own Working Radio 238 p., 83 il.	\$5.95
<input type="checkbox"/> CBer's Handbook of Simple Hobby Projects 168 p., 114 il.	\$3.95
<input type="checkbox"/> Fire & Theft Security Systems 2nd ed. 192 p., 114 il.	\$5.95
<input type="checkbox"/> How to Repair Home Laundry Appliances 280 p., 137 il.	\$5.95
<input type="checkbox"/> Piloting Navigation With the Pocket Calculator 392 p., 233 il.	\$8.95
DO-IT-YOURSELF, AUTOMOTIVE & APPLIANCES	
<input type="checkbox"/> Homeowner's Guide to Saving Energy 196 p., 183 il.	\$5.95
<input type="checkbox"/> Customizing Your Van 192 p., 150 il.	\$3.95
<input type="checkbox"/> The Woodworker's Bible 434 p., 1151 il.	\$5.95
<input type="checkbox"/> Motorcycle Repair Handbook 392 p., 260 il.	\$6.95
<input type="checkbox"/> The Complete Handbook of Locks & Locksmithing 392 p.	\$6.95
<input type="checkbox"/> All About Swimming Pools 182 p., 127 il.	\$3.95
<input type="checkbox"/> Step-By-Step Guide: Carburetor Tuneup Overhaul 224 p.	\$4.95
<input type="checkbox"/> Homeowner's Guide To Solar Heating & Cooling 196 p.	\$4.95
<input type="checkbox"/> Do-It-Yourself's Guide: Home Planning Constr. 238 p.	\$4.95
<input type="checkbox"/> Step-By-Step Guide to Brake Servicing 238 p., 248 il.	\$4.95
<input type="checkbox"/> Step-By-Step Guide: Chrysler Eng. Maint. Rpr 256 p., 195 il.	\$5.95
<input type="checkbox"/> Subcontract Your House: Bldg Remodeling 196 p., 63 il.	\$4.95
<input type="checkbox"/> Auto Electronics Simplified 256 p., 202 il.	\$5.95
<input type="checkbox"/> The Complete Auto Electric Handbook 210 p., 139 il.	\$5.95
<input type="checkbox"/> Concrete & Masonry 392 p., 213 il.	\$5.95
<input type="checkbox"/> Home Appliance Clinic: Controls, Timers, Wiring Rpr 195 p.	\$4.95
<input type="checkbox"/> Practical Home Constr. Carpentry Hdbk 448 p., 180 il.	\$5.95
<input type="checkbox"/> How to Repair Diesel Engines 308 p., 237 il.	\$5.95
<input type="checkbox"/> Central Heating & Air Cond. Repair Guide 320 p., 285 il.	\$6.95
<input type="checkbox"/> Small Appliance Repair Guide—Vol. 2 210 p., 119 il.	\$4.95
<input type="checkbox"/> Electrical Wiring Lighting For Home Office 204 p., 155 il.	\$4.95
<input type="checkbox"/> How to Repair Small Gasoline Engines 288 p., 124 il.	\$5.95
<input type="checkbox"/> How to Repair Home Auto Air Cond. 208 p., over 100 il.	\$4.95
ELECTRONICS TECHNOLOGY/COMPUTERS/CALCULATORS	
<input type="checkbox"/> Modern Electronics Math 686 p., 424 il.	\$9.95
<input type="checkbox"/> Master Hdbk of 1001 Prac. Electronic Circ. 602 p., 1250 il.	\$9.95
<input type="checkbox"/> Impedance 196 p., 90 il.	\$5.95
<input type="checkbox"/> Intro to Medical Electronics—2nd ed. 320 p., 126 il.	\$7.95
<input type="checkbox"/> Computer Programming Handbook 518 p., 114 il.	\$8.95
<input type="checkbox"/> Computer Technician's Handbook 480 p., over 400 il.	\$8.95
<input type="checkbox"/> Microelectronics 266 p., 228 il.	\$5.95
<input type="checkbox"/> Basic Digital Electronics 210 p., 117 il.	\$4.95
<input type="checkbox"/> Switching Regulators & Power Supplies 252 p., 128 il.	\$6.95
<input type="checkbox"/> Advanced Applications for Pocket Calculators 304 p., 275 il.	\$5.95
<input type="checkbox"/> Tower's International Transistor Selector 140 p., 17 il.	\$4.95
<input type="checkbox"/> Electronic Conversions, Symbols & Formulas 224 p., 252 il.	\$4.95
<input type="checkbox"/> Effective Troubleshooting With EVM & Scope 238 p., 185 il.	\$5.95
<input type="checkbox"/> Getting the Most Out of Electronic Calculators 204 p., 28 il.	\$4.95
<input type="checkbox"/> Aviation Electronics Handbook 406 p., 227 il.	\$8.95
<input type="checkbox"/> How to Test Almost Everything Electronic 160 p., 144 il.	\$2.95
<input type="checkbox"/> Digital Logic Electronics Handbook 308 p., 226 il.	\$6.95
<input type="checkbox"/> Modern Applications of Linear IC's 276 p., 301 il.	\$9.95
<input type="checkbox"/> 10-Minute Test Techniques For PC Servicing 216 p., 114 il.	\$4.95
<input type="checkbox"/> Electr. Unraveled—New Commonsense Approach 228 p.	\$4.95
<input type="checkbox"/> How To Shoot Repair Electronic Test Eqp't 252 p., 143 il.	\$6.95
<input type="checkbox"/> Understanding & Using the Oscilloscope 272 p., 170 il.	\$5.95
<input type="checkbox"/> Industrial Electronics: Principles & Practice 416 p., 380 il.	\$8.95
<input type="checkbox"/> Dictionary of Electronics 420 p., 487 il.	\$4.95
RADIO & TV SERVICING	
<input type="checkbox"/> Color TV Trouble Facts—Problems Solutions 3rd ed. 434 p.	\$5.95
<input type="checkbox"/> Solid-State Color TV Photo Symptom Guide 224 p., 169 il.	\$5.95
<input type="checkbox"/> Beginner's Guide to TV Repair 176 p., 50 il.	\$4.95
<input type="checkbox"/> Troubleshooting With the Qual-Trace Scope 224 p., 252 il.	\$5.95
<input type="checkbox"/> TV Troubleshooting's Handbook—3rd ed. 448 p., over 300 il.	\$4.95
<input type="checkbox"/> Color TV Case Histories Illustrated 238 p., 219 il.	\$5.95
<input type="checkbox"/> TV Schematics: Read Between the Lines 252 p., 188 il.	\$5.95
<input type="checkbox"/> Logical Color TV Troubleshooting 240 p., 151 il.	\$5.95
<input type="checkbox"/> TV Bench Servicing Techniques 228 p., 177 il.	\$4.95
<input type="checkbox"/> Modern Radio Repair Techniques 260 p., 36 il.	\$4.95
<input type="checkbox"/> How to Interpret TV Waveforms 256 p., 250 il.	\$4.95
<input type="checkbox"/> Kwik-Fix TV Service Manual 384 p., 100's il.	\$5.95
<input type="checkbox"/> All-In-One TV Alignment Handbook 304 p., 145 il.	\$5.95
<input type="checkbox"/> TV Tuner Schematic/Servicing Manual 224 p., 287 il.	\$6.95
<input type="checkbox"/> 199 Color TV Troubles & Solutions 224 p., 178 il.	\$4.95
<input type="checkbox"/> How to Use Color TV Test Instruments 256 p., 230 il.	\$5.95

<input type="checkbox"/> Home-Call TV Repair Guide 144 p., 20 il.	\$3.95
<input type="checkbox"/> Pinpoint TV Troubles in 10 Minutes 327 p., 394 il.	\$5.95

CB, COMMUNICATIONS & HAM RADIO	
CB Schematic Servicing Manuals, each 200 p. \$5.95 Vol 1 Kris Browning, Hy-gain J.C. Penney, (Pinto) Vol 2 Teaberry, Unimetrics, Pearce-Simpson, Siltronix Vol 3 E.F. Johnson (Messenger), SBE-Linear, Sonar, Royce Vol 4 Pace Fanon Courier Dynascan (Cobra)	
2nd Class FCC Encyclopedia 602 p. 445 il.	\$7.95
The Complete Shortwave Listener's Hdbk 288 p., 101 il.	\$6.95
CB Radio Operator's Guide—2nd ed. 256 p., 139 il.	\$5.95
Pictorial Guide to CB Radio Install Repair 256 p., 304 il.	\$5.95
Practical CB Radio Troubleshooting & Repair 238 p., 108 il.	\$5.95
The Complete FM 2-Way Radio Handbook 294 p., 111 il.	\$6.95
Amateur FM Conversion & Construction Projs 256 p., 187 il.	\$5.95
Broadcast Annc'r 3rd Class FCC Study Guide 168 p., 19 il.	\$3.95
How To Be A Ham—Including Latest FCC Rules 192 p., 25 il.	\$3.95
Commercial FCC License Handbook 444 p., 150 il.	\$5.95
The 2-Meter FM Repeater Circuits Handbook 312 p. 194 il.	\$6.95
RTTY Handbook 320 p., 230 il.	\$6.95
Citizens Band Radio Service Manual 228 p., 84 il.	\$5.95
AMATEUR RADIO STUDY GUIDES <input type="checkbox"/> Novice \$5.95 <input type="checkbox"/> General \$7.95	
<input type="checkbox"/> Advanced \$5.95 <input type="checkbox"/> Extra \$6.95 <input type="checkbox"/> Incentive \$4.95	

HOBBY ELECTRONICS	
How to Read Electronic Circuit Diagrams 192 p., 140 il.	\$4.95
21 Simple Transistor Radios You Can Build 140 p., 122 il.	\$3.95
Basic Electricity & Beginning Electronics 252 p., 191 il.	\$5.95
Radio Control for Models 350 p., 417 il.	\$6.95
MOSFET Circuits Guidebook 196 p., 104 il.	\$4.95
Practical Circuit Design for the Experimenter 196 p. 119 il.	\$4.95
111 Digital & Linear IC Projects 210 p. 275 il.	\$5.95
Radio Astronomy for the Amateur 252 p., 96 il.	\$5.95
Build-It Book of Mini Test Measurement Instr. 238 p., 151 il.	\$4.95
RF & Optical Test Equipment You Can Build 252 p., 217 il.	\$5.95
Miniature Projects For Electronic Hobbyists 168 p., 77 il.	\$3.95
Practical Triac-SCR Projects For The Exp. 192 p., 146 il.	\$4.95
RC Modeler's Handbook of Gliders & Sailplanes 196 p. 90 il.	\$4.95
Integrated Circuits Guidebook 196 p., 119 il.	\$5.95
Solid-State Circuits Guidebook 252 p., 227 il.	\$5.95
Model Sail Power Boats by Remote Control 192 p., 125 il.	\$4.95
Electronics For Shutterbugs 204 p., 109 il.	\$5.95
Practical Test Instruments You Can Build 204 p., 157 il.	\$4.95
How to Build Solid-State Audio Circuits 320 p., 190 il.	\$5.95
Radio-Electronics Hobby Projects 192 p., 214 il.	\$4.95
Handbook of IC Circuit Projects 224 p., 136 il.	\$4.95
Solid-State Projects for the Experimenter 224 p., 228 il.	\$4.95
Electronic Experimenter's Guidebook 182 p., 86 il.	\$4.95
125 One-Transistor Projects 192 p., 125 il.	\$4.95
104 Easy Projects for Electronic Designers 160 p., 105 il.	\$3.95
164 Hobby Projects for Home & Car 192 p., 159 il.	\$4.95

AUDIO, Hi-Fi & ELECTRONIC MUSIC	
Electronic Music Circuit Guidebook 224 p., 180 il.	\$6.95
Questions & Answers About Tape Recording 264 p., 102 il.	\$5.95
Handbook of Multichannel Recording 322 p., 196 il.	\$7.95
Auto Stereo Service & Installation 252 p., 245 il.	\$5.95
Servicing Cassette & Cartridge Tape Players 294 p., 196 il.	\$6.95
Electronic Music Production 156 p., 79 il.	\$3.95
Experimenting With Electronic Music 180 p., 103 il.	\$4.95
Cassette Tape Recorders, How Work Care Repair 204 p.	\$4.95
Acoustic Techniques for Home & Studio 224 p., 168 il.	\$5.95
Pictorial Guide to Tape Recorder Repairs 256 p., 320 il.	\$4.95
How to Repair Musical Instrument Amplifiers 288 p., 50 il.	\$5.95
Japanese Radio, Record, Tape Player Svcs. Manual 228 p.	\$6.95
Servicing Electronic Organs 196 p., 158 il.	\$7.95
Tape Recording for Fun & Profit 224 p., over 200 il.	\$5.95

ALL-IN-ONE COLOR & B&W TV SCHEMATIC/SERVICING MANUALS	
Each vol. has complete service data, parts lists, full-size schematics, and all other info needed. Each 8 1/2" x 11" 196, 212 pps. Each only \$4.95 unless marked. COLOR TV: Adv. Vol. 1 \$5.95	
Vol. 2 \$6.95 GE Vol. 1 \$5.95 Vol. 2 \$5.95 Vol. 3 \$5.95	
Jap. Vol. 1 \$5.95 Vol. 2 Vol. 3 \$4.95 Vol. 4 \$5.95 Vol. 5 \$5.95	
Magnavox Vol. 1 Vol. 2 Vol. 3 \$5.95 Airline \$5.95	
Motrola Vol. 1 Vol. 2 \$5.95 Philco \$5.95 RCA Vol. 1 \$5.95	
Sears Vol. 2 \$5.95 Vol. 3 \$5.95 Vol. 4 \$5.95 Vol. 5 \$5.95	
Serv. Modular Rec. Vol. 1 \$6.95 Vol. 2 \$5.95	
Vol. 1 \$5.95 Vol. 2 \$5.95 Toshiba \$5.95 Zenith Vol. 1 \$5.95	
Vol. 2 \$5.95 Vol. 3 \$5.95 Vol. 4 \$5.95 B&W TV: Adv. \$7.95	
GE \$7.95 Jap. \$6.95 Mag. \$6.95 Mot. \$6.95 Philco \$7.95	
Syl. \$7.95 Zenith \$7.95	

## NO RISK COUPON-MAIL ENTIRE AD

TAB BOOKS, Blue Ridge Summit, Pa. 17214  
Please send me books checked above

☐ I enclose \$\_\_\_\_\_; send postpaid  
☐ Please invoice on 10-day FREE trial

Name \_\_\_\_\_ Phone \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

SAVE POSTAGE by remitting with order.  
Foreign add 10% p.p. Pa. residents add 6%.

PE-116





# Our new Powerhouse receivers outpower the competition.



LR-5555



LR-3030



LR-2020



LR-1515

Lafayette's new Powerhouse receivers have the power, the features and the performance you want. And the competition only promises.

Just check our spec chart. We deliver. With no gimmicks or technical tricks.

Besides incredible specs our new Powerhouse receivers have some features you've never had on any receiver before. Stop in at any of the Lafayette stores or dealers coast to coast and hear what Dolby® FM noise reduction, mike mixing and detent controls can do to give you clean, distortion-free sound.

Lafayette performance goes far beyond sound. We back you up with warranties, in-store service and people who can talk stereo in plain, simple language.

Our new line of Powerhouse receivers was built with power and backed up with consumer services to outpower the competition. Now where does the competition stand?

Specifications	LR-9090	LR-5555	LR-3030	LR-2020	LR-1515
Power Min. RMS 20-20,000 Hz	90+90	55+55	30+30	20+20	15+15*
Total Harmonic Distortion (Less Than)	0.1%	0.5%	0.5%	0.6%	0.7%
Input Sensitivity: phono/Aux/Mike mV	2.5/150/6	2.5/150/6	3.5/150/	4.0/150/	4.0/150/
Tone	Bass/Mid/Treble	Bass/Mid/Treble	Bass/Mid/Treble	Bass/Treble	Bass/Treble
Speakers	A, B, C	A, B, C	A, B, 4/ch	A, B, 4/ch	A, B, 4/ch
FM Sensitivity (Stereo)	21.0 dBf (1.8 $\mu$ V)**	21.0 dBf (1.8 $\mu$ V)**	23.0 dBf (2.0 $\mu$ V)**	23.0 dBf (2.0 $\mu$ V)**	25.0 dBf (2.2 $\mu$ V)**
Selectivity	80dB	80dB	70dB	70dB	60dB
Capture Ratio	1.25 dB	1.25 dB	1.5 dB	1.5 dB	2.0 dB
Price	\$599.95	\$399.95	\$299.95	\$249.95	\$199.95

\* @ 40-20,000 Hz \*\*IHF ('58) Sensitivity (Mono)

## Lafayette

There is no competition.

For more information and a free catalog please write: Lafayette Radio Electronics, Box 159, 111 Jericho Tpke., Syosset, N.Y. 11791  
Copyright 1976 Lafayette Radio Electronics

CIRCLE NO. 47 ON FREE INFORMATION CARD



## cost-effective signal generators

### 100kHz-216MHz 5 band signal generator



B&K-PRECISION  
MODEL E200D—\$234

- Built-in 100kHz and 1MHz crystal calibration system
- 96 dB attenuation in 6 steps
- Leads included

### sine/square wave generator




B&K-PRECISION  
MODEL E310B—\$158

- Sine: 20Hz—2MHz
- Square: 20Hz—200kHz
- Constant voltage output
- 56 dB attenuation in 6 steps

Both available from your authorized distributor, or write for detailed specifications.

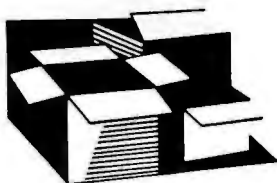**B&K PRECISION**

PRODUCTS OF DYNASCAN  
1801 West Belle Plaine Avenue  
Chicago, Illinois 60613 312/525-3990  
In Canada: Atlas Electronics, Toronto



## New Products

*Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Reader Service Card inside the back cover or write to the manufacturer at the address given.*

### ROYCE IN-DASH CB TRANSCEIVER

The Royce 1-614 is a combination in-dash CB transceiver and AM/stereo FM radio, featuring a PLL circuit that delivers 23-channel CB operation from two crystals, a dual-conversion CB receiver sec-



tion, AM/FM lighted slide-rule tuning dial, slide-type tone and balance controls, a local/distant switch for FM that is also an r-f gain switch on CB, and an LED that acts as a stereo indicator on FM and as a transmit light on CB. Other features include a  $1\frac{1}{8}'' \times \frac{3}{8}''$  S/r-f meter, pushbutton automatic noise eliminator, variable squelch control, and a universal trim plate that is said to match the decor of most cars. Size is 7"W x 6"D x 2"H (17.8 x 15.2 x 5.1 cm). \$269.95.

CIRCLE NO. 85 ON FREE INFORMATION CARD

### AUDIO-TECHNICA HEADPHONES

The AT-705 electret condenser headphone from Audio-Technica features permanently polarized diaphragms that need no external source of power. The headphones plug into a small adapter that matches impedance circuits and contains a speaker/headphone switch. The AT-705 has a claimed frequency response of 20 to 20,000 Hz and has open-back ear cups. \$89.95.

CIRCLE NO. 86 ON FREE INFORMATION CARD

### MICROCOMPUTER POWER SUPPLY

Parasitic Engineering offers a constant-voltage power-supply kit for the Altair 8800 computer. Designed to "make the Altair almost immune to unreliable performance due to power line fluctuations," the power supply is said to deliver full output of 8 V at 12 A and  $\pm 16$  V at 2 A "even when the line

voltage is as low as 90 volts." It is also said to provide increased isolation from line noise and over-voltage protection, with an increase of less than 2% in output when the line voltage rises to 130 volts. Heart of the kit is a ferro-resonant constant-voltage transformer, which replaces all three of the standard Altair 8800 power transformers. \$75.00. Address: Parasitic Engineering, P.O. Box 6413, Albany, CA 94706.


### LAFAYETTE SUPER TWEETER

The Lafayette Model RP-1000 "Criterion Polymer" super tweeter can be used with existing two- and three-way speaker systems. The transducer utilizes a flat polymer diaphragm with an etched voice coil. When an audio signal is applied, the diaphragm is said to be driven equally at all points on its surface. No polarizing voltage or energizer is required. It is housed in a brushed aluminum case with a stand, and can be used as a freestanding unit or can be mounted in a speaker enclosure with the stand removed. Claimed frequency response is 4 kHz to 40 kHz, power handling capacity 30 watts, and impedance 8 ohms. Measures (excluding stand)  $4\frac{1}{2}'' \times 4\frac{1}{2}'' \times 1\frac{1}{8}''$  (11.4 x 11.4 x 3.5 cm), and weighs 1.125 lb (0.51 kg). \$59.95.

CIRCLE NO. 88 ON FREE INFORMATION CARD
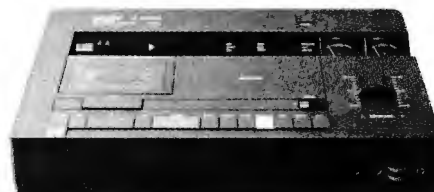
### LENCO CASSETTE DECK

Made in Switzerland and distributed here by Uher, Lenco's first stereo cassette deck is the C-2003, with direct drive, two capstans, three heads, and Dolby equalization. All mechanical functions are solenoid-operated, and logic controls permit changing from one function to another without pressing the stop button. An illuminated panel shows all functions as selected. Automatic tape selection is provided for chrome tapes, with manual selection for three additional types. A tape-motion sen-



sor automatically stops the tape if the cassette jams. Separate record and playback heads permit off-the-tape monitoring. Frequency response is 30 to 18,000 Hz  $\pm 3$  dB without Dolby, S/N is better than 60 dB with Dolby, and wow & flutter is less than 0.10%. \$695.50.

CIRCLE NO. 89 ON FREE INFORMATION CARD

### HICKOK IN-LINE CB TESTER

Hickok's 388 in-line CB tester provides a 7-digit readout of SWR, percent modulation, and frequency. The SWR and percent modulation functions use the "dynamic ratio technique," which permits measurements without a calibrate/set adjustment regardless of power level. The 388 provides one-step connection of the coax connec-

# **afs**® / **Kriket**® Communications Speakers


**means superior sound -- and  
that's a big 10-4!**



Tired of garbled voices and CB static?  
Now, you can hear better with our KC-3035 KRIKET® mobile speaker. Better than you believed possible.

Because AFS offers the first acoustically designed voice communications speaker. And, that means you get outstanding intelligibility across the entire voice range.

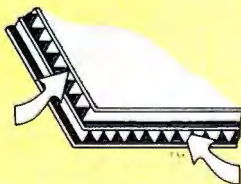AFS — the only company with the "WORKING WALL"® speaker enclosure. Cross-laminated tubular fiberboard deadens channel noise, eliminates voice distortion by controlling rebounding sound waves. Brings the voice through — clean and clear.



Available at CB dealers everywhere

Speakers are our only business. They have to be better!



World Wide Headquarters  
Acoustic Fiber Sound Systems, Inc. 7999 Knue Road, Suite 116 Indianapolis, IN 46250 (317) 842-0620

Exclusive Canadian Distributor  
Muntz Canada Ltd. 1149 Pioneer Road Burlington Ontario, Canada (416) 639-5373

All KRIKET® speakers are manufactured in the U.S.A. using American materials and craftsmen.  
Copyright 1976, Acoustic Fiber Sound Systems, Inc.



# Learn to service Communications/CB equipment at home...with **NRI'S COMPLETE COMMUNICATIONS COURSE**

**Learn design, installation and maintenance of commercial, amateur, or CB communications equipment.**

The field of communications is bursting out all over. In Citizens Band alone, class D licenses grew from 1 to over 2.6 million in 1975, and the FCC projects about 15 million CB'ers in the U.S. by 1979. That means a lot of service and maintenance jobs . . . and NRI can train you at home to fill one of those openings. NRI's Complete Communications Course covers all types of two-way radio equipment (including CB), AM and FM



special instruction so you can go on the air.

The complete course includes 48 lessons, 9 special reference texts, and 10 training kits. Included are: your own electronics Discovery Lab, Antenna Applications Lab, CMOS Frequency Counter, and an Optical Transmission System. You'll learn at home, progressing at your own speed, to your FCC license and into the communications field of your choice.



Transmission and Reception, Television Broadcasting, Microwave Systems, Radar Principles, Marine Electronics, Mobile Communications, and Aircraft Electronics.

The course will also qualify you for a First Class Radio Telephone Commercial FCC License or you get your tuition back.

## **Learn on your own 400-channel digitally-synthesized VHF transceiver.**

You will learn to service all types of communication equipment, with the one unit that is designed mechanically and electronically to train you for CB, Commercial and Amateur communications: a digitally-synthesized 400-channel VHF transceiver and AC power supply. This 2-meter unit gives you "Power-On" training. Then we help you get your FCC Amateur License with

## **NEW CB SPECIALIST COURSE NOW OFFERED**



NRI now offers a special course in CB Servicing. You get 37 lessons, 8 reference texts, your own CB Transceiver, AC power supply and multi-meter . . . for hands-on training. Also included are 14 coaching units to make it easy to get your commercial radio telephone FCC license—enabling you to test, install, and service communications equipment.

# NRI offers you five TV/Audio Servicing Courses

NRI can train you at home to service TV equipment and audio systems. You can choose from 5 courses, starting with a 48-lesson basic course, up to a Master Color TV/Audio Course, complete with designed-for-learning 25" diagonal solid state color TV and a 4-speaker SQ™ Quadraphonic Audio System. NRI gives you both TV and Audio servicing for hundreds of dollars less than the two courses as offered by another home study school.



All courses are available with low down payment and convenient monthly payments. All courses provide professional tools and "Power-On" equipment along with NRI kits engineered for training. With the Master Course, for instance, you build your own 5" wide-band triggered sweep solid state oscilloscope, digital color TV pattern generator, CMOS digital frequency counter, and NRI electronics Discovery Lab.



™ Trademark of CBS Inc.

## NRI's complete computer electronics course gives you real digital training.

Digital electronics is the career area of the future . . . and the best way to learn is with NRI's Complete Computer Electronics Course. NRI's programmable digital computer goes far beyond any "logic trainer" in preparing you to become a computer or digital technician. With the IC's in its new Memory Kit, you get the only home training in machine language programming . . . experience essential to trouble shooting digital computers. And the NRI programmable computer is just one of ten kits you receive, including a TVOM and NRI's exclusive electronics lab. It's the quickest and best way to learn digital logic and computer operation.

**You pay less for NRI training and you get more for your money.**

NRI employs no salesmen, pays no commissions. We pass the savings on to you in reduced tuitions and extras in the way of professional equipment, testing instruments, etc. You can pay more, but you can't get better training.

**More than one million students have enrolled with NRI in 62 years.**

Mail the insert card and discover for yourself why NRI is the recognized leader in home training. No



salesman will call. Do it today and get started on that new career.

**APPROVED UNDER GI BILL**  
if taken for career purposes Check box on card for details.



**NRI SCHOOLS**  
McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue,  
Washington, D.C. 20016



tors between the transmitter and the antenna or dummy load. Frequency measurements are from 1 Hz to 80 MHz, with resolution to 10 Hz. Size is 8½"W × 6"D × 4"H (21.6 × 15.2 × 10 cm). The 388 with standard time base has a frequency accuracy of 10 ppm, at \$349.00. The 388X, with a temperature-compensated crystal oscillator, frequency accuracy of 1 ppm and aging of less than 1 ppm per year, is \$475.00.

CIRCLE NO. 91 ON FREE INFORMATION CARD

#### TANDBERG AM/STEREO FM RECEIVER

Tandberg's TR-2055 AM/stereo FM receiver, based on the top-of-the-line TR-2075, offers most of the same features,



including the same FM tuner. The TR-2055 is rated at 55 watts per channel into 8 ohms at 20 to 20,000 Hz with less than 0.15% THD. Features include tape contour jacks, electronic tuning with varactor diodes, two phono inputs, two tape-monitor inputs with tape copy, two tuning meters, and diode switching for all sources. \$749.00.

CIRCLE NO. 92 ON FREE INFORMATION CARD

#### B&K SEMICONDUCTOR TESTER

The B&K 530 semiconductor tester features measurement of transistor cut-off frequency up to 1500 MHz in three ranges, with display on a separate meter. It permits in-circuit testing and lead identification of diodes, transistors, FET's (including power types) and SCR's. For out-of-circuit tests, transistor beta is measured in two ranges (20-200, 20-600) and Gm of FET's in two ranges (0.4-12, 4-400 milliohms); accuracy for both tests is within 10%. Other measurements include  $f_t$ , gate leakage and  $I_{DSS}$  of FET's, and  $BV_{CES}$ ,  $I_{CES}$  and PIV of diodes. LED displays indicate whether the transistor is good and whether it is an npn, pnp, or n- or p-channel FET. An audible tone also indicates that the transistor is good. \$250.00.

CIRCLE NO. 93 ON FREE INFORMATION CARD

## Looking for an ultimate standard of listening?



Many hi-fi enthusiasts bought a Crown DC-300A power amplifier because they were impressed by its performance specs, and by the quality of its "listening" performance. It was, for them, the "ultimate" amplifier.

Why not do what they did? Compare the specs for the Crown DC-300A with those of any other amplifier. Compare the clean,

pure DC-300A sound that comes from low-distortion circuitry and plenty of headroom. And especially compare the DC-300A with its smaller relatives, the Crown D-150A and D-60. Same clean, pure sound, less power, but may be just what you need.

Use your own judgment. You could find your ultimate listening standard in Crown.

#### DC-300A Stereo Amp

155 watts per channel min.  
RMS into 8 ohms  
(1-20,000 Hz), no more  
than .05% total  
harmonic distortion.

#### D-150A Stereo Amp

80 watts per channel min.  
RMS into 8 ohms  
(1-20,000 Hz), no more  
than .05% total  
harmonic distortion.

#### D-60 Stereo Amp

32 watts per channel min.  
RMS into 8 ohms  
(20-20,000 Hz), no more  
than .05% total  
harmonic distortion.

### Fast playback coupon

When listening becomes an art,



**Crown**

Box 1000, Elkhart IN 46514

Send directly to Crown for fast info on amps.

Name

Address


City

State  Zip


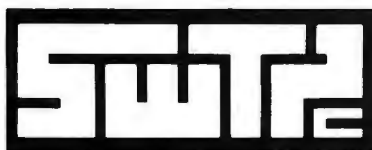
#### DYNACO POWER AMPLIFIER

Rated at 150 watts per channel into 8 ohms, with less than 0.25% THD, the Dynaco Stereo 300 power amplifier kit is designed



# 6800-SOFTWARE

**WARNING** — It has been determined that reading this ad may be hazardous to your health, if you own another type computer system. We will not be responsible for ulcers, heartburn, or other complications if you persist in reading this material.

## 4 K BASIC® — 8 K BASIC®

- \* Full floating point math
- \* 1.0E-99 to 9.99999999E+99 number range
- \* User programs may be saved and loaded
- \* Direct mode provided for most statements
- \* Will run most programs in 8K bytes of memory (4K Version)  
or 12K bytes of memory (8K Version)
- \* USER function provided to call machine language programs
- \* String variables and trig functions—8K BASIC only

### COMMANDS

LIST  
RUN  
NEW  
SAVE  
LOAD  
PATCH

REM  
DIM  
DATA  
READ  
RESTORE  
LET\*  
FOR

### STATEMENTS

END  
GOTO\*  
ON...GOTO\*  
ON...GOSUB\*  
IF...THEN\*  
INPUT  
PRINT\*  
NEXT  
STOP  
GOSUB\*  
PATCH\*  
RETURN  
† DES  
† PEEK  
† POKE

### FUNCTIONS

ABS † VAL † SIN  
INT † EXT\$ † COS  
RND † LEN\$ † TAN  
SGN † LEFT\$ † EXP  
CHR † MID\$ † LOG  
USER † RIGHT\$ † SQR  
TAB

\* Direct mode statements  
† 8K Version only

### MATH OPERATORS

- (unary) Negate  
\* Multiplication  
/ Division  
+ Addition  
- Subtraction  
† † Exponent

### RELATIONAL OPERATORS

= Equal  
< > Not Equal  
< Less Than  
> Greater Than  
<= Less Than or Equal  
>= Greater Than or Equal



© Copyright 1976 by Southwest Technical Products Corp. 4K and 8K BASIC Version 1.0 program material and manual may be copied for personal use only. No duplication or modification for commercial use of any kind is authorized.



You guys are out of your minds, but who am I to complain. Send —

- ☐ 4K BASIC CASSETTE \$4.95    ☐ MP-68 Computer  
☐ 8K BASIC CASSETTE \$9.95    Kit \$395.00

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_


ZIP \_\_\_\_\_

Southwest Technical Products Corp.  
Box 32040, San Antonio, Texas 78284



# THE STORM ALARM.
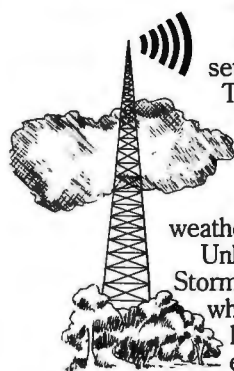
## IT WARNS YOU ABOUT STORMS THE WAY A SMOKE ALARM WARNS YOU ABOUT FIRES.



It sounds an alarm.  
A built-in alarm that's set off any time—night or day—when severe weather threatens.

The alarm is triggered by a signal from your local National Weather Service transmitter.

After it sounds, a complete report on the danger and survival instructions come on.

When conditions are normal, the Storm Alarm picks up the weather station's continuous, up-to-the-minute forecasts.

Unlike ordinary weather radios, which the user must monitor, the Storm Alarm continually monitors itself. The alarm sounds full blast whether or not you have the volume turned up and are listening. You're warned

even when sleeping.

Crystal-controlled and switch-selectable.  
Superior reception from as far out as 40-50 miles. Works on AC. Built-in back-up battery feature. 25" telescoping antenna.

2 1/4" speaker. Unit only 3" x 5" x 1 1/4".

With all these features, it's no wonder a leading electronics magazine called the Storm Alarm a "sensitive weather receiver, and for a relatively low price (under \$40) an excellent disaster alarm."

The increase in U.S. weather emergencies has led to the development of this unit.

Today, tornadoes, hurricanes, severe thunderstorms and marine emergencies are a constant threat to life and property.

For a free "Tornado Tips" booklet and the name of your nearest dealer, write us at 637 S. Dearborn, Chicago, Ill. 60605.

Get the Storm Alarm.

It's a foul and fair weather friend.

# STORM ALARM™

FROM WEATHERALERT

for easy rewiring into a 4-channel unit at 75 watts per channel. Except for output stages, all audio circuits are on two factory-wired, pre-tested circuit boards. The circuit is completely coupled (except the input) with full complementary-symmetry output and features thermally tracking bias. Amplifier and speaker are protected by volt-amp limiting, eight B+ fuses, four speaker fuses, and two thermal breakers, plus the ac line fuse. Behind the black panel, provision is made for either two or four optional rear-lighted output meters. It measures 18 1/8"W x 14 3/8"D x 7 3/8"H (46 x 36.5 x 18.7 cm). \$489, kit form; \$699.00, assembled.

CIRCLE NO. 96 ON FREE INFORMATION CARD

### CHANNEL MASTER CB ANTENNA

Channel Master's "Power Wing" mobile CB antenna "will not bend at any speed," according to the manufacturer, and is said




to provide higher average current and greater radiating efficiency than inductively loaded CB antennas. From base to wing, the antenna measures 16" high, plus an 8" telescoping stub for fine tuning. \$39.95.

CIRCLE NO. 97 ON FREE INFORMATION CARD
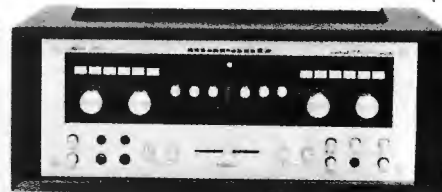
### MARANTZ STEREO PREAMPLIFIER

The Marantz 3800 combines a stereo preamplifier with a control console and a Dolby noise-reduction system. Distortion is rated at no more than 0.02% THD and 0.01% IMD; frequency response is "essentially flat" from 20 Hz to 20 kHz. The dynamic range is greater than 110 dB (high level). Tone controls include detented



straight-line bass, midrange and treble controls for both channels. Features two tape monitoring jacks and an EQ switch that permits equalizing tape-input signals with the tone controls while recording. \$599.95.

CIRCLE NO. 98 ON FREE INFORMATION CARD

POPULAR ELECTRONICS

# Only Technics gives you the world's most precise drive system all these ways.

Technics direct drive. Radio stations use it. Discos abuse it. And now you can get it in virtually any kind of turntable you want. Because Technics puts direct drive into more kinds of turntables than anyone else.

You'll find it in three manuals that start at under \$200\* with the SL-1500.

Or for a little more money you can get a lot more convenience with our newest turntable, the semi-automatic SL-1400. The world's first turntable with a one-chip 321 element IC. That gets the platter to exact speed in only 1/3 of a revolution. There is also the fully automatic single disc SL-1300.

And the world's first direct-drive changer, the SL-1350.

But there's a lot more to Technics direct drive than just more kinds of turntables. There's also more precision, better performance and greater reliability.

Because in our direct-drive system the platter is an extension of the motor shaft. That means there aren't any belts, gears or idlers to produce variations in speed. And that means all our turntables have less than 0.03% wow and flutter (WRMS), (0.04% for the SL-1350).



Direct Drive System

You'll also find an electronically controlled DC motor that spins at exactly 33 1/3 or 45 RPM. Regardless of fluctuations in AC line voltage or frequency. What's more, unlike high-speed, rumble-producing motors, our motor introduces so little vibration into the system that any rumble remains inaudible (-70 dB DIN B).

And it doesn't matter which Technics turntable you choose. Because they all have the extras you need. Like variable pitch controls. A built-in stroboscope. Viscous-damped cueing. Feedback-insulated legs. As well as a dust cover and integral base.

So if you want a turntable good enough for professionals, get the turntables radio stations use and discos abuse. Technics direct drive.

\*Suggested retail price.

## Technics

by Panasonic

CIRCLE NO. 71 ON FREE INFORMATION CARD

SL-1100A

SL-1200

SL-1350


SL-1500

SL-1300

SL-1400





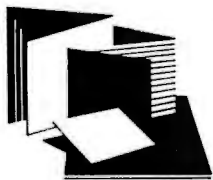

## New Literature

### CIRCUIT DESIGN CATALOG

E&L Instruments offers a new, 26-page catalog of electronic circuit design aids. The illustrated publication, describing over 180 products for experimentation with op-

erational amplifiers, integrated circuit logic and microprocessors, includes solderless breadboarding sockets, tools, component kits and a selection of instruction manuals. Address: E&L Instruments, Inc., 61 First St., Derby, CN 06418.

### CB ANTENNA CATALOG

A new 24-page catalog from Avanti illustrates its line of Citizens Band antennas. Described are seven base-station antennas, including the Moonraker; stacking kits; mobile antennas and accessories; marine antennas and accessories; monitors; switch boxes; and TV filters. All antennas are illustrated and complete

specifications are provided. Also, a discussion of the variable conditions that affect antenna performance and a description of Avanti's co-inductive principle. Address: Avanti Research & Development, Inc., 340 Stewart Ave., Addison, IL 60101.

### BUZZ WORD BOOKLET

An expanded edition of "Sherry's Guide to Data Communication Buzz Words" is available from ICC. The updated, 24-page, pocket-sized booklet first published in 1972 is designed to aid the newcomer to the data communication field. Included are definitions and terms relating to terminals and the EDP field. Address: Public Relations Dept., International Communications Corp., 8600 NW 41st St., Miami, FL 33166.

### ABOUT QUADRAPHONY

"Spatial High Fidelity Through SQ Quadraphonic Recording and Broadcasting," by CBS, is a 22-page, illustrated booklet, that answers questions most often asked by hi-fi listeners about quadraphonic broadcasting, recording and home listening. Included are sections on encoding, recording, decoding and logic systems used to produce ambient and surround sound; a technical summary of stereo-to-quad synthesis; a simple conversion of a home stereo to a quadraphonic system; and an explanation of the SQ quadraphonic system's compatibility with existing stereo and mono broadcasting and playing equipment. Send a stamped, self-addressed envelope (approx. 8½" x 4") to Information Services Dept., CBS Technology Center, 227 High Ridge Rd., Stamford, CN 06905.

### ELECTRONICS SYMBOLS HANDBOOK

The Cleveland Institute of Electronics has available a new 22-page, pocket-sized reference titled "Electronics Symbols Handbook." Listed alphabetically and divided into 19 categories, are more than five hundred of the most frequently used symbols representing electronics components. Also featured is an electronics data guide, including conversion factors and constants, Ohm's Law formulas, resonant frequency, impedance, a decimal table and a color-code chart. Price, 50 cents. Address: Cleveland Institute of Electronics, Inc., Dept. J-103H, 1776 East 17th St., Cleveland, OH 44114.

### CIRCUIT DESIGN RELIABILITY

"Circuit Reliability is not Semiconductor Reliability" is the title of "Tech Tips 3-4," offered by Westinghouse. Using equations and charts, the 3-page pamphlet illustrates that total circuit reliability is the product of the individual reliabilities of each component, and explains how to achieve this in circuit design. Address: Semiconductor Div., Westinghouse Electric Corp., Youngwood, PA 15697.

# tenna-loc®

## THE ANTI-THEFT CB ANTENNA LOCK

## PROTECT YOUR ANTENNA tenna-loc it!

**tenna-loc** is the first, really positive protection designed to keep your antenna intact and in place — year round! Yes, you may remove it for car wash or long term storage but there's no need to every time you park! It works like a charm in all kinds of weather and keeps on working for years. **tenna-loc** features a turn-proof locking stud integrated into a specially notched U-bolt with a 5-tumbler corrosion proof key lock. We also give you a heavy-duty mounting bracket

and an electro-polished, stainless steel replacement cup, where needed, for easy, quick installation. At \$11.95 (approx), it's a steal! Get one today.

- Choice of models, to fit most trunk mount antennas.
- Installs quickly, easily; keeps your antenna secure.
- Chrome plated, 5-tumbler, corrosion proof key lock.
- Exclusive, turn-proof, U-bolt with lock-in stud.
- Made in U.S.A.; patent pending.

See Your Dealer!



A product of:  
**VERNITRON CORPORATION**  
CONSUMER PRODUCTS DIVISION  
Lake Success Park, Community College, Great Neck, N.Y. 11021 (516) 487-0140



TC-800GL

HP-1

## Form follows function.

At Yamaha, it's been that way since 1887, when we began making music by making the finest musical instruments in the world.

Today, the same advanced technology found in our musical instruments has made Yamaha a leader in state-of-the-art audio components.

For example, we engineered our innovative Orthodynamic HP-1 and HP-2 stereo headphones to give both the smooth, crisp highs of the best electrostatic headphones and the rich, clean bass of the best dynamic types at a surprisingly low price.

But it wasn't enough to make them the best sounding headphones ever heard. We consulted world-famous designer Mario Bellini to help us make them the most comfortable headphones ever worn. Because we knew if they were uncomfortable, you wouldn't put up with them.

That's why a soft strap distributes the featherlight weight of the HP-1 and HP-2 evenly over your head. Special foam ear pads form a supple, compliant seal. Height and angle are completely adjustable to your head.

Yamaha musical technology is also highlighted in our superlative TC-800GL and TC-800D stereo cassette decks, offering cassette convenience with performance rivaling that of some of the finest open reel decks.

To satisfy the most sophisticated recordist, both the TC-800GL and TC-800D offer incredibly low 0.06% wow-and-flutter, Dolby\* Noise Reduction, and Variable Pitch Control. (The TC-800GL can even be used for remote recording.) But, if

you don't like to do a lot of fiddling around, both models offer automatic convenience features like Auto Timer Start, Auto Stop, Auto Memory Rewind, and Auto Switching for CrO<sub>2</sub> tape.

Also showing Mr. Bellini's touch, the functional wedge styling and stepped controls of these cassette decks give you easy control and visibility from any standing, sitting, or reclining position.

If you'd like a closer look at some other examples of form following function, send for our free catalog of stereo components. Or see your local Yamaha Audio Specialty Dealer. You'll get a lot more than just a demonstration.

\*Dolby is a registered trademark of Dolby Laboratories, Inc.

Yamaha International Corporation 101  
Audio Division, P.O. Box 6600, Buena Park, Calif. 90622

Please send my free copy of the Yamaha stereo components catalog and a list of Yamaha Audio Specialty Dealers.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_



**YAMAHA**





# Stereo Scene

By Ralph Hodges

## MODS AND MODIFIERS

**B**REATHES there a serious audiophile who has not at some time attempted to modify his equipment, either to personalize it or—if courageous or foolhardy enough—to improve it in some material way? Probably not many nowadays; given the complexity of design in modern audio gear. Interestingly, there are some people who make a business of equipment modification, offering customized versions of several popular components.

For a long time I've wanted to bring some of these business-minded customizers into these pages, to find out what they're doing and why, and to look critically at some of their products. This will be the first of (I hope) several columns that will explore the intricacies of this underground and interesting marketplace.

**Doubling Dyna's.** Dynaco is a company that is traditionally tolerant of unauthorized modifications—an unusually enlightened viewpoint. Consequently, the hills are alive with Dyna modifications. I first became aware of Jensens Stereo Shop and Frank Van Alstine because Dynaco tipped me off.

"He listens," said the Dyna spokesman, in tones meant to convey a certain amount of respect. And so I got involved with the venture.

Van Alstine's flagship product is essentially an augmentation of the Dynaco Stereo 400 power amplifier, dubbed the Double 400. A significant amount of labor goes into the modification. First, it is completely ripped apart to get at the bottom tabs of the heat-sink assembly, which are drilled to accept double the number of output transistors. Then leads from the power supply are brought out to a side-mounted socket, into which is plugged an outboard capacitor box that quadruples the capacity of the supply. A front-panel switch is installed that enables you to bypass the amplifier's front end (including the gain controls and the patented "Dynaguard" protective circuitry). A number of changes are also made in the driver boards. And finally Dyna's optional heat-sink fan is added.

This is not, as you can see, a redesign of the amplifier in any real sense. What does it buy you, other than the satisfaction of owning what is probably the biggest Leyden jar in the his-

tory of consumer audio? I can say, without hesitation or fear of serious contradiction, that it buys you a better-sounding amplifier than the original, for most practical purposes. And by "most practical purposes" I mean the difficult and erratic load presented to an amplifier by many loudspeakers.


The reduced impedance of the power supply and enhanced volt/ampere-handling capability of the output stage really do seem to make a difference. This reminds me of various learned dissertations that have appeared in the press on the subject of difficult temporal shifts in the voltage/current demands placed on the amplifier during its relationship with a typical loudspeaker. But without getting into that, I would characterize the audible difference between the modified and stock amplifiers as: an appreciable difference in the bass (you must decide which is better, because I can't reliably do so); and a reduction in the subjective noise level of the stock amplifier.

Noise level? Yes, because other listeners and I hear a quietness behind and within the flow of music that the stock version seems not to possess. (There is, I assume, no significant noise-level difference between them under non-signal conditions, so this "noise" arises from the program.)

There is general agreement on this verdict among all I have talked to that have compared the two amplifiers, so I don't think we're discussing will-o'-the-wisps here. But it is also rightly pointed out that the Double 400 modification, while possibly doubling the pleasure of very critical listeners, also comes close to doubling in price.

So we have a thoroughly clear picture. Dynaco, while conceding the merits of the modification, would have entirely missed its market by incorporating it into its product. The modification is intended for a much more specialized consumership willing to pay the price. It has been established that the stock Stereo 400 is entirely fit competition for its peers in cost. It remains to be seen whether the same can be said about the modification. But I think it has a good chance.

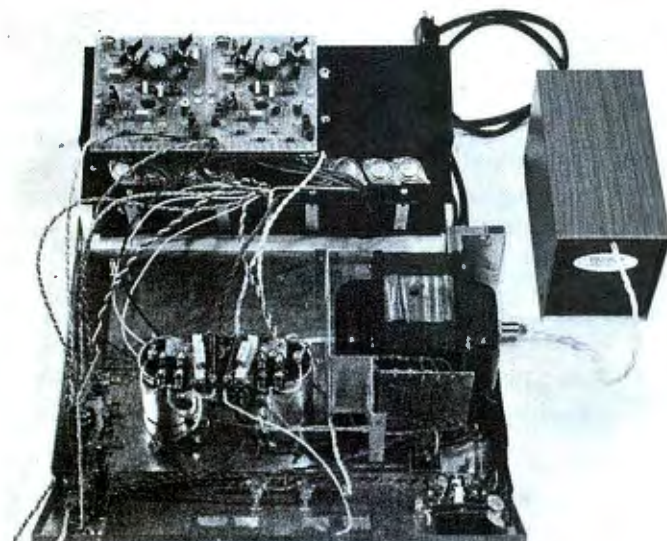**Pre-empting the Preamp.** Van Alstine's modification of the Dynaco PAT-5 preamplifier has been an ongoing process. I have been through several versions, and I understand there is a still-newer one that I haven't heard.



*The "Double 400" is an augmentation of Dynaco's Stereo 400 power amplifier.*



# MAGAZINES AT DISCOUNT!

## You SAVE <sup>UP</sup> TO 50%

Here's your chance for a bargain bonanza on your favorite magazines. You may select as many as four titles at the special introductory rates shown below—up to 50% off! Use the attached card to order or write to: **MAGAZINES AT DISCOUNT**, A Division of Ziff-Davis Publishing Co., P.O. Box 2703, Boulder, Colorado 80323.

**BOATING (01)** You pay only \$6.00  
Reg. Rate: 12 Issues for \$10.00  
**CAR & DRIVER (02)** You pay only \$3.99  
Reg. Rate: 12 Issues for \$7.98  
**CYCLE (03)** You pay only \$3.99  
Reg. Rate: 12 Issues for \$7.98  
**CYCLE WORLD (55)** You pay only \$4.49  
Reg. Rate: 12 Issues for \$8.98  
**ESQUIRE (49)** You pay only \$6.00  
Newsstand Rate: 8 Issues for \$12.00  
**FAMILY HANDYMAN (51)** You pay only \$6.98  
Reg. Rate: 9 Issues for \$8.55  
**FLYING (04)** You pay only \$6.99  
Reg. Rate: 12 Issues for \$9.98  
**PLAYBOY (34)** You pay only \$12.00  
Newsstand Rate: 12 Issues for \$19.00  
**POPULAR ELECTRONICS (06)** You pay only \$6.99  
Reg. Rate: 12 Issues for \$9.98  
**POPULAR PHOTOGRAPHY (07)** You pay only \$4.49  
Reg. Rate: 12 Issues for \$8.98  
**PSYCHOLOGY TODAY (08)** You pay only \$7.00  
Reg. Rate: 12 Issues for \$12.00  
**SKIING (09)** You pay only \$3.49  
Reg. Rate: 7 Issues for \$6.98  
**SPORTS ILLUSTRATED (38)** You pay only \$7.97  
Newsstand Rate: 26 Issues for \$26.00  
**STEREO REVIEW (11)** You pay only \$3.99  
Reg. Rate: 12 Issues for \$7.98  
**TIME (40)** You pay only \$12.50  
Newsstand Rate: 25 Issues for \$25.00  
**TV GUIDE (41)** You pay only \$7.39  
Lowest available rate: 32 issues





# Imagine a microcomputer

Imagine a microcomputer with all the design savvy, ruggedness, and sophistication of the best minicomputers.

Imagine a microcomputer supported by dozens of interface, memory, and processor option boards. One that can be interfaced to an indefinite number of peripheral devices including dual floppy discs, CRT's, line printers, cassette recorders, video displays, paper tape readers, teleprinters, plotters, and custom devices.

Imagine a microcomputer supported by extensive software including Extended BASIC, Disk BASIC, DOS and a complete library of business, developmental, and industrial programs.

Imagine a microcomputer that will do everything a mini will do, only at a fraction of the cost.

You are imagining the Altair™ 8800b. The Altair 8800b is here today, and it may very well be the mainframe of the 70's.

The Altair 8800b is a second generation design of the most popular microcomputer in the field, the Altair 8800. Built around the 8800A microprocessor, the Altair 8800b is an open ended machine that is compatible with all Altair 8800 hardware and software. It can be configured to match most any system need.

MITS' plug-in compatible boards for the Altair 8800b now include: 4K static memory, 4K dynamic memory, 16K static memory, multi-port serial interface, multi-port parallel interface, audio cassette record interface, vectored interrupt, real time clock, PROM board, multiplexer, A/D convertor, extender card, disc controller, and line printer interface.

MITS' peripherals for the Altair 8800b include the Altair Floppy Disc, Altair Line Printer, teletypewriters, and the soon-to-be-announced Altair CRT terminal.


Introductory prices for the Altair 8800b are \$840 for a kit with complete assembly instructions, and \$1100 for an assembled unit. Complete documentation, membership into the Altair Users Club, subscription to "Computer Notes," access to the Altair Software Library, and a copy of Charles J. Sippl's Microcomputer Dictionary are included. BankAmericard or Master Charge accepted for mail order sales. Include \$8 for postage and handling.

Shouldn't you know more about the Altair 8800b? Send for our free Altair Information Package, or contact one of our many retail Altair Computer Centers.

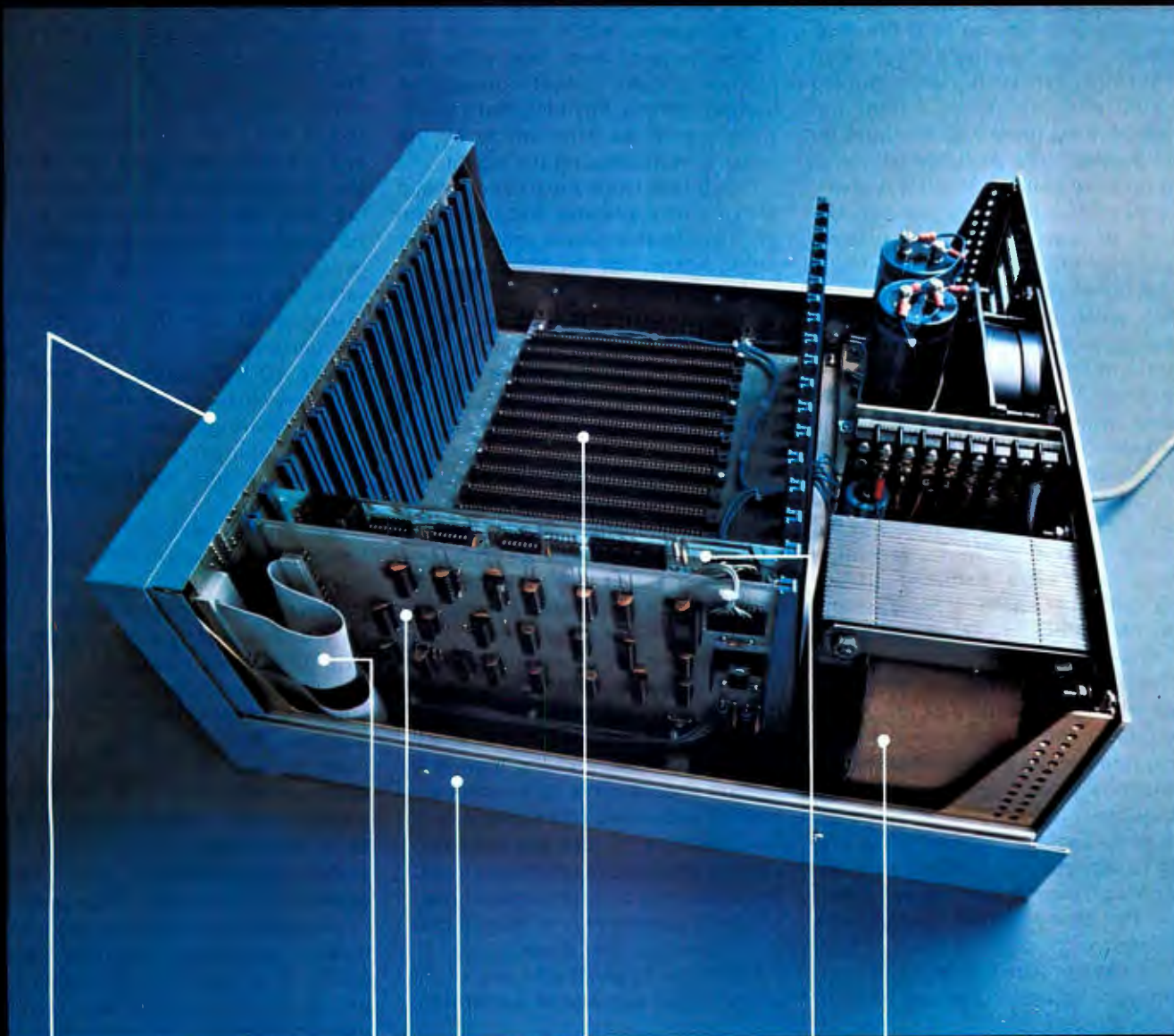mits 2450 ALAMO S.E. ALBUQUERQUE, NEW MEXICO 87106 (505) 243-7821







Redesigned front panel. Totally synchronous logic design. Same switch and LED arrangement as original Altair 8800. New back-lit Duralith (laminated plastic and mylar, bonded to aluminum) dress panel with multi-color graphics. New longer, flat toggle switches. Five new functions stored on front panel PROM including: DISPLAY ACCUMULATOR (displays contents of accumulator), LOAD ACCUMULATOR (loads contents of the 8 data switches (A7-A0) into accumulator), OUTPUT ACCUMULATOR (Outputs contents of accumulator to I/O device addressed by the upper 8 address switches), INPUT ACCUMULATOR (inputs to the accumulator from the I/O device), and SLOW (causes program execution at a rate of about 5 cycles per second—for program debugging).

Full 18 slot motherboard.  
Rugged, commercial grade Optima cabinet.

New front panel interface board buffers all lines to and from 8800b bus.

Two, 34 conductor ribbon cable assemblies. Connects front panel board to front panel interface board. Eliminates need for complicated front panel/bus wiring.

New, heavy duty power supply: +8 volts at 18 amps, +18 volts at 2 amps, -18 volts at 2 amps. 110 volt or 220 volt operation (50/60 Hz). Primary tapped for either high or low line operation.

New CPU board with 8080A micro-processor and Intel 8224 clock generator and 8216 bus drivers. Clock pulse widths and phasing as well as frequency are crystal controlled. Compatible with all current Altair 8800 software and hardware.

## altair 8800-b



2450 Alamo SE/Albuquerque, NM 87106/505-243-7821

Prices, delivery and specifications subject to change

NOTE: Altair is a trademark of MITS, Inc.

CIRCLE NO. 49 ON FREE INFORMATION CARD



The modification has generally been a study on designing a preamplifier in reverse. Mr. Van Alstine *takes out* things, and then devises ways to make the preamp live with the loss. Most of the process has concentrated on the high-level section, constructed around one integrated circuit per channel. First there was a search for the "fastest" IC's available to use as possible substitutes. (I will not reveal the devices ultimately chosen because Mr. Van Alstine feels that his laborious efforts have earned him some right to exclusivity, and I agree.) Then, when the IC's were obtained, frequency-compensation components around the IC began disappearing. Output capacitors also went, together with other devices, reducing the entire output stage to only three components when the tone controls are out of the circuit. Changes were made in the B+ rails, and also in the supply itself. Then tantalum capacitors were brought in for selected spots and now I understand that metal-film resistors are being routinely substituted for carbons.

The modified PAT-5 has proved to be a more controversial product than the Double 400. There is not even universal agreement as to whether all the evolutions have been steps forward rather than steps backward. However, I took the sample provided to me and put it through an exceedingly demanding (though not-always-valid) test: the phase-flipped straight-wire comparison.

The straight-wire test involves comparing the sound of a preamplifier to

the sound of a simple link of cable that bypasses it, switching from one to the other. The phase-flipped test combines the outputs of the preamp and straight wire, while inverting the phase of one of them. Ideally, the two signals should cancel completely, leaving nothing. Anything that's left is, presumably, an error made by the preamp in processing the signal.

The phase-flipped test is not a valid critique of a preamp, because completely tolerable phase shifts, among other things, can legitimately occur within preamps to prevent cancellation. So you can't indict a preamplifier for its failure to pass this test. But you can do nothing but praise a preamplifier that does pass it, and the PAT-5 modification came astonishingly close.

Most of the time, everything was inaudible, including hiss generated in the pre-cancellation stages. On extremely high-level passages (the program chosen was London's new recording of *Turandot*, whose first scene probably contains every berserk manifestation of musical waveform you're likely to encounter) there was an occasional soft "tst" of high-frequency noise. When I find out what this "tst" is, the modified PAT-5's high-level section should serve as a useful test bed for evaluating other products. In the meantime, the unit has to be considered above reproach in the areas of frequency response and phase linearity, and I wouldn't know how to criticize it on noise and distortion.

For those interested in any of the above, Frank Van Alstine's address is


Jensens Stereo Shop, 2202 River Hills Drive, Burnsville, Minn. 55337.

**Armless.** Tonearms are a necessary nuisance, which is probably why many of them are designed to look so pretty. Their function is to serve as a rigid and imperturbable platform for the cartridge, and we haven't yet discovered any practical alternative to them. But few of them are rigid and all of them are perturbable, whether from acoustic feedback, seismic disturbance, or gross undulations of the record surface. The only reasonable solution is to design an arm that interacts with the cartridge to create a fairly high (above 10 Hz) resonance. However, then very close attention must be paid to pivot bearings, leveling, and the distribution of mass, because these factors will now dominate the behavior of the tonearm.

For various reasons, the straight-line-tracking tonearm principle, properly executed, offers great promise. However not a great many such arms have been properly executed, and the principle itself has some intrinsic liabilities. For one thing, skating force, which straight-line arms eliminate, acts as a stabilizing/damping mechanism on rotating arms, as does the skating compensation device that engages in a constant tug-of-war with it. So a radial-tracking arm, lacking this stabilizing set of forces, must be very good in itself in order to succeed.

The Shreve-Rabco tonearm, a modification of the discontinued Rabco SL-8E, is a stab in the direction of proper execution, and an accurate one. The arm itself is fashioned out of balsa wood, (a total of twenty-two pieces, reportedly), except for a magnesium block that houses the pivot sockets and a threaded nylon rod that supports the counterweight. The contact lever for the advance mechanism has been whittled down to a slim (adjustable) wire, and the arm-lift system has been completely altered. Nine threaded counterweights are provided. You pick the one that positions the counterweight as close as possible to the pivot assembly with your preferred cartridge.

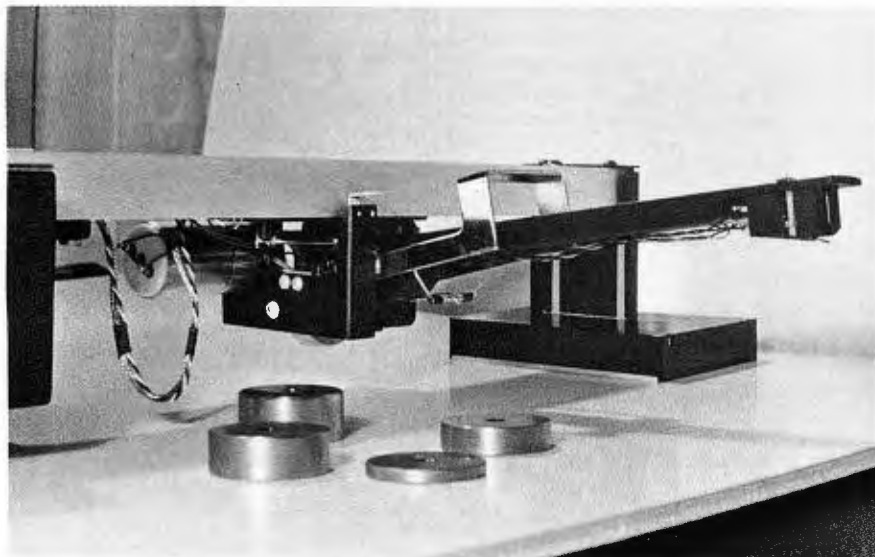All these steps are taken in the interest of low effective mass. For the bearings, perpetually lubricated sockets of the best quality are installed to receive the original Rabco needle-cones after they have been re-polished. And the bearings, as well as the arm cartridge alignment, are ad-



*The Shreve-Rabco tonearm, an adaptation of Rabco's SL-8E, is made of 22 pieces of balsa wood. Nine counterweights are provided.*

# The Control of Power by Sansui.

For the audiophile who wants the finest matched stereo amplifiers and stereo control preamplifiers, Sansui offers the answer — its Definition Series. Look at two of these outstanding components. The Sansui BA 3000 is designed with plenty of power to handle those bursts of percussion and those dynamic fortissimos that give you concert hall presence. The CA 3000 controls and features are a true joy for the creative pro and audiophile who wants to tailor the music to his own personal preferences.

This extraordinary pair is designed for the most demanding tasks; recording studios, sound reinforcement and audiophile home listening. The Definition Series offers the clearest, cleanest fidelity available anywhere. Top of the line Sansui BA 5000, called the "Monster," is one of the most powerful amplifiers available today: 300 watts per channel min. RMS into 2, 4 and 8 ohms from 20 to 20,000 Hz with no more than 0.1% THD.

For complete information on the entire Definition Series  
visit your local Sansui dealer soon or  
write directly to us.

**The CA 3000** phono preamplifier is within  $\pm 0.2$  dB of RIAA equalization curve. Offers everything desirable in a preamplifier and more. Triple tone controls. Left and right input and output channel meters. Tape controls for copy and playback. Sensitivity controls. Phono input capacitance selector.

**The BA 3000** stereo amplifier. 170 watts per channel, min. RMS, both channels driven into 8 ohms from 20 to 20,000 Hz with no more than 0.05% THD. Safety abounds: 4 jumbo heat sinks (Sansui patent pending); triple protection circuits for ample power protection; and front panel LED power/protection indicator on the front panel to show safe operation. Specially damped output power meter.

Each Definition Series component comes with a test data sheet, complete with all performance characteristics. And Sansui offers a limited 5 year warranty.

## SANSUI ELECTRONICS CORP.

Woodside, New York 11377 • Gardena, California 90247

SANSUI ELECTRIC CO., LTD., Tokyo, Japan

SANSUI AUDIO EUROPE S.A., Antwerp, Belgium

In Canada: Electronic Distributors

**Sansui**

CIRCLE NO. 65 ON FREE INFORMATION CARD



# Superb price!!!! Supreme quality!

6-DIGIT  
FREQUENCY COUNTERS

**69.95**  
(30mHz Kit)  
\$99.95 assembled

**119.95**  
(250 mHz Kit)  
\$139.95 assembled

A counter-offer you can't refuse! It's rock-bottom price and sky-high quality make it your best possible buy! We've proved it to thousands. Let us prove it to you!



Perfect for: CBers, Hams, Service Techs, & Experimenters!

• HAM, CB, & COMMERCIAL BANDS • WIRED & TESTED AVAILABLE • 100HZ READOUT • 6 DIGITS  
• CRYSTAL TIME-BASE • 1Hz OPTIONAL • MASTER CHG. / B. AMERICARD OK • ADD \$2 SHIPPING

## Hufco

Incredible counters starting at \$45.95 are also available!  
All counters can be factory wired and tested. Write or call today!  
Box 357, Dept. 52, Provo, UT 84601 (801) 375-8566

CIRCLE NO. 41 ON FREE INFORMATION CARD

## FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



### MX 113

FM/FM STEREO - AM TUNER AND PREAMPLIFIER

## SEND TODAY!

McIntosh Laboratory, Inc.  
East Side Station P.O. Box 96  
Binghamton, N.Y. 13904  
Dept. PE

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

If you are in a hurry for your catalog please send the coupon to McIntosh.  
For non rush service send the Reader Service Card to the magazine.

CIRCLE NO. 48 ON FREE INFORMATION CARD

justed by ear. You can imagine what a laugh that idea gave me until David Shreve stopped in and demonstrated the process, which I in turn demonstrated to friends and colleagues the following night with a similar deflation of mirth. At least all these adjustments are readily accessible, so you can fiddle to your heart's content.

As to the performance of the arm, there is no question about its being superb. When properly leveled it could probably not be dislodged from the groove by an earthquake. It tracks at any force usable with any cartridge, and it is stable. The sample I have, playing a commercial pressing of a very difficult piano recording, can almost match a one-off copy of the master tape—a phenomenon entirely new to me. If you pick the proper cartridge the arm will actually filter out orange-peel (mold grain) noise, and it will make rumble a thing of the past.

But note also that the arm is in short supply, difficult to make and adjust, and difficult to ship. It is also horrendously expensive. If you happen to be in David Shreve's neighborhood (3402 N. Oakland Avenue, Milwaukee, Wis. 53211) and are prepared to write out a check in excess of \$500, be my guest. But be sure to have your spouse cradle it gently in his/her lap on the drive to your home.

**Modify?** You might consider modified components if you are (like me) an all-out audiophile, as well as a tinkerer. Of course there are certain hazards. For example, plugging Van Alstine's output-capacitorless preamp into the wrong power amp could create unbelievable havoc. If you acquire one of Shreve's tonearms, be prepared to follow his written instructions (which are excellent) down to the last comma, despite your own ideas.

And there are other drawbacks. At the manufacturer's discretion, the warranty for your modification can become a worthless piece of paper, and you may create ill will in him that could be troublesome when the time for routine maintenance arises. In either case, you depend on the modifier for satisfaction and abide by his stated policy.

I've mentioned here only people who, on the basis of fairly long acquaintance, I've discovered to be completely trustworthy. Certainly there are other good modifiers out there. However, considering the hazards, I would say: caution. ♦

POPULAR ELECTRONICS

Let Walter H. Buchsbaum, one of the nation's leading electronics experts, show you

# how 4 easy-to-use troubleshooting techniques can solve 99% of your electronic problems in record time!

Act now. Save \$10.97. Publisher's price: \$12.95.

## Yours for just \$1.98.

Don't spend one minute more than is necessary on any troubleshooting job!

It's not a question of being lazy. It's just a matter of knowing a *sure and quick* way to find the defect. And that's the way you're going to know.

Walter H. Buchsbaum, one of the most respected authorities in electronics, has been collecting surefire troubleshooting methods for many years. From experts. In all areas of electronics. Now he's put the best of them, along with his own proven techniques, into **TESTED ELECTRONICS TROUBLESHOOTING METHODS**.

This book is presently selling for \$12.95. But, now you can have it for just \$1.98. YOU SAVE \$10.97!

It's our way of introducing you to the *Electronics Book Service*, the no-risk book club which is currently keeping over 50,000 technicians, troubleshooters and hobbyists informed of the best, more useful new books in the field of electronics.

**TESTED ELECTRONICS TROUBLESHOOTING METHODS** is typical of the selections we offer members. It gives you solid, expert help on all kinds of troubleshooting problems. It shows you how to *save time—money—and work*.

This is why we have chosen it to introduce you to the *Electronics Book Service*. Join now, as a trial member, and you'll receive your copy of **TESTED ELECTRONICS TROUBLESHOOTING METHODS**—for just \$1.98! This is your *only* financial commitment of membership. For the *Electronics Book Service* is a risk-free book club: As a member, you buy only what you want, when you want, and always at a substantial discount!

When you receive your copy of **TESTED ELECTRONICS TROUBLESHOOTING METHODS**, you'll learn an easy method that reduces the bulk of electronic repair to the simple application of 4 basic troubleshooting techniques. *Four minimum-time, maximum-efficiency procedures that will solve 99% of your electronic repair problems. And with record ease, speed and accuracy.*

- **THE SYMPTOM-FUNCTION TECHNIQUE** will quickly isolate the defect to a particular part of the equipment. Once you isolate the trouble spot. . .
- **THE SIGNAL-TRACING TECHNIQUE** will help you find the stage—amplifier—logic gate—or whatever the cause of the trouble.
- **THE VOLTAGE-RESISTANCE TECHNIQUE** will precisely pinpoint for you the defective component.
- **THE VOLTAGE-SUBSTITUTION TECHNIQUE** will verify the trouble and, in some types of equipment, find the solution from among the remaining possibilities.

These 4 basic techniques form the foundation for *all* successful troubleshooting. You can use them singly or in combination. They work like magic for all the top-level electronics experts. *And they'll work for you!*

And these 4 techniques aren't the only sure-fire troubleshooting techniques you'll find in **TESTED ELECTRONICS TROUBLESHOOTING METHODS**. Buchsbaum bring you a *whole* battery of time-saving, work-saving methods

—methods which the nation's most successful electronics experts are using.

For bonuses, Buchsbaum gives you additional guidelines for getting the most out of your equipment. You'll see how to test and calibrate all standard meters. Even how to get the most for your money when you select test equipment.

What's more, you'll discover methods for finding and solving intermittent defects—which are usually hard to find. And for dealing with interference defects—which are often mistaken for component failure.

**TESTED ELECTRONICS TROUBLESHOOTING METHODS** contains over 100 illustrations that simplify these methods and formulas the experts use. You'll have the circuit and block diagrams—tables—charts—schematics—and checklists that make Buchsbaum's troubleshooting techniques easy to apply.


With this battery of simplified troubleshooting techniques, you'll be able to handle all kinds of electronic repair work *quickly—easily—economically*. And without wasting time—doing unnecessary extra work—or going through endless trial-and-error. For these reasons, **TESTED ELECTRONICS TROUBLESHOOTING METHODS** is a perfect introduction to the . . . **ELECTRONICS BOOK SERVICE**.

The *Electronics Book Service* does a job which you don't have time to do for yourself. We carefully screen the hundreds of books on the subject, select those which are the most useful or which bring you the latest information on technical innovations and improvements of prime importance.

Your membership is an ideal way to keep in touch with the onrushing advances in electronics and its applications—to keep on top of a rapidly changing technology.

As a member, you can build a professional library of superb quality and permanent value—one which will meet your every interest and requirement, always available for you to consult for expert help in any need. And you can acquire this library as quickly or as slowly as you choose.

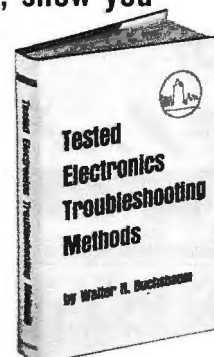Remember, the *Electronics Book Service* has *no minimum purchase requirements* as do many book clubs. Once you've paid \$1.98 for **TESTED ELECTRONICS TROUBLESHOOTING METHODS**, you don't need to purchase any further selections!



Why delay? Mail the coupon below to get your copy of this \$12.95 handbook for only \$1.98—and to receive all the benefits of membership in the *Electronics Book Service* on a risk-free trial basis. Fill out and mail your coupon right away.

### Here is the practical and efficient way in which the Electronics Book Service operates.

**1.** When you enroll as a member, you receive—for only \$1.98 (plus postage and handling, with tax where applicable)—your copy of **TESTED ELECTRONICS TROUBLESHOOTING METHODS**. This is the *only* obligation you are committed to make.

**2.** You are under *no* obligation to accept any minimum number of selections within any time limit. *You can take as many or as few as you wish*. And, you may resign at any time with no obligation once you have paid for your copy of **TESTED ELECTRONICS TROUBLESHOOTING METHODS**.

**3.** On selections you do accept, your membership entitles you to a discount from the publisher's list price. This discount is available to members only and provides you with substantial savings.

**4.** Every four weeks we'll send you a free bulletin describing the current selection. If you want the selection, no action is required; it will be shipped to you automatically. If you don't want it, just return the card enclosed with the bulletin.

**5.** You have at least 10 days to decide whether you want the selection or not. Return the card so we receive it no later than the date specified. If you don't have 10 days to answer and receive an unwanted selection, return it at our expense.

**6.** Each bulletin also describes a number of alternate or additional selections, also available to you at the special discount price for members.

— FILL OUT AND MAIL THIS COUPON TODAY. —

#### ELECTRONICS BOOK SERVICE

Dept. 6651 P1 (5), P.O. Box 42  
West Nyack, N.Y. 10994

Please enroll me in Electronics Book Service on a risk-free trial basis. I am to receive announcements free of charge, and will be entitled to full privileges as a member—without obligation to buy any specific number of club selections. As my first selection under this trial membership, send me **TESTED ELECTRONICS TROUBLESHOOTING METHODS** for only \$1.98 (plus postage and handling, with tax where applicable).

Name

Address

City  State  Zip

Offer limited to new members (U.S. and Canada) only.





Have a problem or question on circuitry, components, parts availability, etc.? Send it to the Hobby Scene Editor, POPULAR ELECTRONICS, One Park Ave., New York, NY 10016. Though all letters can't be answered individually, those with wide interest will be published.

By John McVeigh

## ACOUSTIC FEEDBACK

**Q.** How do the manufacturers and the users of commercial PA and sound equipment reduce or eliminate acoustic feedback, even at high sound pressure levels (such as at rock concerts)? Can I apply the same techniques at home?

—Richard Lei, Rego Park, NY

**A.** In his *Stereo Scene* column in May 1976, Ralph Hodges discussed "The World of Sound Contracting." In that column he touched upon this particular subject and showed sample graphs for equalized and unequalized response of a large hall. By means of a narrow-band equalizer, the sound contractor can flatten out the frequency response and squash acoustic feedback. In the home, it is usually the turntable that is most affected by acoustic feedback. And in almost every case, the oscillations are at a low frequency. The best way to lick this problem is to physically isolate the turntable base, using a commercial shock mount with built-in damping or a home brew mount constructed from thick, spongy foam rubber.

## FM INTERFERENCE

**Q.** I have a 5-band portable radio. When I switch to Public Service Band I (30-50 MHz) or PSB II/Air (108-174 MHz), I receive FM broadcasting stations. What causes this and how can I correct it?

—Barry Sheffield, Chester, VA

**A.** Either the receiver has insufficient selectivity or the front end is being overloaded. You did not mention whether or not you are using the built-in whip or an external antenna. In either case, you could try putting a wave trap at the appropriate input. Use either a series LC circuit from the antenna input to ground or a parallel LC

circuit between the antenna and the input to the r-f amplifier. Adjust either L or C to resonate the circuit and null out the undesired signal. But I'd suggest making the trap switchable (use a low-capacitance switch) so that you can still use the radio on the FM broadcast band!

## COMPUTER RFI

**Q.** I recently got a Sphere Systems computer which is causing interference to nearby television receivers. (I am temporarily operating it outside of its cabinet.) Apparently, most of the interference is coming from the CPU board. Although I constructed a box from window screening and grounded it, the RFI problem remains. Any suggestions?

—Charles Skeldon,  
New Brighton, MN

**A.** The majority of information signals that are generated by a digital system are square waves. Mathematically, a square wave can be described as a summation of sine waves harmonically related in frequency. The high-order harmonics can cause RFI and TVI. The best way to combat the problem is to button up the case tightly, making sure that there are clean metal-to-metal connections. If you must use the microprocessor outside its cabinet, try using very, very fine screening. Also, use a "brute force" filter on the ac line. Finally, you might try using ferrite beads on any lead more than a few inches long.

## WINDSHIELD WIPER DELAY

**Q.** Do you have a circuit for a variable delay control for windshield wipers?

—Doug Swart, Plainview, NY

**A.** The circuit shown is a result of collaboration between myself and reader Jack Rutherford of Burlington, North Carolina. It will provide a sweep rate of from one every 5 seconds to one every


## MIXING WITH A GRID DIP

**Q.** Recently, I accidentally made a discovery that has led to many hours of listening enjoyment. While varying the frequency of my grid dip meter, which was placed near an FM radio tuned off-channel (about 90 MHz), I found that I could receive many different r-f transmissions. Some of those I've received are TV sound, aircraft, police, CB, 2-meter FM, telephone calls, and even WWV. I'm fascinated! But how does it do it?

—Dennis Cole, Lincoln Park, MI

**A.** You have created a frequency converter stage. The grid-dip meter is the local oscillator, and some nonlinear element inside the receiver is acting as a mixer. The result is an additional heterodyne process. Exactly where the heterodyning is taking place is hard to determine, because one variation on Murphy's Law states that a linear circuit will often behave nonlinearly. Furthermore, just imagine how many pn junctions there are inside the radio's case, each of which can act as a diode mixer. Interestingly, you are receiving AM as well as FM transmissions. I imagine that is the result of slope detection. A variation of your technique has been used by many shortwave listeners who copy CW and SSB signals on shortwave portables lacking bfo's. By tuning a signal generator or the local oscillator of another receiver to the proper frequency, they could reinsert a "carrier" for proper detection. Happy Listening!

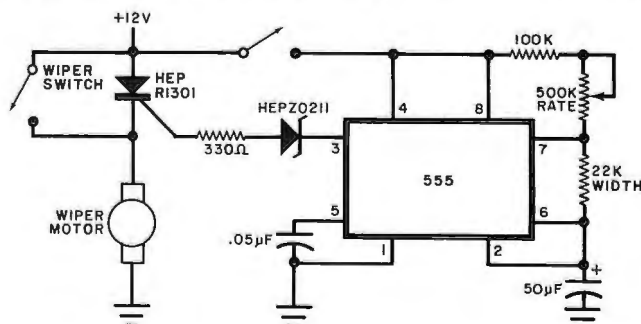37 seconds. An SCR is used for triggering the windshield wiper motor rather than a relay to avoid mechanical bounce problems. The SCR, a HEP R1301, will handle 20 amperes of maximum forward current, sufficient for even a hefty wiper motor. The SCR should be heat-sinked. All resistors are half-watt carbon, and the 50µF capacitor should be a tantalum type.



To SBE

# war-ran-ty

*is not just another word*

We at SBE have built our reputation on the quality and reliability of every single product we sell. To maintain the high standards we have set for ourselves, every SBE product is thoroughly tested to insure meeting our stringent quality control before shipment.

Our insistence upon "out-of-the-box performance" is best evidenced by the fact that every CB radio, every scanner, and all land/mobile and marine transceivers are checked and re-tested before they leave our factory.

Skilled technicians with intricate test equipment insure that every product manufactured receives this double check-out before the SBE "Quality-Assurance Personalized Seal" is affixed to each box. With that seal goes our guarantee, for a full year, that the SBE product will perform up to its specifications—from the sophisticated circuitry to the smooth-functioning controls.

It is just such quality control, coupled with our advanced technology and innovative engineering, that has made SBE a leader in the CB field. The Brute is just one more achievement in this development—a small but precision-built 23-channel transceiver incorporating all the features and performance of a full-size CB.

You can count on every SBE product and accessory for dependable performance and reliability. We have built our reputation on that!



**Better Communications through Creative Technology**

For information write: SBE, Inc., 220 Airport Blvd., Watsonville, CA 95076

INTERNATIONAL OFFICES: E.S. Gould Marketing Co. Ltd., Quebec, Canada/Linear Systems, S.A., Geneva 1, Switzerland

Circle 2 on reader service card

CIRCLE NO. 63 ON FREE INFORMATION CARD



# PROPAGATION FORECASTS FOR RADIO COMMUNICATORS

*How to examine the sun safely and use other sources to determine sunspot activity.*

**I**N ADDITION to being the ultimate energy source for all earthly life, the sun plays a dominant role in the long-range propagation of radio waves. Solar radiation causes atoms in the upper atmosphere to ionize, resulting in the formation of the ionosphere, off which radio waves bounce to return to the earth and provide long-distance communications. The density and height of the ionosphere determine the wavelength and the angle of the reflected wave.

There is also a correlation between the presence of sunspots on the solar disc and the degree of ionization of the upper atmosphere. With all we know about solar activity, however, we cannot yet predict with a high degree

of accuracy ionospheric "weather" and its influence on radio.

Records of sunspot activity have been reliably kept since only about 1750; but this still enables us to develop a plot which shows the so-called sunspot cycle. The up-and-down nature of sunspot count is evident in the plot shown in Fig. 1; but note that irregularities can be detected. Observe, too, that sunspot peaks have been as low as 60 and as high as 200. Moreover, the valleys in the graph have not always reached the zero mark, although some have remained near zero for a year or more. Thus, the 11-year "sunspot cycle" is also an approximation since there have been longer and shorter cycles.

For more than a year now, knowledgeable people have been wondering when Cycle 20 (in the recorded history of cycles) is going to bottom out. Have we already passed the sunspot minimum? When will Cycle 21 begin to show strength? Is it already revealing itself? Will it ever? These are the questions being asked; and the answers given differ widely.

**Equipment.** Active hams, CB'ers, and SWL's have a keen interest in keeping up with the sun's activity. Most radio communication enthusiasts, however, don't realize that they can do so without setting up elaborate solar observatories in their

\* Source of Information: Edward P. Tilton, W1HDQ


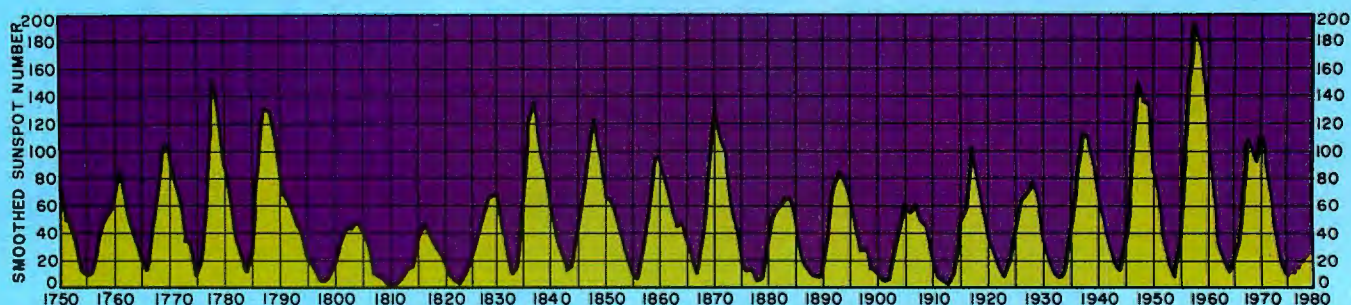


Fig. 1. Smoothed sunspot number plotted from 1750 to present. Cyclic variation is apparent.

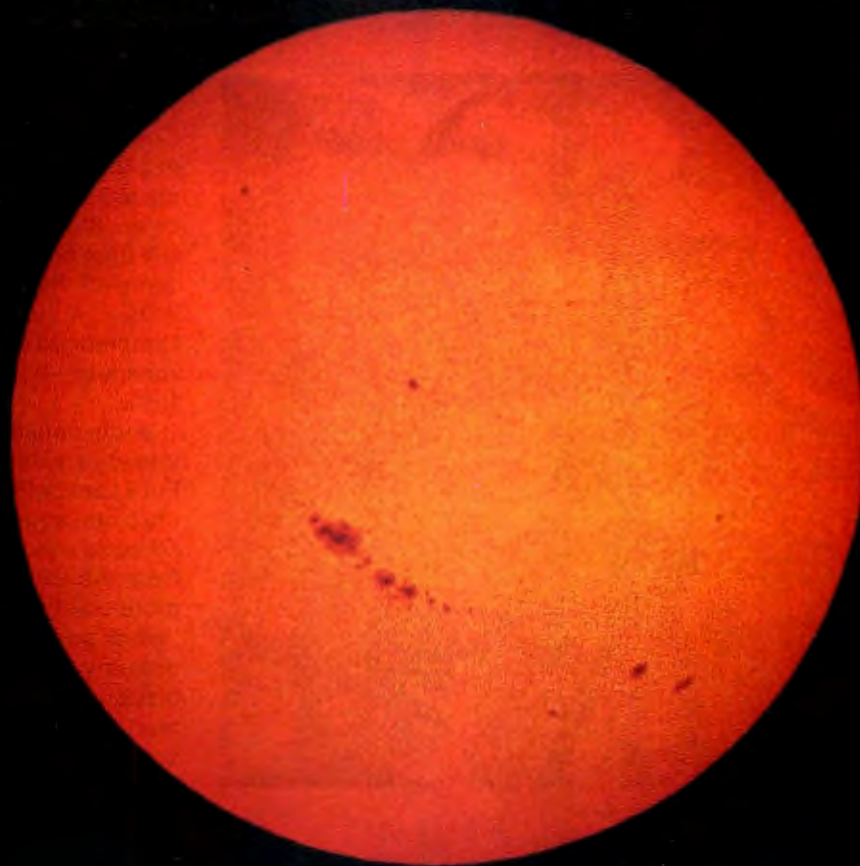



Color photos courtesy Tiern Observatory—Terach Enterprises.

*Photo (above) of entire sun disc, Jan. 30, 1968, when sunspot activity was very high. Spots have dark centers (umbra) and surrounding grey areas (penumbra). Darkening around edge is from looking through more and more of sun's atmosphere.*

*View (below) of sun taken with chronograph. The bright surface (photosphere) is blocked to see atmosphere next to surface. Red chromosphere is seen in the light of hydrogen-Alpha wavelength. Projections from chromosphere are prominences.*







*Fig. 2. Using a 5" reflector telescope and black box to view projected image of the sun.*

back yards. One can keep track of what's happening on the sun even at the bottom of Smog Valley with any old "spyglass." People have used an antique mariner's glass, a surplus military target telescope, bird watchers' telescopes, a \$29 zoom-lens telescope, and the 5" (127-mm) reflector shown in Fig. 2. Whatever you use, though, be sure you don't look directly at the sun with the scope (or your naked eye) except with a filter that is safe for sun use. The various scopes mentioned above should be used for projection viewing only.

In Fig. 3, a Celestron 5 telescope is shown being used for direct viewing of the sun with the manufacturer's full-aperture solar filter in place. This filter passes only 0.01% of the light striking it to the viewer's eye, the minimum

amount of filtering considered safe. You can make your own solar filter by mounting a Wratten neutral-density filter (density No. 4, available from Eastman Kodak dealers) in a lens-cap arrangement of your own fabrication. Be absolutely certain that any such filter is tightly mounted so that it doesn't accidentally slip out of place when you're looking into the scope's eyepiece. Incidentally, the Wratten No. 4 filter is also useful with large telephoto lenses that can be attached to single-lens reflex cameras for solar photography.

With an inexpensive low-power telescope, a camera tripod equipped with a pan-tilt head, and a few viewing accessories, you'll always be ready to check the sun, even on long road trips. To use the equipment, set the scope

on the tripod and tilt it up in the general direction of the sun. Hold a white card in line with the eyepiece and adjust the orientation of the scope until the shadow it casts on the card is circular. Slow movement of the scope will then bring out a bright spot in the center of the shadow. This is the solar image. Adjusting the scope for a sharp-edged solar disc will bring the sunspots—if there are any—into near focus.

Better detail and contrast can be obtained by enlarging the shadow area. Put a card baffle measuring at least 12" (30.5 cm) square over the body of the scope to shade the projection surface from the sun's direct light. For even more clarity, project the image into a "black box" (as shown in Fig. 2). An ordinary cardboard box painted flat black will do. The viewing surface can then be good-quality white paper or any smooth surface inside the box painted flat white. Better still, put a cover on the projection box and cut a hole just large enough to permit you to look into the box and see the projected image at the bottom.

You will discover that the more ambient light you exclude from the projection area, the better will be the detail of the image and the larger the image you'll be able to use effectively. Bear in mind, however, that any gains you make must be paid for, which means that larger images will demand more precise aiming and tracking adjustments.

When you're using a telescope of more than 20 $\times$ , an equatorial mount and rack-and-pinion drive become very helpful. The better scopes are usually equipped with these features, and some have mounted projection devices and electric clock drives. The latter two are also available as options for those telescopes that don't include them as standard features. A moderately priced 2" or 3" refractor that's fully equipped with features and accessories makes an excellent setup for projection viewing.

Interpretation of what you see is an involved process that requires a skill developed through practice and experience. Correlating what you see with observed propagation effects can develop into an absorbing side hobby. You might find it useful to make two sketches of each observation; one to show the locations and general appearances of any spots and the other an enlarged view of major spots or groups of spots.



*Fig. 3. Viewing the sun directly through Celestron 5 telescope equipped with full-aperture solar filter. Hat brim shields eyes from sun and makes fine details on sun easier to resolve. (Photos on this page courtesy American Radio Relay League, Inc.)*



## A LOOK AT SOLAR RADIATION

Sunspots are visible evidence of solar activity, wellsprings of the kinds of radiation that affect radio communication for better or worse. The types of radiation with which we are principally concerned are ultraviolet light and atomic particle emission. As with all electromagnetic waves, UV travels at roughly 300,000 km (186,000 miles) per second. Thus, if we see a sudden change in the appearance of a sunspot group or detect an increase in solar radiation by electronic means, we can expect propagation changes almost immediately.

Ionization of the earth's outer atmosphere (production of the ionospheric layers that make long-distance communication possible) is a sudden effect, much like turning on a fluorescent lamp. The F layer, located some 140 to 200 miles out in space, is "turned on" by solar UV radiation and acts as the principle radio "mirror," reflecting waves back toward the earth. This ionized layer appears to build up gradually each morning and to dissipate each evening.

A sudden burst of UV radiation, such as that which accompanies the appearance of a solar flare, can change the state of the ionosphere almost immediately. (It arrives here about eight minutes after it has left the sun.) The effect of the UV flash is a rise in the maximum usable frequency (muf) which is the highest frequency that will support communication over a given signal path. Also, the received noise level will probably increase, especially if the antenna is directional and is aimed at the rising or setting sun.

Such a burst of UV radiation is accompanied by charged-particle emission. This "solar wind" moves more slowly, however, spraying out into space with what has been called the "garden-hose effect." (For a practical demonstration

of this effect, turn on the water pressure suddenly in a hose lying loose on a lawn.) The solar wind follows devious paths, which means that the effects of the particle burst may not be observed on earth for as long as one to four days after it left the surface of the sun. When the particles enter the earth's magnetic field, you'll know about it quickly, particularly if you live in the Northeastern-US or Canada. Shimmering aurorae may appear and signals in the lower portion of the hf spectrum will take on a wavery sound. This is sometimes followed by partial or complete loss of communication. Frequencies above about 25 MHz (higher in periods of generally higher solar activity) can open up for short skip, and signals may also show the typical auroral "fuzz," or distortion, resulting from multipath scattering in the auroral regions. The distortion tends to increase with increasing frequency.

In times of generally lower solar activity, such as the present, the effects of particle radiation are mostly mild. Aurorae are relatively rare and the disturbances associated with solar-flare activity are much less severe and frequent than they will be in a few years from now.

A widely overlooked fact about solar cycles is that, regardless of the current phase, there are large variations in the level of activity from time to time. It's rare to have more than 10 consecutive days of solar stability. Even near the normal "bottom" of the cycle, solar activity and visible sunspots can increase steadily for several days, reaching peaks more characteristic of middle or even peak years. These anomalies often sneak up on professional forecasters so that even the newest amateur observer will not have to wait long to find "official" forecasts as far off the beam as local weather forecasts are at times. High-activity peaks have appeared in 1974, 1975, and 1976, supposedly the lowest three years of a dying Cycle 20.

agation quality. The *K index* is, in effect, a numerical statement of geomagnetic activity. It reflects an actual reading taken just before bulletin time and is a direct indication of likely propagation quality on high-latitude paths and on frequencies where geo-magnetic field effects are critical (mostly below 15 MHz at times of low solar activity). The *solar flux index* is a measure of solar radiation. It correlates well with the muf (maximum usable frequency) for F-layer propagation and reasonably well with long-term sunspot number information. It is much more useful in planning radio communication than the sunspot number, because it is essentially current information. Both the *K index* and the solar flux are given with the expected direction of change, making them very valuable for short-term forecasting and planning when to use different frequencies.

A typical bulletin sounds like this: "The radio propagation quality forecast for 1900 UTC is *fair to good*. The geomagnetic field is *quiet*. The coded forecast is *November five*. The *K index* for 1800 UTC is *two*, expected to remain the same. The 2800-MHz solar flux index is *72*, expected to rise slowly." What does all this mean?

Since a steady *K index* of two or less means generally low geomagnetic activity, it can be assumed that there is no abnormal amount of charged-particle emission from the sun entering the earth's magnetic field at the moment. And a low, but rising, solar flux indicates a somewhat higher F-layer muf will develop. If the bulletin is correct as to these trends, the propagation forecast will be right — conditions will be above average and the muf will rise. The "November" part of the coded forecast stands for *N*, or "normal," and "five" means fair to good conditions.

A fast-rising *K index* means increased absorption of radio signal energy in the ionosphere and reduced signal levels or perhaps loss of communication entirely. The effects are generally more pronounced in the higher latitudes; hence the forecast for the North Atlantic path — a busy circuit traversing high latitudes from most of the United States. The operator will do well to get his message across as soon as possible since conditions are changing rapidly.

If the *K index* rises above three, there will be a marked deterioration in communication. At five or six, total

**Sources of Information.** There are several information sources for propagation conditions. For example, annual and monthly forecasts are offered by many shortwave club newsletters and amateur radio magazines.

The National Bureau of Standards radio stations WWV and WWVH are another valuable source of information. These stations transmit continuously on 2.5, 5, 10, 15, 20, and 25 MHz, primarily for the purpose of providing accurate time and frequency standards.

Propagation bulletins are given at 14 minutes past the hour on WWV and

are updated four times daily, usually at 0114, 0714, 1514, and 1914 Coordinated Universal Time. UTC is the same as GMT, which is equivalent to EST plus five hours. The following information is given: propagation quality forecast; condition of the geomagnetic field; coded forecast for the North Atlantic path; the *K index*; and the 2800-MHz solar flux.

*Propagation quality* is given in one of nine degrees, ranging from "useless" to "excellent." *Geomagnetic activity* is given as "quiet," "unsettled," or "disturbed." The *coded forecast* is a simple quantized statement of prop-



loss of contact will probably result. An index of seven means that a really severe disturbance is under way, affecting all but transequatorial paths, even those at the low end of the hf range. However, it's good news for vhf enthusiasts because auroral openings are almost certain in the northern US.

Rising solar flux means increased UV (ultraviolet) radiation. The reading broadcast over WWV is derived from information taken on 2800 MHz in Ottawa, Ontario, Canada, at 1700 UTC (noon Ottawa standard time). The 1914 WWV bulletin reflects the 1700 Ottawa observation. Although the language appears to imply that the reading is updated with each bulletin change, this is rarely the case. So, if you can't copy four bulletins each day, concentrate on the one at 1914. It's the best of the lot for fresh solar flux information.

As with the K index, the trend in solar flux is important. So is the rate of change. A slow, steady rise in solar flux — say one point per day — with perhaps no rise at all on some days within a generally upward period means gradually improving conditions on all frequencies, particularly if the K index remains low and fairly constant. The muf will increase per-

ceptibly with each rise in the solar flux. A week of this can mean a great deal to amateur radio operation on the 15-meter band during the fall and winter of 1976-1977 and SWL's monitoring the 16- and 13-meter shortwave bands. A really marked rise can even bring the region above 27 MHz, including the Class D Citizens Band and 10-meter amateur radio band back to life briefly as F-layer DX territory.

Beware of a fast-rising solar flux. If it rockets up at a rate of three or more points per day, there will be short-lived gain, even a spectacular improvement in muf, but communications disaster isn't far away. When the solar flux peaks out, the K index will surely rise and then up goes the ionospheric absorption of hf signals. High-latitude circuits will fade out first, and the 160- and 180-meter amateur and 120-, 90-, and 75-meter shortwave bands will quickly go to pot. This can be followed by deterioration and blackout of the 60-, 49-, 41-, 40-, and 31-meter bands. Even 25 and 20 meters can go under. But be sure to watch the transequatorial circuits at such times. They may become extraordinarily active somewhere along the line, at least for a brief period of time.

**Summing Up.** Every change in the solar flux can be related to what can be seen on the sun by direct viewing or by projection. If your eyesight and viewing equipment are good and you get frequent looks at the sun under good viewing conditions, you'll be able to keep up with the propagation guessing game about as well as the pro's do. With some experience and understanding of the factors involved in charting WWV information and matching it with sketches of the visible variations of activity on the face of the sun, you'll discover a hobby-within-a-hobby that can be pursued at many levels of sophistication.

This is the time to start tracking the sun, when solar activity is generally low. Spots and groups of spots are presently well spread out. The significance of what is seen is far more easily grasped now than it will be in a few years, when the sun will likely be freckled with spots. ♦

**Editor's Note:** As this article was going to press, there appeared evidence that the entire WWV propagation bulletin service might be terminated. Should this happen, ARRL has plans to air such bulletins over W1AW.

## IN WIRE-WRAPPING HAS THE LINE...

### HOBBY-WRAP-30



**STRIP**



**WRAP**



**UNWRAP**

**OK MACHINE & TOOL CORPORATION**

3455 CONNER STREET, BRONX, NEW YORK, N.Y. 10475 U.S.A. • PHONE (212) 954-8600



TELEX: 125091 TELEX: 232395
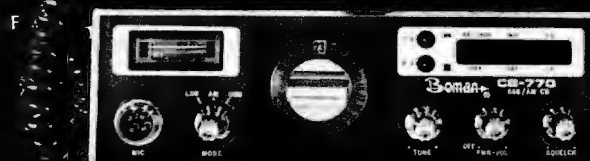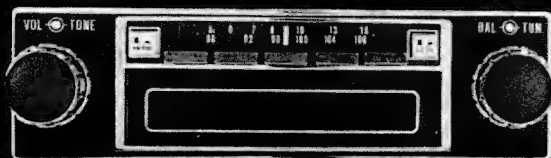
# CB and Stereo in one...in dash



We've got the perfect radio for you who enjoy talking as much as listening. You'll be able to do both with Boman's CBR-9900. It has a 23 channel citizens band transceiver for truckin' down the road or when you're just beatin' around town shootin' the breeze. And when you want music to boogie with, just flip from the CB to the AM/FM stereo radio and let go. This one radio can make your travels more fun than ever before, and you don't have to hassle where to put a second unit because it's CB and Stereo in one . . . in-dash.

- A BM-1335 Deluxe Cassette Stereo Tape Player with AM/FM Stereo Radio
- B BM-1150B 8-Track Tape Player with AM/FM Stereo Radio
- C BM-1125 Deluxe 8-Track Stereo Tape Player with AM/FM Stereo Radio
- D CB-555 23 Channel Citizens Band Transceiver with R.F. Gain Control and Noise Blanker
- E CB-750 23 Channel Citizens Band Noise Free Transceiver with R.F. Gain Control
- F CB-770 23 Channel Single Side Band Citizens Band with Noise Blanker



Whether you want an all in one super radio like the CBR-9900, a conventional citizens band, or an AM/FM stereo radio — (8-track or cassette), check with Boman. We've got 'em all and they all sound great.



**Boman** *Astrosound*

9300 HALL ROAD, DOWNEY, CA. 90241

Toll Free Numbers: Inside California 800-352-2553; Outside California 800-421-2533



# DISAPPEARING ACT

## MOTORIZED CB ANTENNA by FAMOUS ARCHER®



**now you see it.  
now you don't.**



Flip its switch, and the Archer electric antenna extends to its full 33" length *and turns your CB radio on*. Flip again, and it retracts into the fender *and turns your radio off*. Nobody will know you've got ears — it's Archer's automatic answer to CB rip-offs. A top performer that ends the bother of removing your antenna. Adjustable SWR. Center loading coil, excellent for mobile use.

Quality materials and workmanship. Installation hardware and instructions included. Our "disappearing act" is another reason why a million CB'ers will choose Radio Shack's Archer brand this year. Get 21-970 and you'll have something to hide and nothing to lose. Only 59.95\*.

**ASK FOR OUR '77 CATALOG**



FREE! 164 pages, full color, 2000 exclusive items. Come in for your copy today!

LEADING THE WAY IN QUALITY CB SINCE 1960

## Radio Shack®

A TANDY COMPANY • FORT WORTH, TEXAS 76107  
5000 LOCATIONS IN NINE COUNTRIES

\*Price may vary at individual stores and dealers.

# A CB/Ham Selective Calling Project\*

- CODED TONE ACTIVATES RECEIVER
- SILENT CHANNEL UNTIL WANTED

BY MARTIN MEYER

**T**HE ever-increasing activity on the radio communication channels has created an urgent need for a device that will alert you to only those

calls specifically directed at you. Ideally, the device would keep your receiver silent, turning on the audio only when a specially coded signal is re-

ceived. This is exactly what the "Call Selector" described here is designed to do.

The Call Selector eliminates the need for you to monitor the constant "chatter" on the channel to which you are tuned while waiting for a call. The basic one-way Call Selector system consists of an encoder and a decoder (More elaborate arrangements are described later.) The calling party transmits a coded signal on a previously agreed upon channel. You (at the receiving end) leave your transceiver turned on at all times, but you do not hear anything until the special signal is decoded. Then you simply establish contact with no fuss or bother.

The encoded signal consists of a tone whose exact frequency and duration is keyed to the decoder at the receiving end. This tone can be transmitted over any AM, single sideband (SSB), or FM transmitter, making the system usable by CB'ers, hams, and commercial radio operators. There are about 100 combinations of time and frequency that can be selected, ensuring a minimum of false calls even in busy traffic areas. The system is also immune to extraneous noises and voices to further safeguard against false triggering.





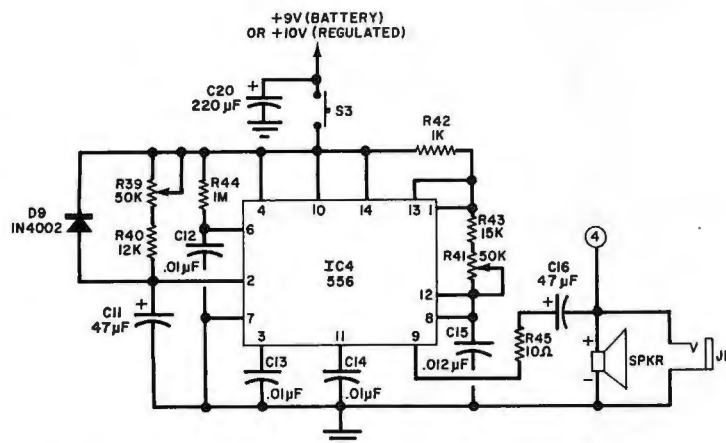


Fig. 1. The encoder uses a timer to generate a tone.

Any number of transceivers can be equipped with the system and tuned to the same frequency/time signal to communicate with each other. For example, you can equip a number of mobile transceivers with only an encoder to allow a base-station operator to listen to only those calls in which he is interested.

**About the Circuit.** The encoder, shown schematically in Fig. 1, consists of dual 556 timer IC4, a small dynamic loudspeaker, and supporting components. Half of IC4 is used as a monostable, or "one-shot," multivibrator, which allows the other timer to free run for a given period of time when activated by closing S3. The output of the second timer is an audio tone with a frequency between 1000


and 4000 Hz. The actual operating frequency is determined by the setting of R41. The width of the monostable multivibrator's output pulse (and thus duration of the audio tone) is controlled by R39 over a range of 1 to 4 seconds. The output of the free-running timer is coupled by R45 and C16 to the speaker.

The encoding tone is acoustically coupled to the microphone of the transmitter with which the Call Selector is being used. This is accomplished by pressing the microphone's housing down on S3 and holding the mike's push-to-talk switch closed for the full duration of the tone. Because the encoder draws no current until S3 is closed, a 9-volt transistor battery is suitable for the power source. However, if a two-way encode/decode sys-

tem is desired, the encoder can be mounted on the same circuit board as the decoder and power can be drawn from a common +12 volt dc or ac supply. (If an on-board encoder is used, C20 should be omitted.) The encoder's output will be the same with either power supply and will be stable over a wide temperature range.

The decoder is shown schematically in Fig. 2. The encoded signal from the receiver is coupled into the circuit through C1 and sensitivity control R1. The signal is passed through C19 and R3 into the inverting (-) input of IC1B. This operational-amplifier stage has a voltage gain of 10 and operates from a single-ended dc power supply, as do all succeeding op-amp stages. Resistors R2 and R4 set the noninverting input of IC1B at approximately half the supply voltage.

The output of IC1B goes to the inverting input of IC1A, which is a very selective bandpass filter whose cutoff frequency can be varied between 1000 and 4000 Hz by R8. When the receiver's audio output contains a component at the center frequency of the filter, a signal appears at the output of IC1A. This signal is coupled by C4 to D1 and D2, which can detect (rectify) it, and the rectified waveform is smoothed by R12, R13, C5, and C6 into a dc voltage. When this dc voltage is applied to Q1, the Darlington transistor conducts and cuts off Q2, at which point, C9 starts charging through R17 and the base-emitter

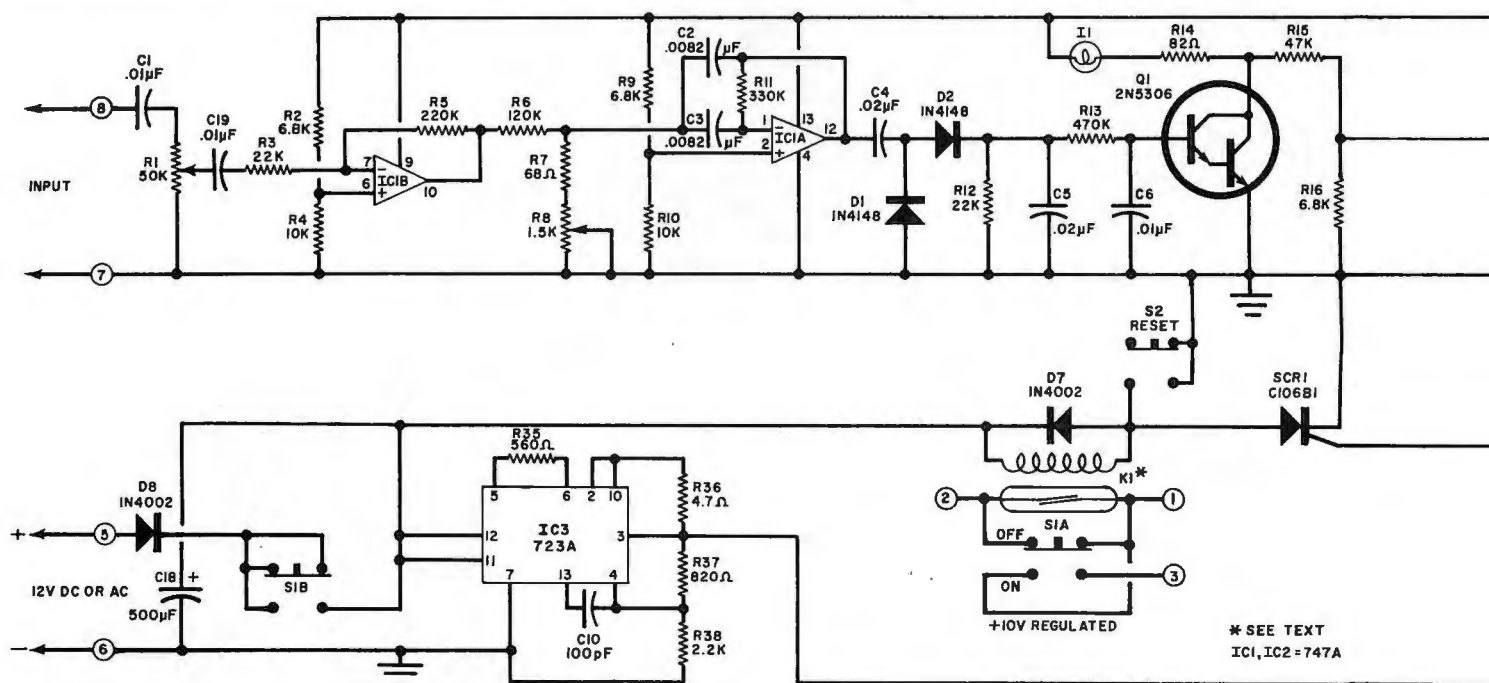

\* SEE TEXT  
IC1, IC2 = 747A

junction of *Q4*. The voltage across *C9* drives *Q3*, the output of which is applied to the noninverting (+) input of *IC2B* and the inverting input of *IC2A* through *R22* and *R26*, respectively.

Normally, the base of *Q6* is positive, and the transistor conducts. However, due to the comparator action of *IC2A* and *IC2B*, the voltage at the base of *Q6* will drop to zero after *C9* begins to charge and then go positive as charging continues. The exact point at which the momentary drop in voltage occurs is determined by the setting of *R20*. Also, *Q5* is always conducting except during the "window" period generated by the charging of *C9*.

Transistors *Q4* and *Q5* are normally conducting as a result of current delivered to their bases through *R29* and *R31*. Both transistors are driven into cutoff only when two conditions are simultaneously satisfied. Transistor *Q5* must be cut off by the drop in the voltage at the output of window generator *IC2*. Transistor *Q4* will be momentarily cut off when the trailing edge of the tone signal discharges *C9*. If these events occur simultaneously, the outputs at the collectors of *Q4* and *Q5* go high and trigger on *SCR1*, which, in turn, energizes reed relay *K1*, closing its contacts. The SCR conducts and the relay remains energized until RESET switch *S2* is closed.

The contacts of *K1* close only when a tone of the proper frequency and time duration is applied to the input of the decoder. Any voice or low-frequency signal that passes through

the active filter will constantly discharge *C9*. This makes the system insensitive to heterodynes, voice components, and noise. For stability, the decoder circuit, except for *K1* and *SCR1*, is powered by voltage regulator *IC3*. If an encoder is mounted on a decoder's circuit board, it will also receive its power from the regulated output of *IC3*.

**Construction.** The encoder and decoder can be assembled on perforated board, using sockets for the IC's, or on a single or separate printed circuit boards. The actual-size etching and drilling and components placement guides for the system are shown in Fig. 3. If you plan to build the encoder and decoder on the same board, use the larger board and install the encoder components in the shaded area of the components placement guide. (Do not forget to omit *C20* in this case.) Alternatively, if you wish to have the encoder and decoder in separate boxes, use both boards, but eliminate the components in the shaded area.

Wire the board or boards as shown, starting with installation of the fixed resistors and nonpolarized capacitors. Then install the electrolytic capacitors, diodes, transistors, and IC's, paying careful attention to polarization, basing, and orientation. Finally, mount the potentiometers, reed relay, and switches. In the author's prototype, *S3* was formed from No. 4 machine hardware and a 1 $\frac{3}{8}$ "  $\times$  1 $\frac{1}{2}$ " (3.5  $\times$  1.3 cm) piece of

springy brass shim stock. The brass shim was formed to take advantage of its natural resilience to keep it from touching the machine screw contact. A short length of wood dowel or plastic rod can be used as the pushbutton for the switch. If you prefer, you can use a standard normally open pushbutton switch, connecting it to the pc board via short lengths of hookup wire

Mount *J1*, *I1*, *I2*, *SPKR*, and the dowel or plastic rod for *S3* (or *S3* itself) on the top of the box in which you house the encoder/decoder. If you are housing the encoder and decoder in separate boxes, install the 9-volt transistor battery for the encoder off the board where it will not interfere with the board, speaker, or *S3*. In either case, mount the activating button of *S3* close to the speaker.

The numbers of the contacts on terminal strip *TS1* on the encoder/decoder components placement guide refer to the same numbered points in Fig. 1 and Fig. 2. This terminal strip provides a convenient means of connecting the system to its power supply, an external speaker, and any other warning device you might want to use, such as a Sonalert, LED, etc., when a properly coded signal is received. The decoder board will also accommodate a Sigma No. 77RE2 dpdt relay in the event the spst reed relay will not provide a sufficient number of contacts.

**Aligning the System.** To get the Call Selector system to operate properly, the decoder must be made to respond


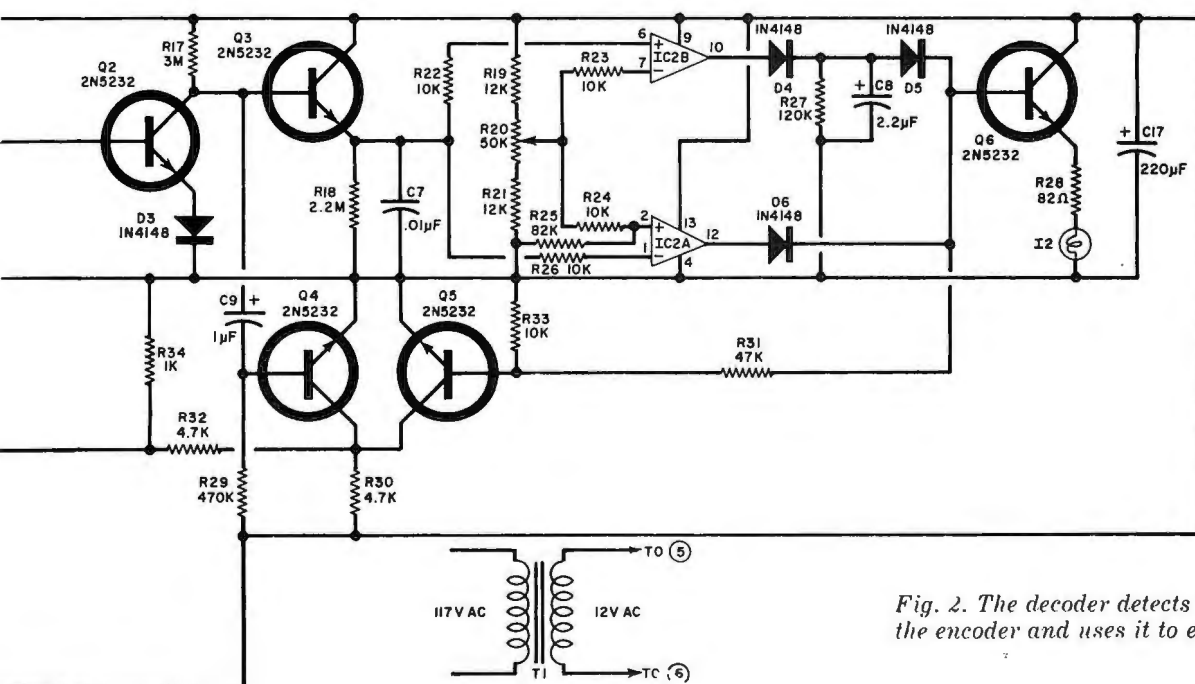


Fig. 2. The decoder detects the audio tone from the encoder and uses it to energize a reed relay.

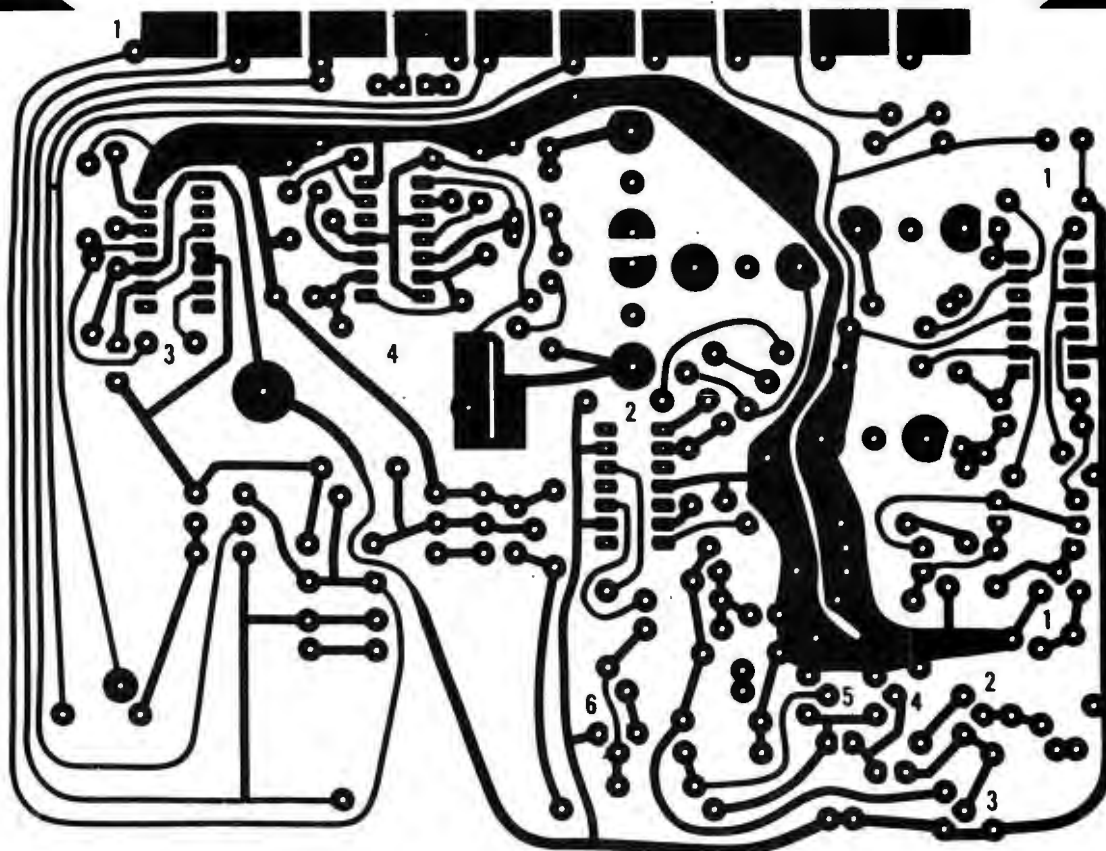



# DECODER PARTS LIST

C1,C6,C7,C19—0.01- $\mu$ F disc capacitor  
C2,C3—0.0082- $\mu$ F, 10% Mylar capacitor  
C4,C5—0.02- $\mu$ F disc capacitor  
C8—2.2- $\mu$ F, 25-volt electrolytic capacitor  
C9—1- $\mu$ F, 25-volt, 5% tantalum capacitor  
C10—100-pF disc capacitor  
C17—220- $\mu$ F, 25-volt electrolytic capacitor  
C18—500- $\mu$ F, 25-volt electrolytic capacitor  
D1 through D6—1N4148 diode  
D7,D8—1N4002 rectifier diode  
I1, I2—6-volt, 100-mA lamp and assembly (Radio Shack No. 272-1535 or similar)  
IC1, IC2—747A dual operational amplifier IC  
IC3—723A voltage regulator IC  
K1—12-volt spst reed relay (or Sigma No. 77RE2 dpdt relay—see text)  
Q1—2N5306 npn Darlington transistor  
Q2 through Q6—2N5232 npn silicon transistor  
R1,R20—50,000-ohm trimmer potentiometer  
R8—1500-ohm trimmer potentiometer  
Following resistors are  $\frac{1}{4}$  watt, 5% tolerance:  
R2,R9,R16—6800 ohms  
R3,R12—22,000 ohms  
R4,R10,R22,R23,R24,R26,R33—10,000 ohms  
R5—220,000 ohms  
R6,R27—120,000 ohms  
R7—68 ohms  
R11—330,000 ohms  
R13,R29—470,000 ohms  
R14,R28—82 ohms  
R15,R31—47,000 ohms  
R17—3 megohms

R18—2.2 megohms  
R19,R21—12,000 ohms  
R25—82,000 ohms  
R30,R32—4700 ohms  
R34—1000 ohms  
R35—560 ohms  
R36—4.7 ohms  
R37—820 ohms  
R38—2200 ohms  
S1—Dpdt pushbutton switch  
S2—Spdt pushbutton switch  
SCR1—C106B1 silicon controlled rectifier  
T1—12-volt, 500-mA transformer  
TS1—8-contact screw-type terminal strip  
Misc.—Perforated or printed circuit board; suitable chassis box; hookup wire; machine hardware; solder; etc.

Note: The following items are available from Netronics Research & Development, Rte. 6, Bethel, CT 06801. Complete kit of parts with instructions for one-way system which includes separate encoder and decoder, wood case for decoder, and plastic case with visor clip for encoder (Kit N5000), \$44.95 + \$1.50 postage; Separate encoder kit with plastic case, visor clip and instructions (Kit N6000), \$14.95 + \$1 postage and handling; Combination encoder/decoder for two way system which includes all parts, instructions, a wood case and built-in heavy-duty speaker (Kit N7000), \$49.95 each + \$1.50 postage and handling. Also available separately: decoder pc board, \$5.25; encoder pc board, \$3.95; reed relay, \$2.60, 12-volt transformer, \$2.75; S3 encoder switch and plunger, \$1.30. Add \$1 postage and handling for separate parts orders.

to the selected frequency/duration characteristics of the encoder's output signal. To align a system consisting of separate encoder and decoder, you will need a shielded cable terminated at one end in a plug that mates with jack J1 in the project. Connect the "hot" lead of the cable terminal 8 and the shield to terminal 7 of TS1. For a system in which the encoder and decoder are on the same board, simply connect a jumper between terminals 4 and 8. This allows the system to be calibrated by direct interconnection, rather than by transmitting test tones on the air.

Connect power to the system. Set R1 in the decoder and R39 in the encoder to maximum clockwise and R8, R20, and R41 for center of rotation. Depress S3 and hold it down for the full duration of the test tone while adjusting R41 until I1 glows. This sets the encoder for the maximum 4-second tone duration. It may be necessary to repeat this procedure several times before R41 is properly set.

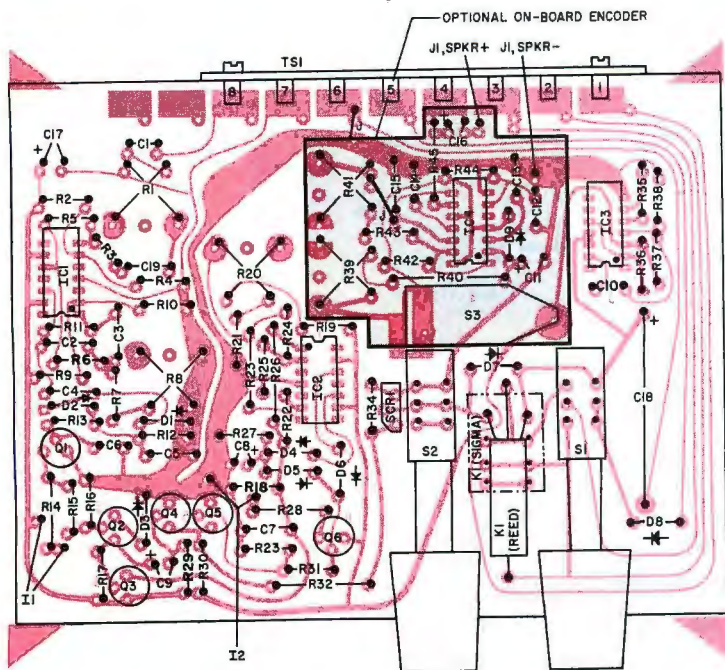


Fig. 3. If you want encoder and decoder together, use board on opposite page and install all components as above. For separate units, leave off components in shaded area above and build separate encoder board shown below.

#### ENCODER PARTS LIST

C11—47- $\mu$ F tantalum electrolytic capacitor  
 C12, C13, C14—0.01- $\mu$ F disc capacitor  
 C15—0.012- $\mu$ F, 10% Mylar capacitor  
 C16—47- $\mu$ F, 25-volt electrolytic capacitor  
 C20—220- $\mu$ F, 25-volt electrolytic capacitor (see text)  
 D9—1N4002 rectifier diode  
 IC4—556 dual timer IC  
 J1—Miniature phone jack  
 R39, R41—50,000-ohm trimmer potentiometer



Following resistors are  $\frac{1}{4}$  watt, 5% tolerance:

R40—12,000 ohms  
 R42—1000 ohms  
 R43—15,000 ohms  
 R44—1 megohm  
 R45—10 ohms

S3—Spst switch (see text)

SPKR—8-ohm,  $2\frac{1}{4}$ "-diameter dynamic speaker

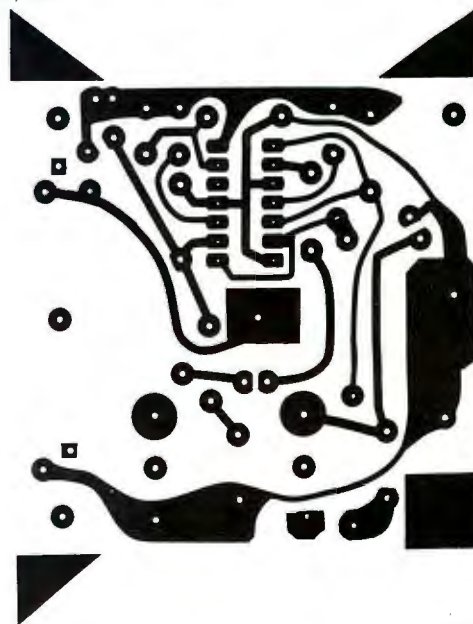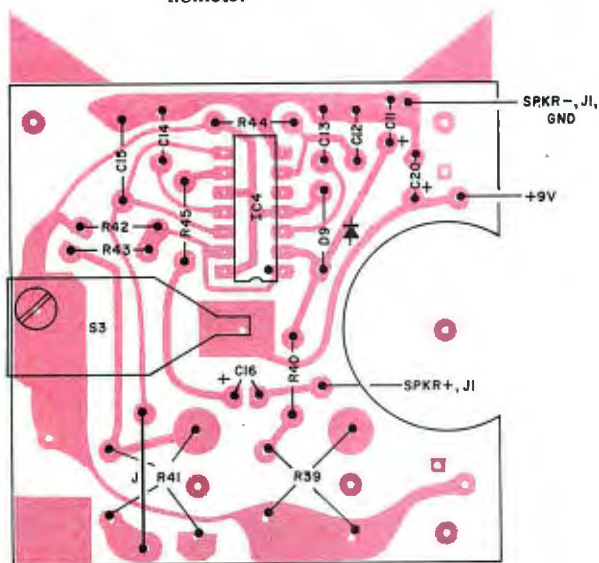Misc.—Perforated or pc board; suitable chassis box (if assembled separately); machine hardware; hookup wire; solder; etc.



Once I1 comes on while S3 is depressed, I2 should blink about half way through the tone burst. Adjust R39 so that I1 turns off just after I2 blinks. Once this adjustment has been made, depress RESET switch S2.

Connect an ohmmeter between terminals 2 and 3 on TS1. The meter should indicate an open circuit. With power switch S1 off, the ohmmeter should indicate short circuit (zero ohms) with S1 on. Depress S3 for the full duration of the tone burst; I1 should turn off immediately after I2 blinks and the meter should indicate a short circuit. Depress S2; the relay's contacts will open and the meter should indicate an open circuit. If you do not obtain the proper results, repeat the alignment procedure until you do.

**In Use.** You can recalibrate the Call Selector system for any frequency between 1000 and 4000 Hz and for any tone duration between 1 and 4 seconds. Sensitivity control R1 can be set for any desired signal level threshold. In practice, you use the microphone to



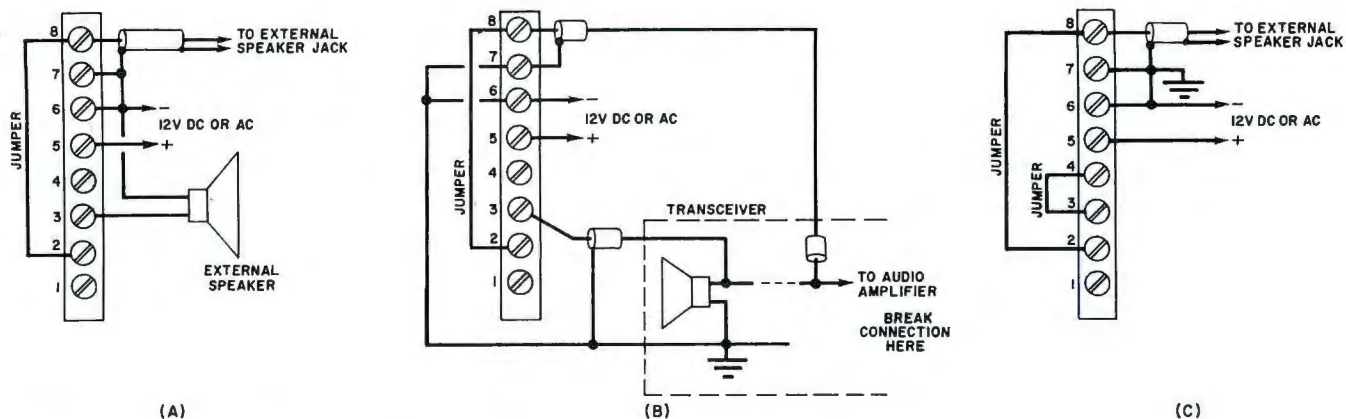


Fig. 4. Ways to use the system: with external speaker (A); with transceiver's speaker (B); and with the combination encoder/decoder's internal speaker (C).

depress S3, holding the mike's pickup element directly over the Call Selector's speaker for the entire duration of the tone burst. This keeps the activating signal modulating the carrier at a constant level because the mike will be stationary with respect to the speaker.

There are several different ways to connect the system to your transceiver, three of which are illustrated in Fig. 4. If you plan to use the decoder with an external speaker and do not want to touch the "insides" of the transceiver, follow the wiring scheme

detailed in Fig. 4A. Use a length of shielded cable to transfer the audio signal from the receiver's external-speaker jack to the decoder's terminal strip. Terminate the cable with a plug that mates with the transceiver's jack.

You can wire the system to the transceiver's internal speaker as shown in Fig. 4B. This connection requires a slight rewiring of the transceiver's circuit. Break the connection between the audio output stage and the speaker. Rewire the circuit as shown, using shielded cable. When the relay contacts close, the

audio path to the internal speaker will be completed.

The diagram shown in Fig. 4C is for systems in which the encoder and decoder are assembled on the same board. This wiring scheme allows you to use the decoder/encoder's built-in speaker as an encoder transducer and as the transceiver's external speaker.

For all three interconnections detailed in Fig. 4, the decoder can be bypassed by placing S1 in the OFF position. The receiver's audio signal will then be applied directly to the internal or external speaker. ♦



## Fix it Quick... with an Ungar® Cordless Quick-Charge Soldering Iron

- Cordless portability
- Quick 4-hour charge
- Holder automatically charges high performance NI-CD battery
- Rigid coaxial tip rotates to desired working position
- Easy-touch switch, tunnel light
- Quick heat-up

### SPECIAL OFFER

#### Free Micro-Spade Element Tip

Present this coupon to your local participating Ungar electronic distributor and receive a FREE #195 Micro-Spade Element Tip worth \$1.99 with your purchase of a #200 QUICK-CHARGE CORDLESS SOLDERING STATION.

HURRY! Offer EXPIRES December 1, 1976.



Division of Eldon Ind., Inc. • Compton, CA 90220







# TIE INTO HAM REPEATERS WITH THIS LOW-COST AUTOPATCH

*Crystal-controlled Touch-Tone®  
pad for initiating telephone  
calls from vehicles.*

BY JOE JARRETT

**A**N INCREASINGLY important part of amateur radio operation these days is the vhf/uhf repeater (automatic relay station) and its common accessory, the autopatch. A repeater is usually located on top of a high building, a tower, or a mountain and in many cases it is able to increase the usual 3-to-10-mile range of low-power equipment to more than 100 miles.

An autopatch is an automatic telephone patch that enables repeater users to initiate and dial telephone numbers from a vehicle or hand-held transceiver without assistance from a phone operator or other amateur stations. An autopatch is legal as long as it is not used to avoid toll charges and approved interface equipment connects the repeater to the phone line.

Most repeaters operate under remote control (not legal for CB radio use) and many of them have autopatch provisions. There must be a way of remotely turning these systems on and off in case of equipment malfunction or illegal use. Also, the users of autopatch must have a way of connecting or disconnecting the telephone line to the repeater phone patch and dialing the desired number.

One of the easiest ways to accomplish these jobs is by using the Touch Tone® approach.

The Touch Tone system uses eight different audio tones at frequencies carefully selected not to be harmonically related. The keyboard is arranged in rows (horizontal) and columns (vertical) so that, when a particular key is depressed, two tones are generated—one for the row and the other for the column. These tones are then transmitted to the remote decoding equipment that "recognizes" the tones being transmitted as one of ten digits or six special codes (\*, #, A, B, C, D). The four letters are extra keys and are not the same as those on conventional number keys. They are used in military systems and some computers.

Recently, the Mostek Corp. announced two dual-tone, multi-frequency (DTMF) generators, MK5085 and MK5086, that can be used to build a low-cost (under \$25) Touch-Tone encoder. The only difference between the two IC's is in the method of keyboard entry. In the MK5086 (used in this project), the row and column keys are switched to the positive supply when a key is operated. The

MK5085 uses a calculator-type scanning technique that allows the use of single-pole switches on the keyboard.

**Circuit Operation.** The complete circuit is shown in Fig. 1. The reference frequency is determined by a conventional 3.579 MHz color-TV crystal, with R5 used as the bias resistor. Operating one of the pushbuttons on the keyboard starts the oscillator. (See box for details of IC operation.)

The TONE output of IC1 (pin 16) is coupled to modulation level potentiometer R3, whose rotor is connected through R4 and C3 to the transmitter microphone input. The circuit consisting of IC2, an audio power amplifier, is used to drive an internal loudspeaker for monitoring the tones, while R2 determines the speaker volume.

Operational amplifier IC3 is used as a 0-4-second timer for the transmit hold-on delay. The MUTE output (pin 10) of IC1 is held to ground when no key is depressed. Thus capacitor C4 is discharged through R6 to cause the non-inverting (+) input of IC3 to be at ground. The inverting input (−) is at a voltage level determined by the setting of hold-on time potentiometer R7.



Since the voltage at pin 5 is lower than the voltage at pin 4, the output of IC3 (pin 10) is at ground so both Q1 and Q2 are turned off. These two transistors are connected in a Darlington configuration and are used to key the push-to-talk (PTT) line of the transmitter when they are turned on.

When a key is depressed, the MUTE output of IC1 is pulled up to the positive supply. Diode D1 becomes forward biased and C4 is charged (within several milliseconds) to the positive supply less the diode drop of D1. The (+) input of IC3 is now at a higher voltage than the (-) input so the output of IC3 switches to the positive supply. Resistors R8 and R9 reduce the drive to the transistors. When Q1 turns on, so does Q2 and the PTT line is pulled down to the ground level. This causes the transmitter to key and transmit the tone signal.

When the key is released, the MUTE



View of the inside of the author's prototype.


output drops, D1 becomes reverse biased, and C4 begins to discharge through R6. As this happens, the vol-

tage on the (+) input of IC3 decreases until it is no longer greater than the voltage on the (-) input. At this time, the output of IC3 switches to the ground level, thus turning off the two transistors and stopping the transmitter. Capacitor C4 will not discharge far enough for this to happen however as long as the keys are operated reasonably fast. Complete discharge will occur after the last key entry and depends on the setting of R7.

The value of resistor R4 is the coarse adjustment of the tone level. Depending on the transmitter used, the value of R4 can range from 1000 to 100,000 ohms.

Some older types of equipment may require high current for keying, or may key the positive supply instead of ground. In this case, a low-current relay can be used in the PTT line (connected to the 12-volt supply), with the relay contacts keying the transmitter.

Fig. 1. Outputs of IC1 drive audio amplifier and operate transmitter PTT circuit.

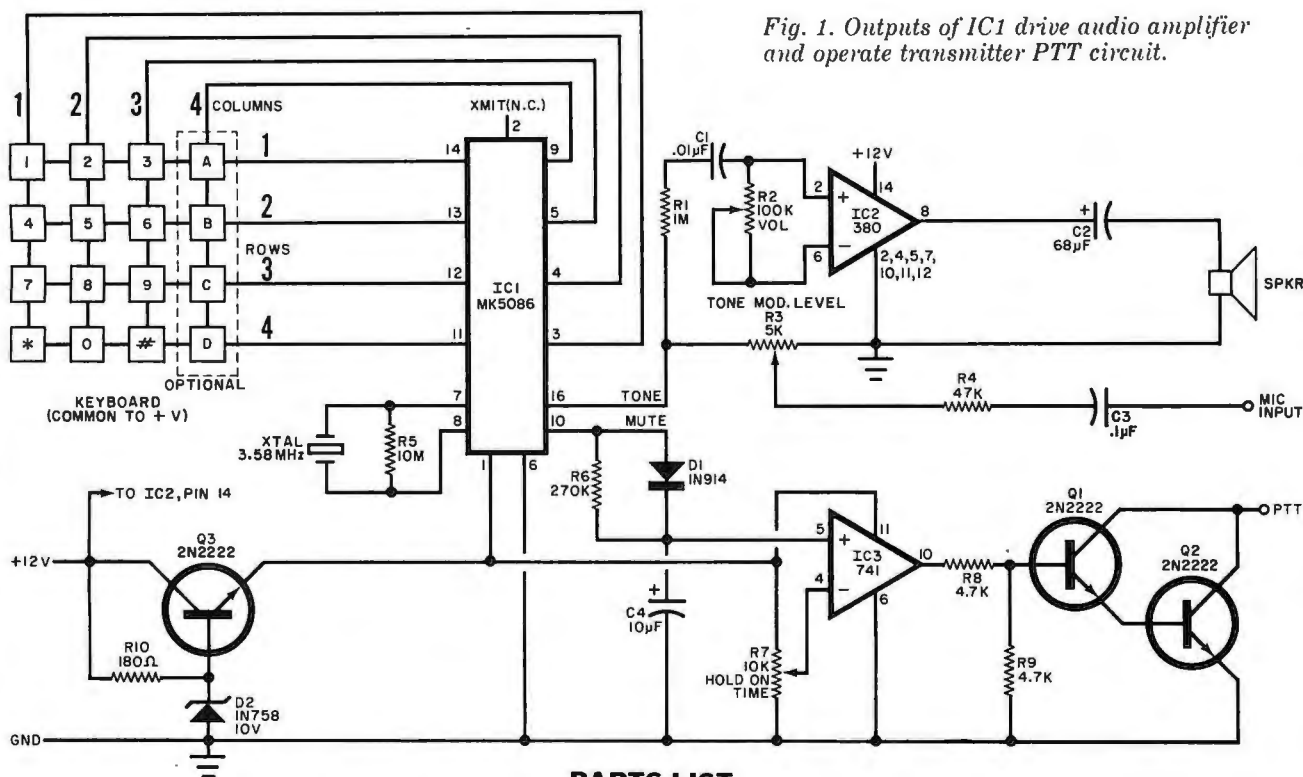

#### PARTS LIST

C1—0.01μF, 50-V disc capacitor.  
C2—68-μF, 25-V electrolytic capacitor  
C3—0.1-μF, 50-V disc capacitor  
C4—10-μF, 25-V electrolytic capacitor  
D1—1N914 diode  
D2—1N758, 10-V zener diode  
IC1—MK5086, DTMF generator (Mostek)  
IC2—LM380 audio power amplifier (National)  
IC3—741 op amp  
KEYBOARD—Digitran Corp. KL54 (12 keys); KL0049 (16 keys)


Q1, Q2, Q3—2N2222 transistor (or similar)  
R1—1-megohm resistor  
R2—100,000-ohm pc potentiometer (see text)  
R3—5000-ohm pc potentiometer  
R4—47,000-ohm resistor (see text)  
R5—10-megohm resistor  
R6—270,000-ohm resistor  
R7—10,000-ohm pc potentiometer  
R8, R9—4700-ohm resistor  
R10—180-ohm resistor

SPKR—8-ohm, small diameter loudspeaker  
XTAL—3.57 9545 MHz color-TV crystal  
MISC.—Suitable chassis 4¼" × 2½" × 1½" (Vero Co. #90-20-087), 4-lead flexible cable, mounting hardware, etc.  
Note: The following is available from S. D. Sales, Box 28810, Dallas, TX 75228: kit of all parts except chassis, speaker, and interconnecting cable at \$22.50 plus \$0.75 for postage.
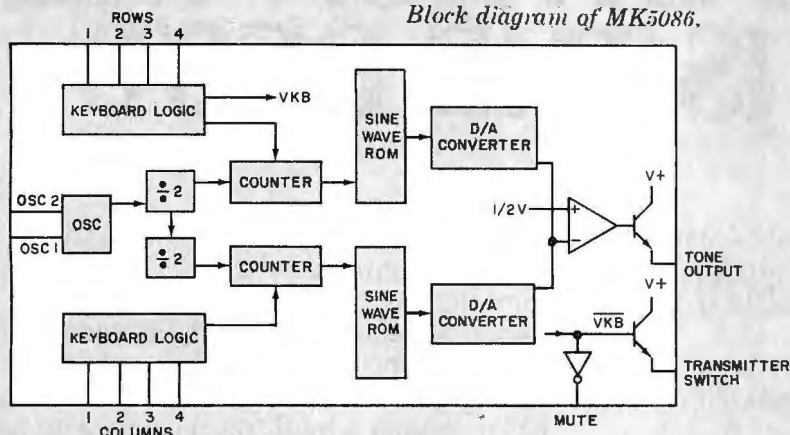
## IC OPERATION

As shown in the block diagram of the MK5086, the row and column select keys are switched to the positive supply in the standard 2-of-8 format. (One key operates both the selected row and column.


The output of the crystal oscillator is divided by two counters—one for the rows and the other for the columns—and the amount of frequency division is determined by the keyboard entry switching.



Each sine-wave synthesizer is formed by a 5-bit, 32-state counter, decode ROM, and R-2R ladder network D/A converter. The output of each D/A converter

Block diagram of MK5086.

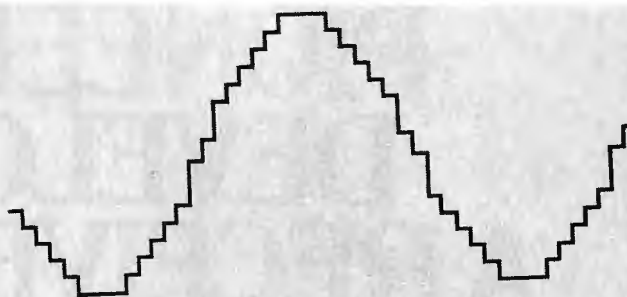is the 26-step sine wave shown in the waveform diagram. Six steps are missing out of the possible 32 to give the best-fit, least-distortion sine wave.



Output of D/A converter.

The two waveforms (row and column) are mixed in an op amp (on chip) to produce a true dual-tone signal. This is fed to a bipolar transistor (on chip) that supplies enough current to drive a 1000-ohm load to a typical 450 mV for the row tones and 640 mV for the column tones. (Telephone specifications require that the column tones be 2½ dB greater in amplitude than the row tones.)

Besides the TONE output, the MK5086 has outputs called XMIT (pin 2) and MUTE (pin 10). The XMIT output is an npn bipolar transistor that is turned on and pulls to the positive supply when no keys are operated. It is an open circuit when any key is depressed. The MUTE output is a standard CMOS circuit that is at the negative supply (when used) and switches to the positive supply when a key is depressed.

**Construction.** The entire circuit can be assembled on a small pc board. An etching and drilling guide and component placement are shown in Fig. 2. Observe the polarities of diodes and polarized capacitors. Sockets for the IC's are optional. Note that IC1 is a CMOS device and must be handled with the usual precautions. The IC comes in a shorting carrier and should be kept in the carrier until time for installation. Handle it only by the

edges of the plastic package. In soldering the CMOS IC, use a clip lead between the soldering iron tip and the positive foil pattern on the board. Note also that volume control *R2* is mounted on the control board. If remote control is needed, use an out-board potentiometer and run the connecting leads to the *R2* pads on the board.

After all components are installed, connect the leads for the keyboard

and accessory cable. The latter should have four leads (PTT, microphone, ground, +12 V) and should be as long as necessary for the installation. The physical size of the keyboard will determine the finished size of the project and the case used to hold it. The 9-pin connector shown in the photograph was used to connect the project to an IC-230 transceiver.

**Operation.** After assembly, power up the system and determine the correct value for the combination of *R3* and *R4* to produce the required modulation level.

The dialer enables hands-off operation without annoying carrier drop between each dialed digit. The amount of hold-on time can be set by adjusting *R7*. The speaker volume is adjusted by *R2*.

The dialer should produce no r-f interference. A 5-watt rig has been keyed with its antenna resting on the dialer box with no discernable effect.

Because each section of the country has different rules regarding how to use repeaters, you must check your local repeater group for details before using the dialer.


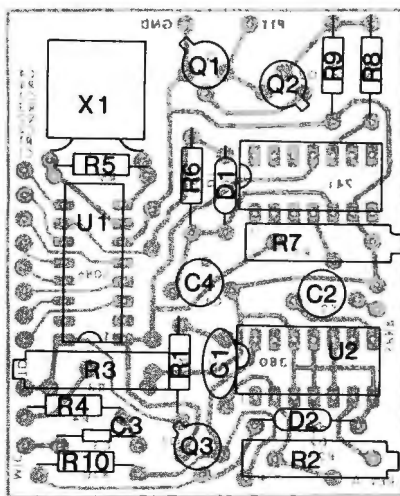


Fig. 2. Etching and drilling guide (left) and component placement.

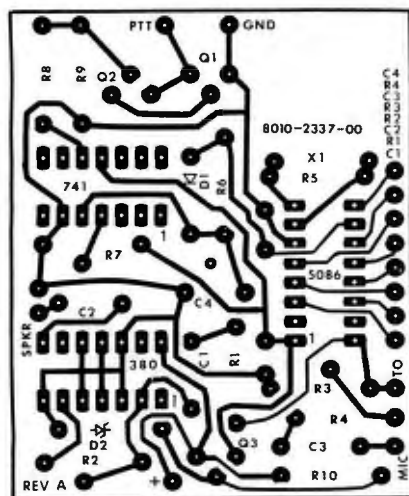

# PIONEER HAS DEVELOPED A RECEIVER EVEN THE COMPETITION WILL ADMIT IS THE BEST.

One look at the new Pioneer SX-1250, and even the most partisan engineers at Marantz, Kenwood, Sansui or any other receiver company will have to face the facts.

There isn't another stereo receiver in the world today that comes close to it. And there isn't likely to be one for some time to come.

In effect, these makers of high-performance receivers have already conceded the superiority of the SX-1250.

Just by publishing the specifications of their own top models.

As the chart shows, when our best is compared with their best there's no comparison.

To begin with, the SX-1250 is at least 28% more powerful than any other receiver ever made. Its power output is rated at 160 watts per channel minimum RMS at 8 ohms from 20 to 20,000 Hz, with no more than 0.1% total harmonic distortion.

And, for critical listening, no amount of power is too much. You need all you can buy.

To maintain this huge power output, the SX-1250 has a power supply section unlike any other receiver's, with a large toroidal-core transformer and four giant 22,000-microfarad electrolytic capacitors.

But power isn't the only area in which the SX-1250 excels. The preamplifier circuit has an unheard-of phono overload level of half a volt (500 mV). This means that no magnetic cartridge in the world can drive the preamp to the point where it sounds strained or hard. And the equalization for the RIAA recording curve is accurate within

$\pm 0.2$  dB. A figure unsurpassed by the costliest separate preamplifiers.

Turn the tuning knob of the SX-1250, and you'll know at once that the AM/FM tuner section is also special. The tuning mechanism feels astonishingly smooth, precise and solid.

FM reception is loud and clear even on weak FM stations because the tuner combines extremely

high sensitivity with highly effective rejection of spurious signals.

Of course, the Pioneer SX-1250 carries a price tag commensurate with its position at the top. But if you seek perfection you won't mind paying the price.

If, on the other hand, you'd mind, look into the new Pioneer

SX-1050 or SX-950. They're rated at 120 and 85 watts, respectively, per channel (under the same conditions as the SX-1250) and their design is very similar. In the case of the SX-1050, virtually identical.

That means you don't just come to Pioneer for the world's best.

You also come to us for the next best.

For informational purposes only, the SX-1250 is priced under \$900. The actual resale price will be set by the individual Pioneer dealer at his option.




**PIONEER®**

Anyone can  
hear the difference.

U.S. Pioneer Electronics Corp., 75 Oxford Drive, Moonachie, New Jersey 07074.

CIRCLE NO. 73 ON FREE INFORMATION CARD

	PIONEER SX-1250	MARANTZ 2325	KENWOOD KR-9400	SANSUI 9090
POWER, MIN. RMS, 20 TO 20,000 HZ.	160W+160W	125W+125W	120W+120W	110W+110W
TOTAL HARMONIC DISTORTION	0.1%	0.15%	0.1%	0.2%
PHONO OVER- LOAD LEVEL	500 mV	100 mV	210 mV	200 mV
INPUT: PHONO/AUX/MIC	2/1/2	1/1/no	2/1/mixing	1/1/mixing
TAPE MON/DUPL.	2/yes	2/yes	2/yes	2/yes
TONE	Twin Tone: Bass-Bass- Treble-Treble	Bass-Mid- Treble	Bass-Mid- Treble	Bass-Mid- Treble
TONE DEFEAT	Yes	Yes	Yes	Yes
SPEAKERS	A,B,C	A,B	A,B,C	A,B,C
FM SENSITIVITY (IHF '58)	1.5 $\mu$ V	1.8 $\mu$ V	1.7 $\mu$ V	1.7 $\mu$ V
SELECTIVITY	83 dB	80 dB	80 dB	85 dB
CAPTURE RATIO	1.0 dB	1.25 dB	1.3 dB	1.5 dB

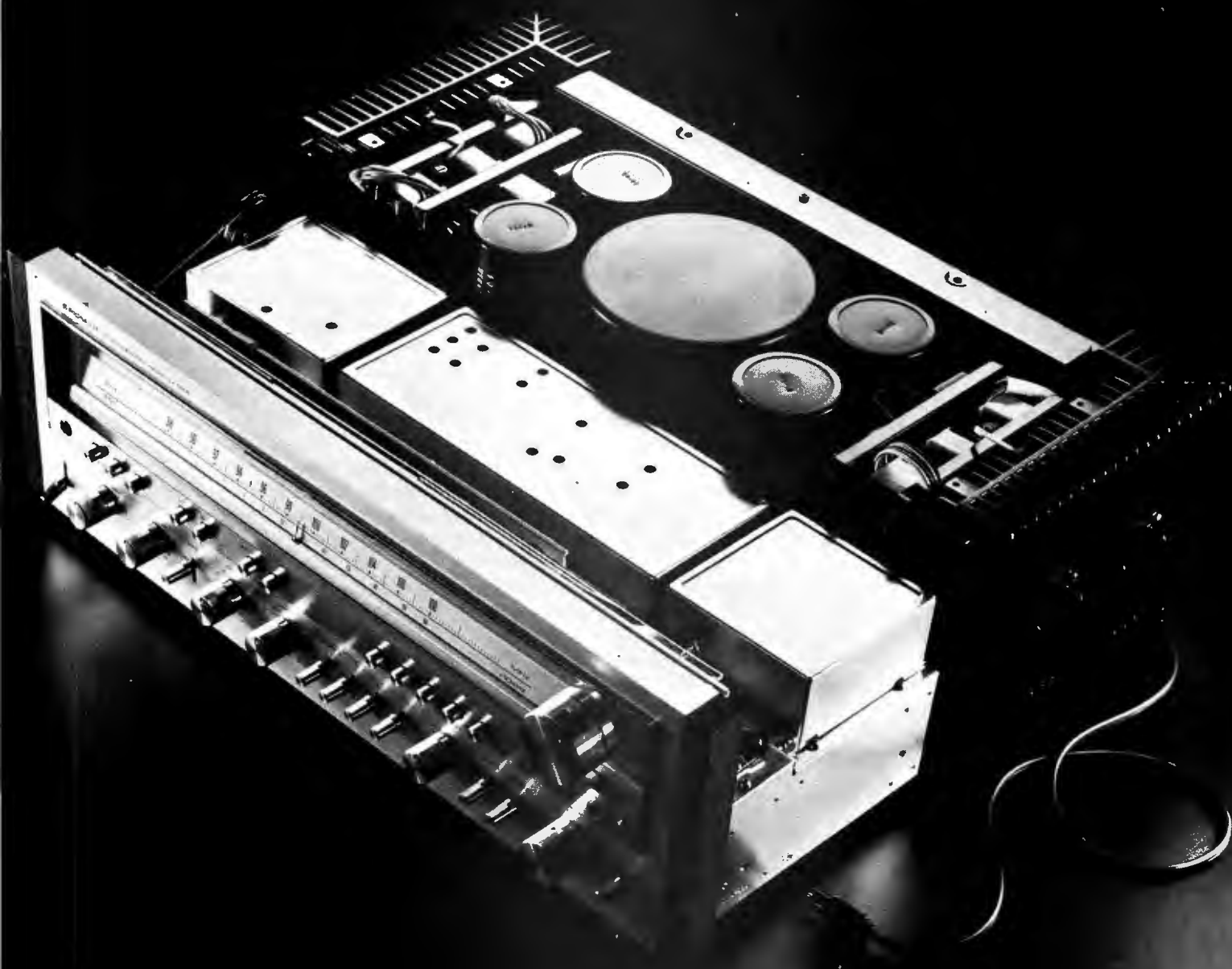



# PROTECTING YOUR POWER SUPPLY

*Components in modern power supplies cost too much to leave them unprotected from shorts, overloads, etc.*

BY ROBERT C. ARP, JR.

**T**HE COST of modern sophisticated power supplies is high enough to warrant as much consideration for their protection as that given to their rectification and regulation circuits. While fuses and circuit breakers have been the traditional means of protecting power supplies, they are often not fast enough to prevent solid-state devices in newer supplies from destructing due to overloads and the like. The devices most able to protect semiconductors are other semiconductors.

Here are ways to protect a power supply from the three primary causes of failure: shorted output; shorted filter capacitors; and excessive current through the load. There are two general methods of protection. The first is the control of the transformer's primary circuit. The second is the removal of base drive from a transistor in series with a load.

In either case, we will assume that the protection circuit is part of a more complex power supply. High-current power supplies are used in some examples simply to indicate that the methods of protection are not limited to low-current applications. Obviously, devices with lower current and power ratings can be used where possible.

**Primary Circuit.** The block diagram in Fig. 1 shows a basic method of power supply protection. Characteristic of this arrangement is the triac in series with the primary of the transformer. During normal operation, the

trigger control allows the trigger circuit to apply a brief gate signal to the triac for every alternation of the ac line voltage. After the triac is turned on by the gate signal, it remains on for the complete half cycle until the zero-crossing point is reached at the end of the alternation.

If the trigger control inhibits the trigger circuit while the triac is conducting, the triac cuts off when the line voltage approaches zero. It remains off until another gate signal is applied. Hence, the ac input to the transformer can be removed within a half cycle of the line voltage by designing the transformer's secondary circuit to inhibit the trigger circuit when a filter-capacitor short or supply output overload occurs.

The circuit shown in Fig. 2 is one type of control technique used in the primary circuit of a power supply. Under normal conditions, the gate of triac Q1 receives a brief gate signal from the IC2 zero-voltage switch at the beginning of each line alternation while the line voltage is near zero. Resistor R1, in series with the MT2 terminal of Q1 and gate terminal of Q2, permits a continuous flow of alternating current through the gate of Q2. The primary of T1, in series with Q2, receives the full ac line voltage under these conditions.

Zero-voltage switch IC2 can be used to provide pulses that are synchronized with the time of zero voltage in the ac cycle to the gate of a triac. Triac firing can be inhibited by the application of a positive (TTL-compatible) voltage to pin 1 of IC2.

The triple 3-input NAND gate used for IC1 converts short-circuit logic-0 conditions to a logic-1 condition for inhibition of IC2. (A 5-volt dc supply was used for the IC's power and, consequently, for the inhibit signal.)

The inhibit signal appears at pin 1 of

IC2 when points A or B (at Q3) are shorted to point O (common). With IC2 inhibited, Q1 cannot provide ac to flow through the gate of Q2. When the line voltage falls to zero at the end of the alternation, during which the short occurs, Q2 will cut off and remain off. After the short condition is removed, Q1 turns on with the next gate signal from IC2 and the system returns to normal operation.

If no filter capacitors were used (as in a simple battery-charging circuit), the self-resetting action would take place within one alternation of ac line voltage. Unfortunately, the inclusion of filter capacitors in the secondary circuit causes a resetting time lag on the order of one second for each 1000  $\mu$ F used. If the resetting time is of no concern, no other consideration need be given this point. If you desire quick resetting time, you can do one of two things: First, include a dpst reset switch to momentarily break the connections between points A and B and IC2. Secondly, you can omit the connection between point A and IC1 and include an isolation diode in the secondary circuit (Fig. 3); IC2 will not, however, be inhibited by a shorted filter capacitor.

The circuit in Fig. 2 will not reset if a short occurs across the output terminals while a load is connected. In such a case, the load must be removed, or a reset switch must be used as explained above.

Although Q2 will remove power from T1's primary immediately when the output terminals of the supply are shorted, a spark will occur. The amplitude of the spark can be considerably reduced by incorporating the transistor stage shown in Fig. 3.

**Removing Base Drive.** If a transistor is placed in series with the output terminals of a power supply, an ar-

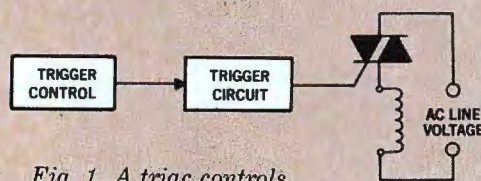


Fig. 1. A triac controls voltage across primary.



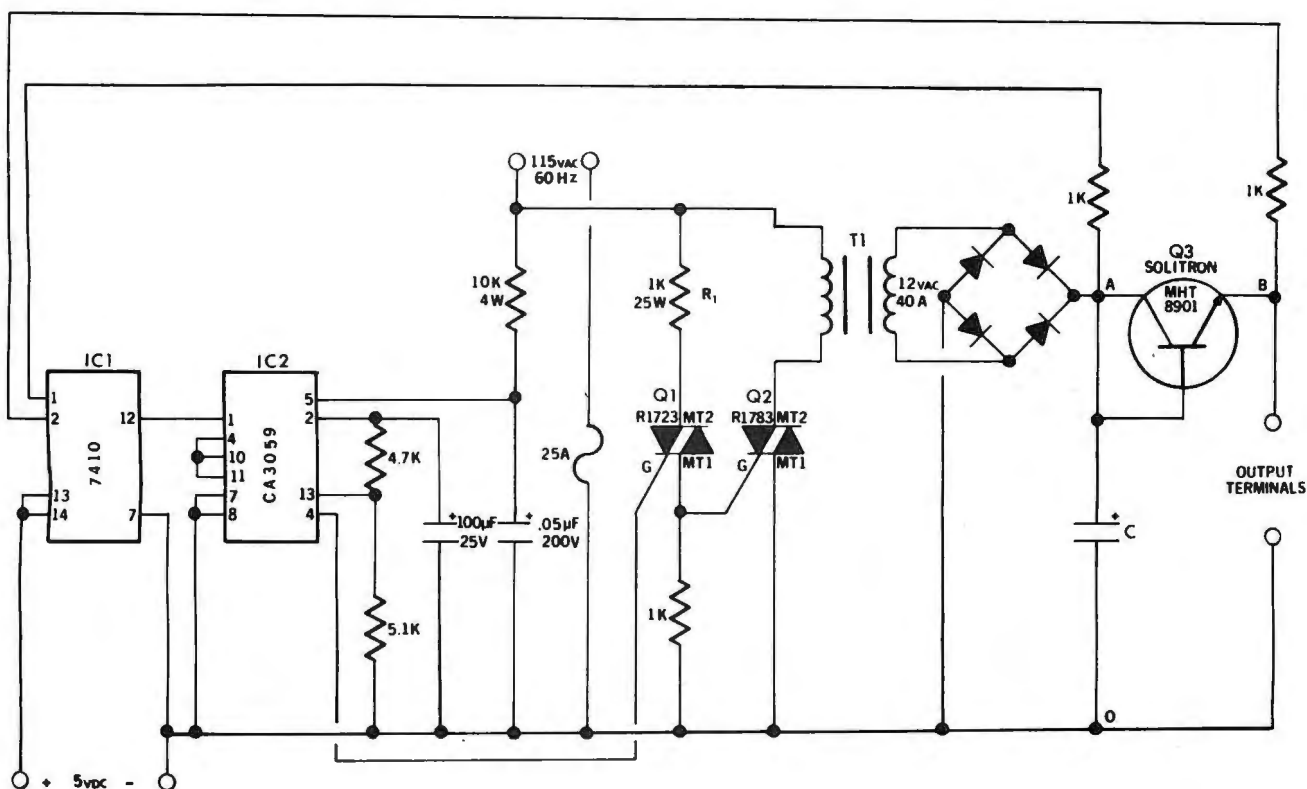


Fig. 2. One type of control technique used in the primary circuit.

range commonly used in series voltage regulators, the secondary circuit can be turned off by any action that removes base drive from this transistor. This can be done by shunting the base to ground with an SCR, optical coupler, or another transistor.

A method of removing base drive with an SCR when a desired maximum flow of current is exceeded is shown in Fig. 4. By varying  $R_k$  and  $R_s$ , the transistor can be cut off at any desired level of current flowing through the output of the supply.

Under normal operating conditions, the transistor is biased on by  $R_b$ . The current flowing through the output develops a voltage drop across  $R_s$ . Because a very low amplitude gate voltage is needed to trigger on the SCR, the resistance and power rating of  $R_s$  can be relatively small for high-current applications. The voltage drop across  $R_s$  is used to provide a gate signal for the SCR that is proportional to the level of the current flowing through the load. If the resistance of  $R_s$  is high enough, the level of load current at which the SCR shunts the transistor's base drive to ground can be varied by  $R_k$ . When the voltage drop across  $R_s$  is sufficient to trigger on the SCR, the transistor cuts off within microseconds. (A reset switch must be provided as shown to return the circuit to normal operation.)

Because of  $R_b$ , the transistor must

operate in the active region. If the resistance of  $R_b$  is too low, the SCR will be required to handle a large current. Conversely, if the resistance of  $R_b$  is too high, the transistor will be forced to dissipate considerable power. Usually, a value for  $R_b$  must be chosen to keep the transistor's power dissipation and the current through the SCR at reasonable levels. The necessary current rating of the SCR can be determined (after  $R_b$  is chosen to provide the desired transistor power dissipation) by dividing the input voltage by the value of  $R_b$ .

Assume you're working with the following components and conditions:  $V_{in} = 34$  volts dc,  $C = 18,300 \mu F$  (40 V),  $R_b = 30$  ohms (50 W),  $R_k = 1780$  ohms,  $R_s = 2.2$  ohms (220 W), SCR = 2N682, and  $Q = \text{HEP S7000}$ . Here, the SCR will trigger on when the current reaches 10 A. You can also measure the following parameters:  $V_{CE} = 11.5$  V dc,  $V_{BE} = 1.5$  V dc,  $I_B = 350$  mA, and  $I_{SCR} = 1.1$  A. And the power dissipation of the transistor can be found by using the for-

mula  $P_D \approx V_{CE} I_C$ , which would yield 115 watts.

Light-emitting diodes can be switched on and off in nanoseconds, and optical couplers with transistor detectors can switch at speeds of 2 to 5  $\mu s$ . It is logical, therefore, to consider a protection system based on these high-speed devices. A typical optical coupler protection circuit is shown in Fig. 5.

It is not necessary for the series transistor in Fig. 5 to dissipate large amounts of power because this transistor ( $Q1$ ) can be operated in or near the saturation region. Heavy base drive is applied to  $Q1$  through  $Q2$  according to the formula  $I_{B(Q1)min} = I_{C(Q1)} / h_{FE(Q1)}$ , where  $I_{B(Q1)min}$  is the minimum base current that assures saturation of  $Q1$ ,  $I_{C(Q1)}$  is the maximum expected collector current, and  $h_{FE(Q1)}$  is the minimum expected  $h_{FE}$ . Transistor  $Q2$  is used to supply base drive for  $Q1$  so that only  $Q2$ 's relatively small base current need be shunted to ground to turn off  $Q1$ .

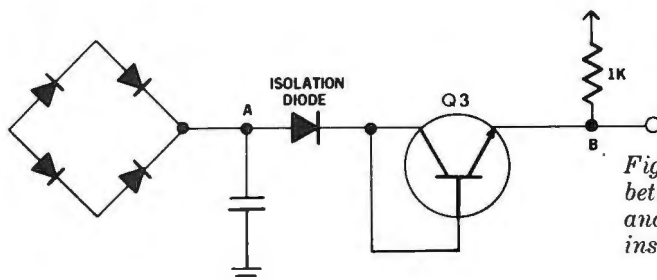


Fig. 3. Isolation diode between filter capacitor and transistor permits instantaneous reset.



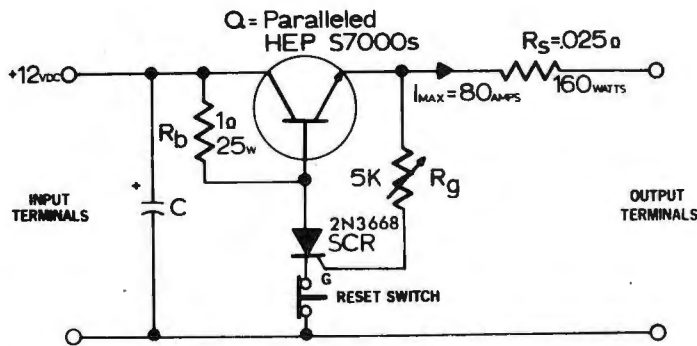


Fig. 4. A gate signal for the SCR is developed by the current through  $R_S$ .

There are many variations of the circuit shown in Fig. 5, but we will limit our discussion to this specific circuit configuration. It should be noted that  $R_S$  can have a value much lower than 1 ohm, which results in a lower wattage rating for this resistor. The optical coupler should consist of an infrared LED and a silicon transistor detector.

After assembling the circuit as shown, disconnect the anode lead of the LED from point A. Power up the supply, and monitor  $I_{C(Q1)}$  and  $V_{CE(Q1)}$  while decreasing  $R_B$  until  $Q1$  goes into saturation. Then adjust  $R_B$  until  $Q1$  is operating in the active region, just short of saturation. (This speeds up the cutoff action of  $Q1$  and keeps the photodetector current low.) When adjusting  $R_B$ , monitor  $I_{B(Q2)}$  to make sure you don't exceed the current rating of the photodetector.

Connect the LED's anode back to point A and short the output of the supply. Adjust the  $R_{LED}$  control for an  $I_{C(Q1)}$  short-circuit current of 15 mA. (Actually, the short-circuit current can be set to about 1 mA, but the adjustment of  $R_{LED}$  becomes critical for currents below 15 mA.)

With the adjustments performed as described and a 5-ohm value for  $R_L$ ,  $I_{C(Q1)}$  would be 640 mA. Reducing  $R_L$  to 3.33 ohms would drop  $I_{C(Q1)}$  to 27 mA and  $V_{CE(Q1)}$  to 4.4 V. This yields a 0.195-W  $P_{D(Q1)}$ . This current-limiting circuit produces an  $I_C$  versus  $R_L$  curve with a very steep slope, which results in very little overshoot of the desired maximum current.

With  $R_B$  and  $R_{LED}$  properly adjusted,  $Q1$  will operate in or near the saturation region with a heavy base drive supplied by  $Q2$ . If the current through  $R_S$  exceeds the maximum for which the circuit is adjusted, determined by the resistance of  $R_S$ ,  $R_B$ , and  $R_{LED}$ , the LED will emit enough light to reduce the resistance of the photodetector. The result is that  $Q2$ 's base drive will

be shunted to ground and the transistor will be cut off.

Because this circuit is very temperature sensitive, a reset switch must be provided as shown. When power is first applied to the system, no current flows through  $Q2$  until the reset switch is operated to momentarily disconnect  $R_L$  from ground. After a few minutes warm-up, the system is self-resetting.

**A Current Limiter.** The self-resetting circuit shown in Fig. 6 lacks some of the advantages of the previous circuits. Transistor  $Q1$  is again in series with the load, while  $Q2$  supplies sufficient base current to keep it operating in the saturation region for a significant range of loads.

In the following discussion, we will assume that a wide range of loads will be applied to the output of an unregulated power supply rated at 40 amperes. (If the load is to be fixed, circuit

components can easily be chosen so that  $Q3$  provides a sharp turn-off of  $Q1$  if  $I_{C(Q1)}$  increases beyond a chosen maximum. However, if the load is variable,  $R_L$  must be selected so that  $Q1$  passes the desired range of currents, with  $R_B$  and  $R_E$  chosen to provide rapid turn-off for the loads that will cause excessive current to pass through  $Q1$ .)

The graphs shown in Fig. 7 are plots of  $I_{C(Q1)}$  versus  $R_L$  for the circuit shown in Fig. 6. From plot A, it can be seen that as  $R_L$  is decreased (increased load), the current through  $Q1$  increases to a maximum of 14.5 A when  $R_L$  is 0.3 ohm. Decreasing  $R_L$  further yields a reduction in  $I_{C(Q1)}$  instead of an increase. This  $I_{C(Q1)}$  decrease with increasing load continues until  $R_L$  is 0.25 ohm, at which point the circuit becomes unstable. When a load of 0.25 ohm is connected to the supply's output,  $I_{C(Q1)}$  momentarily goes to 12 A, after which  $Q1$  turns off and  $I_{C(Q1)}$  reduces to zero. For load resistances less than 0.25 ohms,  $Q1$  is in the cutoff region and  $I_{C(Q1)}$  is zero.

Plot B, an expanded view of  $I_{C(Q1)}$  for small values of  $R_L$ , shows how the  $Q1$  collector current varies when load resistance approaches zero. When  $R_L$  is 0.3 ohm,  $I_{C(Q1)}$  is at the maximum 14.5-A value. For loads between 0.3 and 0.25 ohm,  $I_{C(Q1)}$  decreases almost linearly. Load resistances of less than 0.25 ohm are a virtual short circuit at the output terminals of the supply and cause  $Q3$  to keep  $Q2$  at cutoff.

The operation of the circuit is quite

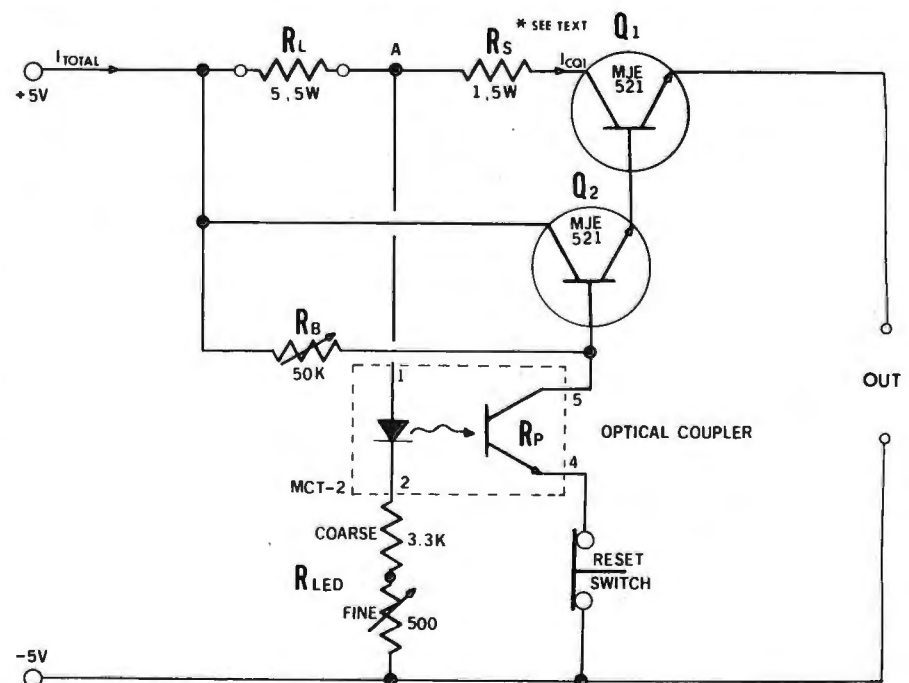


Fig. 5. Opto-coupler controls  $Q2$  on basis of current in  $Q1$ .

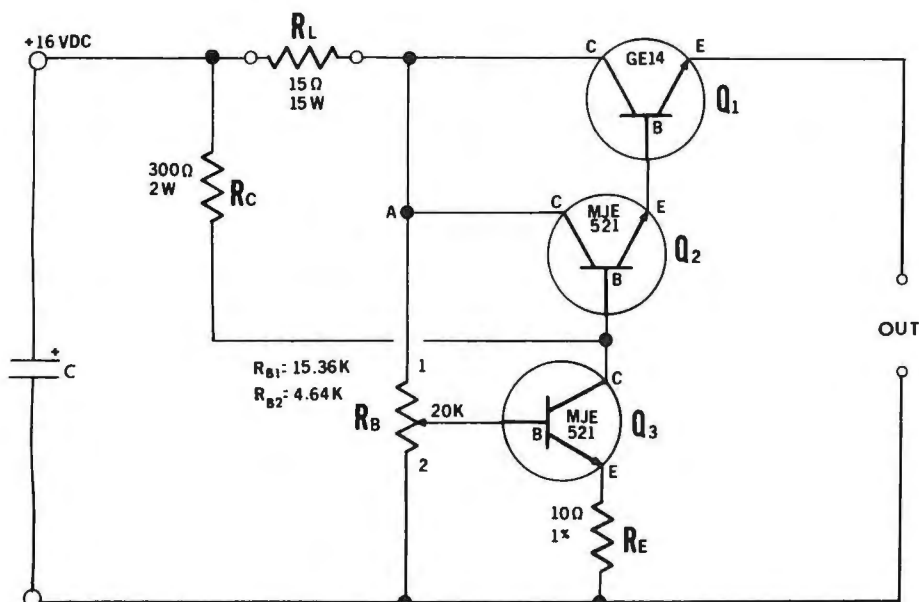


Fig. 6. A self-resetting current limiter with short-circuit protection.

TABLE I—CIRCUIT PARAMETERS FOR DIFFERENT LOAD RESISTORS

	(A) $R_L = 15$ ohms			(B) $R_L = 0$		
Parameter	Q1	Q2	Q3	Q1	Q2	Q3
$V_{CE}$	0.61 V	0 V	1.49 V	16 V	15.8 V	0.25 V
$V_{CB}$	-0.143 V	-0.74 V	1.3 V	15.8 V	15 V	-0.35 V
$V_{BE}$	0.75 V	0.74 V	0.17 V	0.42 V	0.385 V	0.65 V
$I_C$	1.09 A	38 mA	0	23 mA	14 $\mu$ A	48 mA
$I_B$	9 mA	46 mA	0	15 $\mu$ A	9 $\mu$ A	0.7 mA
$I_{RB1}$	32 $\mu$ A	—	—	1 mA	—	—
$I_{RB2}$	32 $\mu$ A	—	—	0.3 mA	—	—
$V_{in}$	16 V	—	—	16 V	—	—
$V_L$	15.9 V	—	—	0 V	—	—
$P_D$	0.7 W	0 W	0 W	0.37 W	$2 \times 10^{-4}$ W	0.012 W

straightforward. However, the adjustment of  $R_B$  and value of  $R_E$  that allow self-resetting are critical. Before  $R_B$  and  $R_E$  can be adjusted to the proper values,  $R_C$  must be chosen to allow the desired maximum  $I_{C(Q1)}$ . To select  $R_C$ , disconnect point 1 of  $R_B$  from junction A. The minimum value of  $I_{B(Q1)}$  to keep  $Q1$  in saturation can be estimated from the formula  $I_{Bmin} \approx I_C / h_{FE}$ . For a maximum of 15 A for  $I_{C(Q1)}$  using a GE14 transistor ( $h_{FE} = 45$ ) for  $Q1$ ,  $I_{Bmin}$  would be 0.333 A. The minimum value of  $I_{B(Q2)}$  is found by using the  $I_{B(Q1)min}$  value for  $I_{C(Q2)}$ . Hence, using an MJE521 transistor whose  $h_{FE}$  is 40 for  $Q2$ , we obtain  $I_{B(Q2)min} = 0.33 / 40 = 8$  mA. Then, determining the value for  $R_C$  we have  $R_C = V_{in} / I_{B(Q2)} = 15 / 0.008 = 1875$  ohms.

You can select a potentiometer for  $R_B$  by using the formulas given in "A Simple Method For Biasing Transistors" (June 1975). Let the base voltage of  $Q3$  be approximately 0.7 V,  $I_{C(Q3)} = I_{B(Q2)} = 8$  mA, and  $I_{bias} \approx 0.1 \times I_{C(Q3)} = 0.8$  mA. Assume that  $R_B$  consists of two resistors,  $R1$  for the portion of the pot above the wiper and  $R2$  for the lower portion. Now,  $R2 = V_{base} / I_{bias} = 0.7 / 0.0008 = 875$  ohms. Then for  $R1$ , consider the output of the power supply to be shorted and determine  $R1$  from the formula  $R1 = (V_{in} - V_{base}) / I_{bias} = (15 - 0.7) / 0.0008 = 17,875$  ohms. Adding the results obtained, we end up with a total resistance of 18,750 ohms. A

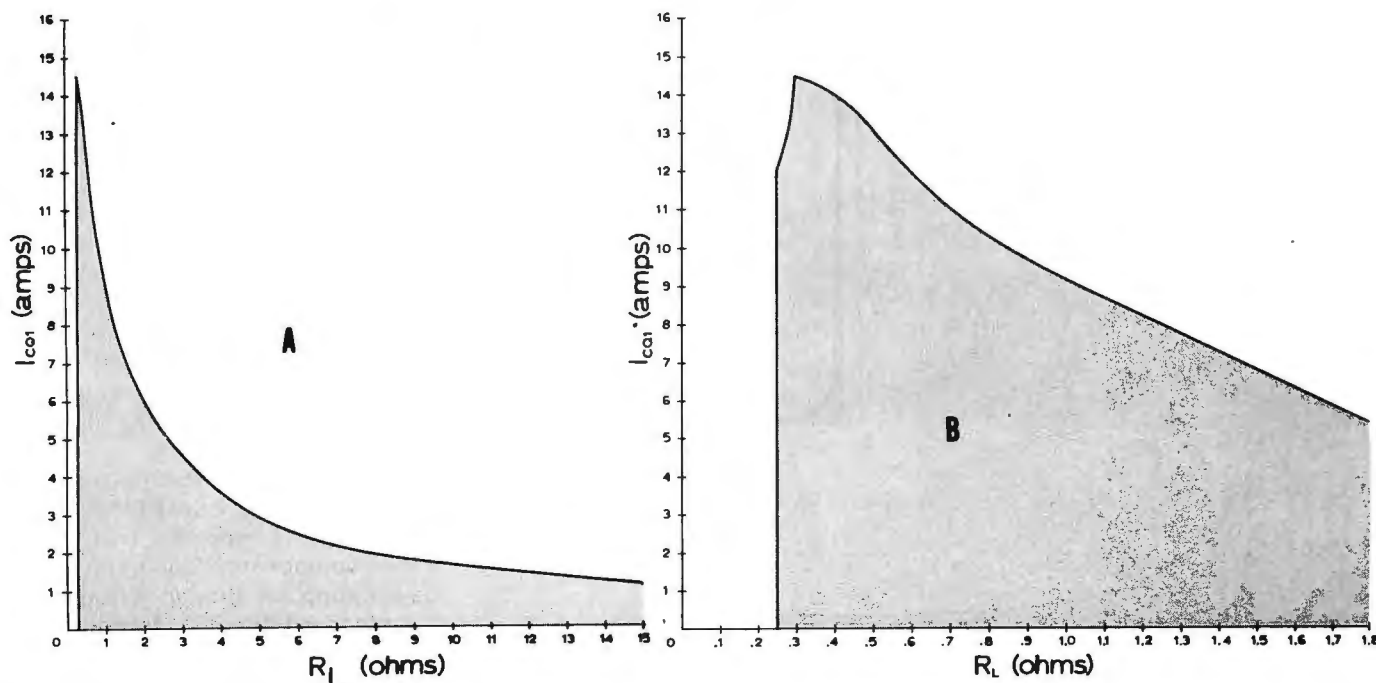


Fig. 7. In (A) load varies from 15 to 0 ohms; (B) load approaches zero.



standard 20,000-ohm potentiometer can, therefore, be used for  $R_B$ .

The adjustment of  $R_B$  is accomplished by connecting point 1 of the pot to junction A and installing a resistance decade box set to zero ohms as  $R_E$ . With a 15-ohm load connected to the output of the supply,  $I_{C(Q1)}$  should measure 1 A. (The collector current for Q1 should be monitored during all adjustments. Also, the power supply should be shut off when installing and removing ammeters.) Start with a 0-to-1-A ammeter and adjust  $R_B$  until  $I_{B(Q3)}$  is nearly zero. Continue in this manner, using a more sensitive ammeter, until  $I_{B(Q3)}$  is exactly zero.

Remove the ammeter from the supply and connect the base of Q3 as shown in Fig. 6. The decade box in the emitter leg of Q3 should still be set to zero. Short the supply's output terminals;  $I_{C(Q1)}$  should drop to zero. If the current through the collector of Q1 doesn't drop to zero,  $I_{B(Q3)}$  or  $R_E$  has not been set to zero. Remove the short from across the supply's output, leaving only the 15-ohm load. The collector current of Q1 should remain at zero; if it doesn't and the circuit self-resets, no  $R_E$  is needed. (This is not likely to occur.) With no self-reset, increase  $R_E$  in 1-ohm steps until  $I_{C(Q1)}$  goes back to 1 A. Short the output of the supply again;  $I_{C(Q1)}$  should go to zero and the circuit should restart when the short is removed.

The higher the resistance of  $R_E$ , the greater will be the off current of Q1. With repeated trimming of  $R_B$  and  $R_E$ , the collector current of Q1 when the supply's output is shorted can be brought down to 5.4 mA. The circuit can be made much less dependent on the setting of  $R_B$ , and  $R_E$  can be zero, if a reset switch is used to return the circuit to normal operation after an overload. In this case,  $R_B$  would be adjusted as before, and a reset switch would be operated to momentarily break the  $R_B$  connection to junction A. The pot could then be trimmed to yield a minimum collector current in Q1.

The capacitor shown across the input of the circuit in Fig. 6 is not part of the protection system. It is simply representative of the filter capacitor in the power supply. Under normal conditions, Q2 supplies the base current to Q1. Both Q1 and Q2 operate in the saturation region to assure that full power is delivered to the load. The A section of Table I shows the measured and calculated parameters for Q1, Q2, and Q3 for the 15-ohm load,  $R_L$ .

If  $R_L$  is reduced to zero (shorted output terminals), Q3 will conduct and Q1 and Q2 will be driven into cutoff. The B section of Table I shows the parameters for the transistors when  $R_L = 0$ .

For intermediate values of  $R_L$ , the transistors pass through all three regions of operations. These regions and the loads that cause the transi-

**TABLE II—OPERATING REGIONS FOR DIFFERENT LOAD RESISTORS**

$R_L$ (ohms)	Region Of Operation		
	Q1	Q2	Q3
15	saturation	saturation	cutoff
1.66	saturation	saturation	active
0.296	active	active	active
0.25	unstable	unstable	unstable
0	cutoff	cutoff	saturation


tions are listed in Table II. When  $R_L$  is reduced to 1.66 ohms, enough forward bias is applied to the base of Q3 to bring it out of cutoff. As  $R_L$  is further reduced,  $I_{B(Q3)}$  increases until, finally, when  $R_L$  is 0.296 ohm, Q3 is shunting a large enough portion of Q2's base drive to ground to cause both Q2 and Q1 to come out of saturation and begin operating in the active region. Eventually, when  $R_L$  is reduced to less than 0.25 ohm, Q3 is driven into saturation and Q2 and Q1 go into cutoff.

Because Q1 and Q2 must operate in the active region, even for so narrow a range of loads as from 0.296 to 0.25 ohm, the voltage drop across these transistors over this range causes the power dissipation of the devices to increase tremendously while they are operating in the active region. Plots of  $P_D$  versus  $R_L$  for Q1 and Q2 are shown in Fig. 8. Plot A shows that, for maximum protection, Q1's  $P_D$  rating should be greater than 80 watts at the desired operating temperature. Plot B shows that Q2's  $P_D$  rating should be greater than 5 watts.

Although the  $P_D$  ratings of Q1 and Q2 must be much greater than is necessary while the transistors are operating strictly at saturation, they need not handle the power dissipation that would be necessary in an unprotected series voltage regulator. For example, with a 14.5-A  $I_{C(Q1)}$  and a 16-volt  $V_{in}$ , the  $P_D$  rating of a transistor used as an unprotected series regulator would have to be 232 watts at the operating temperature under shorted conditions. This would require a very expensive transistor.

**Conclusion.** We have proposed only a few of the many possible ways of protecting the more expensive and fragile components found in modern power supplies. Proper utilization of the proposed circuits, individually or in combination, will produce protection systems that are relatively inexpensive and reliable. ♦

*Fig. 8. Power vs load for Q1 (A) and Q2 (B).*

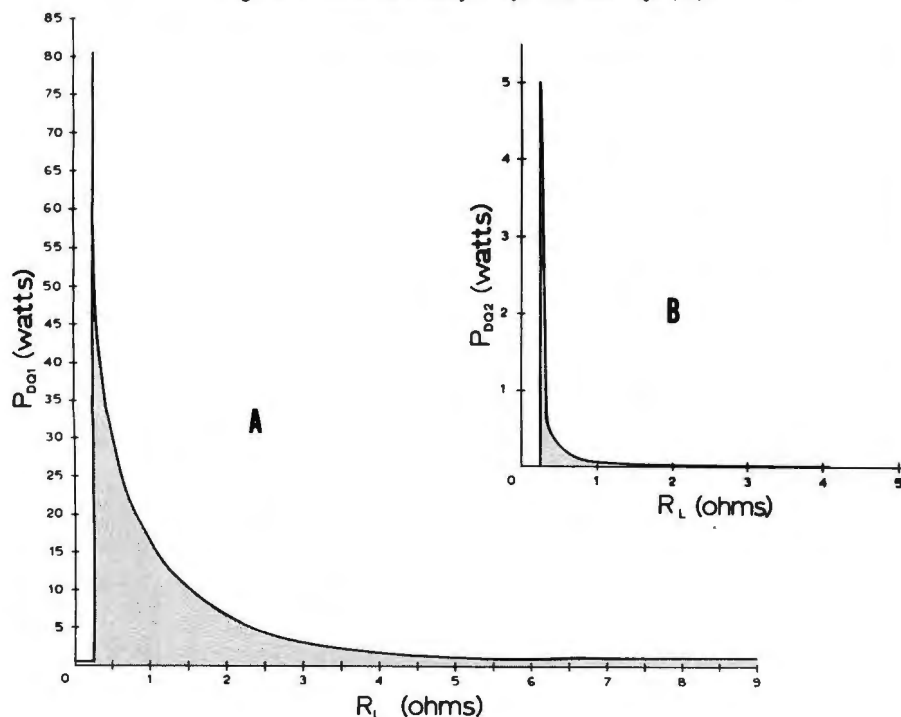

**T**HERE ARE digital electronic clocks with all sorts of variations—alarms, radios, calendars, etc. Now, here is one for the music lover. It plays the famous Westminster chime tune. On the quarter-hour, the first  $\frac{1}{4}$  of the tune is played; on the half hour,  $\frac{1}{2}$  of the tune; on three-quarters,  $\frac{3}{4}$  of the tune; and the full tune on the hour. On the hour, the tune is followed by a monotone chiming of the hour. By using "surplus" parts, you can build this clock for a very low cost, though it does have 19 IC's.

**How It Works.** The complete circuit of the clock is shown in three parts in Figs. 1 to 3. The clock element is IC19 an MM5316 IC that drives conventional fluorescent readouts DIS1 through DIS4. This clock IC was selected because it has continuous outputs that minimize the chime circuit interface requirements. If you select a clock IC that has multiplexed outputs, additional circuits will be required. The fluorescent readouts are used because they can be driven directly by the MM5316 and they require very little operating power.

In Fig. 1, IC1 and IC2 decode the conditions of the 15, 30, 45, and 00 minutes. The outputs are OR'd by part of IC4, whose output then initiates a one-shot circuit formed by C1, R12, and part of IC3 (Fig. 2). The pulse from this one-shot sets a flip-flop formed by two elements of IC5, which in turn, activates the tone output through part of IC9. The one-shot pulse also resets the remainder of the chime circuits.

The Westminster chime sequence uses four different tones. Instead of having four different frequency oscillators which may be difficult to keep correctly tuned, a single tone oscillator formed by IC15 (Fig. 3) is used, with its output divided down to form the four required tones. In this way, even if the basic tone oscillator frequency were to vary, the relationship between the four Westminster tones will be maintained and a harmonious melody is ensured. The frequency division is performed by IC11 and IC12, with portions of IC13, IC14, IC15, and IC4. The output of counter IC3, pin 12 (Fig. 2), consists of narrow pulses. These are used to toggle IC9, which divides the frequency by two and produces a square-wave output. The latter is filtered by R20 and C7 and is used to drive Q1, which is the audio output stage.

The tone sequence is programmed



Photo courtesy British Tourist Authority, 680 Fifth Ave., NY, NY 10019.

# Digital Electronic "Westminster" Clock

BY ALAN ROEHL

*The famous "Big Ben" tune  
is played every hour with  
portions every 15 minutes.*

by a 10-stage Johnson counter formed by IC8 (Fig. 3). This counter is driven by the 1-Hz output from IC19 so that each tone has a 1-second duration.

Since the first half of the melody is identical to the second half, a single 10-stage counter is adequate to program the eight tones and two pauses





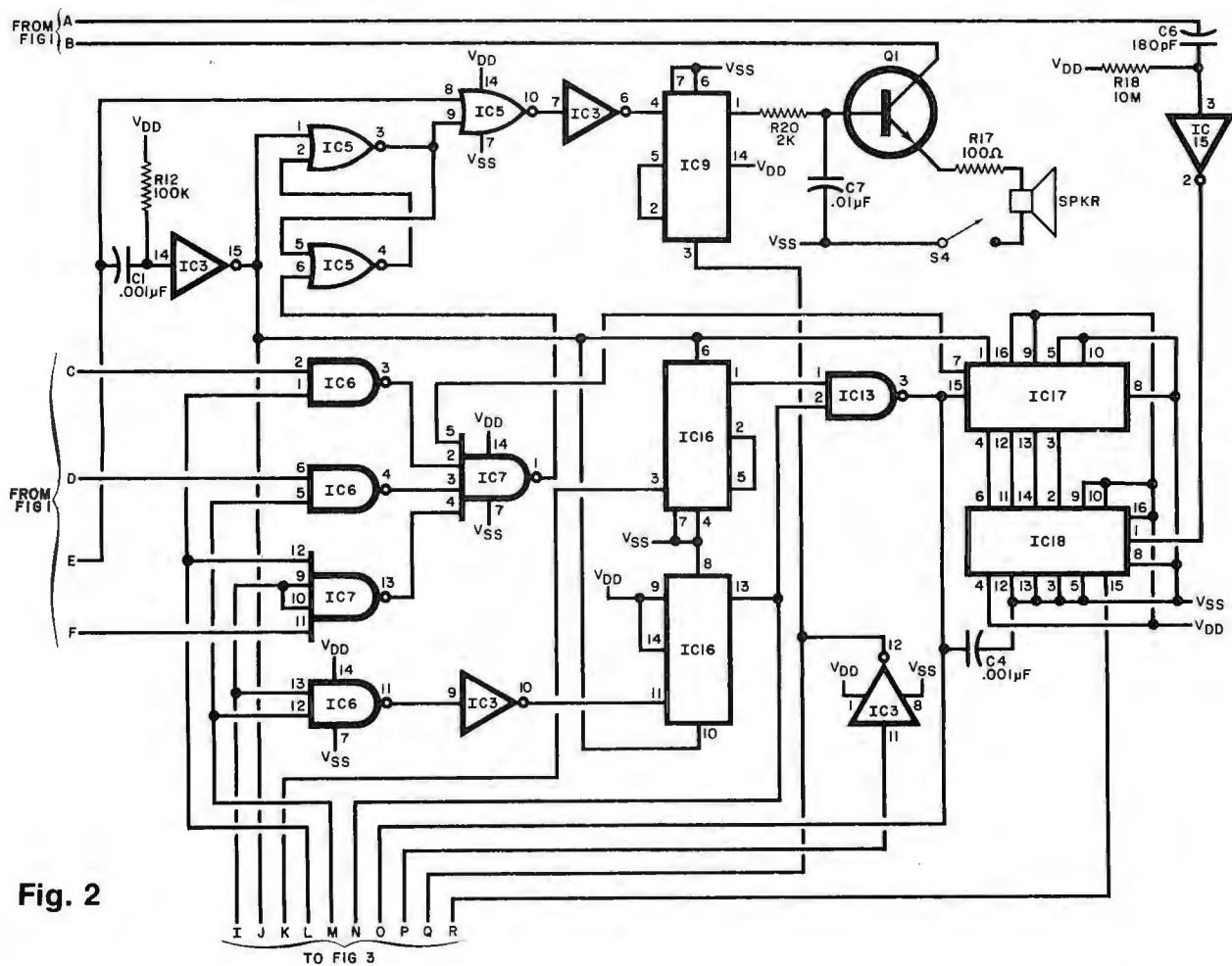


Fig. 2

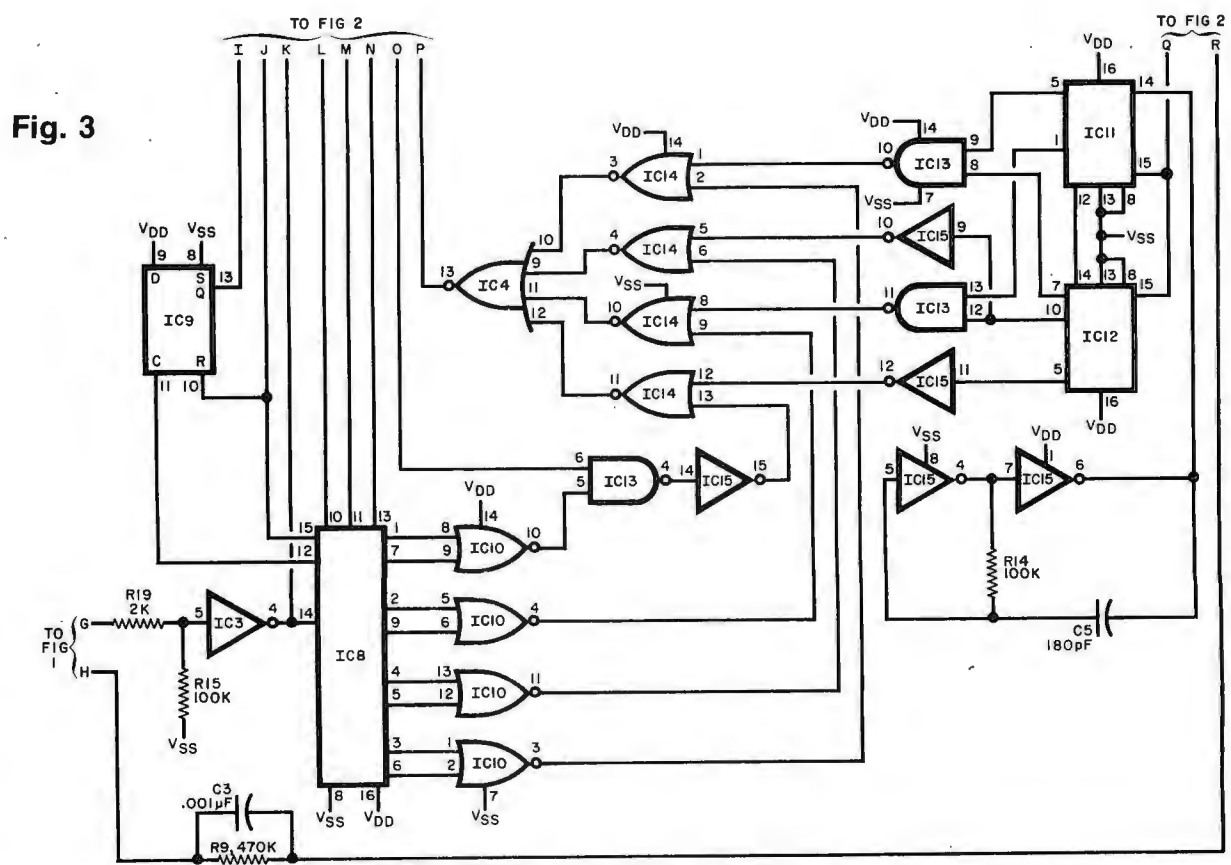


Fig. 3



# Be the “New Professional” in electronics

**CREI trains you at home  
for one of the most important  
career levels in electronics—  
plus offers you special  
arrangements for engineering  
degrees**

Most people think there are only two levels of careers in electronics: the technician level and that of the degree engineer.

There is, however, a third and very important level. It is that of the engineering technician or *practical* engineer. The growing importance of this career level has created what might well be called the “New Professional” in electronics.

If you look at the various levels of employment in electronics, you will understand why this “New Professional” is so important.

The average technician is a person who has had vocational training in electronics. He understands the basic principles of electronics so he can troubleshoot, repair and maintain equipment. He usually works under close supervision in performing his duties.

The engineer has college training in electronics. He usually supervises technician personnel and is responsible for planning and developing of electronic equipment and systems. Frequently, however, engineers are more heavily trained in the scientific principles of electronics and less in their practical application.

The engineering technician, by contrast, is a specialist in the practical application of electronics. His training usually consists of a two-year college program in electronic engineering technology. In many organizations, the engineering technician handles several of the responsibilities of the degree engineer. He often has the title of engineer.

CREI programs are designed to give you at home the same level and depth of training you receive in a two-year college program in electronic engineering technology. CREI programs are, in fact, more extensive than you will find in many colleges. And CREI gives you the opportunity to specialize in your choice of the major fields of electronics.

## **Unique Design Lab**

CREI gives you both theory and practical experience in circuit design with its Electronic Design Laboratory Program. The professional equipment included in this program allows you to construct, test out and correct the circuits you design until you have an effective circuit.

This Lab Program helps you understand advanced electronics. It also gives you practical experience in many other important areas of electronics, as in pro-

# Career Training at Home

totype construction, breadboarding, test and measurement procedures, circuit operation and behavior, characteristics of electronic components and how to apply integrated circuits.

Only CREI offers the unique Lab Program. It is a complete college Lab and, we believe better than you will find in most colleges. The "Lab" is one of the factors that makes CREI training interesting and effective. And the professional equipment in this program becomes yours to keep and use throughout your professional career after you complete the training.

## Engineering Degree

CREI offers you special arrangements for earning credit for engineering degrees at certain colleges and universities as part of your home study training program. An important advantage in these arrangements is that you can continue your full time job while "going to college" with CREI. This also means you can apply your CREI training in your work and get practical experience to qualify for career advancement.

## Wide Program Choice

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

## Free Book

In the brief space here, there isn't room to give you all of the facts about CREI college-level, home study programs in electronics. So we invite you to send for our free catalog (if you are qualified to take a CREI program). The catalog has over 80, fully illustrated pages describing your opportunities in advanced electronics and the details of CREI home study programs.

## Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

**Send for this FREE Book  
describing your opportunities  
and CREI college-level  
programs in electronics**



Mail card or write describing qualifications to

**CREI** **CAPITOL  
RADIO  
ENGINEERING  
INSTITUTE**

**McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue Northwest  
Washington, D.C. 20016**

**Accredited Member National Home Study Council**

## GI Bill

*CREI programs  
are approved  
for training of  
veterans and  
servicemen under  
the G.I. Bill.*





BY DAVID L. HEISERMAN



# BUILD

# ODDS-ON

## A GAME OF CHANCE AND STRATEGY

*Simple, low-cost parlor game*

*can be challenging and interesting.*

**I**F YOU enjoy playing electronic games, grab your soldering iron and build "Odds-On," a low-cost game that combines the best elements of chance and strategy. Even though the readout is a single LED, don't get the idea that the game is easy to beat.


Odds-On uses a relatively high-speed oscillator to drive a counter and decoding system when its PLAY button is pressed. When the button is released, the count stops. If, when it stops, the LED turns on, you win. This is the chance feature. The element of

strategy enters the game when you're allowed to select your own odds of winning. In this mode, you set a rotary switch to one of nine positions, each of which gives different odds ranging from 1:10 to a conservative 9:10.

Two or more players can compete with each other. The player who selects the longest odds, and wins, wins the game. The actual scoring technique is up to the players, but keep in mind that a more conservative player can consistently score and win, if his opponent is not just lucky.

Odds-On can be used to play a variety of games, including coin toss (odds 5:10), Russian Roulette, or any other games that call for playing against odds of 1:10 to 9:10.

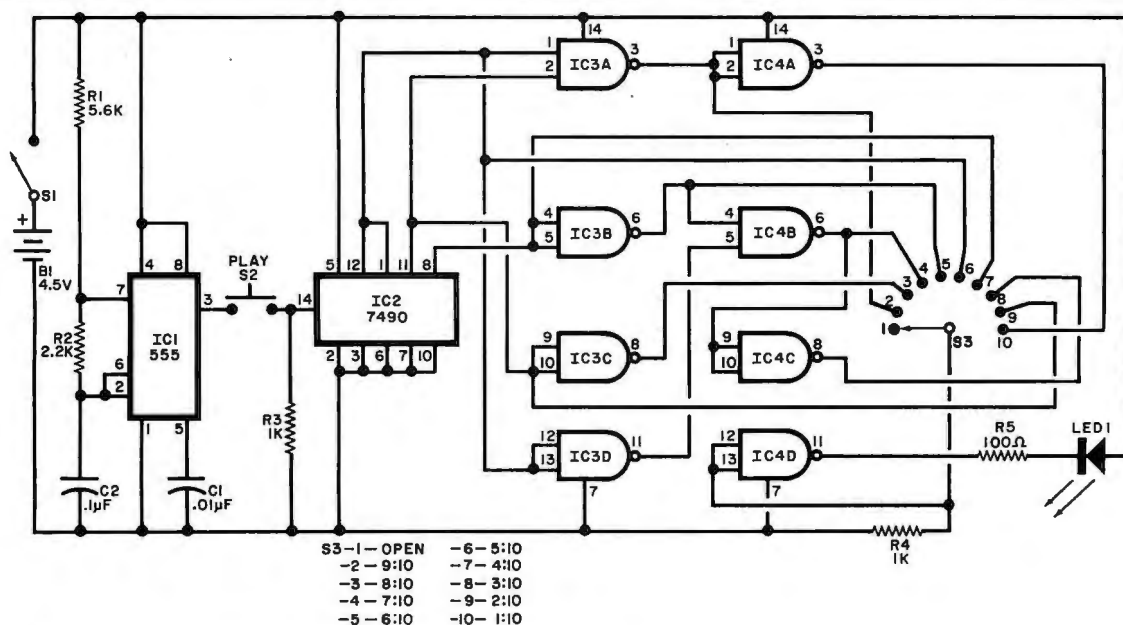**How It Works.** Free-running oscillator IC1 operates at a frequency of about 1000 Hz as a result of the values specified for R1, R2, and C2. When PLAY pushbutton S2 is depressed, the output pulses from the oscillator drive decade counter IC2, which cycles from 0 through 9 (10 different output



In the circuit, IC1 operates at 1000 Hz, S2 starts the play, and S3 determines the odds.

### PARTS LIST

B1—Three 1.5-volt AA cells in series  
C1—0.01-μF disc capacitor  
C2—0.1-μF disc capacitor  
IC1—555 timer  
IC2—7490 decade counter  
IC3, IC4—7400 quad two-input NAND

gate  
LED1—Any discrete light-emitting diode  
R1—5600-ohm, ¼-watt resistor  
R2—2200-ohm, ¼-watt resistor  
R3, R4—1000-ohm, ¼-watt resistor  
R5—100-ohm, ½-watt resistor

S1—Spst Switch  
S2—Normally-open spst switch  
S3—Single-pole, 10-position rotary switch  
Misc.—Suitable box; battery holder; perforated or pc board; hookup wire; machine hardware; solder; etc.

states). When the PLAY button is released, the counter holds its last output state.

Since IC2 produces 10 different output states, the chances are 1 in 10 that the count will stop at any particular state. However, it is possible to use the decoding logic of IC3 and IC4 and switch S3 to weight the odds. For example, if S3 is set to the 5:10 position, there is a 50/50 chance that LED1 will be on.

**Construction.** Because of the simplicity of the circuit, any type of construction will suffice, but a printed circuit board of your own design or perforated board will be most convenient. Sockets for the IC's are optional. Switches S1, S2, and S3 should be mounted on the top of the box in which you house the circuit. Also mounted on the top of the box and held in place with a small rubber grommet or a bead of cement should be LED1. The three 1.5-volt AA cells that make up B1 should be mounted in a suitable holder inside the box.

**Game Hints.** Consider a game in which two or more players are par-

ticipating with one player being very conservative. Suppose the conservative player selects odds of 6:10. When he presses and releases the PLAY button, he has six chances out of 10 to score a hit (LED comes on). If this happens, he scores 6 points. If the LED remains off, his score is 10.

The next player selects his own odds, say, 2:10. If after pressing and releasing the PLAY button the LED comes on, he gets a score of 2; if the LED stays off, he gets a score of 10.

From the foregoing, a player gets 10 points every time he loses and the first digit of the odds figure if he wins. The play continues until one player's score reaches 100, at which time he loses. If there are more than two players, odds selection and play continue until all scores but one are 100. The one player whose score doesn't reach 100 is the winner.

To play "coin-flip," set the selector switch to the 5:10 position and operate the PLAY button. At each depression and release, there is a 50/50 chance that the LED will turn on and you win.

To play Russian Roulette, assume a six-shot revolver has a cartridge in

only one chamber. The PLAY button becomes the "trigger." Set the odds selector switch to the 2:10 position. If at any time the LED comes on, you definitely lose. ♦



"What do you mean, does a horse come with it?"





BY LARRY ZIDE

# Professional vs. Consumer Tape

*Would there be an advantage for the home recordist in using studio-type tape?*

**M**AGNETIC tape manufacturers optimize the characteristics of their open-reel tapes according to the requirements of the markets they serve. Professional mastering tapes, for example, provide their best performance at a speed of 30 or 15 ips, both of which are commonly used by the pro's. Consumer tapes, on the other hand, are best for the commonly used 7½ and 3¾ ips speeds of consumer decks.

One might ask if a professional tape, used on a consumer deck, will yield superior performance when compared with a consumer tape. At least one major manufacturer says no. However, might it not be possible to adjust a consumer machine to favor the professional tape? To answer this question, we embarked on a project to examine both professional mastering and consumer tapes, after idealizing a consumer tape deck for each type of tape to be used.

**Bias and Equalization.** We know that tape deck bias should be adjusted to suit the tape being used. What is

less well known is that the precise amount of bias used in any given tape deck is a compromise of frequency re-

*Frequency response curves are decibels versus frequency in hertz.*

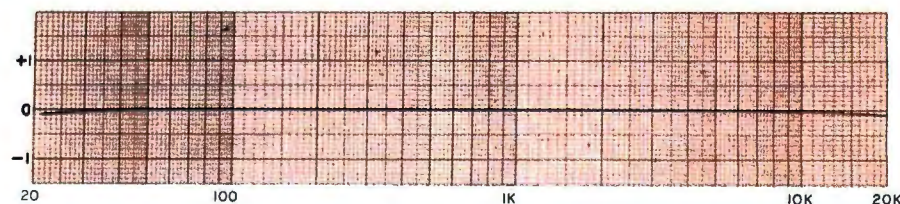


Fig. 1. Overall response of the entire test set-up without a tape.

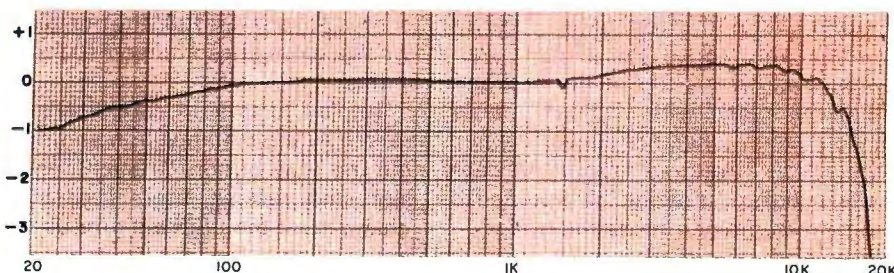


Fig. 2. Maxell UD-50 at 3¾ ips, bias 2 dB beyond peak at 10,000 Hz.



sponse versus distortion and/or noise. There is no one bias setting that will simultaneously provide both the widest absolute response and the lowest absolute distortion/noise. Bias is generally set in professional decks for lowest distortion and noise and let the frequency response fall as it may, while the bias in consumer machines is set to provide the widest frequency response.

Once the bias adjustment is made, the high-frequency equalization can be used to compensate for the record electronics so that a playback response as nearly flat as possible is obtained. All professional and many consumer tape decks, therefore, can be adjusted for high-frequency equalization. Many professional decks provide this equalization on the play side of the preamplifier, but all offer it on the record side. Playback equalization is always preset to a standard test tape. The record equalization attempts to adjust the response to match the standardized playback.

The normal manner in which bias is adjusted is to set the deck so that the tape is moving at the speed for which adjustment is to be made, with the mode set to record. An audio signal generator is then used to record a sine-wave signal and the bias is adjusted while the output of the tape is monitored. As the bias is advanced, the output of the tape increases until it reaches a point where additional bias reduces the output (particularly at the higher frequencies). This is because increased bias begins to erase very short wavelengths.

A common professional way to adjust the bias on a high-speed deck is to record a 10,000-Hz signal and adjust the bias beyond the peak until a 1-to-2-dB reduction in output occurs. This yields the lowest noise and distortion and an acceptable frequency response. If the bias were to be set at peak, the response might be so good at the high end that there would not be enough equalization to bring it down, but distortion would be high and noise might suffer.

**Our Test Setup.** The basic tape deck we selected for making our tests was the Revox Model A-700. This deck has 15, 7½, and 3¾ ips speeds, covering both the consumer and the professional ranges, and provides complete bias and equalization adjustment con-

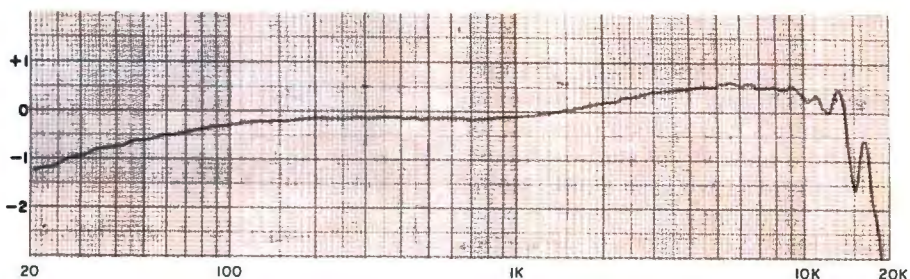


Fig. 3. Same as Fig. 2, but with bias set to peak at 1000 Hz.

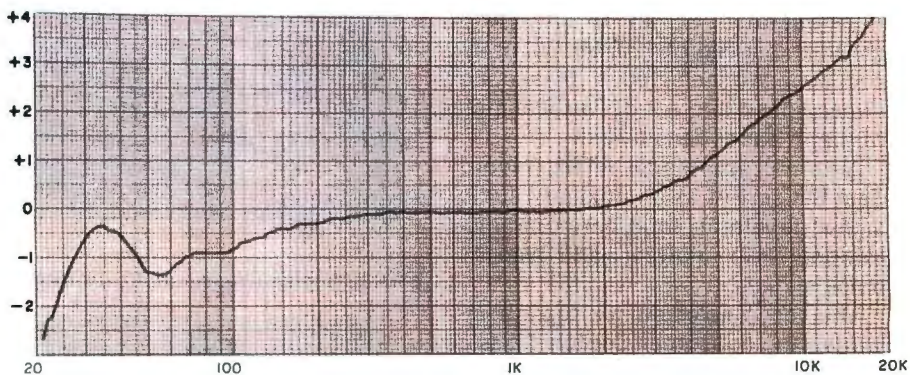


Fig. 4. Same as Fig. 2, with 15-ips speed.

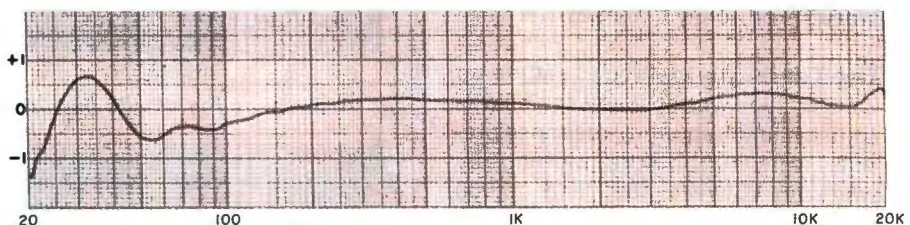


Fig. 5. Same as Fig. 3, with 15-ips speed.

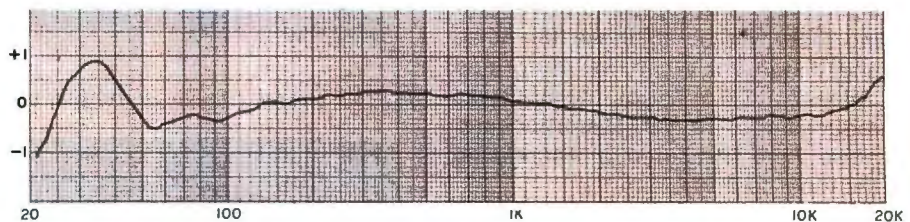


Fig. 6. 3M's Scotch 250 at 15 ips with bias 2 dB beyond peak.

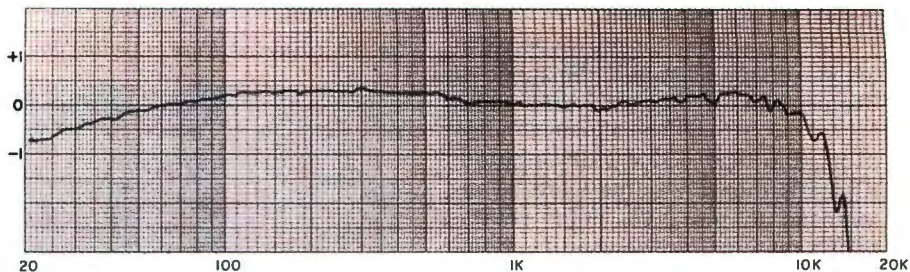


Fig. 7. Same as Fig. 6, with speed at 3¾ ips.



trols for each speed and channel. Needless to say, this deck provides all the controls and speeds required for making a meaningful study of tapes.

For the tests, we used a UREI Model 200 X-Y frequency plotter with built-in automatic 20-to-20,000-Hz sweep frequency generator. On the receive end of this instrument, the signal returns, after going through the equipment under test, and drives the X-Y plotter that operates at an exactly synchronized speed of 120, 60, 30, or 15 seconds. We selected a 60-second sweep speed and a 2-dB/vertical inch of graph paper sensitivity.

A Ferrograph Model RTS2 Record Test Set served as an auxiliary audio signal generator, total harmonic distortion (THD) analyzer, and also as noise meter.

The tapes selected for testing included the consumer Scotch Classic and professional 250 types from 3M, the consumer Maxell UD-50, and the professional Ampex Grand Master 456. We believe these tapes to be representative examples of the tapes available on today's market.

**The Tests.** The method of setting up for each tape was as follows: bias was adjusted and frequency-response pretests were run before plotting by sweeping between 1000 and 10,000 Hz. The recording equalization was then adjusted to bring the 10,000-Hz response as much in line with that of the 1000-Hz response as possible.

For the tests conducted at 15 ips, all testing was performed at 0 VU recording input, including those for noise and distortion. When we performed out tests at  $3\frac{3}{4}$  or  $7\frac{1}{2}$  ips, the input was reduced to -10 VU. Distortion and noise were measured by increasing the input to 0 VU.

Our first frequency plot made on the UREI recorder is shown in Fig. 1. This is the overall response of the entire system without a tape running. As you can see, variations between 20 and 20,000 Hz are negligible.

The graph in Fig. 2 is the response of the Maxell UD-50 tape at the speed of  $3\frac{3}{4}$  ips, with the bias set 2 dB beyond peak at 10,000 Hz. The signal-to-noise (S/N) ratio was -52 dB unweighted. (Our S/N measurements were all referenced to the 0-VU point on the deck's meters. Had we used the common 3% distortion point, the S/N figures for this and all subsequent tapes would have been better by 7 to 8 dB.)

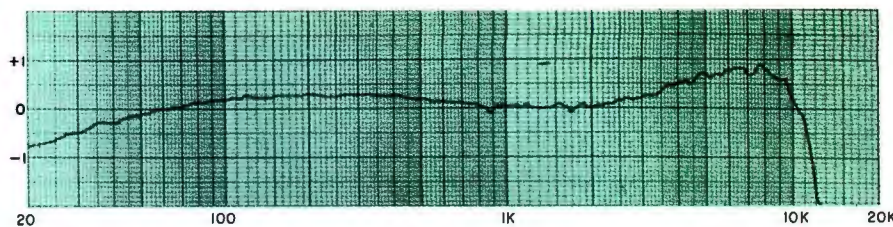


Fig. 8. Same as Fig. 7, with bias set to peak at 1000 Hz.

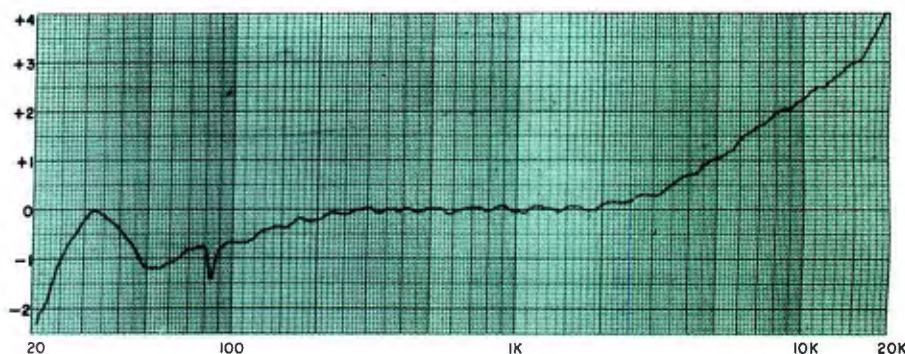


Fig. 9. Scotch Classic at 15 ips and minimum equalization.

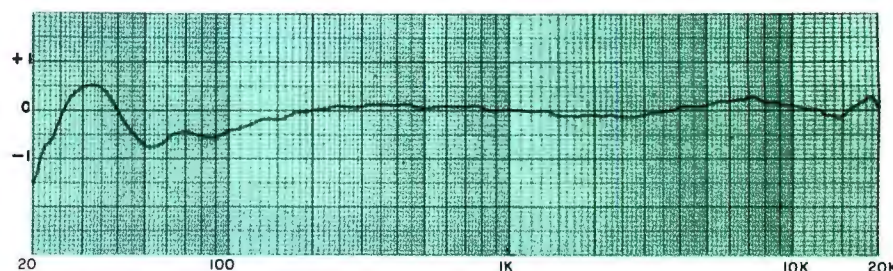


Fig. 10. Same as Fig. 9 with bias to peak at 1000 Hz.

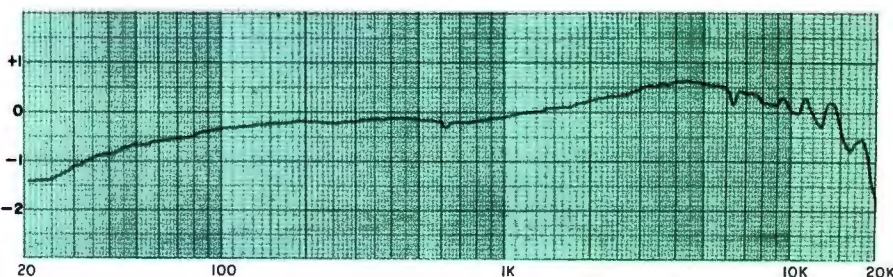


Fig. 11. Scotch Classic at  $3\frac{3}{4}$  ips, bias 2dB beyond peak at 10,000 Hz.

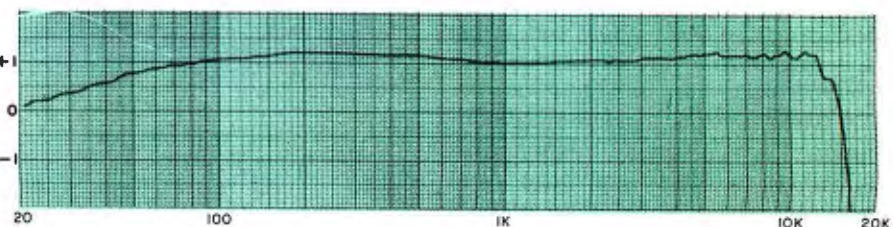


Fig. 12. Same as Fig. 11, with bias set to peak.

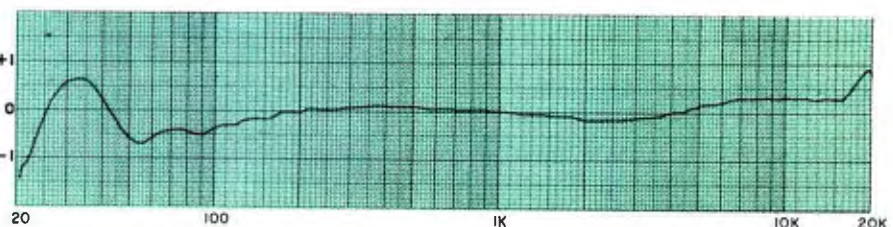


Fig. 13. Ampex 456 at 15 ips, bias 2 dB beyond peak at 10,000 Hz.



Note that the response of this tape is essentially flat to -2 dB at 17,000 Hz.

When we adjusted the bias to peak at 1000 Hz, note, in Fig. 3, the slight roughness of the high end, although the actual response is still about the same. At 1.2%, the distortion was slightly greater, but the S/N remained the same at -52 dB.

Changing the speed to 15 ips produced the curve shown in Fig. 4 at 10,000 Hz and bias set at 2 dB beyond peak and Fig. 5 at 1000 Hz and bias set to peak. The Fig. 4 curve was obtained with minimal setting of the high-frequency equalization. The sharply rising high end is obvious, almost 5 dB at 20,000 Hz. At this setting, the THD was 1% and the S/N was -55 dB. The bass end response of the Fig. 5 curve is typical of many tapes and is well within  $\pm 1$  dB from 22 Hz. At the high end, the response is smooth and goes well beyond 20,000 Hz. This time, distortion was 0.75% and S/N was -55 decibels.

3M's Scotch 250 studio mastering tape, first tested at 15 ips, responded very well when the bias was set 2 dB beyond peak, as seen in Fig. 6. S/N was -58 dB and distortion measured 0.7%. We saw no reason to alter the bias and left the setting alone.

The curve shown in Fig. 7 is for the Scotch 250 tape at the consumer speed of  $3\frac{3}{4}$  ips. At 2 dB beyond peak, the response is 2 dB down at 15,000 Hz, while S/N was -53 dB and distortion was 1.1%. The curve in Fig. 8 is for the same tape and speed, but this time, the bias was set to peak at 1000 Hz. The high end suffers, S/N remains at -53 dB, and distortion improves to 0.9%—not a very significant gain. It can certainly be assumed that this is not a tape to use at low speeds.

The response of the consumer-grade Scotch Classic tape is shown in Fig. 9. The tape speed was 15 ips and high-end equalization was at a minimum. While the S/N figure is a healthy -57 dB, distortion is an unhealthy 2.8%. Obviously, with the bias set at 2 dB beyond peak, this is not a good tape to use at the higher speed.

Setting the bias to peak at 1000 Hz and correcting the equalization provided the curve shown in Fig. 10. Note that the response has smoothed out to professional-grade full range; S/N remains at -58 dB; and distortion has dropped to an excellent 0.7%. Classic can obviously qualify as a good professional tape.

Now, operating Scotch Classic at the consumer speed of  $3\frac{3}{4}$  ips, as shown in Fig. 11, the response was flat to -2 dB at 20,000 Hz. However, at 2 dB beyond peak at 10,000 Hz, S/N was -53 dB and distortion was 2.5%. With the bias set to peak, the response was -2 dB at 16,000 Hz, with distortion down to 1.1% and S/N -54 dB (Fig. 12). These two settings clearly reveal the tradeoffs of bias versus distortion and frequency response.


The professional mastering Ampex 456 tape was very similar to the Scotch 250 tape in its bias requirements and performance characteristics. We performed our Ampex 456 tape tests with the bias set 2 dB beyond peak at 10,000 Hz. The Fig. 13 curve was obtained at 15 ips; S/N was -57 dB and distortion was 0.8%. This is clearly a professional tape. At  $3\frac{3}{4}$  ips, the tape's response was rough but actually only 2 dB down at 20,000 Hz. The tape had a response of 1 dB at about 10,000 Hz at the minimum setting of the tape recorder's equalization adjustment. The distortion was an unimpressive 2.4% and S/N was a good but not impressive -53.5 dB. Ampex 456 is a superb studio mastering tape, but much like the Scotch 250, it is not an idealized slow-speed tape.

**Summing Up.** What have our tests proved? Depending on the bias and equalization settings of the tape deck, Scotch Classic, Scotch 250, and Maxell UD-50 performed very much the same at  $3\frac{3}{4}$  ips. We expected this of the Classic and UD-50 tapes, but seeing the performance of the 250 at this speed came as a bit of a surprise. At the high, and presumably professional, speed of 15 ips, each of the tapes tested was capable of nearly identical frequency response, distortion, and noise performance.

We feel, therefore, that part of our original contention that, at low speeds, tapes designed for that speed range are best, has been proven. But at high speeds, it would appear that the best buy is the lowest priced and most readily available tape—at least among those tested by us.

It is evident that proper performance from any tape means that the tape deck on which it is used must be properly set up for it. Bias must be set for distortion versus frequency response, but the setting must permit an acceptable normalizing of the high-end response.

# The \$750 alternative.

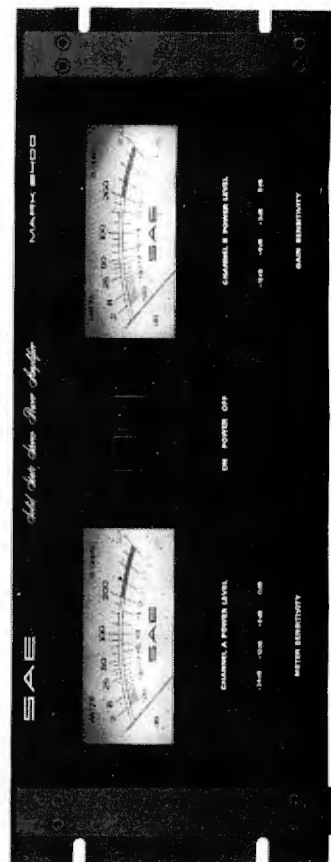

SAE 2400 Professional Dual-Channel Power Amplifier

☐ 200 Watts RMS, per channel, both channels driven into 4 or 8 Ohms from 20Hz to 20KHz at no more than 0.05% Total Harmonic Distortion.

- ☐ 0.05% IM into 4 or 8 Ohms
- ☐ (signal to noise) greater than 100dB
- ☐ plug-in board modules
- ☐ forced air cooling
- ☐ only 11" deep
- ☐ weighs less than 42 lbs.
- ☐ superb construction using only the finest materials and component parts
- ☐ available in black rack mount (as shown) or our traditional satin gold and black

You'd have to look a long time to find a power amplifier that delivers this much value.



Scientific Audio Electronics, Inc. PE11/76  
P.O. Box 60271, Terminal Annex  
Los Angeles, California 90060  
Please send me the reasons (including available literature) why the SAE 2400 Professional Amplifier is the "\$750 Alternative."


NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

CIRCLE NO. 62 ON FREE INFORMATION CARD



# **Herb Laney's a tough-minded optimist. How about you?**

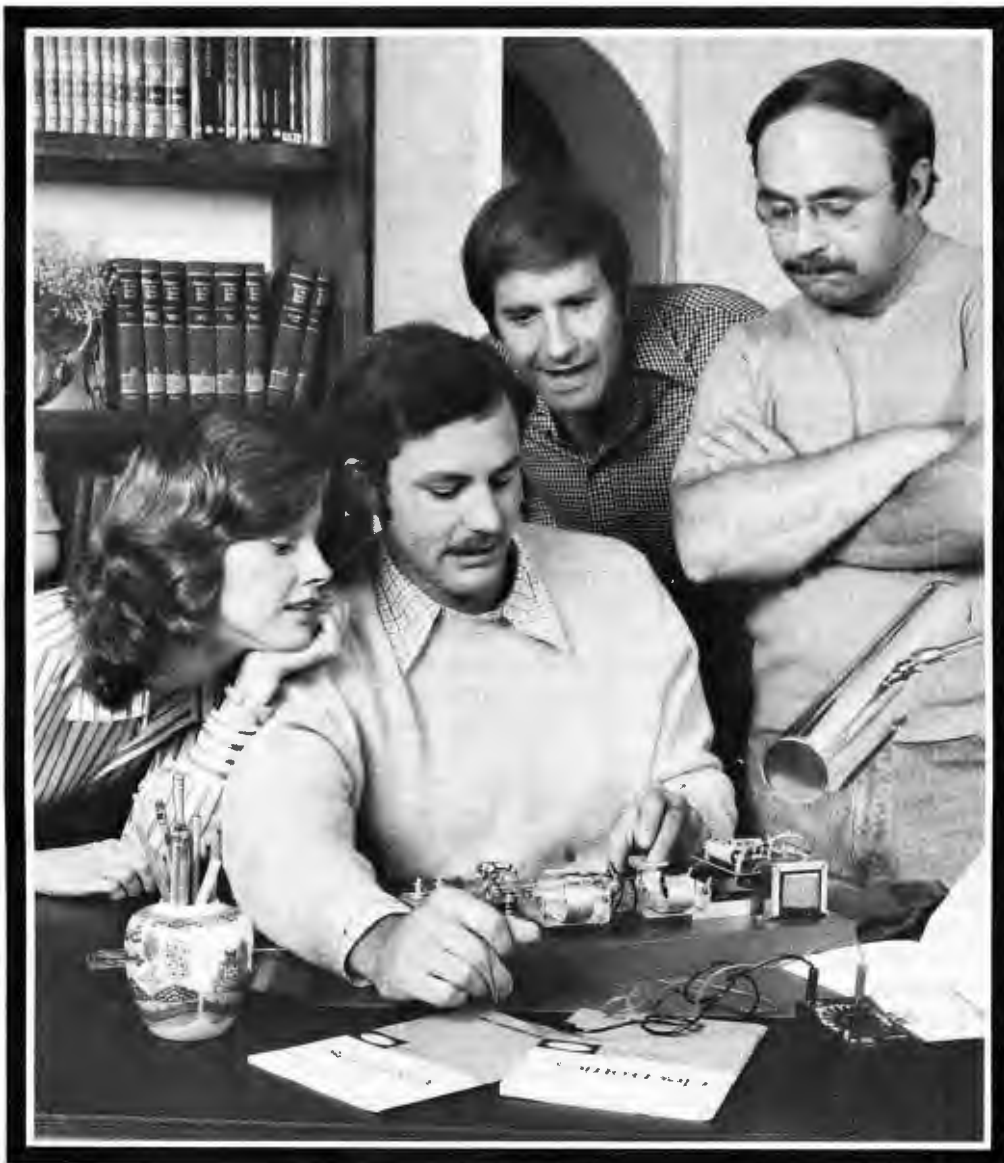**Herb takes his future seriously. Without worrying about it. He knows his CIE training is giving him valuable skills in electronics. Skills a lot of people will be glad to pay for. And that's good reason for all the optimism in the world. How about you?**



Learning new skills isn't something you just breeze through. Especially in electronics. You've got to really *want* success if you're going to build your skills properly.

Herb knew that right from the start. But he also knew what rewards he could earn if he took some time and did it right. He knew that, in today's world, people who really *know* electronics find a lot of other people... even whole industries... looking for their help.

How about you? How much do you want that thrilling feeling of success... of being in demand? Enough to work for it?

### Why it pays to build skills and know-how.

One of the things that got Herb interested in electronics is that electronics seems to be something just about *everybody* needs. Almost everywhere you look these days—in a business office... a manufacturing plant... a department store... a doctor's office... a college... even your own home you'll find all kinds of electronic devices.

That spelled "opportunity" to Herb. Plus he liked the idea of having a set of skills that might lead to jobs in places as different as a TV station... a hospital... an airport... a petroleum refinery.

But what Herb liked *most* about electronics is that it's just plain *interesting*. Even though it takes time and effort to learn, the subject is so fascinating it *almost* doesn't seem like "studying" at all!

### How CIE

### keeps you interested.

CIE's unique study methods do a lot to *keep* you interested. Since electronics starts with ideas... with principles... CIE's Auto-programmed® Lessons help you get

the idea—at your own most comfortable pace. They break the subject into bite-size chunks so you explore each principle, step by step, until you understand it thoroughly and completely. *Then* you start to use it.

### How CIE helps you turn ideas into reality.

Depending on the program you choose, CIE helps you apply the principles you learn in a number of different ways.

If you're a beginner, you'll likely start with CIE's Experimental Electronics Laboratory. With this fascinating workbench lab, you actually perform over 200 experiments to help you grasp the basics! Plus you use a 3-in-1 precision Multimeter to learn testing, checking, and analyzing.

In some programs, you build your own 5MHz triggered-sweep, solid-state oscilloscope—and learn how to "read" waveform patterns... how to "lock them in" for closer study... how to understand and interpret what they tell you.

To help you develop practical, skill-building knowledge you then receive a Zenith 19" diagonal



solid-state color TV featuring nine removable modules. You learn how to trace signal flow... how to detect and locate malfunctions... how to restore perfect operating standards.

### What to do first.

Get all the facts. Send for CIE's FREE school catalog and career information package TODAY. Check *all* the CIE programs—and see which one's right for you. Do it now.


### Why it's important to get your FCC License.

More than half of CIE's courses prepare you for the FCC License exam. In fact, based on continuing surveys, better than 4 out of 5 CIE graduates who take the exam get their License!

That's important. For some jobs in electronics, you *must* have your FCC License. For others, employers often consider it a mark in your favor. It's *government-certified proof* of specific knowledge and skills!
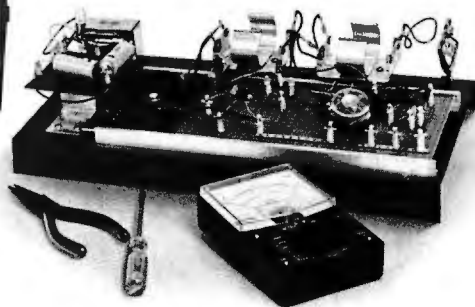
### Free catalog!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name of this magazine. We'll send you a copy of CIE's FREE school catalog—plus a complete package of independent home study information! For your convenience, we'll try to have a representative call to help you with course selection. Mail the card or coupon... or write: CIE, 1776 East 17th Street, Cleveland, Ohio 44114.



## CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114

Accredited Member National Home Study Council

☐ **YES...** I want to succeed in electronics. Send me my FREE CIE school catalog—including details about all electronics courses—plus my FREE package of home study information! PE-19

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_ (please print) APT. \_\_\_\_\_  
CITY \_\_\_\_\_  
STATE \_\_\_\_\_ ZIP \_\_\_\_\_  
AGE \_\_\_\_\_ PHONE (area code) \_\_\_\_\_

Check box for G.I. Bill information: ☐ Veteran ☐ Active Duty

## Mail today!






# BUILD THE 35-mm Slide Syncer

*A low-cost programmer for  
audio-visual presentations.*

**T**HE Slide Syncer is a programming device which enables you to record musical or talking material and a slide projector advance signal on the same tape track. It can be built using readily available, inexpensive parts, and will provide reliable and quiet performance. Incorporated into the Slide Syncer is a speaker for use with the external speaker jack on a cassette or open-reel tape recorder. The self-contained power source consists of four "AA" cells which should last for one year with moderate use.

**About the Circuit.** As shown in Fig. 1, IC1, a 567 tone decoder phase-locked loop, is the heart of the Slide Syncer. This eight-pin DIP contains a

POPULAR ELECTRONICS

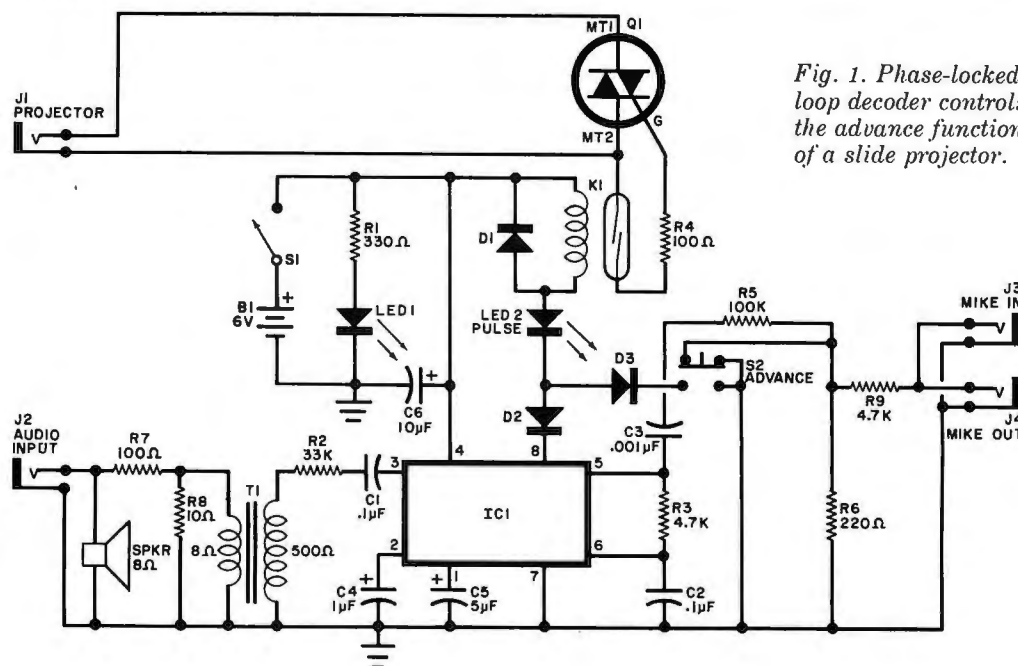

## PARTS LIST

C1, C2—0.1- $\mu$ F Mylar or disc ceramic capacitor  
C3—0.001- $\mu$ F disc ceramic capacitor  
C4—1- $\mu$ F, 10-volt electrolytic capacitor  
C5—5- $\mu$ F, 10-volt electrolytic capacitor  
C6—10- $\mu$ F, 10-volt electrolytic capacitor  
D1, D2, D3—1N4001 diode  
IC1—567 tone decoder PLL IC  
J1— $\frac{1}{4}$ " insulated phone jack  
J2, J3, J4—miniature two-conductor open-circuit phone jacks

K1—4.8-volt reed relay with SPST contacts  
LED1, LED2—20-mA light emitting diode  
Q1—200-volt, 6-ampere triac (Radio Shack 276-1001 or equivalent)  
The following resistors are 1/4-watt, 10% tolerance components.  
R1—330 ohms  
R2—33,000 ohms  
R3, R9—4700 ohms  
R4, R7—100 ohms  
R5—100,000 ohms  
R6—220 ohms

R8—10 ohms  
S1—Spst switch (see text)  
S2—Spdt pushbutton switch  
SPKR—8-ohm, 4" × 2½" (10.2 × 6.7 cm)  
oval speaker — Sanyo R-S6367A or  
equivalent  
T1—8-ohm/500-ohm audio transformer  
(Radio Shack 273-1381 or equivalent)  
Misc.—Suitable enclosure, shielded ca-  
ble, hookup wire, dry transfer lettering,  
printed circuit or perforated board, IC  
socket or Molex Soldercons, hookup  
wire, solder, machine hardware, etc.

control oscillator, phase-locked circuitry, and an output stage that can sink up to 100 mA of direct current.

It is customary to use an external tone generator to trigger the 567. However, the output of an external oscillator would have to be very close to the response frequency of the tone decoder for proper triggering to occur. This means that high-tolerance, low-drift components would have to be used. Fortunately, the output of the internal oscillator of the 567 can be picked off at pin 5 so the tone generated can be coupled from pin 5 to the microphone input of the tape recorder. Then it will be recorded on the same track as the commentary. The frequency at pin 5, determined by  $R3$  and  $C2$ , is exactly that which is required as an input signal to trigger the phase-locked loop.

When S2, a spring-loaded SPDT pushbutton switch, is tapped, the "beep" at pin 5 is coupled onto the microphone line (the hot side of J3 and J4) through C3 and the attenuating network R5R6R9. This switch also allows current to flow through the coil

of reed relay *K1*, *LED2*, and *D3*. When the relay contacts close, gate current is provided for triac *Q1* if a low-voltage source is connected to jack *J1*. This triac is used to control the slide advancing mechanism in the projector, which is most often an ac-actuated circuit.

However, there is no need to have the projector set up when you are recording a program. When *LED2*, the PULSE indicator, is lit, the command tone is being recorded on the audio track at about 10 dB down from the commentary level. The Slide Syncer eliminates the need for a two-track recorder (one track for the commentary, the other for the advance tone). But you will find that the tone is not loud enough to be distracting.

On playback, the audio output of the recorder is taken from the external speaker jack and applied to the Slide Syncer's internal speaker and transformer *T1* through *J2*, the audio input jack. Resistors *R7* and *R8* attenuate the audio to a level that *IC1* can handle. The drive signal for the phase-locked loop is coupled from the sec-

ondary of *T1* through *R2* and *C1*. When the tone that was taken from pin 5 and recorded on the tape appears at pin 3, pin 8 is grounded and sinks current for the coil of *K1* and *LED2* through *D2*. Then the contacts of *K1* close, and *Q1* turns on and activates the advance mechanism in the projector. The 567 will not sink current unless a sustained tone of the proper frequency appears at pin 3, so normal speech and music will not cause the projector to advance to the next slide.

Most inexpensive cassette recorders have better audio sections than their small speakers would lead you to believe. For this reason, the 8-ohm speaker is included in the Slide Syncer circuit. It is a 4" x 2½" (10.2 x 6.7 cm) oval speaker, and should improve the sound quality of your audio-visual presentations.

The Slide Syncer requires +6 volts dc at about 25 mA quiescent current, which increases to 47 mA when S2 is depressed. At these low current levels, four AA penlight cells mounted in a battery holder form an inexpensive power source.



**Construction.** The circuit is not too complex, so you can use perforated board or printed circuit construction techniques. Be sure to observe polarities on the electrolytic capacitors and the semiconductors. It is suggested that an IC socket or Molex Soldercons be used in mounting the 567 IC on the board. This will avoid heat damage to the chip. All LED's, jacks, and switches are mounted off the board. Use shielded cable for all audio lines.

The Slide Syncer should be mounted in an enclosure about  $6\frac{1}{2}'' \times$

$5\frac{1}{2}'' \times 2''$  ( $16.5 \times 14 \times 5.1$  cm). The speaker cutout can be made with a nibbling tool. Current limiting resistor *R1* is mounted on the lugs of *S1*. (The author used a DPDT slide switch wired as an SPST, with the unused contact lugs for tie points to the power leads and *R1* and *LED1*.) Jack *J1* should be insulated from the front panel if a metallic enclosure is used. Rubber or fiber washers can be used for insulation and mechanical support. A small bracket can be fashioned from a piece of scrap aluminum stock to secure the battery holder to the enclosure. Dry

transfer lettering can be used to label all jacks, LED's, and switches. Spray the lettering with clear Krylon spray after it has been transferred to the panel.

Prepare shielded jumper cables for the audio inputs and outputs (external speaker jack to *J2*, microphone jack to *J4*) and terminate them with plugs compatible with your cassette recorder. Connect a  $\frac{1}{4}''$  phone plug to the advance control cable from your projector.

**Checkout and Use.** Insert all plugs into their corresponding jacks, and plug the recorder microphone into jack *J3*. Record a short test program on the cassette recording, pushing *S2* each time you want the projector to advance to the next slide. Then turn the projector on and play back the tape. The projector should advance each time the control "beep" is heard.

The 567 tone decoder requires an input level of 100 to 500  $\mu$ V for reliable operation. The Slide Syncer is designed so that normal audio levels from a small cassette recorder placed in an average-sized living room will consistently advance the projector. Resistors *R8*, *R7*, and *R2* attenuate the audio to the working level of the IC. For high-volume audio-visual use—say, in a classroom—*R2* should be increased to a value between 68 and 82 kilohms. For low-level use, *R2* can be reduced to 10,000 ohms or so. If you prefer, you can mount these three attenuating resistors on the foil side of the printed circuit board so they can be easily changed (if necessary) to prevent false triggering.

The tone output from the Slide Syncer is very low, but is sufficient to trigger the tone decoder. However, if you have a recorder with automatic gain control, the advance tone will be loud on playback. If possible, use a recorder with a manual gain control to keep the tone almost inaudible. But the Slide Syncer will work with either type of tape recorder. The advance tone, using the values given for *R3* and *C2*, is about 2200 Hz. You can change it to any other frequency simply by using different values for these two components. You can also build two decoders sharing a common audio input and output to trigger two projectors. In that case, the two tones should be somewhat removed from each other—say, 1000 and 2200 Hz—so that each projector will advance only on its proper tone command.

**SPECIAL  
OFFER!**

**Buy 23-channel  
CB now. Get new  
40-channel later  
at  $\frac{1}{2}$  price!**

UPON FCC TYPE ACCEPTANCE

**"Don't be without CB while waitin' for the FCC"**  
NO MODIFICATION FEES—NO MODIFICATION DELAYS—OWN AND KEEP TWO UNITS



**handic®**

handic USA, Inc., 14560 NW 60th Ave., Miami Lakes, FL 33014  
THE ORANGE EQUIPMENT KNOWN FOR  
PROFESSIONAL QUALITY THE WORLD OVER

CIRCLE NO. 39 ON FREE INFORMATION CARD

# FLUKE PROVES AN INEXPENSIVE, HANDHELD DMM CAN BE BUILT WITHOUT LEAVING EVERYTHING OUT.

Let's face it.

Before now, if you bought an inexpensive, handheld digital multimeter you didn't get much—they just left most everything out.

We knew that was no answer.

So we built the 8030A 3½-digit DMM. It's a small, portable, inexpensive, handheld DMM, but it performs like our benchtop units.

With one basic difference. The 8030A was designed, built and tested to a size and shape proven best for field service and laboratory technicians. There's a built-in hood that can be slipped forward to shade the readout in sunshine. It has rms capability. The best overload protection. Diode test. It weighs 2.2 pounds, and will take a beating without failing. Finally, we guarantee accuracy specifications for one year.

And it only costs \$235\*.

True rms.	Fluke
1-year accuracy specs.	Fluke
High voltage protection.	Fluke
Diode test.	Fluke

A full line of accessories offering rf voltage, high current ac, high voltage dc, and temperature measurement probes. Fluke

*There's only one place to go for all the performance you need in a handheld DMM.*

There are measurement functions in five selectable ranges for dc volts, ac volts (true rms), dc current, ac current (true rms), and resistance. DC voltage measurement is from 100  $\mu$ V to 1100V with basic accuracy of  $\pm 0.1\%$ , ac measurement is from 100  $\mu$ V to 750V rms with basic accuracy of  $\pm 0.5\%$ . DC and ac current is from 100 nanoamps to 1.999 amps with basic dc accuracy of  $\pm 0.35\%$  and basic ac accuracy of  $\pm 1\%$ . Resistance measurement is from 100 milliohms to 2 megohms with a basic accuracy of  $\pm 0.4\%$ .

We added true rms response for ac measurements. Specified accuracy is still attainable when the measured waveform is distorted.



*"Fluke does the impossible again."*

There is extensive overload protection. It has been tested with transients up to 6000V peak across the input terminals.

Options include two battery operations: a rechargeable NiCad for 8 hours operation and throw-away alkaline cells. Accessories include probes for measure-

ment of rf voltages, high current ac, high voltage dc and temperature.

80T-150 Temperature Probe	
Sensitivity:	1 mV/°C or 1 mV/°F
Accuracy:	
+15°C to +35°C ambient:	$\pm 2^\circ\text{C}$ (3.6°F) — 25°C to +125°C $\pm 3^\circ\text{C}$ (5.8°F)
—50°C to —25°C and +125°C to +150°C	
0°C to 15°C, 35°C to 50°C ambient:	Add 1°C (1.8°F) to above

*You can also get temperature measuring capabilities with the 8030A.*

And because the 8030A gives you so much in performance, let us remind you once more of the price.

Only \$235\*.


For the first handheld DMM that's small in size, small in price, but huge in performance.

For data out today, dial our toll-free hotline, 800-426-0361.

John Fluke Mfg. Co., Inc., P.O. Box 43210, Mountlake Terrace, WA 98043  
Fluke (Nederland) B.V., P.O. Box 5053, Tilburg, The Netherlands.

Phone: (013) 673-973 Telex: 52237

\*U.S. price only.

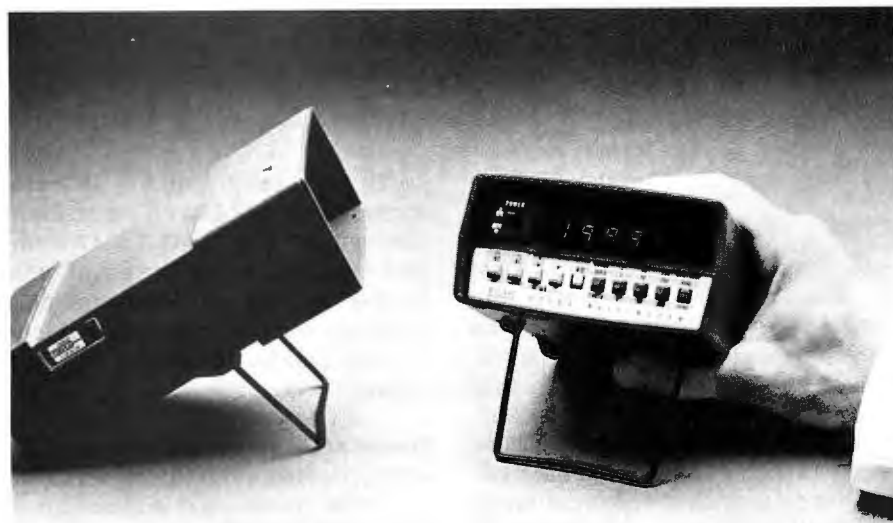

**A NEW ADVANCE. 8030A DMM. **





# Product Test Reports

## ABOUT THIS MONTH'S HI-FI REPORTS


*In addition to being a very fine 10-octave equalizer, the Spectro Acoustics Model 210 has enough front-panel switching to permit completely flexible operation. It can be used with a tape deck or any other program source you can use with your amplifier. Part of the excellent performance of the Model 210 can be credited to its gyrator inductors, which replace the usual bulky, hum-sensitive wire-wound components.*

*Pickering, in its broad line of cartridges, offers units that share a common body and electrical configuration, differing only in stylus parameters and prices. The XV-15 series illustrates this philosophy. The newest member of the series, the XV-15/625E, is third from the top of the line in tracking ability, yet has frequency response and sonic characteristics almost identical to other members of the family. However, this cartridge tracks at forces between 1 and 1.5 grams, making it ideal for use in high-grade automatic record players. Our tests also show that it has above-average ability to play heavily recorded discs with low distortion.*

—Julian D. Hirsch
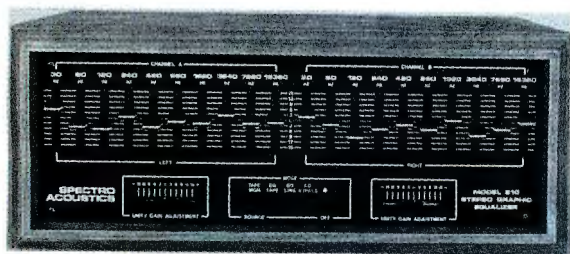
## SPECTRO ACOUSTICS MODEL 210 GRAPHIC EQUALIZER

*Features great versatility; uses gyrator inductors.*



On the Spectro Acoustics Model 210 stereo graphic equalizer there are 10 separate

octave-band controls to adjust the frequency response of each channel. The center frequencies of the octave filters are at 30, 60, 120, 240, 480, 960, 1920, 3840, 7680, and 15,360 Hz. The slide-type potentiometers in each octave range provide a boost/cut range of  $\pm 13$  dB within each filter passband. The Q of the filters, which is  $2.5 \pm 10\%$ , has been selected to provide maximum versatility in shaping the frequency response with a minimum of ripple.

The equalizer measures 17"W  $\times$

6½"D  $\times$  6"H (43.2  $\times$  16.5  $\times$  15.2 cm) and weighs 6 lb (2.7 kg). It is also available with a 19"  $\times$  7" (48.3  $\times$  17.8 cm) rack-mounting panel. The equalizer is finished in black with white and blue markings and control knobs. It retails for \$295, plus \$40 for an optional wood cabinet.

**General Description.** The equalizer employs active circuit elements called "gyrators" to simulate inductors in its filters. The elimination of actual inductors in the signal-processing circuits makes it completely immune to induced hum from external fields. Since the overall gain of the signal channels can be considerably changed when several of the equalizer potentiomet-

ers are moved from their zero positions, there is a small horizontally oriented pot under each group of filter controls to change the gain of each channel by  $\pm 15$  dB and reestablish a unity-gain condition. With all controls centered, the gain of the equalizer is unity and its response is flat to within  $\pm 0.5$  dB from 20 to 20,000 Hz.

The operating mode of the equalizer is controlled by five pushbutton switches located at the lower center of the front panel. One button controls the power and has adjacent to it a red LED that glows when power is on.

The equalizer is normally connected into an audio system via the recording inputs and outputs, but it can also be installed between the preamplifier and power amplifier. A duplicate set of tape input and output jacks is provided on the rear apron of the equalizer so that the tape facility is not lost when the equalizer is connected to an amplifier or receiver. The TAPE MON pushbutton switch connects the tape recorder playback into the signal path for playing tapes or monitoring a recording while it is being made.

The EQ BYPASS pushbutton completely bypasses all of the equalizer's circuits. (The power need not be applied to the equalizer when this button is depressed.) The EQ LINE button is pressed for most normal operation of the equalizer, inserting the equalizer's circuits into the signal path and returning the equalized program to the amplifier. A most useful feature is the EQ TAPE button, which places the equalizer in the signal path going to the tape recorder. The program played through the amplifier can be either the unequalized input signal or the playback from the equalized recording. It is also possible to record an unequalized signal and place the equalizer in the recorder's playback line.

On the rear apron of the equalizer are all the input and output jacks, the tape recorder jacks, and a single unswitched ac accessory receptacle.


The equalizer is designed to do only one thing—modify the frequency response of a program to compensate for sound-system or listening room deficiencies. Its noise and distortion have been reduced to the point where they can barely be measured, much less heard. With all controls centered, the signal-to-noise ratio is rated at better than 90 dB below 2 volts. Since the equalizer can deliver a maximum of 10 volts rms, its total dynamic range can

be greater than 105 dB. The 600-ohm output impedance makes it possible for the equalizer to drive a 10,000-ohm load (the lowest that will be presented by any power amplifier) at full output. The input impedance of 30,000 to 50,000 ohms is compatible with any commercially made preamplifier or tape deck.

The distortion of the equalizer is specified at less than 0.05% at 1 volt output over the full 20-to-20,000-Hz audio range when the controls are set to the flat, or zero, positions. The IM distortion is rated at less than 0.0075% at any output up to 10 volts equivalent sine-wave signal with the standard 60- and 7000-Hz test signals.
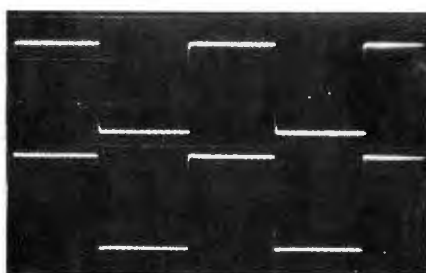
### Laboratory Measurements.

Measuring the distortion of the equalizer taxed the capabilities of our test instruments. Up to a 1-volt output, the distortion was less than 0.005% between 20 and 20,000 Hz. At 2 volts output, the results were the same, except that at the high end, the distortion reached 0.01%. At a 3-volt output, it was 0.01% to 0.018% over the entire audio range, while at 10 volts, just before clipping occurred, it was between 0.022% and 0.056%. The IM distortion reading was the residual of our Crown IM analyzer—0.002% to 0.003%—up to 3 volts output, reaching 1% at a 10-volt output. At the minimum measurement level of 60 mV, the IM was a negligible 0.01%.



*Response of the equalizer to 1000-Hz square-wave input.*

At 120 Hz, the hum was 82 dB below 1 volt, or 88 dB below the rated 2-volt output. The noise was not measurable, being less than the 100- $\mu$ V minimum indication of our meter. We could only determine that it was much better than 90 dB down, referred to a 2-volt output.

Each of the equalizer's filter controls had a range of  $\pm 13$  dB, and the shape of their individual response curves conformed to the expected response with a filter Q of 2.5. With the controls centered, the response was flat to within  $\pm 0.25$  dB from 20 to 20,000 Hz. A check with a 1000-Hz square-wave signal revealed that the phase characteristics of the equalizer were as good as its amplitude response (controls centered). The square-wave signal output was virtually indistinguishable from the input signal.

**User Comment.** It is generally agreed that an octave-band equalizer

is the most practical and effective means for correcting normal hi-fi system aberrations caused by speaker system and listening-room characteristics. Fewer than 10 bands would sacrifice versatility, while more bands would make adjustment too difficult. The center frequencies of the filters in this equalizer have been well chosen.

The equalizer comes with an instruction manual that could serve as an excellent primer on equalization techniques. It is also a model of how an instruction manual should be written. Only the omission of the equalizer's schematic diagram prevents us from giving the manual a 100% rating.

We experimented at some length with the equalizer and are convinced that it can do anything any other equalizer we have used can do and that it can do more than most of the others. The control switching is especially versatile, making it possible to equalize before or after a tape recorder, to listen to an equalized or unequalized signal (whether or not the recorded program is being equalized), or to replace the equalizer's circuits with, literally, a straight wire connection.

Our only criticism of the equalizer's design is that it has no center detents on the controls to simplify locating the flat positions. Otherwise, the equalizer represents an excellent hi-fi system accessory that is well worth its price.

CIRCLE NO. 80 ON FREE INFORMATION CARD

## PICKERING MODEL XV-15/625E PHONO CARTRIDGE

*Excellent tracking ability at moderate price.*



Pickering's XV-15 series of stereo phono cartridges includes a number

of models that share a common body and coils but have different stylus

characteristics. The interchangeable styli are designed for use with tracking forces as high as 5 grams and as low as 0.75 gram. They are rated according to what Pickering calls "Dynamic Coupling Factor" (DCF), which is essentially a measure of tracking ability, called "Track-A-Bility" by the company.

The latest addition to the XV-15 family is the Model XV-15/625E cartridge whose  $0.3 \times 0.7$ -mil elliptical stylus is designed to track with a force between 0.75 and 1.5 grams, with a nominal 1-gram rating. It is best suited for the higher-grade automatic turntables with low-friction tonearms as well as with manual players. The nominal output at 5.5 cm/s is 4.4 mV; recommended load is 47,000 ohms in parallel with 275 pF.

As with other Pickering cartridges, this new cartridge's stylus assembly has an integral hinged "Dustmatic" brush that rides on the record surface to remove surface dust. The brush can easily be removed if desired. When it is used, however, the indicated tracking force of the tonearm must be set 1 gram higher than the actual tracking force desired to compensate for the upward thrust of the brush.

The cartridge is supplied with snap-in plastic mounts that simplify installation in several popular record-player tonearms, including models from BSR, Dual, and Garrard. With the snap-in mounts, screws are not required to fasten the cartridge to the tonearm shell. Without the mounts, the cartridge can be installed in any tonearm in the conventional manner.




# The better the training the better you'll

Send for  
**FREE**  
illustrated  
career  
guide

NTS guide  
to careers in  
Electronics

IN-CIRCUIT TRANSISTOR TESTER  
COMPU-TRAINER  
TROUBLESHOOTER  
VOM

SOLID-STATE  
OSCILLOSCOPE

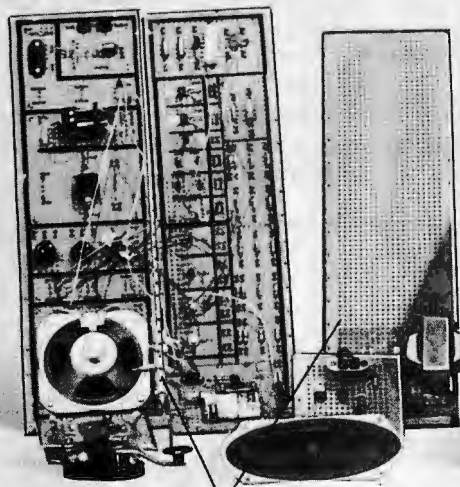

ELECTRO-LAB



(Simulated TV Reception)

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath Digital GR-2000 Solid State color TV** with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multimeter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

**Choose from 12 NTS courses** covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

**Compare our training; compare our lower tuition.** We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

# and the equipment be equipped.

COMPARE OUR  
KITS AND LESSONS.  
COMPARE OUR  
TUITION.



tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

**NO OBLIGATION. NO SALESMAN WILL CALL**

**APPROVED FOR VETERAN TRAINING**

Get facts on new 2-year extension

**NATIONAL TECHNICAL SCHOOLS**

TECHNICAL-TRADE TRAINING SINCE 1905

Resident and Home-Study Schools

4000 So. Figueroa St., Los Angeles, Calif. 90037

**NATIONAL TECHNICAL SCHOOLS**

4000 South Figueroa St., Los Angeles, Calif. 90037

Dept. 205-116

Please send FREE Color Catalog and Sample Lesson.  
NO OBLIGATION. NO SALESMAN WILL CALL.

- ☐ Color TV Servicing  
☐ B & W TV and Radio Servicing  
☐ Electronic Communications  
☐ FCC License Course

- ☐ Electronics Technology  
☐ Computer Electronics  
☐ Basic Electronics  
☐ Audio Electronics Servicing

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_ APT # \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

Please fill in Zip Code for fast service \_\_\_\_\_

- ☐ Check if interested in G.I. Bill information.  
☐ Check if interested ONLY in classroom training in Los Angeles.




The retail price of the Pickering Model XV-15/625E cartridge is \$59.95.

**Laboratory Measurements.** With the recommended load and the cartridge installed in the tonearm of a popular high-quality record player, the output signal level was about 3.5 mV at a velocity of 3.54 cm/s. The levels from the two channels differed by only 0.4 dB. The vertical tracking angle of the stylus measured 24°.

The cartridge tracked our high-velocity test records, including the low-frequency Cook 60 and the mid-frequency Fairchild 101 records, at its nominal 1-gram force. The 30-cm/s 1000-Hz tones of the Fairchild record were played with virtually no visible waveform distortion. At 1 gram, the cartridge played the 60-micron level of the German Hi-Fi Institute record. With an increase in stylus force to 1.5 grams, it played the 80-micron level. The performance at 1 gram is typical of many good-quality and medium-priced cartridges, while only a few of the best cartridges can cope with the 80-micron level of the 300-Hz tones on the test record. We used a 1-gram force for all other tests.

The frequency response of the cartridge, using the CBS STR 100 record, was very closely matched between the channels, sloping slightly downward at frequencies beyond 500 Hz and a small-amplitude high-frequency stylus resonance at about 18,000 Hz. The overall frequency response was a very good  $\pm 2$  dB from 40 to 20,000 Hz. Channel separation was somewhat better than that of most cartridges over the major portion of the audible range, measuring 25 to 30 dB up to nearly 10,000 Hz. It was still a good 12 dB at 20,000 Hz. The low-frequency resonance in the tonearm we used was at about 10 Hz.

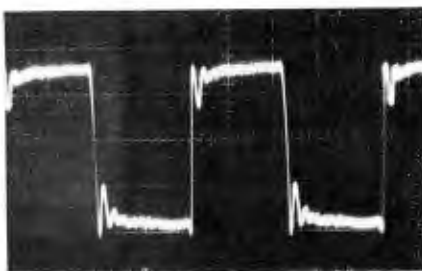We measured the tracking distortion with the aid of two Shure test records. The TTR-102 is an IM record that contains 400- and 4000-Hz tones recorded in a 4:1 level ratio at velocities from about 7 cm/s to 27 cm/s. The cartridge revealed a smoothly rising IM distortion characteristic over



*Square-wave response using CBS STR112 test record.*

that full range, increasing from about 1.7% at the lower velocities to 6% at the maximum level. This contrasts with the behavior of some cartridges, which may have slightly less distortion at low velocities but often mistrack and severely distort well below the maximum level on the record. There is probably little to choose from between the two types of cartridge distortion, since both have satisfactorily low levels at the velocities found on most commercial recordings, which rarely exceed about 15 cm/s.

The second test used the Shure TTR-103 record, a high-frequency tracking test involving 10,800-Hz tone bursts at a 270-Hz repetition rate. Failure to track the specially shaped bursts results in an increase in the 270-Hz component of the cartridge's output. In this test, the Pickering cartridge had low distortion, measuring less than 1% up to about 20 cm/s and a smooth rise to 3.8% at 30 cm/s.


The square-wave response, using the CBS STR112 record, revealed an almost perfectly square output

waveform, with one or two cycles of moderate-amplitude ringing at the 18,000-Hz stylus resonance. A listening test of tracking ability, using the Shure TTR-110 "Audio Obstacle Course—Era III" record, confirmed the excellent tracking ability of the cartridge. At 1.5 grams, the cartridge handled everything on the record with ease; but at 1 gram, it mistracked on the highest level of the sibilance test and sounded strained at the highest levels of bass drums and violins.

**User Comment.** The cartridge sounded much as one would expect it to from its measured performance. The sound was very smooth and natural. In fact, those listeners who expect sparkle and dazzle from a cartridge will be disappointed in the Model XV-15/625E's relatively bland sound. To us, however, this is a sign that the cartridge is not significantly altering either the waveform or the frequency balance of a record it is playing at the time.

Perhaps if one selected some especially difficult recording, it would be possible to find something the cartridge could not track. But among the various records we heard, the cartridge was always unstrained and thoroughly unflappable, even when operated at a 1-gram tracking force. Our conclusion, therefore, is that this moderately priced cartridge for today's market represents an excellent value for any purse.

CIRCLE NO. 81 ON FREE INFORMATION CARD

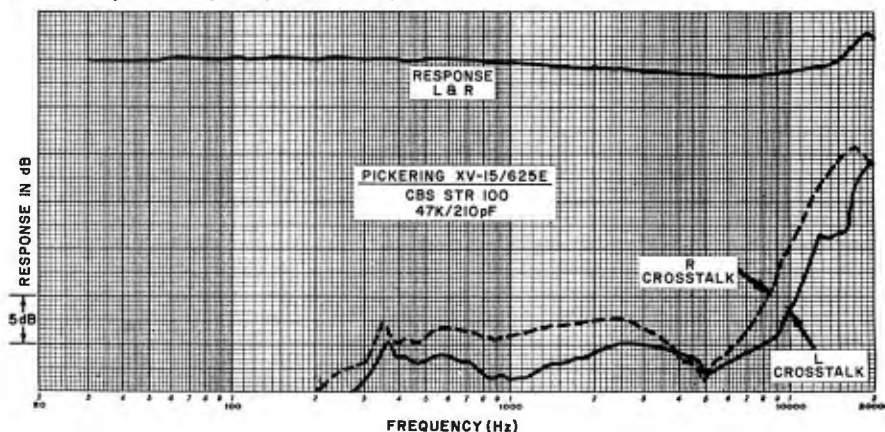

*Left and right response and crosstalk.*

## SILTRONIX MOHAWK AM CB MOBILE TRANSCEIVER

*Popularly priced, compact unit with frequency synthesis.*

**T**HE Siltronix Mohawk is a compact AM CB mobile transceiver, employing crystal frequency synthesis to provide operation on all 23 CB chan-

nels. Among its standard features are adjustable squelch, volume control with on/off switch, r-f gain control, switchable automatic noise limiter

(anl), S/r-f meter, PA operation, external-speaker jacks, full legal power, and detachable high-impedance dynamic microphone. The transceiver is designed to be operated from any nominal 12-volt dc positive- or negative-ground mobile electrical

POPULAR ELECTRONICS

system. Built into its power supply are a line filter and reverse-polarity protection.

The transceiver measures  $9\frac{1}{2}$ "D  $\times$   $6\frac{1}{2}$ "W  $\times$   $2\frac{7}{16}$ "H (24.1  $\times$  16.5  $\times$  6.2 cm). It retails for \$169.95.

**General Description.** The receiver section employs dual conversion with a first i-f of 10.000, 10.010, 10.020, or 10.040 MHz, obtained by heterodyning the CB signal with one of six crystals in the 16.965-to-17.215-MHz range, depending on the channel selected. The first i-f signal is then converted to a 455-kHz i-f by beating the first i-f signal with one of four crystal frequencies in the 9.545-to-9.585-MHz range and using the difference frequency that results.



The receiver's grounded-base r-f stage is diode protected. The r-f gain control is a potentiometer that functions as a variable attenuator at the antenna input. Grounded-emitter transistors are used in the remaining stages that make up the receiver. There are two mixers, followed by a ceramic filter that feeds the two i-f stages. The filter provides the i-f bandpass and selectivity. R-f selectivity for good image and other unwanted-signal rejection, while maintaining a uniform bandpass over the CB range, is ensured with a double-tuned antenna-input circuit.

A voltage-doubling detector and a series-gate anl precede the audio section that consists of three stages, including a class-B output section that is also used for PA operation and modulating the transmitter. Voltage-doubling diode rectifiers provide a high degree of agc. A single diode rectifier at the i-f output provides voltmeter action for the S meter. An amplified squelch is activated by a separate voltage-doubling agc-type setup.

The transmitter frequency is obtained by using the sum of one of the

nominal 17-MHz synthesizer crystal frequencies and one of four crystal frequencies in the 10.000-to-10.040-MHz range. The transmitter mixer for this purpose is a dual-gate FET, followed by a triple-tuned bandpass circuit for minimizing spurious output responses.

An unusual setup is that there is a buffer stage preceding the r-f section. The r-f section consists of predriver, driver, and power-amplifier stages. The output section for matching to a 50-ohm load consists of a multisection network that includes a TVI trap.

Another not often found arrangement is that the driver and power-amplifier stages are operated in a grounded-collector configuration and are both emitter modulated. Automa-

tic modulation control (amc) is built-in. Antenna and other switching is accomplished with a relay.

**Test Results.** We measured the receiver sensitivity at  $0.4\mu\text{V}$  (rated  $1\mu\text{V}$ ) for 10 dB (S + N)/N at 30% modulation and 1000 Hz. Image rejection and i-f signal rejection were 72 and 80 dB, respectively. Other unwanted spurious-signal rejection was a minimum of 60 dB. Adjacent-channel rejection and desensitization measured 40 to 45 dB. The overall 6-dB audio response was 300 to 3000 Hz. Audio output power with a 1000-Hz sine-wave test signal at the onset of clipping was 2 watts at 8% THD into 8 ohms.

The squelch threshold sensitivity range was from 0.3 to 1000  $\mu\text{V}$ . The agc figure of merit exhibited only a 4-dB audio output change with an r-f input change of 80 dB at 1 to 10,000  $\mu\text{V}$ . The meter registered S9 with a nominal input signal of 100  $\mu\text{V}$ .

With the transceiver operated in the receive mode from a 13.8-volt dc source, the current drain was 0.2 to 1.5 ampere.

# FREE EICO CATALOG

## 358 Ways To Save On Instruments, Citizens Band, Burglar Alarms, Automotive & Hobby Electronics!

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

**"Build-it-Yourself" and save up to 50% with our famous electronic kits.**

For latest EICO Catalog and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

**EICO—283 Malta Street,  
Brooklyn, N.Y. 11207**

*Leadership in creative electronics  
since 1945.*



CIRCLE NO. 23 ON FREE INFORMATION CARD



Using the same 13.8-volt dc source, the transmitter carrier output measured 4 watts. (This was also the power indicated on the rig's r-f output meter, which is calibrated in actual watts when working into a 1:1 SWR.)

Raising the microphone input level 16 dB above that required for 50% modulation held the modulation to a sine wave at 100% modulation with 12% THD at 1000 Hz. Adjacent-channel splatter under this condition was 50 dB down. The mike gain with voice operation was quite high, resulting in greater than 16 dB of compression and a tendency toward clipping and negative-peak overmodulation. Nevertheless, the splatter still held to within 50 dB down.

**User Comment.** The selector control is a good size and easy to manipulate. The r-f gain, volume, and squelch controls are rather small, with a bark-like grip to make it easy to "feel" or see their positions. The PA/CB and ANL ON/OFF switches are miniature toggles types.

The pointer of the edgewise-mounted meter is readily visible. A lamp illuminates the meter on transmit to provide an indication that the transmitter is live. Although the channel selector's numerals are quite small, they are easy to read under most conditions.

When operating the transceiver, the setting of the volume control is a bit critical, requiring only a slight ad-

vance for normal output volume. The S meter was very sensitive, moving about 25% upscale with r-f input signal level of nominally 1  $\mu$ V. The performance of the anl was most effective in the presence of low-level signals (less than 5  $\mu$ V), for which it is mostly needed. In this respect, noise attenuation could be improved even more by reducing the r-f gain while still maintaining an adequate signal level for good readability. This is also a good measure for reducing normal background noise since the overall gain of the receiver is quite high.

There is no volume control for PA operation. The speaker, as usual, faces down.

CIRCLE NO. 82 ON FREE INFORMATION CARD

## SCHOBER THEATRE ORGAN KIT

*Produces true cinema-organ sound in a compact, curved step-board design.*



**T**HE OLD cinema pipe organ, sometimes called a "theatre organ," never failed to entertain and intrigue listeners. The rich, wide-ranging sounds and special effects produced by those instruments are still available today in some electronic organs.

The Schober Theatre Organ kit is an example of the genre—in compact form. It can give an excellent impression of the exciting tones and special effects reminiscent of the original theatre pipe organ. Moreover, it suggests the pipe organ's appearance through a curved stop board that has 48 colorful, illuminated tongue tablets—including 35 voice stops with five pitch registers and eight percussion stops. The solid-state organ's two 61-note keyboards and 25 flat, radiating pedal claviars cover eight octaves of tone. There are also four couplers, three intensity settings of vibrato, pedal balance control, manual balance control, and percussion balance control.

The Theatre Organ is available as a

series of sub-kits. Kit No. ETC-1 consists of all the electronic sections that make up the organ (\$849.50). Kit No. BTC-1 includes all the special organ parts such as keyboards, stop tablets, swell shoe, and final-assembly materials (\$907.50). Kit No. PTC-4 includes the pedal clavier assembly made up of a 25-note, full-length pedal/switch assembly (\$199.50). Kit No. CTT-1, priced at \$529.50, includes the organ console and bench that must be assembled from precut and preshaped pieces of walnut and walnut-veneered lumber, plus all materials needed for furniture finishing. A considerable number of options are available. Included here are the percussion group kit, and a variable echo device Schober calls the "Reverbatape" kit.

The organ measures 50"H x 44"W x 41"D (1.3 x 1.1 x 1.0 m) with pedals. It weighs approximately 225 lb (102 kg).

**Kit Assembly.** According to Schober, the estimated assembly time for the organ is between 200 and 300 hours, which gives some idea of the complexity of the kit. We spent slightly more than 250 hours assembling our kit. In essence, this is a two-step kit: assembly of the electronic portion and assembly and finishing of the fine-furniture cabinet. One must exercise patience in accomplishing both steps.

Each of the printed circuit boards that make up the kit comes in a separate package that contains all the components to be mounted on the board with assembly instructions.

The pc boards are well made. All component locations are clearly iden-

tified on the top sides of the boards, and in many cases the foil sides too. Sockets are provided for every transistor, numbering in the hundreds. All components appear to be of the highest quality.

The circuit-board assemblies are more densely packed than in most other kits we have assembled. Even so, the boards are easy to wire. Each board has rubber feet to facilitate proper mounting and spacing. External connections to the pc board assemblies are made via tubular terminals, each clearly identified.

Because of the interlocking nature of the many circuits that make up the organ, the only elements that can actually be tested after assembly are the power supply and the 12 tone-generator boards. (The tone generators are stand-alone audio oscillators.) After checking that the power supply is delivering the proper output, each generator board is in turn connected to it; any type of audio amplifier is used to check for the various tone outputs. At this time, each board can be tuned to the correct frequency. Although the use of a frequency counter is suggested for the tuning procedure, it is not really needed because the coil/capacitor tuning elements come pretuned from the factory. If they need adjustment, only a minimum of "touching up" is required. In our kit, the tone oscillators were pretty much "on the nose" during testing.

At first glance, the various wood pieces look as though they are impossible to assemble into the finished organ console. In reality, however, the console goes together quite easily.

Each piece of wood is supplied carefully cut to size, drilled and shaped as required. Pieces exposed to view are either solid walnut or walnut veneer.

Lots of glue and screws are used in assembling the console. This results in a very rigid, durable structure. After assembling the main body of the console, one gets a pretty good idea of what the finished organ will look like and how much it weighs. We recommend that if you decide to build this organ, you assemble it in the same location where it will be used—it is that large and heavy.

Before the keyboards, stop-tablet horseshoe, pedal assembly, and electronics are installed, the exterior of the console must be finished. This involves the use of several grades of fine sandpaper, special stain and finishing compounds, and plenty of elbow grease. Once the console is sanded and stained, the first finish coat is applied. By this time, if care was exercised on the sanding and staining process, the console will reveal its fine-furniture qualities. (Schober supplies enough material for many finish coats, but leaves the number up to the builder.)

The 12 tone-generator assemblies fit into a small wooden "card cage" enclosure inside the console. The remaining board assemblies mount in various locations inside the console, each secured in place by its rubber feet. Then the keyboards mount in place, also with the aid of rubber feet.

Interconnections between the circuit-board assemblies, keyboards, power supply, and decoupling board are accomplished with lengths of color-coded hookup wire. It would have been nice if a wiring harness had been supplied, but we can understand the practicality and economy behind the decision not to provide one. In any event, interconnecting the various elements is not a difficult task. It is merely time-consuming.

The audio output of the organ is brought to a phono connector mounted on a small bracket on the back of the console. We connected the output to the AUX input of a home hi-fi system, crossed our fingers, and turned on the power. The small lamps over the voice-switch stop tablets in the horseshoe came on and illuminated the colored tabs. We then depressed a couple of tablets for each keyboard, put a foot on the swell pedal, and depressed it slightly, and touched a few keys on the keyboards.

Happily, there was the full sound of a real theatre organ filling the room. Once we knew the organ was operating properly, all we had to do was adjust the various trimmer potentiometers in accordance with the detailed instructions.

With the organ working, we put together the curved-leg bench and assembled the pedal clavier kit. The 25-note clavier kit keyboard is meant to be played with the toe of one foot, while the other foot is operating the swell shoe pedal. It contains 25 full-length maple struts and sharps made from unbreakable black plastic. The pedal clavier assembly slides into a slot on the bottom of the organ and is screwed into place. This completes the assembly of the basic organ.

The optional percussion group produces the sounds of a celesta, chrysoglott (organ harp), orchestral bells that can also be played with reiteration, piano, harpsichord, xylophone, and mandolin. It consists of a number of almost identical pc boards that mount inside the organ console along the rear brace. The activating switches for the percussion group mount directly below the top keyboard.

A considerable amount of wiring is required to install the optional percussion group, but the organ would really be incomplete as a theatre instrument without it. Schober suggests using a separate audio amplifier for this option, which we did.

The other option built and installed in the organ was Schober's "Reverbatape," a form of modified endless-loop tape recorder that provides a variable echo.

**User Comment.** Assembling the Schober Theatre Organ kit is obviously a major undertaking. Although a knowledge of electronics is not really necessary to complete the project, time and patience are. However, once completed, one has a magnificent-sounding musical instrument worth thousands of dollars more than the basic kit price. Moreover, the organ is a striking piece of furniture.

Although the organ is compact for its type, it does require more space than, say, a "spinet" organ. For example, its pedals, which are pivoted front and back, jut rather far out into the room. But the benefits of easier heel-and-toe playing are worth it if you have the space.

Most importantly, the "sound" of

this Theatre Organ is very impressive especially if you use good-quality audio equipment, which includes speaker systems with full, powerful bass response. This is truly a theatre-type organ, with the number and types of voices needed for full musical appreciation of light music of all types. (It can also be used to play organ classics, of course, but the choice of voices was not made for playing mostly "church" music.)

The organ's vibrato sound is very satisfying, with ample adjustment of the range achieved through a potentiometer that changes the frequency of a phase-shift oscillator. With this system, vibrato does not operate on the pedals, unlike most commercial types of popularly priced electronic organs. This is as it should be, since low pedal notes sound terrible with tremolo added.

The instrument's four couplers, which add stops from one manual to another and change pitch registers,

## SCHOBERT THEATRE ORGAN VOICES

### Solo (upper manual):

Tibia 16'	Oboe 8'
Cello 16'	Diapason 8'
Stentorphone 16'	Brass Trumpet 8'
Tuba Mirabilis 16'	Violina 4'
Viola d'Amore 8'	Tibia 4'
Vox Humana 8'	Tromba Clarion 4'
Solo String 8'	Piccolo 2'
Clarinet 8'	Fifteenth 2'
Tibia 8'	Flageolet 1'
	Fife 1'

### Accompaniment (lower manual):

Tibia 16'	Diapason 8'
Dulciana 8'	Harmonic Tuba 8'
Vox Humana 8'	Harmonic Flute 4'
Tibia 8'	Octave 4'
Orchestral	Tuba Clarion 4'
Strings 111	

### Couplers:

Solo to Solo 16'
Solo to Solo 4'
Solo Unison Off
Solo to Accompaniment 8'

### Pedal:

Dulciana 16'	Tuba Profunda 16'
Tibia 16'	Brass Flute 8'
Diaphone 16'	Tuba 8'


### Percussion Group (optional):

Celesta	Piano
Chrysoglott	Harpsichord
Orchestra Bells	Xylophone
Orchestra Bells (reit)	Mandolin


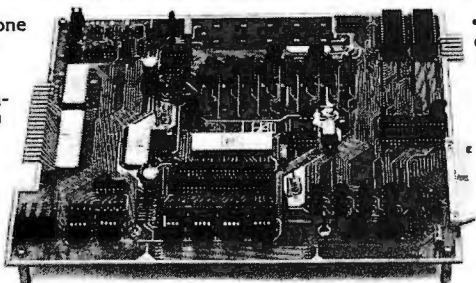
## If you want a microcomputer with all of these standard features...

- 8080 MPU (The one with growing software support)
- 1024 Byte ROM (With maximum capacity of 4K Bytes)
- 1024 Byte RAM (With maximum capacity of 2K Bytes)
- TTY Serial I/O
- EIA Serial I/O
- 3 parallel I/O's
- ASCII/Baudot terminal compatibility with TTY machines or video units
- Monitor having load, dump, display, insert and go functions



- Complete with card connectors
- Comprehensive User's Manual, plus Intel 8080 User's Manual
- Completely factory assembled and tested—not a kit
- Optional accessories: Keyboard/video display, audio cassette modem interface, power supply, ROM programmer and attractive cabinetry... plus more options to follow. **The HAL MCEM-8080. \$375**

## ...then let us send you our card.

HAL Communications Corp. has been a leader in digital communications for over half a decade. The MCEM-8080 microcomputer shows just how far this leadership has taken us... and how far it can take you in your applications. That's why we'd like to send you our card—one PC board that we feel is the best-valued, most complete



microcomputer you can buy. For details on the MCEM-8080, write today. We'll also include comprehensive information on the HAL DS-3000 KSR microprocessor-based terminal, the terminal that gives you multi-code compatibility, flexibility for future changes, editing, and a convenient, large video display format.

**HAL Communications Corp.**  
**Box 365, 807 E. Green Street, Urbana, Illinois 61801**  
**Telephone (217) 367-7373**

CIRCLE NO. 38 ON FREE INFORMATION CARD

## BREADBOARD CAPACITY YOU'LL NEVER OUTGROW.

No matter how big (or small) your circuit design and testing needs, we have the answer; CSC's QT Sockets and Bus Strips.\* The expandable, interlocking solderless breadboarding system that accommodates virtually all types of components with plug-in ease. Resistors. Transistors. DIP's. LED's. You name it. All instantly connect and reconnect without damage.


On your next project, save time, save money, save effort for as little as \$3.00.\*\* See your CSC dealer, or write for our catalog and distributor list.

CONTINENTAL SPECIALTIES CORPORATION



EASY DOES IT

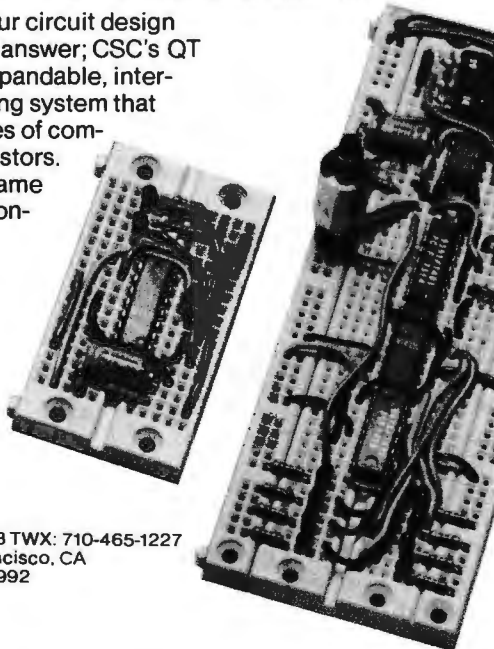44 Kendall Street, Box 1942  
New Haven, CT 06509 • 203-624-3103 TWX: 710-465-1227  
West Coast office: Box 7809, San Francisco, CA 94119 • 415-421-8872 TWX: 910-372-7992



© 1976, Continental Specialties Corp.

\*U.S. Pat. No. D235,554

\*\*Manufacturer's suggested list, QT-7S. Prices and specifications subject to change without notice.

CIRCLE NO. 18 ON FREE INFORMATION CARD


We are particularly pleased with the Percussion Group option. It provides eight special effects that give the feel and substance of the old cinema pipe organs (see box). The percussive "strike" is made when the key is pressed and the voice decays even if the key is held down. Thus, any other organ stops can be used when a key is held down. Two percussion voices—mandolin and xylophone—repeat constantly, while a separate orchestra bells reiteration tab is employed to repeat bells. Each voice represents the finest percussive simulation we have heard. For an authentic Theatre Organ sound, we would not be without this option.

Another option, Schober's Reverbatape unit in kit form, is an excellent means of achieving artificial reverberation. It uses a continuous loop of tape upon which a series of time-spaced repetitions of the program being played is recorded and reproduced in succession by three playback heads. Another head erases the material, and the cycle continues. A reverb control varies the time delay for a 60-dB decay of 0 to 6 seconds. To appreciate the effect of this reverb unit in combination with the organ, you must play an electronic organ with a spring-type reverb device. The former produces a realism that genuinely simulates a large room or hall, while the latter, although an improvement at low volume levels (it "twangs" at high volume levels) does not really fool the listener. But beware! Once you hear the Reverbatape unit, you will never again be satisfied without it.

There are other options available from Schober that we have not tried. For example, a proficient organist would probably wish to add Combination Action, an electro-pneumatic system of 10 buttons that can preset stop tablets and a cancel button to turn all present stops off. Less competent players could well add a rhythm assembly to imitate bongos, cymbals, snare drums, etc., and possibly an automatic rhythm device to provide a myriad of rhythms.

To fully appreciate the Schober Theatre Organ's potential, the audio gear used should be top notch, with at least 20 watts rms per channel power amplifiers for relatively high-efficiency speaker systems. Be sure, however, that your woofers can handle sustained 32-Hz tones without burning out.

CIRCLE NO. 83 ON FREE INFORMATION CARD

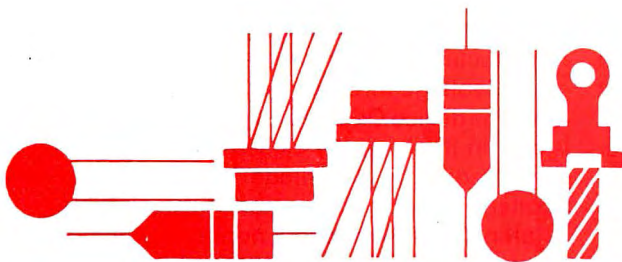

# Solid State

By Lou Garner

## RARA AVIS

**I**N CASE you've forgotten your high school Latin (or didn't study it), the title of this column, loosely translated, means "rare bird." And that's exactly what we're going to discuss this month—some of the "rare birds" among semiconductor devices. Not rare in the sense of availability, for most may be obtained through the larger industrial and better-stocked mail order distributors, but in terms of familiarity among hobbyists and experimenters.

n-channel JFET's with on-chip metallization to provide the source-gate short and a nominal pinch-off of six volts. Depending on type, current ratings range from 0.22 mA to 4.23 mA.

A sampling of constant-current diode applications is given in Fig. 2. Perhaps the simplest and most obvious is the constant current power supply, Fig. 2A. Here, the prime dc power source, whether batteries or a line operated

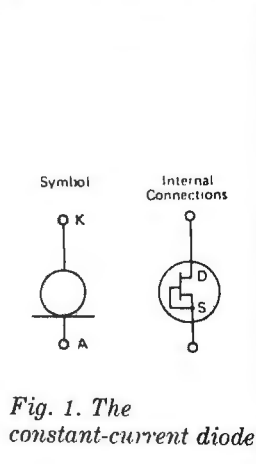


Fig. 1. The constant-current diode.

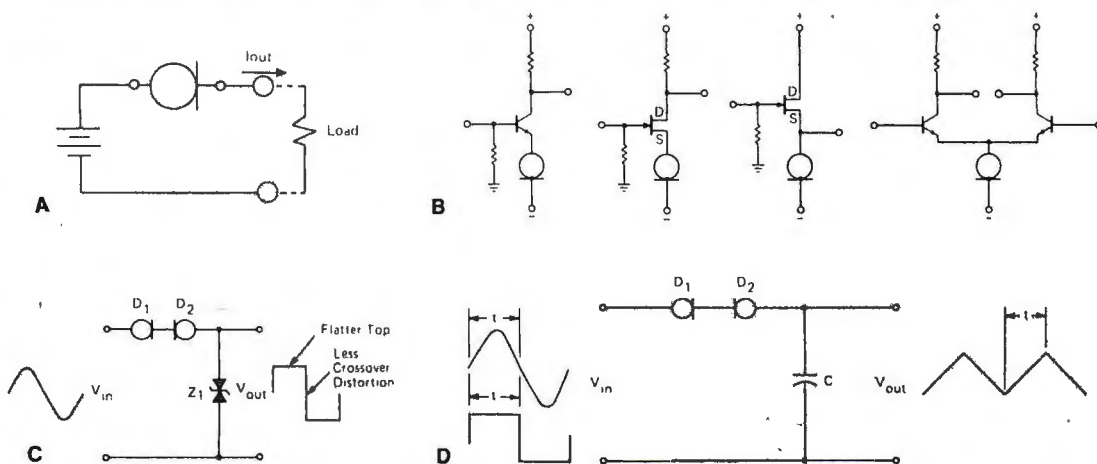


Fig. 2. Some applications for the constant-current diode.

Offered by several manufacturers, including Teledyne Crystallonics (147 Sherman St., Cambridge, MA 02140), the *constant current diode* is identified by a special schematic symbol as shown in Fig. 1. It is essentially a field effect transistor (FET) with an internal connection between its source and gate electrodes. Some firms refer to the device as a "current regulator diode." Regardless of its name, however, the internal short maintains a gate-to-source voltage of zero, causing the device to act as a high-impedance, constant-current source when operated at drain voltages higher than its pinch-off rating. Typical units are types 1N5283 through 1N5314, all of which are basically

power supply, is set for a voltage greater than pinch-off (i.e., 6 volts for the types listed above). Under these conditions, the load current will remain essentially constant at the value set by the diode regardless of variations in load impedance. The device also can serve as a constant-current bias source for bipolar transistors, FET amplifiers, FET emitter followers, and differential amplifiers, as shown in Fig. 2B.

For a change of pace, connect a pair of the devices back-to-back, add shunt back-to-back zener diodes, and you have a simple, but effective, square-wave generator or clipper, as shown in Fig. 2C. Due to the current limiting

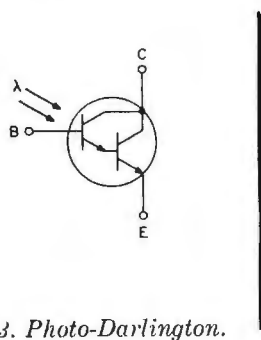


Fig. 3. Photo-Darlington.


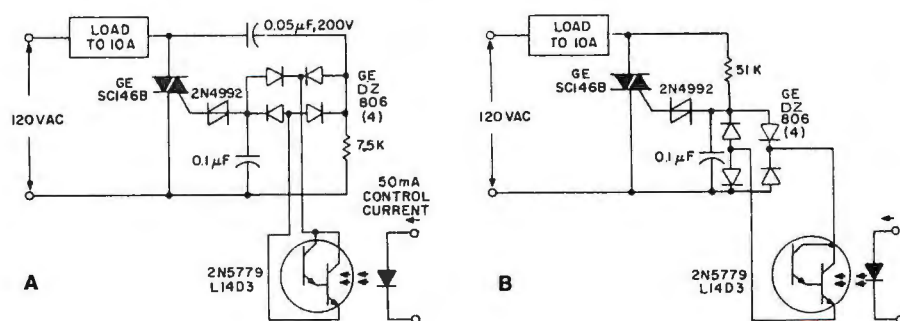


Fig. 4. Photo-Darlington applications: NO and NC relays.

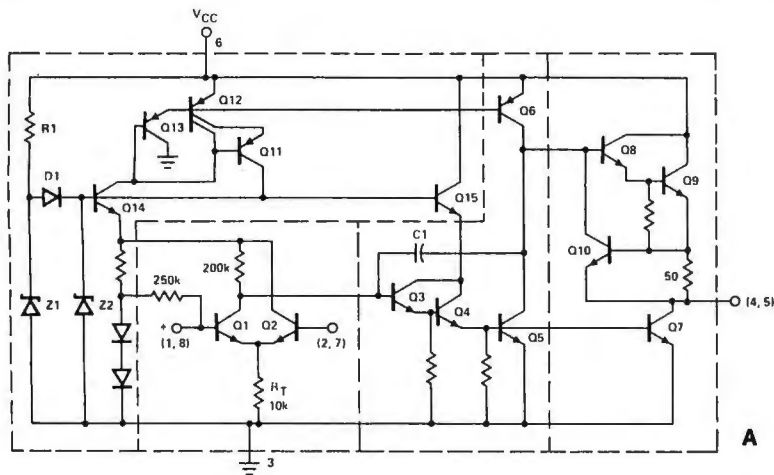

action of diodes *D1* and *D2*, this circuit provides an output waveform with a flatter top and less crossover distortion than the more conventional resistor-zener clipper. What's more, with a lower power dissipation, it's also a more efficient circuit. For optimum performance, the square-wave clipper should be driven with a signal several times larger than the zener diodes' voltage rating. Replace the zeners with a capacitor, and the circuit becomes a triangular wave shaper, as in Fig. 2D. Triangular output signals will be produced with either sine- or square-wave inputs, but the latter will provide a cleaner output waveform at zero crossover. The circuit's output amplitude is directly proportional to the diode current and the time period of a half-cycle is inversely proportional to the value of the shunt capacitor.



The photo-Darlington in another of our rare birds. Comprising photosensitive and amplifier transistors in a single package, (Fig. 3), the device behaves as if it were a single, but highly sensitive, phototransistor. It is capable of detecting changes in light levels as well as the absolute presence or absence of light. Photodarlingtons can be used in virtually all types of light-controlled systems and serve as rate sensors, frictionless potentiometers, smoke detectors, thickness gauges (for translucent materials), modulated-light-beam detectors, and sound-on-film detectors.

With suitable support circuitry, photo-Darlingtons can be used in solid-state relays, choppers, intruder alarms, card and tape readers, door openers, liquid level indicators and controls, safety interlocks, vehicle light controls, and various types of test equipment. Typical units are GE types 2N5777 through 2N5780, with  $V_{CE0}$  ratings of 25 and 40 volts and minimum  $h_{FE}$  (gain) specifications of 2500 and 5000, depending on type.

Two of the photo-Darlington's many possible applications are shown in Fig. 4—normally open (A) and normally closed (B) ac line-operated solid-state relays. Both circuits employ medium-current (10 A) triacs in conjunction with silicon bilateral switches (SBS). In each, the photo-Darlington is activated by a LED source to provide full line isolation.

In Fig. 4A, the photo-Darlington is connected across a diode bridge between the ac source and the SBS serving to trigger the triac. When the photodarlington is dark, it acts as a high impedance, preventing conduction through the bridge circuit and, therefore, the application of gate drive voltage through the SBS. The triac, then, remains in a nonconducting state. When a control current is applied to

the LED, illuminating the photo-Darlington, the latter starts conducting. This allows the diode bridge to conduct and apply voltage through the SBS to the triac's gate, switching this device On and permitting current flow through the load. In the normally closed circuit, Fig. 4B, the action is reversed. Here, the diode bridge is between the SBS's voltage source and circuit "ground." With the photo-Darlington dark and in a nonconducting state, the bridge also acts as a high impedance, allowing full drive voltage to be applied to the triac's gate through the SBS, thus holding the triac On and permitting current flow through the load. When the photo-Darlington is illuminated, however, it and, of course, the bridge shift to a low-impedance state, dropping the SBS's source voltage across the 51k series resistor and reducing the triac's gate drive below the level

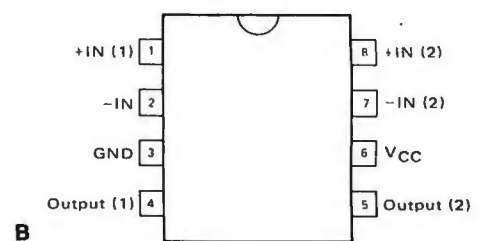


Fig. 5. Equivalent schematic (A) and pin connections (B) for LM387.

needed to maintain conduction. When this happens, the triac switches to a high-impedance or Off condition, blocking load current. In either of the light-controlled ac power switching circuits, the load can be a solenoid, lamp, heater, or other device, as long as the triac's maximum ratings are observed.

Although not "rare" in the same sense as the constant current diode and photo-Darlington, the LM387 dual preamplifier probably is not as familiar to most experimenters as are such devices as the 741 op amp or 555 timer, yet

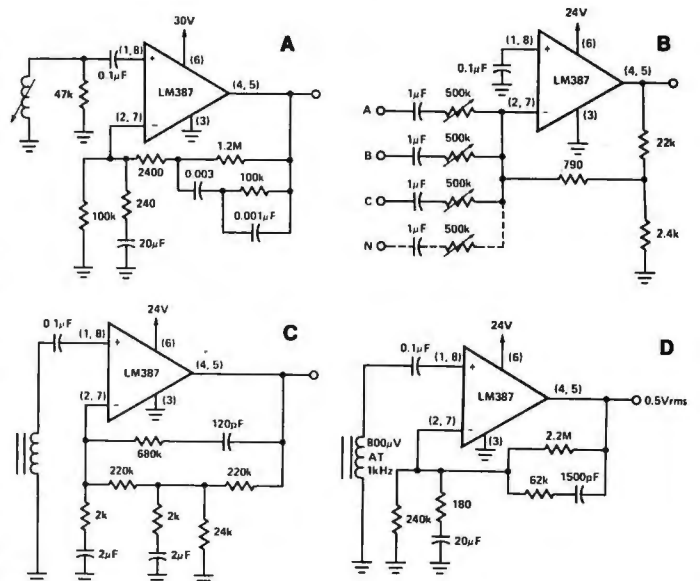



Fig. 6. Applications for the LM387 preamplifier.

it can be just as useful in quite a variety of projects. Manufactured by the Signetics Corporation (811 East Arques Ave., Sunnyvale, CA 94086), the LM387 is a low-noise device comprising some thirty transistors, four zeners, and six diodes in an 8-pin mini-DIP. Half of these are used in each of the independent preamp circuits, as shown by the equivalent single-channel schematic diagram, Fig. 5A. Actual lead connections are identified in Fig. 5B. The device features an internal power supply decoupler-regulator which provides 110 dB power supply rejection and 60 dB channel separation. In addition, it offers an open-loop gain of 104 dB, a noise level of only 0.8  $\mu$ V, an output voltage swing within 2 V of the dc source, and unity gain bandwidth of 15 MHz. With internal short circuit protection, the unit can dissipate up to 500 mW, and can be operated on single-ended dc supplies from 9 to 40 volts. It is internally compensated for all gains above 10, offers an input resistance of 100,000 ohms (or more), an output resistance of only 150 ohms, and a THD at 75 dB gain of only 0.1%.

Four of the LM387's many possible applications are illustrated in Fig. 6. A magnetic phono preamplifier is shown in Fig. 6A, a multi-channel audio mixer in Fig. 6B, a two-pole fast-turn-on NAB tape preamplifier in Fig. 6C, and a tape playback preamplifier in Fig. 6D. Only one channel is shown in each schematic, although both sets of input and output lead connections are identified. In addition to the suggested circuits, the LM387 can be used in the audio sections of radio transmitters and receivers, in TV sets, in intercoms, in hearing aids, in PA systems, and in many types of test instruments.

Chances are you have at least a nodding acquaintance with operational amplifiers, but how about *power* op amps—those with outputs specified at *multiwatt* rather than milliwatt levels? Such devices are offered by a number of manufacturers. Regardless of manufacturer or specific type, most of these share certain common characteristics. Most of them are hybrid rather than monolithic IC's, have comparatively limited bandwidth (though more than adequate for general audio applications), require heat sinks to realize their full output potentials, and are relatively expensive, although not overly so when compared to the cost of assembling an amplifier with comparable power output using discrete devices. The 833-21C is a typical unit. Manufactured by Beckman Instruments, Inc. (2500 Harbor Boulevard, Fullerton, CA 92634), the device can deliver output currents in excess of  $\pm 1$  A when operated on a  $\pm 12$ -V dc power source. With an open-loop gain of 100 dB, a full power bandwidth of 15 kHz, and a typical input impedance of 1 megohm, the 833-21C requires only one external compensation capacitor and two current-limiting resistors for proper operation. A hybrid device comprising a small-signal monolithic op amp and a complementary-symmetry power output stage using chip transistors, the unit is supplied in an 8-pin TO-3 package and is, therefore, no larger physically than a conventional power transistor.

**Reader's Circuits.** Indicating that he would welcome pen pals, one of our overseas readers, Ulf Nordquist (Fregas Väg 34, 240 21 Löddeköpinge, Sweden), contributed the circuits shown in Figs. 7 and 8. Ulf has specified standard American devices in his designs, implying that these must be readily available in Europe. In Fig. 7, a 555 timer (IC1) is used as the basis for an electronic "coin flipper" featuring red (LED1) and green (LED2) visual readouts.

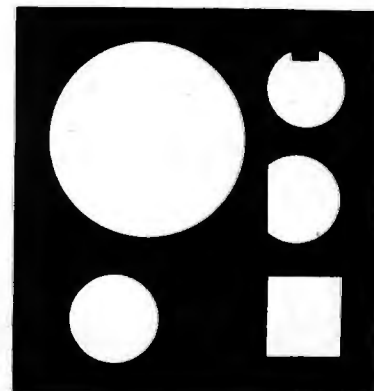

## Put more punch in your work.

With a Greenlee Chassis Punch you can punch clean, true holes in seconds. Round, square, key or D. In 16-ga. metal, hard rubber, plastic or epoxy. Available at radio and electronics parts dealers. Write for catalog E-730. Greenlee Tool Co, Rockford, Ill. 61101.

### GREENLEE TOOL CO

a subsidiary of

### Ex-Cell-O Corporation

CIRCLE NO. 37 ON FREE INFORMATION CARD

## 1702A MANUAL EPROM PROGRAMMER

Features hex keypad, two digit hex address and two digit hex data display. Controls include load, clear, go! (step), key/copy, data in/data out, and counter up/down. Profile card includes high voltage pulse regulator, timing, 8 bit address and 8 bit data drivers/receivers. Two 6½" x 9" stacked cards with spacers. Allows programming in 20 minutes — copying in 5 minutes. Requires +5, -9, and +80 volts.



ASSEMBLED ..... \$299.95  
KIT ..... \$189.95

### NOW

The best of two worlds... use our 1702 EPROM programmer as a manual data/address entry programmer... or connect it to your processor.

IMSAI/ALTAIR computer interface (requires 3 output ports, +1 input port) and software ..... \$49.95

Briefcase unit with power supplies and interface connectors (assembled and tested only) ..... \$599.95

### ANNOUNCING

Our NEW 16K Byte Pseudo-Static, IMSAI/ALTAIR compatible RAM. Single card slot. Uses less power than equivalent low power RAM. All memory chips socketed. Uses all prime, factory fresh ICs. High quality, two-sided, through-hole-plated circuit board. Crystal controlled, totally invisible refresh system requires NO software management. Just plug it in and use like STATIC memory.

Complete kit ..... \$349.95  
Assembled, tested, and burned in ..... \$549.95

### ASSOCIATED ELECTRONICS

12444 Lambert Circle • Garden Grove, CA 92641  
(714) 539-0735

CIRCLE NO. 10 ON FREE INFORMATION CARD



# BREAKER BREAKER

## ...for a 10-5 from the BLACK CAT®

Whether you're rolling in a convoy or copying the mail from your home twenty, you get a four roger every time with Black Cat® CB accessories from Wawasee Electronics. So if you've got your ears up copy the following list of rugged accessories:

- Antenna Whip
- JB 700 Mobile Antennas
- Trunk Lid Antenna Mount
- West Coast Antenna Mount
- 3-Ft. Jumper Cable
- 20-Ft. Jumper Cable
- Co-Phase Harness
- JB 1000 Dummy Load
- JB 1000 SM Oscilloscope / RF Wattmeter / SWR Bridge
- JB 2000 SW Power Meter / SWR Bridge



For a complete listing of all Black Cat® CB accessories and dealers, drop us a line and we'll get right back to you.

# WAWASEE ELECTRONICS

"HOME OF BLACK CAT® PRODUCTS"

Wawasee Electronics Co., Inc.

P.O. Box 36 • Syracuse, Indiana 46567

Phone: (219) 457-3191

With power on, the circuit is operated simply by touching a small metallic plate. In addition to the 555 and the two standard LED's, all that is required for assembly is four half-watt resistors, two small ceramic or plastic film capacitors, a spst switch (S1), a 9-to-15 volt battery (B1), a small touch plate (about 1 cm on each side), and, of course, wire, solder, a suitable case, and mounting hardware. Component values are not overly critical and, if desired, 1-k resistors can be substituted for the 470-ohm units specified for R1 and R2 to reduce battery current drain.

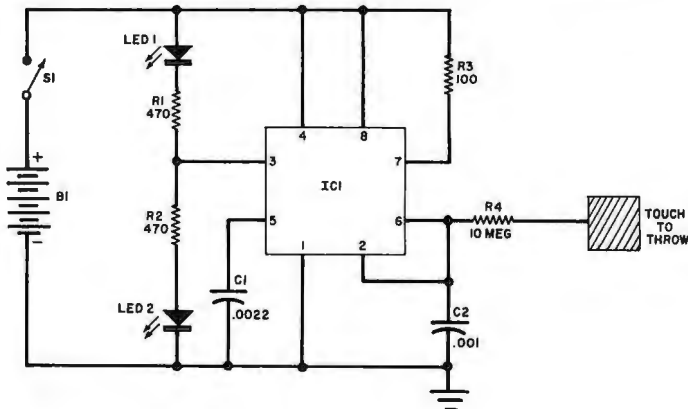


Fig. 7. Electronic coin flipper is operated by touching metallic plate.

Ulf's second circuit, Fig. 8, is an alternate LED flasher featuring a standard 7400 quad NAND gate IC. Here, a 5-volt dc power source is required and a large electrolytic feedback capacitor is employed to achieve a low flashing rate. According to Ulf, the value specified in Fig. 8 establishes a flashing rate of about 1 Hz. This rate may be increased by using a lower value or decreased (made slower) by using a higher value capacitor for C1.

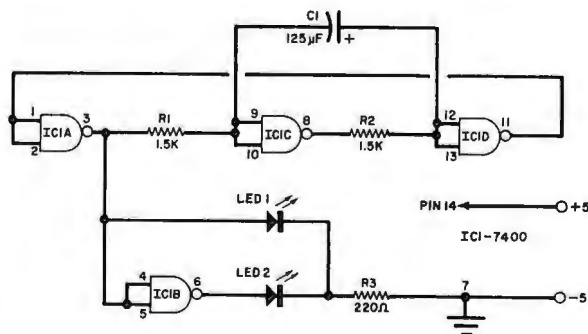


Fig. 8. Flashing rate of LED circuit is determined by value of large capacitor.

**Device/Product News.** Working with Tate Audio, Ltd. (4324 Promenade Way, Suite 311, Marina del Rey, CA 90291), the National Semiconductor Corp. (2900 Semiconductor Drive, Santa Clara, CA 95051) has developed a group of integrated circuits which will accurately separate and reproduce "quadraphonic" four-channel audio programs from phonograph records and tape cassettes. Designed to decode SQ™ (CBS) type programs, the Tate/National system employs three different IC's and is said to provide separation of channels in any direction approaching 40 dB from 20 Hz to 30 kHz while maintaining a signal-to-noise ratio of 70 dB and a THD of 0.05 percent.

# Three "power mike" gift ideas from Telex.

"Power mikes?" you say, "but two of them look like headsets." And you're right! And if you're a seasoned CBER

ready to move up, take a second look at the aviation-type Telex CB-88 power-mike headset. Your CB listening is private; lets others around you visit, relax or sleep without a blaring speaker. You hear better and transmit better. Weighs less than 3 oz. Uniquely, you can wear it without the headband by attaching it to your eyeglasses (adapter included). Check out the CB-1200, especially right for high-noise environments, and the aviation-inspired Double-Header power mike. Then move up to Telex, the quality standard of the aviation communications industry, now producing the most powerful CB gift ideas around. And if you want to drop a loud-and-clear hint, just tear out this ad and leave it where your gift-giver will find it...or take it to your Telex CB dealer for a gift-idea demonstration.



Can be worn without headband. Easy-to-use eyeglass adapter.



Boom pivots for left/right ear.

**CB-88**

Fully cushioned for comfort.

Soft earpiece adjusts to fit.

Boom adjusts for precise mike position.

Noise-cancelling variable-gain power mike.

Use as conventional power mike or as superior noise-cancelling, power mike thanks to Double-Header feature.

Built-in variable gain power amplifier.



Fully adjustable head band.

**CB-1200**

Fully cushioned to block out highway and vehicle noise.

Both headsets include in-line push-to-talk switch.

High quality mike with fixed-level FET amplifier.

Adjustable mike boom, 310° swivel, close to lips.

**CB-73**

Style used by pilots around the world, fits every hand.

Front mount ends mike fumbling. Mike comes off bracket in talk position. Rear mount also included.

Long-life coil cord.



The Pilot People

## TELEX

COMMUNICATIONS, INC.

9600 Aldrich Ave. So., Minneapolis, MN 55420 U.S.A.

Europe: 22 rue de la Legion d'Honneur 93200 St. Denis, France

Canada: Telak Electronics, Ltd., Scarborough, Ontario.

CIRCLE NO. 72 ON FREE INFORMATION CARD





# CB Scene

By Ray Newhall, KWI6010

## 40-CHANNEL EXPANSION AND PURAC II

**T**HE LATEST FCC rule-making decision adds 17 new AM/SSB channels to the existing 23, effective January 1, 1977. Thus, the new frequency band for Class D CB will extend from 26.965 to 27.410 MHz, a bandwidth of 445 kHz.

The FCC has decided that no manufacturer should have a headstart in placing 40-channel units on the market. Consequently, all manufacturers will have an opportunity to present 40-channel CB transceivers for type acceptance by the FCC between Sept. 10 and Nov. 1, 1976. The FCC indicates that any transceivers received during this period that are accepted will get the go-ahead for selling Jan. 1, 1977. After Nov. 1, it will be the first come, first served. However, there is a debate concerning to whom these new units can be sold. The FCC appears to mean selling to distributors, while some manufacturers feel that the date restriction should apply to consumers, not distributors or dealers. Consequently, that first batch of 40-channel CB models may not see the light of dealers' shelves too quickly.

It will likely be many months after Jan. 1, 1977 before extended-channel rigs start crowding out 23-channel ones in dealers' showcases. Indications are that 40-channel units will probably be in short supply until next summer. Furthermore, the new rigs (mobile) are expected to sell for about \$20 to \$40 more than the 23-channel transceivers. That's on the basis of a suggested selling price. In the marketplace, however, prices of 23-channel rigs will undoubtedly be reduced. So you will do well to pick up some 23-channel units at bargain prices before the end of 1976.

Led by Pathcom and Hy-Gain, a growing number of CB radio manufacturers have announced that anyone buying one of their phase-locked loop (PLL) types of transceivers will be able to have it "re-manufactured" so that frequencies can be extended to 40

channels and interference radiation can meet new FCC requirements. Cost of the re-manufacturing ranges from "up to 20%" of the unit's original suggested selling price to a flat \$25 or \$30, depending on the manufacturer.

**Other Changes.** FCC Docket 20120 made several other changes to the FCC Rules, also. For example, it will no longer refer to channels by number, specifying them, rather, by frequency only. Note that two of the new frequencies will be added between present channels 22 and 23, while channels 26 through 40 (15 channels) will be added at 10-kHz intervals above channel 23. However, the EIA has suggested an industry standard that will doubtlessly be adopted—to have the frequencies numbered as consecutive channels, with the new frequencies numbered 24 through 40. The two out-of-order frequencies would be channels 24 and 25, with internal changes that won't be apparent to users.

Other revisions are as follows:

- Channel 11 has been released for general communications, leaving channel 9 the only one of the 40 channels reserved for specific use (emergency and mobile assistance). Technical specifications for type-acceptance have been tightened, requiring that harmonic radiation be suppressed at least 60 dB below the base frequency, with the stipulation that the CB operator is responsible for reducing harmonic radiation even further by the use of external low-pass filters where specific TVI complaints have been filed against him. The Docket makes it evident to the manufacturers that even more stringent standards will be imposed in the near future.

- As of January 1, 1977, all new rigs must be *engraved* with a permanent serial number. The Commission also urges all users to engrave their own personal identification numbers into

the equipment, as well, to reduce the saleability of stolen equipment.

- A copy of Part 95, as well as Forms 505 and 555-B, must be shipped with all new rigs.

**The PURAC Meeting.** The second general meeting of the Personal Use Advisory Committee (PURAC) was held last July at the FCC Laboratory Facility at Guilford, Maryland. The PURAC group consists of leaders of user groups, CB journalists, and companies that have a vital interest in CB. These people volunteer their time and their organizations' facilities to develop joint recommendations to guide the FCC in future rule-making for the Citizen's Radio Service.

Many of the new FCC Rules were in accordance with earlier PURAC recommendations, and much of the business of this PURAC meeting dealt with interpretations of new regulations. Some highlights follow:

**Local Interference.** Task coordinator, Richard E. Horner, President of E.F. Johnson Co., and his subcommittee leaders presented a dramatic picture of the interference problems being created by the proliferation of CB transceivers. These problems are real, devastating and on an uncontrollable increase. The primary effects of local interference are felt on TV channels 2, 5 and 6, and also on unshielded solid-state audio equipment.

Causes of local interference are numerous. Some are caused by insufficient harmonic suppression, while others are caused by excessive spurious emissions from CB receiver sections. However, the biggest interference problems result from insufficient filtering incorporated into commercial entertainment equipment. It is evident that interference problems must be attacked on two fronts: the technical specifications for CB equipment must be tightened considerably (even though tighter specs will result in higher prices), and TV and audio equipment manufacturers must be required to include adequate filtering and shielding in their equipment in order to exclude unwanted harmonics and spurious interference.

**Information Dissemination.** There are actually three subcommittees studying the problems of information, education and training. One of the least understood informational problems deals directly with interference. Both the CB public and the general

public must be made aware of the causes of interference and actions which can be taken to prevent it. TV service technicians must also be educated to recognize the various types of TVI, and know the cures for each. At least one group of TV stations has agreed to produce educational TV programming to acquaint TV viewers with the problems of TVI.

**Personal Use Radio Needs.** This "blue-sky" subcommittee is charged with examining the future needs of the public for personal radio communications. It is headed-up by Ted Andros, Executive Vice President of Hy-Gain Electronics. Ted has recruited CB notables such as Dave Thompson, President of SBE, to work with him on this important project. He plans to enlist the aid of psychologists, sociologists and economists to predict the future course of personal radio communications. His subcommittee may have a major effect on the future course of CB radio. He asks the logical question, "Why should the general public, in this day of personal mobility, be tied to the end of a telephone line?"

**Personal Observations.** While at

the Guilford Laboratory, I spent some time checking out rumors regarding the extent of FCC activities. One such rumor suggested strongly that the Commission has not adhered strictly to its own type-acceptance policies. I believe that if type acceptance is to succeed, it must be stringently controlled. Because CB is a nontechnical service the CB'er must place his trust in the manufacturer's advertised specs and its compliance with type-acceptance requirements. I feel that type-acceptance testing must extend to random sampling of production models as well as pre-production prototype examination. The manufacturer must share some of the blame if type-accepted rigs fail to meet FCC performance specifications, unless it can be proved that the rig has been tampered with.

I questioned Milton Mobley, Chief Engineer at the FCC Laboratory, on this subject. He assured me that he, personally, had conducted type-acceptance tests on all submitted samples since April, 1976, and that every model receiving a type-acceptance certificate had earned it by passing all aspects of these tests. He would not comment on type-

acceptance testing procedures in effect before that date, even though the regulation has been in effect since 1974. Mr. Mobley concedes that it has not been FCC practice to retest production samples unless complaints had been filed. But he explains that testing will be automated in the near future and that production models will be sampled at that time. We certainly hope so.

**Congressmen, Please Note.** We are all aware that the FCC is "taking in" about \$2,000,000 each month in new CB licensing fees. Many of us are not aware that these fees go directly into the U.S. Treasury, not to the FCC. The Commission continually blames many of its short-falls upon the lack of budgeting to cope with the CB problem.

It is about time that Congress recognized the Citizen's Band as a new national force which encompasses from 5% to 10% of all Americans, and growing fast. The FCC must be budgeted to accommodate the growth of CB, and should certainly receive a lion's share of its own proceeds *allocated* for use to administer the Citizen's Band. ♦

# Get More from Your Car with a Mark 10 System.

**The best-selling CDI system of its kind in the world—now at discount prices!**

Would you like more power? Better mileage? And could you stand to eliminate 3 out of 4 of those expensive tune-ups? Well, that's what the MARK 10 capacitive discharge electronic ignition system is all about. Very simply, it boosts the spark to your engine—promoting better combustion, and minimizing combustion contaminants. Spark plug life is extended, all-weather starts are insured, and you can feel an increase in acceleration and overall engine performance—*no matter what kind of car you drive.* Learn more about a MARK 10 CDI system for your car (and take advantage of year-end discount prices), when you write today for a catalog and price list.



**DELTA PRODUCTS, INC.**

P.O. Box 1147, Dept. PE  
Grand Junction, CO 81501  
(303) 242-9000


I want to know more about Mark Ten CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name

Address

City  State  Zip



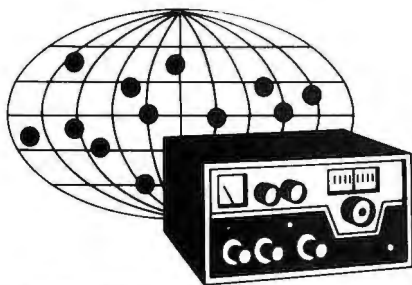

# DX Listening

By Glenn Hauser

## CHANGE IN THE AIR

**R**EALLOCATION of the radio spectrum, on an international basis, is long overdue. Despite some adjustments, the frequency ranges allocated at the World Administrative Radio Conference in Atlantic City in 1947 have remained essentially the same ever since. Many of the developments in radio communications which have taken place in the last few years were not foreseen at that time.

Consider, for instance, the advent of satellite communications, which require a lot of space in the spectrum at super-high-frequencies and reduce the need for some high-frequency circuits. Other factors include the growth of CB in the USA, the prolonged trough in the sunspot cycle, and in-

formed speculation that subsequent peaks in the cycle will not attain previous levels. (The latter means there will be less need for the higher part of the hf spectrum and more need for the already overcrowded lower part.

Groundwork for the 1979 WARC conference has been underway for several years. Each administration wants to have its position solidified, in time for the multi-national negotiations, where third-world nations are expected to hold the balance of power.

To arrive at the U.S. position, the FCC has been sponsoring meetings in Washington of various interest groups. International broadcasting is but one of the subject areas of these

meetings. Representatives of FCC-licensed hf broadcasters, listeners' groups such as the North American Shortwave Association and the Association of North American Radio Clubs, and interested individuals have worked toward formulating U.S. policy. At this writing, some proposals have been made, but are not formally adopted. The FCC will have the final say, after several more meetings. However, it is not too soon to discuss some of the initial ideas.

Satellite communications are so superior, both in capacity and quality, to hf point-to-point links, that the latter seems destined to be used mainly as backup, and for contacting the few spots on the globe still without earth stations. This means that a very large fraction of the hf spectrum, presently allocated to international fixed public service (point to point) is no longer needed for that purpose.

International broadcasting, next to CB, suffers most from overcrowded bands. Much of this is the broadcasters' fault because they use more power and more frequencies than are necessary. It's a vicious cycle. Radio Nederland's Jim Vastenhouout pointed out at a meeting of the European DX

# YOU CAN BE SURE

## MORE TIMES IN MORE CIRCUITS WITH SENCORE DIGITAL MULTIMETERS

### SENCORE

A NEW BREED OF DVM's BACKED BY 25 YEARS OF ALL AMERICAN CRAFTSMANSHIP, WITH SIX EXCLUSIVE FEATURES, SO YOU CAN BE MORE SURE, MORE OFTEN . . . . . AND ALL WITH HI & LO POWER OHMS FOR MEASURING ACCURATELY IN SOLID STATE CIRCUITS.



**DVM35 \$124**  
3 digit LED display,  
1% DCV accuracy,  
battery or AC operated



**15 MEG** ONE THIRD LESS CIRCUIT LOADING to make you sure that you are affecting the circuit being tested as little as possible for more accurate measurements. Sencore digitals are 15 megohm, others are 10 megohm.



**2KV** 2000 DCV range to make you sure that you can measure TV boost volts, scope voltages, medical equipment, etc. Other digitals stop at 1000 volts. High voltage probe extends measuring capabilities to 50 KV.



**PROTECTED** PROTECTED INSIDE AND OUT so you can be sure that your meter is working and not in the repair shop. Drop it from 10 feet, apply 1000 volts overload and even apply volts on ohms accidentally and Sencore digitals keep right on working.

Council last May that there were about 600 shortwave transmitters in the world with 250 kW or more of power. And many more were being installed, especially in China and the Middle East. Yet there are at present only about 400 channels available on the hf bands, and many of these in the 21- and 25-MHz bands are of little use during the sunspot trough.

There is no prospect that nations will voluntarily cut back their broadcasting to alleviate the present average level of three mutually interfering transmissions at once on each channel. So the solution is to expand the broadcasting bands into regions presently occupied by IFPS.

**Out of Band.** Band limits cannot be enforced (though one imaginative layman suggested jamming as a means of enforcement). Many stations already operate outside the allocated broadcasting bands. Some have historical precedent on their side—using frequencies that were theirs before the 1947 limits were established. Others have taken up *OOB* (out of band) broadcasting more recently, as a strategy to escape in-band congestion.

Until this year, Voice of America broadcast strictly in-band, while employing more and more PTP channels *OOB*. Some of the latter are independent sideband (ISB), with different programs on each side; others are compatible single sideband (CSSB). Domestic in-band transmitters themselves are considered by the VOA to be feeders for relay, with the exception of some broadcasts to Oceania and Latin America.

Last summer, VOA decided to make use of a loophole in ITU regulations (which the U.S. adheres to, though it is not forced to), allowing *OOB* broadcasting, as long as no interference is caused to the primary service on a given frequency. The VOA relay in Liberia began using 12000 kHz, which is 25 kHz above the nominal limit of the 11-MHz band. There could hardly be any PTP complaints, as the frequency was already used by Radio Moscow! This new VOA policy lessens its competitive disadvantage against Radio Moscow, which has always felt free to use any channel it pleases.

Though there is no sign that Radio Moscow is giving up *OOB*, a number of Soviet regional stations have begun a minor counter-trend toward in-band


broadcasting. Alma Ata on 9380 and 10,530 and Magadan on 12,240 kHz recently vacated those long-established frequencies far *OOB*.

The bands have already been widened, *de facto*. But the proposal is to make it *de jure*. If this is done, all countries will feel free to use the new frequencies, not just those bold ones leading the way. Before long, the congestion would also expand, (though, we hope, at a reduced level). The International Broadcasting Service Group proposes the following band expansion, to be used *worldwide*. (At present, one of the problems is usage of certain bands in certain regions only.)

Present kHz	Proposed kHz
3900-4000	3900-4060
none	4450-4650
5950-6200	5740-6200
7100-7300	7300-7700
9500-9775	9400-9900
11700-11975	11500-12000
none	13600-14000
15100-15450	15050-15700
17700-17900	17500-18000
21450-21750	21450-21850
25600-26100	no change



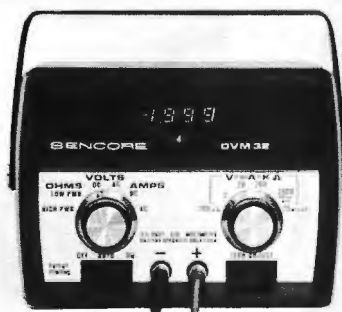**DVM36 \$148**  
3 1/2 digit LED display,  
.5% DCV accuracy,  
battery or AC operated



**DVM32 \$198**  
3 1/2 digit LED display,  
.5% DCV accuracy,  
battery or AC operated  
with automatic battery saver



**DVM38 \$348**  
3 1/2 digit LED display,  
.1% DCV accuracy,  
AC operated, auto-ranging,  
auto-zero, king size pushbuttons



**[I] BATTERY SAVING FEATURES WHEN INSTRUMENT IS NOT IN USE** so you can be sure that your meter will be ready the next time you need it. Push the button on the probe on the

DVM35 and DVM36 and only then do you start drawing current from your battery. An automatic patented circuit does the same job for you automatically when you apply voltage to the DVM32. The DVM38 is AC operated.



**[E] 100% MADE RIGHT LIFETIME GUARANTEE** so you can be sure your meter was made right. If at any time you discover that a Sencore DVM was not made right, Sencore will make it right, parts and labor free of charge, for the lifetime of the product.

Plus other "make sure" features such as - direct reading with no parallax error - no effect from magnetic fields such as motors & RF fields - lab accuracy with high resolution - auto-polarity auto-zeroing and auto-ranging on the DVM38 . . . and you can see why you can be sure more times, in more circuits, than with any other multimeter on the market today - and for less money than old fashioned analog meters.

**TEN DAY FREE TRIAL**

**[E] 10 DAY FREE TRIAL** to be sure that Sencore digitals are all that we say they are. Simply march into your Sencore distributor and ask for a free trial or pay cash with a promise of a 10 day money back guarantee, if not 100% satisfied. Or, write Sencore, and we will see that our distributor contacts you.

**SENCORE** 3200 SENCORE DRIVE  
SIOUX FALLS, S.D. 57107



# The "giftbook" of is in the

and if you aren't already on our customer mailing list,


The Heathkit Christmas Catalog is off the press, and that's good news for gift-givers, kitbuilders and everyone else, too. It's brim-full of the latest electronic products in easy-to-build kit form. Everything from lamp dimmers to color TV's, nearly 400 great gift ideas. Gifts for homeowners, businessmen and people interested in electronics, sports, fishing,


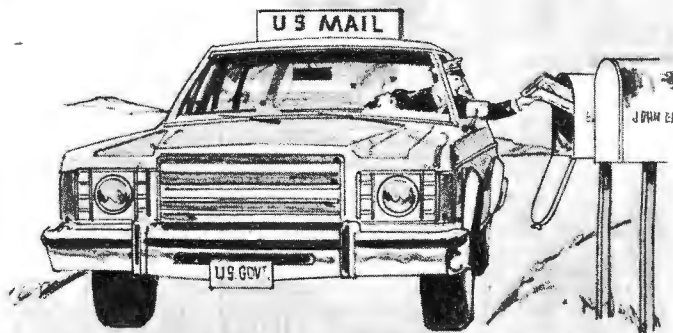
# electronics mail

now's the time to send for your copy

amateur radio—gifts for anyone you can think of. And giving a Heathkit product is the way to make someone really happy this Christmas. They're interesting and fun-to-build. They give pride and satisfaction along with great performance. So send the coupon today and get your **FREE** copy of the Heathkit "giftbook". It will help you have a happier holiday, too.



## THE NEW HEATHKIT CHRISTMAS CATALOG

World's largest selection of easy-to-build electronic kits—stereo components, color TV, test equipment, Amateur Radio, digital clocks and weather instruments; marine, aircraft and auto accessories, nearly 400 kits in all. Plus special buys on CB radios and antennas, and many special sale and bonus offers just in time for the holidays. Send coupon for your copy today. It's

# FREE

## MAIL COUPON TODAY!



# FREE

Send for your **FREE** "Heathkit Giftbook" today—in time for early-bird Christmas shopping!

Heath Company, Dept. 10-23  
Benton Harbor, Michigan 49022

HEATH  
Schlumberger

Heath Company,  
Benton Harbor, Michigan 49022

Please send me my **FREE** Catalog.  
I am not on your mailing list.

Dept. 10-23

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

CL-619

Zip \_\_\_\_\_

I'd like to do a favor for a  
friend — send another catalog to:

Dept. 10-233

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_



# BOOKS

by Donald J. Grantham

Check (✓) books you are ordering, and see below.

□ **GRANTHAM'S F.C.C. LICENSE STUDY GUIDE.** Includes 1475 FCC-type multiple-choice practice questions, covering all subjects (technical and non-technical), with answers and discussions, for 3rd, 2nd, and 1st class commercial radiotelephone license exams. Four information sections. 192 illustrations. 7×10½, 377 pages. ©1975. \$9.95

□ **INTRODUCTORY ELECTRICITY WITH MATHEMATICS.** For beginners (and for technicians who need a better understanding of "the basics"). Includes circuit diagrams, practice problems with answers, multiple-choice examinations. Written for self-study. 169 illustrations. 7×10½, 288 pages. ©1975. \$9.95

□ **FUNDAMENTAL PROPERTIES OF AC CIRCUITS.** Continues where *Introductory Electricity With Mathematics* (listed above) leaves off. Same format. 215 illustrations. Written for self-study. 7×10½, 267 pages. ©1976. \$9.95

□ **MATHEMATICS FOR BASIC CIRCUIT ANALYSIS.** Continues where *Fundamental Properties of AC Circuits* (listed above) leaves off. Same format. 104 illustrations. ©1976. \$9.95

□ **GEOMETRY FOR SCIENCE AND TECHNOLOGY.** Covers basic and analytic geometry, as needed by science and technology students at the community college level. Many illustrations. Practice problems with answers. Multiple-choice examinations. 7×10½, 141 pages. ©1976. \$4.25

■ Check the books you are ordering, complete the form below, clip ad and mail with your payment to:

## GSE BOOKS

2000 Stoner Ave., Los Angeles, CA 90025

Please send the book(s) I have checked above. The price of the book(s) is \$\_\_\_\_, and I am sending 75¢ extra to cover postage and handling of my complete order. Thus, I am enclosing a total of \$\_\_\_\_

Name \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

PE-76

Put Professional Knowledge and a  
**COLLEGE DEGREE**  
in your Electronics Career through

## HOME STUDY

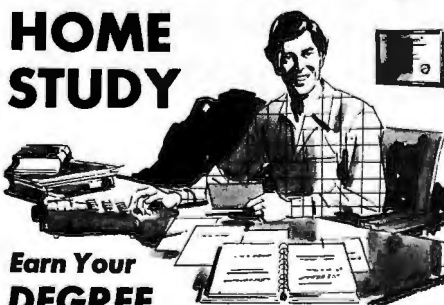

Earn Your  
**DEGREE**

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home study instructors.

The Grantham electronics degree program begins with basics, leads first to the A.S.E.T. degree, and then continues through the B.S.E.E. degree level. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write for BULLETIN E-76A.

**Grantham School of Engineering**  
2000 Stoner Ave., Los Angeles, CA 90025

● Worldwide Career Training thru Home Study ●

CIRCLE NO. 36 ON FREE INFORMATION CARD

## ENGLISH-LANGUAGE SHORTWAVE BROADCASTS FOR NOV. THRU FEB.

by Richard E. Wood

TO EASTERN NORTH AMERICA				
TIME-EST	TIME-GMT	STATION	QUAL*	FREQUENCIES, MHz
6:00-6:00 a.m.	1000-1100	**Montreal, Canada	G	5.97, 9.57
6:00-6:25 a.m.	1100-1125	Tirana, Albania	F	9.50, 11.865
6:00-7:30 a.m.	1100-1230	London, England	G	5.99 (via Sackville), 15.07
6:00-8:00 a.m.	1100-1300	Melbourne, Australia	G	9.58
6:00-9:00 a.m.	1100-1400	**VOA, Washington, USA	G	5.955, 9.73
6:05-7:25 a.m.	1105-1225	Trans-World Radio, Bonaire, N.A.	G	11.815
6:15-7:15 a.m.	1115-1215	Montreal, Canada	G	5.97, 9.655
6:30-9:00 a.m.	1130-1400	**Montreal, Canada (Northern Service)	G	5.96, 9.625 (includes French, etc.)
7:00-7:30 a.m.	1200-1230	Jerusalem, Israel	F	11.655, 15.10, 15.485
7:00-7:55 a.m.	1200-1255	Peking, China	F	11.685
7:10-7:30 a.m.	1210-1230	**Santiago, Chile	F	9.566, 11.81, 15.15
7:15-7:30 a.m.	1215-1230	Athens, Greece	F	15.345
7:15-11:30 a.m.	1215-1630	HCB, Quinto, Ecuador	F	11.745, 15.115
7:30-8:30 a.m.	1230-1330	London, England	G	15.07
7:30-9:00 a.m.	1230-1400	Trans-World Radio, Bonaire, N.A.	G	15.255 (Sat., Sun.)
8:00-8:30 a.m.	1300-1330	**Bucharest, Rumania	G	11.94, 15.25
8:15-8:45 a.m.	1315-1345	Berne, Switzerland	G	15.14
8:30 a.m.-3:00 p.m.	1330-2000	**London, England	G	9.41, 15.07
8:30-9:00 a.m.	1330-1400	Helsinki, Finland	G	15.11
9:00-9:30 a.m.	1400-1430	Oslo, Norway	G	17.80 (Sun.)
		Stockholm, Sweden	G	15.305
9:00 a.m.-7:00 p.m.	1400-2400	**Montreal, Canada (Northern Service)	G	9.625, 11.72 (includes French, etc.)
10:00-11:15 a.m.	1500-1615	London, England	G	17.84 (via Ascension)
10:15-10:30 a.m.	1515-1530	Athens, Greece	F	15.345
11:00-11:30 a.m.	1600-1630	Oslo, Norway	G	15.175 (Sun.)
11:00 a.m.-12:09 p.m.	1600-1709	London, England	G	9.58 (via Sackville, Sun. from 1500)
12 noon-3:00 p.m.	1700-2000	**Kuwait, Kuwait	F	9.555, 11.845
12:04-12:56 p.m.	1704-1756	**Paris, France	G	9.52, 9.63, 11.705, 11.73, 11.735, 11.745, 11.89, 11.905, 11.94, 15.30, 15.425, 17.72
1:00-1:57 p.m.	1800-1857	**Montreal, Canada	G	11.865, 15.325, 17.82
1:45-3:00 p.m.	1845-2000	**Abidjan, Ivory Coast	F	11.92 (Mon-Sat.)
2:00-3:00 p.m.	1900-2000	**Algiers, Algeria	F	11.91, 15.42
2:00-5:00 p.m.	1900-2200	**Jeddah, Saudi Arabia	F	11.855
2:45-5:30 p.m.	1945-2230	**Delhi, India	F	9.525, 9.912, 11.62
3:00-3:30 p.m.	2000-2030	**Tehran, Iran	F	9.022 (11.77 alternate)
		Jerusalem, Israel	G	5.90, 7.395
3:00-4:00 p.m.	2000-2100	Accra, Ghana	F	11.85
3:00-4:15 p.m.	2000-2115	**London, England	G	9.41, 11.75, 15.07
3:00-4:20 p.m.	2000-2120	**Hilversum, Holland	F	11.73 (via Talata)
3:45-4:15 p.m.	2045-2115	**Valletta, Malta	F	6.035 (Sat.)
3:50-4:50 p.m.	2050-2150	**Havana, Cuba	G	11.865, 17.75
4:00-4:45 p.m.	2100-2145	**Rawalpindi, Pakistan	F	9.445, 11.672
4:00-4:50 p.m.	2100-2150	**Johannesburg, S. Africa	G	7.27, 9.585, 11.80, 11.90
4:00-5:00 p.m.	2100-2200	**Brasilia, Brazil	G	11.78
		**Montreal, Canada	G	9.54, 11.895
4:15-5:00 p.m.	2115-2200	London, England	G	5.975, 9.58, 15.26 (via Ascension)
4:30-5:00 p.m.	2130-2200	Sofia, Bulgaria	G	6.07, 9.70
4:30-5:50 p.m.	2130-2250	Hilversum, Holland	G	9.715, 11.73 (Sun., Dutch)
5:00-5:15 p.m.	2200-2215	**Belgrade, Yugoslavia	F	6.10, 7.24, 9.62
5:00-5:30 p.m.	2200-2230	Oslo, Norway	F	9.645 (Sun.)
5:00-6:15 p.m.	2200-2315	**Cairo, Egypt	G	9.805
5:00-7:30 p.m.	2200-0030	**Ankara, Turkey	F	11.88
5:00-10:30 p.m.	2200-0330	London, England	G	5.975, 7.325, 9.58 (via Ascension)
5:30-6:00 p.m.	2230-2300	Jerusalem, Israel	G	5.90, 7.395, 9.412, 9.435
		Vilnius, U.S.S.R.	G	5.915, 5.94, 7.31, 7.355, 7.44 (Sat., Sun.)
5:30-6:20 p.m.	2230-2320	Johannesburg, S. Africa	G	5.98, 9.585, 11.80, 11.90
5:50-6:10 p.m.	2250-2310	**Santiago, Chile	F	9.566, 11.81, 15.15
6:00-6:30 p.m.	2300-2330	Stockholm, Sweden	F	6.12, 9.605, 11.705
		Moscow, U.S.S.R.	G	5.94, 6.02, 6.045, 7.205, 7.235, 7.355, 9.635, 9.79, 9.80, 12.05, 15.14, 15.18, 15.45, 17.72
6:00-6:50 p.m.	2300-2350	**Buenos Aires, Argentina	G	11.71 (Mon-Fri.)
6:00-8:00 p.m.	2300-0100	Montreal, Canada	G	6.04 (Mon-Fri.)

6:30-7:00 p.m.	2330-2400	Moscow, U.S.S.R.	G	4.86, 5.94, 6.02, 6.02, 6.045, 7.105, 7.115, 7.15, 7.205, 7.235, 7.355, 9.635, 9.79, 9.80, 12.05, 15.14, 15.18, 15.45, 17.72
6:45-7:00 p.m.	2345-2400	**Voice of Org. of American States, Washington, USA	G	6.13, 9.64, 11.74
6:45-7:45 p.m.	2345-0045	Tokyo, Japan	F	11.705, 15.30
7:00-7:25 p.m.	0000-0025	Tirana, Albania	F	7.065, 9.75
7:00-7:30 p.m.	0000-0030	Oslo, Norway	G	6.18, 9.55 (Sun.)
		Moscow, U.S.S.R.	G	4.86, 5.94, 6.045, 7.105, 7.115, 7.15, 7.165, 7.205, 7.355, 9.80, 12.05, 15.14, 15.18, 15.45, 17.72
7:00-7:55 p.m.	0000-0055	Sofia, Bulgaria	F	9.70
7:00-9:00 p.m.	0000-0200	Peking, China	F	9.94, 11.675, 11.945
7:00-8:00 p.m.	0000-0100	**Luxembourg	F	6.09
7:00 p.m.-12:06 a.m.	0000-0606	**VOA, Washington, USA	G	6.19, 9.67, 11.83, 11.895
		**Montreal, Canada (Northern Service)	F	5.96, 9.625 (includes French, etc.)
7:15-7:30 p.m.	0015-0030	Athens, Greece	F	9.76
7:15-7:45 p.m.	0015-0045	Brussels, Belgium	F	9.73
7:30-7:55 p.m.	0030-0055	Prague, Czechoslovakia	F	6.055, 9.74
7:30-8:00 p.m.	0030-0100	Stockholm, Sweden	F	6.035
		Kiev, U.S.S.R.	G	6.02, 7.15, 7.205, 7.26, 9.78, 12.05, 15.14, 15.18, 15.455
7:40 p.m.-12 mid.	0040-0500	Vilnius, U.S.S.R.	G	5.94, 7.355 (Sat., Sun.)
8:00-8:15 p.m.	0100-0115	HCJB, Quito, Ecuador	G	6.095, 9.56, 11.915
8:00-8:20 p.m.	0100-0120	Vatican City	G	5.995, 6.015, 9.605
8:00-8:30 p.m.	0100-0130	Rome, Italy	G	6.01, 9.575
		Moscow, U.S.S.R.	G	4.86, 5.94, 6.02, 6.045, 6.175, 7.105, 7.115, 7.15, 7.205, 7.355, 9.635, 9.78, 9.79, 9.80, 12.05, 15.14, 15.45
8:00-8:45 p.m.	0100-0145	Berlin, Ger. Dem. Rep.	F	9.73
8:00-8:55 p.m.	0100-0155	Peking, China	G	7.12, 9.78 (via Tirana), 9.94, 11.945, 12.055
8:00-8:57 p.m.	0100-0157	Montreal, Canada	G	6.085, 9.65
		Prague, Czechoslovakia	G	5.93, 7.345, 9.54, 9.63, 11.99
8:00-10:00 p.m.	0100-0300	Melbourne, Australia	P	15.32, 17.795
8:00-10:30 p.m.	0100-0330	Havana, Cuba	G	11.725, 11.93
8:00-11:00 p.m.	0100-0400	Madrid, Spain	G	6.065, 11.88 (Mon.-Sat.)
8:10-8:30 p.m.	0110-0130	**Santiago, Chile	F	9.566, 11.81, 15.15
8:30-8:50 p.m.	0130-0150	Cologne, Ger. Fed. Rep.	G	6.04, 6.075, 6.10 (via Malta), 9.565, 9.69, 9.745, 11.865 (via Malta)
8:30-8:55 p.m.	0130-0155	Tirana, Albania	G	6.20, 7.30
8:30-9:00 p.m.	0130-0200	Vienna, Austria	P	6.155, 9.77
		Moscow, U.S.S.R.	G	4.86, 5.94, 6.02, 6.045, 7.105, 7.115, 7.15, 7.205, 7.355, 9.635, 9.78, 9.79, 9.80, 11.86, 12.05, 15.14
8:30-9:25 p.m.	0130-0225	Bucharest, Rumania	F	5.99, 9.57, 9.68, 11.775, 11.94
8:45-9:15 p.m.	0145-0215	Berne, Switzerland	G	5.965, 6.135, 9.725, 11.715
9:00-9:30 p.m.	0200-0230	Budapest, Hungary	G	6.00, 7.215, 9.585, 9.833, 11.91 (Exc. Sun.)
		Oslo, Norway	F	6.18 (Sun.)
		Warsaw, Poland	P	6.095, 6.135, 7.27, 9.675, 11.815, 11.84, 15.12
9:00-9:55 p.m.	0200-0255	Peking, China	F	7.06, 9.94, 12.055
9:00-10:00 p.m.	0200-0300	Moscow, U.S.S.R.	G	4.86, 5.94, 6.02, 6.045, 7.105, 7.115, 7.205, 7.26, 7.355, 9.635, 9.78, 9.79, 9.80, 11.86, 12.05, 15.14
9:00-10:20 p.m.	0200-0320	Hilversum, Holland	G	6.165 (via Boneire)
9:00-10:30 p.m.	0200-0330	Cairo, Egypt	G	9.475
9:10-9:30 p.m.	0210-0230	**Santiago, Chile	F	9.566, 11.81, 15.15
9:15-9:30 p.m.	0215-0230	Athens, Greece	F	9.76
9:30-9:55 p.m.	0230-0255	Tirana, Albania	G	6.20, 7.30
9:30-10:00 p.m.	0230-0300	Libson, Portugal	G	6.025, 11.935
10:00-10:30 p.m.	0300-0330	Helsinki, Finland	F	6.12
		Budapest, Hungary	G	6.00, 7.215, 9.585, 9.833, 11.91
		Kiev, U.S.S.R.	G	5.98, 6.02, 7.245, 7.26, 7.40, 9.58, 9.78, 11.86
10:00-10:35 p.m.	0300-0335	Warsaw, Poland	P	6.095, 6.135, 7.27, 9.675, 11.815, 11.84, 15.12
10:00-10:55 p.m.	0300-0355	Peking, China	G	7.12, 9.78 (via Tirana)
10:00-11:00 p.m.	0300-0400	Buenos Aires, Argentina	G	9.69 (Mon.-Fri.)
		Prague, Czechoslovakia	G	5.93, 7.345, 9.54, 9.63, 11.99
		Moscow, U.S.S.R.	G	4.86, 5.94, 6.045, 7.115, 7.205, 7.355, 9.70, (via Sofia)

# FREE catalog

over 2000

unique tools, handy kits, precision instruments, technical supplies.

Our 23rd year of service to the World's finest craftsmen and technicians.

A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.

## National Camera

2000 West Union Ave., Dept. GGA  
Englewood, Colo., U.S.A. 80110  
(303) 789-1890

CIRCLE NO. 50 ON FREE INFORMATION CARD

## 512 MHZ PRESCALER

Enhances Your FM-7 SC-5



With Rechargeable Batteries & Charger Unit. **\$127**

Features Include:

- Extends the range of the NLS FM-7 Frequency Meter - and almost any 50 MHz frequency meter - to the upper VHF and UHF frequency bands.
- 30 mV sensitivity.
- Accurate to one part per million.
- Rugged, portable and battery powered.
- Small size: 1.9" H x 2.7" W x 4.0" D.
- Interface cable and input cable with probe included.

See your local distributor!  
Distributor Inquiries invited.

## NLS Non-Linear Systems, Inc.

Originator of the digital voltmeter.  
Box N, Del Mar, California 92014  
Telephone (714) 755-1134 TWX 910-322-1132

CIRCLE NO. 52 ON FREE INFORMATION CARD



## A Logical Solution to your Digital Logic Problems!



### THE NEW CATCH-A-PULSE® LOGIC PROBE!

- Multi-family
- Open circuit detection
- High input impedance
- Pulse stretching
- 60 Nsec pulse response
- Replaceable tip and cord

Compatible with RTL, DTL, TTL, CMOS, MOS, and Micro-processors using a 3.5 V to 15 V power supply. Thresholds automatically programmed for multi-logic family operation. Automatic resetting memory for single or multi-pulse detection. No adjustment required. Visual indication of logic levels, using LEDs to show high, low, bad level or open circuit logic and pulses. Highly sophisticated, shirt-pocket portable (protective cap over tip and removable coiled cord). Eliminates need for heavy test equipment. A definite plus in time and money for engineer and technician.



**ELECTRONICS**

Pat. Pend.

Introductory Price  
**\$24.95**  
Plus 1.25 shipping & handling  
Calif. residents add 6% sales tax  
AVR Electronics  
P.O. Box 45167  
San Diego, Ca. 92145  
(714) 566-1570

Dealer inquiries invited

CIRCLE NO. 2 ON FREE INFORMATION CARD

## DIXIE SAVE ON Brand Name Audio Components

**BY MAIL**

### Write Today for Our FREE Audio Catalog

DIXIE is one of the oldest and largest audio component mail order houses in the country. Our prices on brand name components are actually LOWER than "Discounters". See our new catalog or call us for a price quote. Everything shipped factory-sealed with full manufacturer's warranty.



#### DIXIE HI-FIDELITY

PE-11

2040 Thelro Street, Richmond, Va. 23230  
804-257-4241

Please rush me your FREE Audio Catalog, and complete information. I understand there is no obligation.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

10:00-11:25 p.m.	0300-0425	**Johannesburg, S. Africa	G	3,995, 5,98, 7.27, 9.585
10:10-10:30 p.m.	0310-0330	**Santiago, Chile	F	9.566, 11.81, 15.15
10:30-10:55 p.m.	0330-0355	Tirana, Albania	G	8.20, 7.30
		Vienna, Austria	P	6.155, 9.77
10:30-11:30 p.m.	0330-0430	London, England	G	5.975, 9.58 (via Ascension)
10:30-11:50 p.m.	0330-0450	Havana, Cuba	G	11.725, 11.76, 11.83
11:00-11:15 p.m.	0400-0415	Budapest, Hungary	G	6.00, 7.215, 9.585, 9.833, 11.81 (Tue., Fri.)
11:00-11:25 p.m.	0400-0425	Bucharest, Rumania	F	5.99, 6.155, 6.19, 9.57, 9.68, 11.775, 11.94
11:00-11:30 p.m.	0400-0430	Oslo, Norway	F	6.18, 9.55 (Sun.)
		Sofia, Bulgaria	G	9.70
11:00 p.m.-12 midt.	0400-0500	Moscow, U.S.S.R.	G	4.86, 5.94, 6.045, 7.115, 7.15, 7.205, 7.355
11:00 p.m.-1:00 a.m.	0400-0600	Montreal, Canada	G	6.135, 9.655
11:30 p.m.-12 midt.	0430-0500	**London, England	G	6.005, 9.58 (via Ascension)
11:50 p.m.-1:00 a.m.	0450-0600	Havana, Cuba	G	11.725, 11.76
12 midt.-12:15 a.m.	0500-0515	Jerusalem, Israel	G	5.90, 7.395, 7.412
12 midt.-1:00 a.m.	0500-0600	**London, England	G	6.005, 7.27, 9.60 (via Ascension)
12 midt.-2:00 a.m.	0500-0700	HCJB, Quito, Ecuador	G	6.095, 8.56
1:45-3:35 a.m.	0645-0835	**Lagos, Nigeria	G	7.275, 15.12

### TO WESTERN NORTH AMERICA

TIME PST	TIME GMT	STATION	QUAL*	FREQUENCIES, MHz
3:00-3:15 a.m.	1100-1115	Tokyo, Japan	G	5.99
3:00-4:25 a.m.	1100-1225	Trans-World Radio, Bonaire, N.A.	G	11.815
3:00-5:30 a.m.	1100-1330	London, England	G	5.99 (via Sackville), 11.75 (via Tabrau)
3:00-6:00 a.m.	1100-1400	**VOA, Washington, USA	G	5.955, 9.73
4:00-4:15 a.m.	1200-1215	Tokyo, Japan	P	5.99
4:00-4:30 a.m.	1200-1230	**Tashkent, U.S.S.R.	F	9.60, 11.925
4:10-4:30 a.m.	1210-1230	**Santiago, Chile	F	9.566, 11.81, 15.15
4:15-8:30 a.m.	1215-1630	HCJB, Quito, Ecuador	G	11.745, 15.115
4:30-6:00 a.m.	1230-1400	Trans-World Radio, Bonaire, N.A.	G	15.255 (Sat., Sun.)
5:00-5:15 a.m.	1300-1315	Tokyo, Japan	F	5.99
5:30-7:00 a.m.	1330-1500	**Delhi, India	F	11.81, 15.335
5:30-8:15 a.m.	1330-1615	**London, England	F	9.74, 11.75, 15.31 (via Tabrau)
6:00-6:30 a.m.	1400-1430	Tokyo, Japan	G	5.99
		**Tashkent, U.S.S.R.	F	9.60, 11.925
6:00-7:20 a.m.	1400-1520	**Hilversum, Holland	G	11.73 (via Talata)
6:00-8:55 a.m.	1400-1655	Manila, Philippines	F	9.58 (closes 1555 Sun.)
7:00-7:15 a.m.	1500-1515	Tokyo, Japan	G	5.99
7:00-8:15 a.m.	1500-1615	London, England	G	17.84 (via Ascension)
8:00-8:15 a.m.	1600-1615	Tokyo, Japan	G	5.99
8:00-8:30 a.m.	1600-1630	Oslo, Norway	F	11.895 (Sun.)
8:00-9:09 a.m.	1600-1709	London, England	G	9.58, 15.365 (via Sackville, opens 1500 Sat.)
8:42-8:51 a.m.	1642-1651	Hilversum, Holland	G	11.82, 15.19 (via Bonaire, Mon.-Fri.)
9:00-9:15 a.m.	1700-1715	Tokyo, Japan	F	5.99
10:00-10:15 a.m.	1800-1815	Tokyo, Japan	F	5.99
10:30-11:30 a.m.	1830-1930	Taipei, Taiwan	F	9.51, 11.86, 15.37
10:30 a.m.-12 noon	1830-2000	**London, England	F	11.82 (via Ascension)
11:00-11:07 a.m.	1900-1907	**Papete, Tahiti	F	11.825, 15.17 (exc. Sun.)
11:00-11:15 a.m.	1900-1915	Tokyo, Japan	G	9.505
12 noon-12:15 p.m.	2000-2015	Tokyo, Japan	G	9.505
12 noon-1:20 p.m.	2000-2120	**Hilversum, Holland	G	11.73 (via Talata)
1:00-1:15 p.m.	2100-2115	Tokyo, Japan	F	9.505
1:15-3:00 p.m.	2115-2300	London, England	G	9.58 (via Ascension)
2:00-2:15 p.m.	2200-2215	Tokyo, Japan	G	15.105
2:00-4:00 p.m.	2200-2400	**VOA, Washington, USA	G	17.82, 17.895, 21.61
2:30-3:00 p.m.	2230-2300	Jerusalem, Israel	F	5.90, 7.395, 7.412, 9.435
2:30-3:20 p.m.	2230-2320	Johannesburg, S. Africa	G	5.98, 9.585, 11.80, 11.90
2:50-3:10 p.m.	2250-2310	**Santiago, Chile	F	9.566, 11.81, 15.15
3:00-3:30 p.m.	2300-2330	Tokyo, Japan	G	15.105
3:00-4:30 p.m.	2300-0030	London, England	G	6.175, 9.51 (via Sackville), 9.58 (via Ascension)
3:00-5:00 p.m.	2300-0100	Montreal, Canada	F	6.04
3:45-4:00 p.m.	2345-2400	**Voice of Org. of American States, Washington, USA	G	6.13, 9.64, 11.74
4:00-4:15 p.m.	0000-0015	Tokyo, Japan	G	15.105
4:00-5:00 p.m.	0000-0100	**VOA, Washington, USA	G	11.83, 11.895, 15.40

4:30-5:30 p.m.	0030-0130	**Trans-World Radio, Bonaire, N.A.	G	11.925
4:30-7:30 p.m.	0030-0330	London, England	G	6.175 (via Sackville), 9.51 (via Greenville), 9.58 (via Ascension)
4:40-9:00 p.m.	0040-0500	HCJB, Quito, Ecuador	G	6.095, 9.56, 11.915 (includes some Eskimo)
5:00-5:15 p.m.	0100-0115	Tokyo, Japan	G	15.105
5:10-7:00 p.m.	0100-0300	Melbourne, Australia	G	15.32, 17.795
5:00-8:00 p.m.	0100-0400	Madrid, Spain	F	6.065, 11.88 (Mon-Sat.)
5:10-5:30 p.m.	0110-0130	**Santiago, Chile	F	9.566, 11.81, 15.15
5:30-6:30 p.m.	0130-0230	Tokyo, Japan	G	15.195, 15.42, 17.725, 17.825
6:00-6:15 p.m.	0200-0215	Tokyo, Japan	G	15.105
6:00-7:50 p.m.	0200-0350	Taipei, Taiwan	G	11.825, 15.345, 17.89
6:10-6:30 p.m.	0210-0230	**Santiago, Chile	G	9.566, 11.81, 15.15
6:30-7:00 p.m.	0230-0300	Stockholm, Sweden	F	6.045, 9.695
7:00-7:15 p.m.	0300-0315	Tokyo, Japan	G	15.105
7:00-7:30 p.m.	0300-0330	Kiev, U.S.S.R.	G	5.98, 6.02, 7.245, 7.26, 7.40, 9.58, 9.78, 11.86
7:00-7:55 p.m.	0300-0355	Peking, China	G	7.12, 9.78 (via Tirana), 9.46, 9.94, 11.85, 12.055
7:00-8:25 p.m.	0300-0425	**Johannesburg, S. Africa	G	3.995, 5.98, 7.27, 9.585
7:10-7:30 p.m.	0310-0330	**Santiago, Chile	G	9.566, 11.81, 15.15
7:20-8:25 p.m.	0320-0425	**TIFC, San José, Costa Rica	F	6.035, 9.645 (opens 0300 Sat., Sun.)
7:22-7:28 p.m.	0322-0328	Erevan, U.S.S.R.	G	11.69, 11.96, 15.13, 15.18, 15.456 (Sat., Tue., Wed., Fri.)
7:30-8:00 p.m.	0330-0400	Moscow, U.S.S.R.	G	5.905, 6.02, 7.26, 9.54, 9.58, 9.61, 9.635, 9.735, 9.78, 11.69
7:30-8:15 p.m.	0330-0415	Berlin, Ger. Dem. Rep.	P	5.955, 6.08, 9.56, 9.73
7:30-8:30 p.m.	0330-0430	London, England	G	6.175 (via Sackville), 9.58 (via Ascension)
8:00-8:15 p.m.	0400-0415	Tokyo, Japan	G	9.505
8:00-8:30 p.m.	0400-0430	Sofia, Bulgaria	P	9.70
		Budapest, Hungary	P	6.00, 7.215, 9.585, 9.833, 11.91 (Tues., Fri.)
		Seoul, Rep. Korea	F	9.64, 11.86
8:00-8:55 p.m.	0400-0455	Peking, China	G	9.46, 9.94, 11.65, 12.055
8:00-9:00 p.m.	0400-0500	Moscow, U.S.S.R.	G	5.905, 6.02, 7.175, 7.26, 9.54, 9.58, 9.61, 9.635, 9.735, 11.69
8:00-10:00 p.m.	0400-0600	Montreal, Canada	G	6.135, 9.655
8:20-9:00 p.m.	0430-0500	Vienna, Austria	P	6.015
		Berne, Switzerland	F	6.045, 9.725
8:30-11:30 p.m.	0430-0730	London, England	G	6.175 (via Montserrat)
9:00-9:15 p.m.	0500-0515	Jerusalem, Israel	F	5.90, 7.395, 7.412
9:00-9:30 p.m.	0500-0530	Tokyo, Japan	G	9.505
9:00-9:30 p.m.	0500-0530	Lisbon, Portugal	P	6.025, 11.935
9:00-10:20 p.m.	0500-0620	Hilversum, Holland	G	6.165, 9.175 (via Bonairs)
9:00-9:30 p.m.	0500-0530	Moscow, U.S.S.R.	G	5.905, 6.02, 7.11, 7.26, 9.54, 9.58, 9.61, 9.635, 9.735
9:00-11:00 p.m.	0500-0700	HCJB, Quito, Ecuador	G	6.095, 9.56
		**London, England	G	6.005, 7.27, 9.60 (via Ascension)
9:30-9:50 p.m.	0530-0550	Cologne, Ger. Fed. Rep.	G	6.10 (via Malta), 6.185, 9.545
9:30-10:00 p.m.	0530-0600	Moscow, U.S.S.R.	G	5.905, 6.02, 7.11, 7.175, 7.22, 7.26, 7.30, 9.52, 9.54, 9.58, 9.635, 9.735
10:00-10:15 p.m.	0600-0615	Tokyo, Japan	G	9.505
10:00-10:30 p.m.	0600-0630	Oslo, Norway	P	9.645 (Sun.)
		Moscow, U.S.S.R.	G	5.905, 6.02, 7.11, 7.175, 7.175, 7.22, 7.26, 7.26, 9.52, 9.54, 9.58, 9.635, 9.735
10:00-11:00 p.m.	0600-0700	Buenos Aires, Argentina	G	9.69 (Mon-Fri.)
10:30-11:30 p.m.	0630-0730	Moscow, U.S.S.R.	G	6.02, 7.11, 7.15, 7.175, 7.22, 7.26, 7.30, 9.54, 9.58, 9.635, 9.735
10:30 p.m.-12:30 a.m.	0630-0830	Havana, Cuba	G	9.525
10:30 p.m.-12:55 a.m.	0630-0855	Kuala Lumpur, Malaysia	G	7.22, 11.90, 15.275
11:00-11:15 p.m.	0700-0715	Tokyo, Japan	G	9.505
11:00-11:30 p.m.	0700-0730	**London, England	G	6.005, 9.60 (via Ascension)
11:30 p.m.-12:15 a.m.	0730-0815	**London, England	G	9.60, 11.86, 15.40 (via Ascension)
11:30 p.m.-2:30 a.m.	0730-1030	**Wellington, New Zealand	G	6.105
12 mid.-12:15 a.m.	0800-0815	Tokyo, Japan	G	9.505
1:00-1:15 a.m.	0900-0915	Tokyo, Japan	G	9.505
2:00-2:30 a.m.	1000-1030	Seoul, Rep. Korea	F	9.635, 11.86
		Tokyo, Japan	G	5.99
2:00-3:00 a.m.	1000-1100	Pyongyang, Dem. Rep. Korea	G	9.42, 11.535

\* Reception quality, East Coast (West Coast) location: G-good, F-fair, P-poor

\*\* Not intended for North America, but receivable satisfactorily.

Days refer to local date in target area.

# avanti ASTROPLANE CB base antennas give you patented performance



The unique construction features are so exceptional they are covered by U.S. Patent #3587109. 4.46 db gain over isotropic provides a stronger signal in and out.

To make use of the better signal, the Astroplane radiates the signal from higher up than other CB antennas and at a better angle. According to Dr. Alva Todd of the Midwest College of Engineering, "it possesses an unusually low angle of maximum radiation." This low angle of radiation means that your power is radiated at the horizon and not up into the clouds for greater efficiency.

You'll also get long lasting, trouble-free performance because it is compact in design—without long drooping radials, without coils to burn or short out, and high power capacity for lightning and static dissipation.

\$36.95 Suggested Retail  
Length 12 Ft. • Dia. 30 in.

**Free 24 page color catalog**

Avanti makes a complete line of high performance base and mobile CB antennas from \$11.95 to \$373.95.


**avanti**  
RESEARCH AND DEVELOPMENT, INC.  
340 Stewart Avenue, Addison, IL 60101

Creators of the famous

MOONRAKER

CIRCLE NO. 11 ON FREE INFORMATION CARD



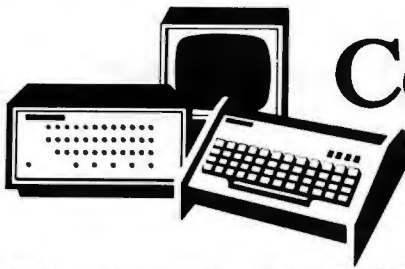

# Computer Bits

By Hal Chamberlin

## MASS-STORAGE SYSTEMS

**M**ANY interesting and useful applications of hobbyist computers require a program-controlled mass-storage device. Although a simple audio-cassette interface can be used, there are other more automatic, practical storage systems.

**Applications Needing Mass Storage.** Home accounting is a computer application that is often mentioned as needing a mass storage. One would expect a double-entry bookkeeping method to be used here, with all incomes and expenditures divided into a number of accounts according to the nature of the transaction. Once a week, or as needed, new transactions would be added to the appropriate accounts. Ideally, a verbal description of each transaction would be retained with the account record as well as the amount and date. Monthly, or as required, the system could be instructed to compute and print a personal financial statement. Also, if the accounts were set up properly, preparing a tax return could be a relatively simple task. The amount of mass storage needed, however, can become substantial. Assuming a moderately detailed system of 30 accounts and an average of 25 transactions per account per year, yields a total of 2250 transactions to save for the 3-year record-holding period required by the IRS. Allowing 30 bytes for a description, 4 bytes for a date and 4 bytes for an amount, gives a total of 85k bytes required for the application.

Learning games are an exciting application that benefit from mass storage. A learning approach to implementing complex game-playing programs such as checkers is often easier and can give better results than a direct approach. Such a program, when first run, would only be cognizant of the game rules. As it plays human opponents, files of data concerning fatal mistakes made by the program and

winning tactics employed by the opponent would be accumulated. Eventually the program would acquire a skill level just below that of the best opponent and would not suffer from "stupid" mistakes. Additionally, intermediate data files at various skill levels may be retained. Such files may get rather large. They are also subject to frequent change as the program learns. High-speed access to the data is helpful in keeping the game moving along.

Text editing for letters, reports, and other documents is another mass-storage-oriented application. The editing process may involve frequent changes, insertions, and deletions of blocks of text in the document. Also, it may be desirable to move a block of text from one portion of a document to another. The amount of storage needed varies with the type of document. A thesis may require 300k bytes, an article 30k and a letter 3k. Large insertions in the middle of a document may cause problems with certain types of mass storage.

**Mass-Storage Terminology.** Over the years, many terms have been developed to describe mass-storage systems. Perhaps most fundamental is the *on-line storage capacity* of a system. On-line storage capacity is the amount of data that can be accessed automatically by the program without requiring human intervention to change tapes, etc.

On all mass-storage systems, data is organized into blocks called *records*. When a data transfer between the storage system and the computer is performed, an entire record must be transferred. Some systems utilize a fixed record size, which means that all records are of the same length. Most tape systems, however, allow a variable record size, which means that a record may be as short as one byte or as long as desired. Note that the use of

short records may reduce the storage capacity substantially due to gaps between records.

The *transfer rate* of a system is a measure of how fast data can be read from, or written into, the storage media. Often this is qualified further by specifying a "burst" transfer rate and an "average" transfer rate. The burst rate is the actual speed during reading or writing. The average rate is measured for a long transfer of several thousand bytes. It is usually less than the burst rate because of the gaps between blocks of data or time spent searching for the next block of data.

In a *sequential access* storage system, all of the data is stored as one long string of records. The access mechanism (usually a magnetic head) can be located at any point in the string. In the simplest systems, only two operations are allowed; rewind (place the head at the beginning of the string); and read forward, starting at the current head position. Writing of new data is always done at the end of the string. More sophisticated sequential-access systems may allow reading backward and high-speed search in both directions. Some may even allow records in the middle of the string to be updated.

Data records in a *random-access* storage system are organized in a rectangular array consisting of a number of rows and columns. A particular record is read or written simply by giving its row and column numbers. The storage device goes directly to the requested location, usually without any searching. Individual records may be rewritten at will. Random-access storage systems almost always utilize fixed record lengths.

### **Tape Mass-Storage Systems.**

Tape, particularly in cassettes, is a popular, inexpensive mass-storage medium. The on-line storage capacity of a C60 cassette, for example, ranges from 50k bytes using the Computer Users Tape System or CUTS (see "Computer Bits," March, 1976) audio format (also known as Kansas City format) to approximately 600k bytes using the Digital Group's "group coded recording" digital format. Transfer rates range from about 25 bytes per second for standard audio to over 1000 bytes per second for high-performance digital recording. Most tape systems for hobbyist use allow variable-length records with perhaps a maximum allowable length.

# STEREO CHORD EGG



THE ULTIMATE  
MEDITATION  
ENVIRONMENT  
MACHINE


The EGG plugs into any stereo amp to create soothing, flowing environmental sound textures - and through headphones it's incredible. The chords and notes EXIST in your mind, they pan and swell and phase their way through your psyche in unpredictable patterns never repeating.

The combination of LSI organ technology with synthesizer-type processing and digital randomizing/control elements make the EGG an altogether intriguing package from either technological or metaphysical viewpoints.

Kit includes: Circuit board, parts and step-by-step instructions.  
CHORD EGG Kit \$24.95 postpaid  
\*Encephalo Gratification Generator

**PAIA** - FREE CATALOG -  
ELECTRONICS DEPT. 11-P  
1020 W. WILSHIRE BLVD.  
OKLAHOMA CITY, OK 73116

CIRCLE NO. 55 ON FREE INFORMATION CARD

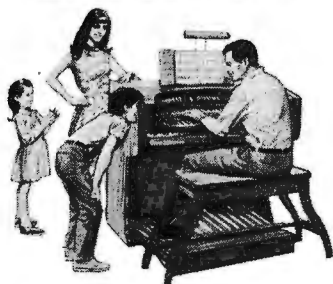

## Our whole family helped assemble this wonderful Schober Organ... and now we all play it!

Talk about real family fun! We all worked together, for a few hours almost every day. Almost too soon, our Schober Organ was finished. Our keen-eyed daughter sorted resistors. Mom soldered transistor sockets, although she'd never soldered anything before. And it did our hearts good to see the care with which our son - he's only 12 - installed the transistors. Me? I was the quality control inspector - they let me do the final wiring.

Our completed Schober Organ compares favorably with a 'ready-made' one costing twice as much! (The five models range from \$650 to \$2850.)

Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a 12-inch LP record that lets you hear as well as see Schober quality).

The Schober Organ Corp., Dept. PE-68  
43 West 61st Street, New York, N.Y. 10023

- ☐ Please send me Schober Organ Catalog.  
☐ Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

CIRCLE NO. 66 ON FREE INFORMATION CARD

NOVEMBER 1976

Magnetic tape is inherently a sequential-access storage medium. Here, data records are strung out along the length of the tape with enough blank space between records to allow for starting and stopping the tape. Finding a desired record on the tape and reading it into the computer's memory is a fundamental operation. If the record's location is not known, about the best that can be done is to rewind the tape and start reading until the needed record is reached and read. This, of course, can take several minutes even on a high-performance digital cassette system. One possibility for speeding up is to maintain an "index record" at the beginning of the tape that contains the location of all of the other records on the tape. The program would keep the index in memory while that particular tape is loaded on the drive. Then, on a simple system, at least a decision between reading forward and rewinding and starting over can be made. On a system with read-backward capability, the average search time may be shortened further by reading backward when appropriate, rather than rewinding. A system with high-speed search allows records to be counted at two to ten times the normal tape speed in either direction. When the required number of records has been skipped, normal read speed is resumed and the desired record is read. Using the high-speed search feature allows average random-access times of less than 30 seconds on a 600k byte tape with one currently available cassette system.

All three applications described earlier required data records to be updated (read, modified, and rewritten) frequently. With a simple tape system the only possible method of updating is to make a copy of the "old" tape onto a "new" tape, changing the records to be updated during the copying. Besides requiring two tape drives, the process can be quite slow if individual, random updates are required, as in the game application. Some sophisticated systems will allow records to be updated in the middle of the tape provided the updated record length is the same as the original. One possibility, if records are expected to grow as in the accounting application, is to start with a long record padded with zeroes and then gradually replace the zeroes with new data as updates take place. Large insertions and deletions such as in the text-editing

## The POLY 88 Microcomputer System

The POLY 88 Microcomputer System brings to the user, in one compact package, the capability of developing programs and hardware as well as enjoying the interaction with computers.



The POLY 88 System uses a video monitor for display, a keyboard for input and cassette tape for storage. The system will also connect to a hard-copy terminal. Poly 88 hardware consists of an 8080 based CPU circuit card with on-board memory and I/O, video display circuit card with keyboard input port and graphics capability, and mini-cards that connect to the CPU board via ribbon cable for cassette or serial interface.

The Firmware Monitor is integral to the POLY 88 System. This 1024 byte program in ROM allows the user to display data on a TV screen, enter data into memory using a keyboard, read and dump data to the cassette interface in Kansas City format, and single step through a program while displaying the contents of each of the 8080's internal registers.

**Prices:** Basic kit including chassis, CPU and video cards — \$595, \$795 assembled. Cassette option — \$90 kit and \$125 assembled. 8K of RAM — \$300 in kit form or \$385 assembled.

**Dealers:** This system will sell itself.

All prices and specifications subject to change without notice. Prices are USA only. California residents add 6% sales tax. Prepaid orders shipped postpaid. BankAmericard and Master Charge accepted.


## PolyMorphic Systems

737 S. Kellogg Avenue, Goleta, Ca. 93017  
(805) 967-2351

CIRCLE NO. 59 ON FREE INFORMATION CARD



# Does your computer talk to you?

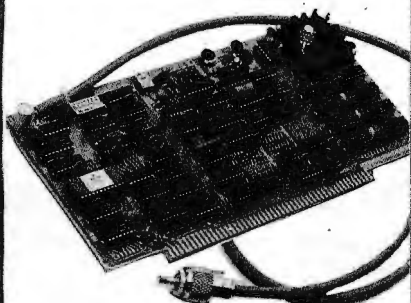

The intelligence of your 8080 system is only as great as its capacity to communicate. Processor Technology's **VDM-1** will function as a highly cogent link to that intelligence. This **ultra-high speed output device** plugs into your Altair or IMSAI to provide fast, versatile human interface. It generates 16 lines of display: 64 characters each, **both upper and lower case**. 1024 bytes of random access memory are on the card. The VDM-1 scrolls upwards or downwards, up to a top speed of **2000 lines per minute!** Any combination of cursors (up to 1024) can be displayed as black-on-white or vice versa—perfect for video games. The VDM-1 will work with any standard video monitor, or your own TV set can be easily modified. The module comes with **free terminal mode software**, for teletype replacement when used with BASIC or assemblers.

Our detailed VDM-1 Owner's Manual is available for \$4, refundable with purchase of the VDM-1.  
**Kit Price:** (eff. 7/1/76): **\$199** (premium grade, low profile IC sockets included).

**Write Us,**  
about our other  
plug-in modules,  
compatible with  
the 8800 system,  
**Processor  
Technology**  
6200-N Hollis Street  
Emeryville, CA 94608

application are still best handled by the update/copy technique when using a tape mass-storage system.

**Disk Mass-Storage Systems.** A disk-based mass-storage system has several very desirable characteristics. On-line storage capacity ranges from about 300k bytes for a floppy-disk system to over 200M bytes for some high-performance commercial systems. The range on transfer rates is considerably less, being from 32k bytes per second for the floppy to about 1.5M bytes per second for large hard-surfaced disk systems.

Although most disk mass-storage systems are very expensive, floppy-disk systems are reasonable and are becoming much more numerous among hobbyist users. The components to build a floppy-disk system cost about \$600 while complete kits list for around \$1500. The disk itself is housed in a flexible plastic envelope measuring eight inches square and one-sixteenth-inch thick and costs seven to ten dollars each. Each disk holds over 300k bytes and can be inserted into or removed from the disk drive in a couple of seconds.

Unlike tape, mass-storage disks are random-access devices. The circular disk surface is divided into a number of concentric *tracks*. Each track is further subdivided into a number of *sectors*. This is equivalent to the rectangular array of records mentioned earlier. Each sector contains one data record which is fixed in size. To access a particular record, the magnetic head is first positioned to the correct track by moving it radially in or out. This is called *seeking*. Then the system waits for the proper sector to rotate under the head for reading. The amount of time necessary to do these operations varies but is relatively unaffected by where the data is on the disk. All disk systems allow individual sectors to be updated.

A floppy disk may have, for example, 77 tracks and 32 sectors on each track for a total of 2464 possible data records. Each record has 128 useful data bytes. Moving the head from one track to another takes about 10 milliseconds per track moved. At 360 rpm it takes 166 milliseconds for the disk to rotate one revolution. Thus the longest required time to find and read a record will be just under a second. The average time is less than half that figure. Since a search of the whole disk would take considerably longer

than this, some kind of index is always maintained so that the exact track and sector numbers of the desired data are known.

A floppy-disk mass-storage system is nearly ideal for all three example applications. The accounting system, for example, can be set up so that each transaction would be stored on one sector. Thus three years of financial records may fit on one \$7 floppy disk. In the game program, many random data accesses and updates can be performed in the time allowed for the computer to make its move. Even the


## Stamp out



Hot soldering irons can be murder on delicate electronic components such as IC's. That's why the DIGI-DESIGNER will become your bugs' best friend. It's a solderless breadboarding instrument that can save you time and burned out parts.

DIGI-DESIGNER comes complete with clock, dual pulsers, logic monitors, voltage switches, built-in 5 volt supply, binding posts for external power, input/output BNC's, and more. Everything you'll need for fast, efficient circuit design.

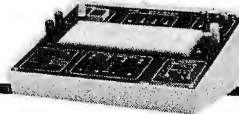Use the coupon below to order your kit today. U.S. price - \$70.00



### CIRCUIT DESIGN, INC.

Division of E & L Instruments, P.O. Box 24,  
Shelton, Conn. 06484

☐ Please send your model DD-1K DIGI-DESIGNER in kit form (price \$70.00).

Name

Address

City  State

Zip  Telephone

Enclose check, money order or numbers from BankAmericard or Master Charge. We will ship post paid anywhere in continental U.S.

# SAVE!

**MONEY • TIME • FREIGHT**

QUALITY STEREO EQUIPMENT  
AT LOWEST PRICES.

YOUR REQUEST FOR QUOTA-  
TION RETURNED SAME DAY.

FACTORY SEALED CARTONS—  
GUARANTEED AND INSURED.

SAVE ON NAME BRANDS LIKE:

A.D.C.	KLH
A.R.	SHURE
DYNACO	KOSS
SONY	FISHER

PIONEER  
AND MORE THAN 50 OTHERS  
BUY THE MODERN WAY  
BY MAIL—FROM


**ia**  
**illinois audio**

Department 217S  
12 East Delaware  
Chicago, Illinois 60611  
312-664-0020

CIRCLE NO. 42 ON FREE INFORMATION CARD

# FREE BA 1977

**GOLDEN  
ANNIVERSARY  
CATALOG**

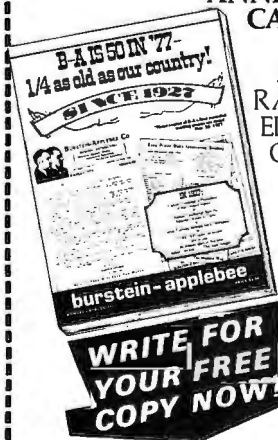

260 PAGE  
RADIO, TV &  
ELECTRONIC  
CATALOG

Your buying  
guide for  
Everything in Electro-  
nics...Stereo,  
Hi-Fi, TV's,  
Radios, Tape  
Recorders,  
CB, Kits,  
Tools, Books  
and Elec-  
tronic parts.

**burstein - applebee**

Dept. PE-11 3199 MERCIER ST.  
KANSAS CITY, MO. 64111

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_  
STATE \_\_\_\_\_ ZIP \_\_\_\_\_

NOVEMBER 1976

large insertions and deletions re-  
quired in the text-editing application  
are readily handled. With such quick  
random access to records, the in-  
serted text may be stored in any un-  
used positions on the disk. Deleted re-  
cords are simply marked as unused  
and will later be overwritten. Sorting  
of records using a single disk drive is  
not only possible but is relatively easy.  
With a tape system, at least three  
drives and a number of update/copy  
operations are required to do sorting.

**Error Handling.** Unfortunately it is a  
fact of life that magnetic recording  
media can have defects and can be  
damaged by improper handling. The  
result of a defect is that data recorded  
over it is subject to error. Since altera-  
tion of even a single bit can be disas-  
terous (such as a difference between  
\$1081 and \$9081 in the accounting  
application), methods must be em-  
ployed to detect the presence of these  
errors and to allow recovery from  
them.

Errors can be detected in a number  
of ways. The most common employs a  
*checksum* byte at the end of a record.  
A checksum is simply the sum of all of  
the data bytes in the record with over-  
flows ignored. If the sum of the data  
read back is the same as the check-  
sum byte for the data written, then the  
data is assumed to have been read ac-  
curately.

To prevent writing over a bad spot  
on the media, the data is typically read  
back and compared immediately after  
it is written. If an error is detected, then  
the record is erased and rewritten  
further on or in another sector. ♦

#### More Hobbyist Clubs

##### Canada

Amateur Microprocessor Club of  
Kitchener—Waterloo, % Reading Rm.  
Eng. II, Dept. Electrical Engineering,  
University of Waterloo, Waterloo, Ont-  
ario, Canada N2L 3G1.

TRACE, Toronto Region Association  
of Computer Enthusiasts, Box 545,  
Streetville, Ontario, Canada L5M 2C1.

##### Connecticut

Southern New England Computer  
Society, 267 Willow St., New Haven,  
CT 06511.

##### Florida

Space Coast Microcomputer Club  
% Ray O. Lockwood, 1825 Canal Ct.,  
Merritt Island, FL 32952.  
(305) 452-2159.

# Our most expensive AM mobile...

# the NEW Sabre



... featuring  
phase-lock loop  
circuitry (PLL)  
and LED digital readout.  
For complete  
specifications write . . .

**browning®**  
bringing people together

browning laboratories, inc., laconia, n. h. 03246

CIRCLE NO. 13 ON FREE INFORMATION CARD

109



# **Experimenter's Corner**

By Forrest M. Mims

## THE SILICON SOLAR CELL

**Y**OU CAN now buy silicon solar cells for less than a nickel per milliwatt of output power. This is still too costly to make high-power solar panels economically feasible in most (especially experimenters') applications. But it is low enough to allow many of us to assemble small solar panels for charging nickel-cadmium batteries.

This month, we'll take a look at the design factors and construction procedures involved in fabricating small solar batteries. But first, let's review how solar cells work and examine some of the reasons for their high cost.

**Solar Cell Theory.** The construction of a typical silicon solar cell is shown in Fig. 1. It is essentially a *pn*

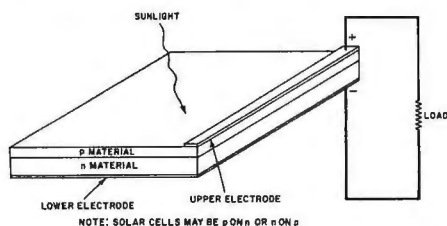


Fig. 1. Make-up of a cell.

semiconductor junction diode, and depends on the *photoelectric effect* for its operation. When the cell is in darkness, no current flows through it. The barrier potential of the junction keeps the charges from crossing from one side to the other. But when photons (light particles) strike the silicon, electron-hole pairs are created resulting in an output voltage. If the output terminals of the cell are connected to a load, a current will flow. The cell voltage is relatively independent of the light level, and is usually from 0.45 to 0.55 volt. Output current, however, is directly related to the intensity of the light striking the cell's surface.

The theoretical maximum conversion efficiency (the ratio of cell power output to light power input) of a "per-

fect" silicon solar cell is 20 to 25 percent. No such cell exists, but some laboratory cells have demonstrated an efficiency of nearly 20 percent. Commercially available cells range in efficiency from 8-10 percent for older devices to 10-15 percent for the superior grade of cells developed over the past few years.

**How They Are Made.** Silicon is the second most abundant element on earth, and, at \$600 per ton, bulk metallurgical grade silicon is actually rather cheap. But silicon solar cell efficiency is directly related to the purity of the silicon used to make the cell, and ultra-pure silicon costs 100 times more than metallurgical grade material.

Materials cost is only part of the picture. The major reason for the expense of silicon solar cells are these five production steps:

- Growth of boules of silicon from molten silicon.
  - Slicing of the boules into thin wafers.
  - Smoothing the surface of the wafers by chemical etching or mechanical polishing.
  - Formation of a *pn* junction by heating the wafers in a furnace in the presence of appropriate dopants.
  - Affixing metal electrodes to the front and back surface of the cell.
- Actually, these five steps are only the minimum required to produce a working solar cell. More efficient cells can be produced by additional etching of the front surface, formation of better electrodes, oxidizing the front surface to reduce reflection losses, and careful attention to junction formation.

Considering the materials cost and complex procedure, the high cost of silicon solar cells is certainly justified. Fortunately, improved production techniques promise to lower solar cell prices considerably in years to come.

**Building Practical Solar Cell Arrays.** Figure 2 shows how a silicon

solar battery is connected to a nickel-cadmium storage cell. The five solar cells in the battery produce a total of about 2.75 volts *open circuit* in bright sunlight, and perhaps 1.5 volts when loaded down by the NiCd cell. Blocking diode *D1* keeps the cell from discharging through the solar battery during hours of darkness. If the NiCd cell is disconnected from the circuit during darkness, *D1* and one of the five solar cells can be omitted from the circuit. (The fifth solar cell compensates for the forward voltage drop across the diode.)

Designing practical chargers requires a knowledge of the charging requirements of the storage cells and

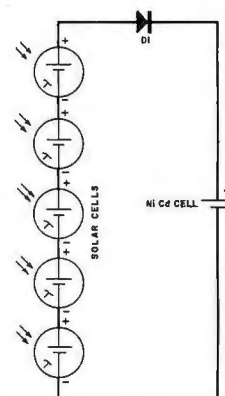


Fig. 2. Simple charging circuit.

the maximum current output of the solar battery. The maximum charging rate for most NiCd cells is 10 percent of the cell's capacity in milliamperes-hours (mA-h). Therefore the maximum charging rate for a 500-mA-h cell is 50 mA. A higher charge rate can damage or destroy the cell. Most cells require 12-14 hours at the maximum charge rate to achieve full capacity. But fast-charge units which can be charged to full capacity in only about 4 hours have recently become available. They are charged at 30 percent of the mA-h rating (for example, 150 mA for a 500-mA-h battery).

With these facts in mind, here are some useful guidelines to follow when designing your own solar battery charger:

- Use 3-4 solar cells in series for each series connected NiCd cell (e.g. 2 cells in series require 6-8 solar cells in series).
- Add one solar cell if a blocking diode is used.
- When assembling the array, temporarily wire the solar cells together and connect them to the batteries through a milliammeter as shown in Fig. 3. The current level should not

exceed the maximum allowable for the NiCd cells when the solar battery is in bright sunlight. If the current level is too high, remove one or more solar cells until the current falls to a safe level. If the current is too low, add cells as required.

Remember that you can achieve any combination of voltage and current from a solar battery by employing appropriate series and parallel connections of solar cells.

**Practical Chargers.** I recently built two solar-cell chargers for NiCd batteries to take with me on a bicycle trip in the mountains of New Mexico.

One charger had 9 series-connected 2-cm square solar cells connected to two series-connected NiCd cells. The other consisted of 18 series-connected cells connected to 4 NiCd batteries. You can make similar chargers yourself.

In making the chargers, it is convenient to solder (carefully) the cells together in groups of three. Use a low-power soldering pencil and tinned, stranded hookup wire. Next, use small squares of masking tape to temporarily secure the strips of cells face down on a Plexiglas panel. Then apply GE RTV-108 or a similar clear silicone cement between the rows of cells. Smooth the cement across the backs

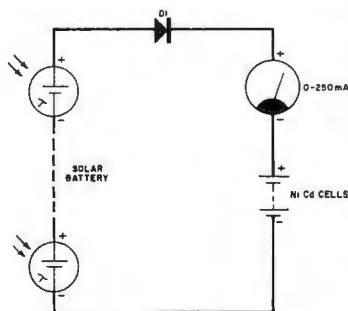


Fig. 3. Using a milliammeter.

of those cells not secured with masking tape.

Allow the adhesive to cure for 12 hours. Then carefully solder the strips of cells to one another to make the desired total. Attach output leads and a 1N914 blocking diode to the battery. Next, spread adhesive across the backs of all the cells (masking tape removed) and place a sheet of clear vinyl over the adhesive. Secure the vinyl in place for 24 hours with tape.

These simple assembly methods will permit you to produce a reliable NiCd solar-battery charger quickly and easily. Both of the panels I built provide 5 to 15 mA of charging current on overcast days.

# 47st. photo

YOUR ONE STOP SHOP FOR...QUALITY AND HUGE SAVINGS

FOR TOLL FREE PHONE ORDERS ONLY

CALL (800) 223-5661

TI CALCULATOR SPECIALS

SR 52.....	215.00
PC 100 Printer.....	214.00
SR 56.....	89.00
TI 5050M.....	94.00
TI 2550 II.....	29.50
SR 51.....	62.50

HP CALCULATOR SPECIALS

HP 25.....	125.00
HP 25C.....	179.00
HP 27.....	177.00
HP 22.....	139.00
HP 65.....	645.00
SONY BETAMAX ....CALL OR WRITE	
CB SPECIALS—23 CH. MOBILE	
Panasonic RJ 3200.....	138.00
Midland 884 Headset.....	127.95
Pace 145.....	157.00
Pace 144.....	124.95
Pace 2300.....	152.95

CALL OR WRITE TO US FOR DISCOUNT PRICES ON ALL PHOTOGRAPHIC, AUDIO, TV, CB, CALCULATOR EQUIPMENT TOLL FREE Add 2.95 for shipping and insurance

RETAIL STORE 67 W. 47th ST. NYC, 10036 N.Y. TEL. (212) 260-4410  
MAIL ORDER DIV. 36 E. 19th ST. NYC, 10003 N.Y.

CIRCLE NO. 32 ON FREE INFORMATION CARD

TI 30, 40, 51-II CALL OR WRITE

# PRICE WAR

AMERICA'S #1 VALUE LEADER  
STEREO CORPORATION OF AMERICA



AUDIO DISCOUNTING STARTED IN NEW YORK & NOW WITH THE END OF FAIR-TRADE WE ARE SURE THAT NO ONE CAN BEAT OUR PRICES:

- WE DISCOUNT OVER 60 MAJOR BRANDS
- OVER 10 YEARS OF RELIABLE SERVICE IN THE MAIL ORDER FIELD.
- LARGEST INVENTORY/LOWEST PRICES! WE GET THE BEST DEALS FROM THE MANUFACTURERS; YOU GET THE BEST DEAL FROM US. DON'T DELAY!!!

WRITE US NOW FOR LOWEST PRICE QUOTE

WRITE OR CALL  
**FREE**  
STEREO  
PRICE CATALOG

SHOP BY PHONE!  
**(212) 253-8888**  
N.Y. TIME  
9-5 MON. THRU SAT.  
Mastercharge/BankAmericard


STEREO CORPORATION OF AMERICA



P-E 1629 Flatbush Ave.,  
Brooklyn, New York 11210



CIRCLE NO. 70 ON FREE INFORMATION CARD

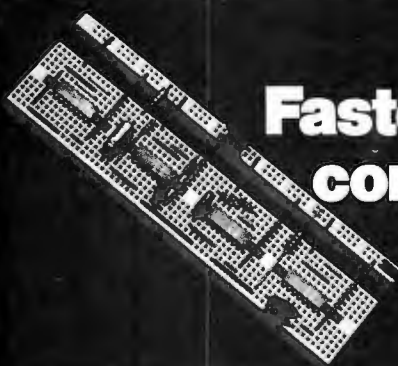

# Faster and Easier comes Stripped for action.

## TERMINAL STRIPS

Part No.	Model No.	Terminals	Tie Points	Price each
923273	217L	34	5	\$ 4.75
923291	154R	54	4	\$ 6.00
923269	234L	68	5	\$ 8.50
923265	248L	96	5	\$10.00
923289	264R	128	4	\$10.00
923261	264L	128	5	\$12.50

## DISTRIBUTION STRIPS

Part No.	Model No.	Terminals	Tie Points	Price each
923285	206R	12	4	\$ 2.00
923281	209R	18	4	\$ 2.25
923277	212R	24	4	\$ 2.50
923293	606R	36	4	\$ 3.50

Ohio and California residents add sales tax. All orders subject to acceptance at factory.

Send for our new A P catalog, The Faster and Easier Book. Dealer inquiries invited.

A P Terminal Strips and Distribution Strips give you full-performance solderless breadboards in ten comfortably priced building-block sizes. Electronic components plug right into the spring-clip terminals behind each hole. Hookup wire jumpers between terminals complete your circuit. Terminal Strips are groups of 4-tie-point or 5-tie-point terminals. Distribution Strips are interconnected groups of 4-tie-point terminals. They're both faster and easier to use.

Faster and easier is what we're all about.



**A P PRODUCTS INCORPORATED**

Box 110-H Painesville, Ohio 44077  
(216) 354-2101 TWX: 810-425-2250

For the name of the  
A P Products dealer near you,  
call our toll-free number:  
800-321-9668



# ELECTRONICS MARKET PLACE

**NON-DISPLAY CLASSIFIED: COMMERCIAL RATE:** For firms or individuals offering commercial products or services, \$2.25 per word (including name and address). Minimum order \$33.75. Payment must accompany copy except when ads are placed by accredited advertising agencies. Frequency discount; 5% for 6 months; 10% for 12 months paid in advance. **READER RATE:** For individuals with a personal item to buy or sell, \$1.35 per word (including name and address). No minimum! Payment must accompany copy. **DISPLAY CLASSIFIED:** 1" by 1 column (2-1/4" wide), \$260.00. 2" by 1 column, \$520.00. 3" by 1 column, \$780.00. Advertiser to supply film positives. For frequency rates, please inquire.

**GENERAL INFORMATION:** First word in all ads set in caps at no extra charge. All copy subject to publisher's approval. All advertisers using Post Office Boxes in their addresses **MUST** supply publisher with permanent address and telephone number before ad can be run. Advertisements will not be published which advertise or promote the use of devices for the surreptitious interception of communications. Ads are not acknowledged. They will appear in first issue to go to press after closing date. Closing Date: 1st of the 2nd month preceding cover date (for example, March issue closes January 1st. Send order and remittance to **POPULAR ELECTRONICS**, One Park Avenue, New York, New York 10016, Attention: Hal Cymes.

## FOR SALE

FREE! Bargain Catalog—I.C.'s, LED's, readouts, fiber optics, calculators parts & kits, semiconductors, parts. Poly Paks, Box 942PE, Lynnfield, Mass. 01940.

MECHANICAL, ELECTRONIC devices catalog 10 cents. Greatest Values — Lowest Prices. Fertik's, 5249 "D" Philadelphia, Pa. 19120.

SOUND SYNTHESIZER KITS—Surf \$12.95. Wind \$12.95. Wind Chimes \$17.95. Electronic Songbird \$6.95. Musical Accessories, many more. Catalog free. PAIA Electronics, Box J14359, Oklahoma City, OK 73114.

GOVERNMENT Surplus Receivers. Transmitters. Snooper scopes. Radios, Parts, Picture Catalog 25 cents. Meshna, Nahant, Mass. 01908.

LOWEST Prices Electronic Parts. Confidential Catalog Free. KNAPP, 3174 8th Ave. S.W., Largo, Fla. 33540.

ELECTRONIC PARTS, semiconductors, kits. FREE FLYER. Large catalog \$1.00 deposit. BIGELOW ELECTRONICS, Bluffton, Ohio 45817.


RADIO—T.V. Tubes—36 cents each. Send for free catalog. Cornell, 4213 University, San Diego, Calif. 92105.

AMATEUR SCIENTISTS, Electronics Experimenters. Science Fair Students... Construction plans—Complete, including drawings, schematics, parts list with prices and sources... Robot Man — Psychedelic shows — Lasers — Emotion/Lie Detector — Touch Tone Dial — Quadraphonic Adapter — Transistorized Ignition — Burglar Alarm — Sound Meter... over 60 items. Send 50 cents coin (no stamps) for complete catalog. Technical Writers Group, Box 5994, University Station, Raleigh, N.C. 27607.

METERS—Surplus, new, used, panel or portable. Send for list. Hanchett, Box 5577, Riverside, CA 92507.
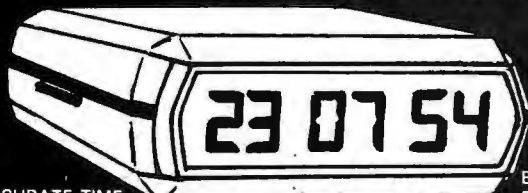
## 12 or 24 HOUR LED CLOCK

12 VOLT AC or DC POWERED FOR FIXED OR MOBILE OPERATION.



KIT OR ASSEMBLED

MODEL 2001

ACCURATE TIME WITH ADJUSTABLE XTAL TIME BASE

Approx. Size: 1 1/4" H x 4" W x 4 1/2" D

BATTERY BACK-UP FOR POWER FAILURE OR TRANSPORTING FROM HOUSE TO CAR, ETC.

- 6 JUMBO .4" RED LED'S BEHIND RED FILTER LENS WITH CHROME RIM.
- SET TIME FROM FRONT VIA HIDDEN SWITCHES • 12/24-Hr. TIME FORMAT
- STYLISH CHARCOAL GRAY CASE OF MOULDED HIGH TEMP. PLASTIC
- BRIDGE POWER INPUT CIRCUITRY — TWO WIRE NO POLARITY HOOK-UP
- OPTIONAL CONNECTION TO BLANK DISPLAY (Use When Key Off in Car, Etc.)
- TOP QUALITY PC BOARDS & COMPONENTS - EXCELLENT INSTRUCTIONS

KIT #2001

COMPLETE KIT (Less 9V. Battery)

**29<sup>95</sup>** EA.

3 OR MORE **\$27<sup>95</sup>** EA.

115 VAC Power Pack #AC-1 **\$25<sup>00</sup>** EA.

ASSEMBLED UNITS WIRED & TESTED ORDER #2001 WT (LESS 9V. BATTERY)

**\$39<sup>95</sup>** EA.

3 OR MORE **\$37<sup>95</sup>** EA.

Assembled Units May Be Mixed With Kits for Qtr. Price

SCHOTTKY TTL		DTL	UART		EXAR	OP AMPS	
74S00	\$ .35	930	\$ .09	AYS-1013	\$ 6.95	XR556	\$ 1.75
74S01	.40	932	.09			XR2567	\$ 1.95
74S04	.55	937	.09	DIODES		TRANSISTORS	
74S05	.60			IN 4002	1A, 100 PIV	2N2222A	TO-18 5/1.00
74S09	.55			IN 4003	1A, 200 PIV	2N3415	TO-92 5/1.00
74S10	.40	7447	.95	IN 4005	1A, 600 PIV	2N3704	TO-92 5/1.00
74S15	.55	7448	.95	IN 4007	1A, 1000 PIV	2N4248	TO-92 5/1.00
74S20	.50	75491	.65	RECTIFIER	2.5A, 1000 PIV	2N4400	TO-92 5/1.00
74S22	.45	75492	.65	RECTIFIER	3A, 1000 PIV	2N4437	TO-92 5/1.00
74S40	.45			IN 5400	3A, 50 PIV	2N5089	TO-92 5/1.00
74S50	.45			IN 914	SIL. SIGNAL		
74S51	.55			IN 4148	SIL. SIGNAL		
74S60	.85			DIAC	28V.		
74S64	.55	LM 309 H TO-5	.95	PLUG TRANSFORMERS		7-SEG LED's	
74S73	1.25	LM 309 K TO-3	1.25	12VAC at 150 MA	\$ 2.50	FND-359	.4" CC RED \$ .95
74S74	.85			12VAC at 500 MA	3.50	FND-503	.5" CC RED 1.35
74S75	1.75	7805	TAB .95	LINEAR		FND-510	.5" CC RED 1.35
74S78	1.50	7812	TAB 1.25			DL-750	.6" CC RED 2.95
74S86	.95	7815	TO-3 1.25			DL-747	.6" CC RED 2.95
74S107	.95	7815	TAB 1.25			XAN-654	.6" CC GREEN 2.95
74S112	.95	78L15	TO-5 .75	555 TIMER	2/1.00	XAN-664	.6" CC RED 2.95
74S113	1.40	7824	TO-3 1.25	556 DUAL TIMER	.95	TIL-308 A	.3" RED 6.95
74S114	.95	723	DIP .75	566 FUNCTION GEN.	1.75	NYLON WIRE TIES	
74S121	.95	723	TO-5 .75	567 TONE DECODER	1.75	8" TIE-WRAP	100/1.95
74S133	.75			IC SOCKETS		4" TIE-WRAP	100/1.75
74S134	.75					MOLEX PINS	
74S138	1.75			PINS	1-24 25 100	REEL OF 1000	\$ 8.50
74S139	1.50	MM 5312	\$ 4.95			STRIP OF 100	1.25
74S151	1.95	MM 5314	3.95			MISC. PRIME IC's	
74S153	1.95	MM 5316	4.95			FAIRCHILD 3316 (74161)	\$ .95
74S155	1.95	MM 5375 AB	3.95			75234 DUAL CORE SENSE AMP	1.50
74S156	1.95	CT-7001	7.95			MM 502H TO-5 SHIFT REG	.95
74S157	1.80	CT-7002	13.95				
74S158	2.50	50380	3.95				
74S174	2.50	MM 5369	2.50				
74S175	2.50						
74S181	2.95						
74S182	1.95						
74S251	2.75	3.579545 MHZ	\$ 1.95				

BUY 100 OR MORE IC's [Any Mix] TAKE 10% DISCOUNT.

## OPTOELECTRONICS, inc.

BOX 219 • HOLLYWOOD, FLA. 33022 • (305) 921-2056



ORDER BY PHONE OR MAIL  
COD ORDERS WELCOME  
\$1.00 C&G I  
Orders Under \$15 Add \$1.00  
Handling  
Fla. Res. Please Add 4%  
Sales Tax

WE PAY ALL SHIPPING IN CONTINENTAL U.S.A. - OTHERS ADD 5% (10% For AIRMAIL)

**Send for your information packet today—**  
which also includes circuit functions, component line-up, and accessories. Information Packet \$1.00 (refundable with order).

**visulex** P. O. Box 4204P Mountain View, CA 94040

BUGGED??? New locator finds them fast. Write, Clifton, 11500-L N.W. 7th Avenue, Miami, Florida 33168.

YOU WILL SAVE BIG MONEY! Surplus, Clearouts, Bankruptcy, Inventory, Deals. Catalog \$1 (refundable). ETCOA Electronics, Box 741, Montreal, H3C 2V2, U.S. inquiries.

HEAR POLICE/FIRE Dispatchers! Catalog shows exclusive directories of "confidential" channels, scanners. Send postage stamp. Communications, Box 56-PE, Commack, N.Y. 11725.

SURPRISE! Build inexpensively, the most Unusual Test Instruments, Futuristic Gadgets using Numerical Readouts! Catalogue Free! GBS, Box 100A, Green Bank, West Virginia 24944.

TELEPHONES UNLIMITED, equipment, supplies. Catalog 50 cents. Box 1654E, Costa Mesa, Calif. 92626.

UNSCRAMBLERS: Fits any scanner or monitor, easily adjusts to all scrambled frequencies. Only 4" square \$29.95, fully guaranteed. Dealer inquiries welcomed. PDQ Electronics, Box 841, North Little Rock, Arkansas 72115.

RECONDITIONED Test Equipment. \$0.50 for catalog. Walter's Test Equipment, 2697 Nickel, San Pablo, CA 94806.

**ORGAN KITS KEYBOARDS**  
THE ULTIMATE IN DESIGN AND SOUND  
FREE LITERATURE

Wurlitzer reproductions  
**DEVTRONIX ORGAN PRODUCTS, Dept. C**  
5872 Amapola Dr. • San Jose, CA 95129

DESCRAMBLERS: Several Professional Models that work with all Scanners. Tone Encoders/Decoders, Scanmate, AAPP, Radar Detectors, Big Ears, Alarms, Books, Kits, parts. Catalog 25 cents: KRYSTAL KITS, Box 445, Bentonville, Ark. 72712.

CARBON FILM RESISTORS. Brand new as low as 1.7 cents. Discounts of 20%. Prompt delivery. FREE samples/specifications. COMPONENTS CENTER, Box 134P, N.Y., N.Y. 10038.


JAPANESE TRANSISTORS, all transistors original factory made. Free catalog. West Pacific Electronics, P.O. Box 3879, Torrance, CA 90510.

**FAIRCHILD**
**ANNOUNCES THE**
**FAIRCHILD**
**SOLID STATE**

# TECHNOLOGY KIT

- FOR THE EXPERIMENTER WITH TASTE FOR "STATE OF THE ART" PRODUCTS
- COMPLETE SPECIFICATIONS ARE PRINTED ON THE BACK OF EACH TECHNOLOGY KIT

**FTK0020**

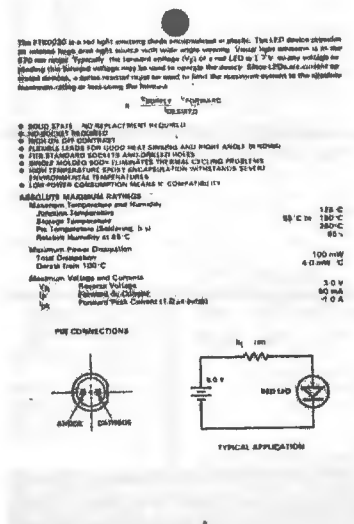**CARD FRONT**
**FTK0020**

**CARD BACK**
**FTK0106**

**CARD FRONT**

## DIGITS

FTK0001	0.5" High Common Cathode Digit	\$1.00
FTK0002	0.5" High Common Anode Digit	1.00
FTK0003	.357" High Common Cathode Digit	.75
FTK0004	0.8" High Common Cathode Digit	2.00
FTK0005	0.8" High Common Anode Digit	2.00

## 0.8" HIGH DISPLAY ARRAYS

FTK0010	12 Hour, 3½ Digit Clock Display	7.00
FTK0011	24 Hour, 4 Digit Clock Display	8.00

## LED LAMPS

FTK0020	10 Red LED Lamps	1.00
FTK0021	5 Mixed Colored LED Lamps	1.00
FTK0022	10 LED Mounting Clips	1.00
FTK0023	5 Three Piece LED Mounting Adapters	1.00

## PHOTO TRANSISTORS

FTK0030	5 Flat Lens Photo Transistors	1.00
FTK0031	5 Round Lens Photo Transistors	1.00
FTK0032	3 Flat Lens Photo Darlington	1.00
FTK0033	3 Round Lens Photo Darlington	1.00

## PHOTO ARRAYS

FTK0040	9-Element Tape Reader Array	16.00
FTK0041	12-Element Card Reader Array	24.00
FTK0042	Reflective Opto Coupler	4.00

## COUPLERS

FTK0050	3 General Purpose Opto Couplers	1.00
FTK0051	Darlington Opto Coupler	1.00

## MOS CLOCK CIRCUITS

FTK0400	Digital Clock/Calendar Circuit (FCM7001)	7.00
FTK0401	Digital Clock/Calendar with BCD Outputs (FCM7002)	7.00
FTK0402	Direct Drive Digital Clock Circuit with AC Output (FCM3817A)	5.00
FTK0403	Direct Drive Digital Clock Circuit with DC Output (FCM3817D)	5.00
FTK0405	Direct Drive Digital Clock/Calendar Circuit (FCM7015)	6.00

## KITS

FTK0106	Automobile Clock Kit	40.00
---------	----------------------	-------

- THESE PRODUCTS ARE PACKAGED FOR OUTSTANDING WALL DISPLAY APPEARANCE

- FULL **FAIRCHILD** PRODUCT LINE TO FOLLOW

- DEALER'S AND WHOLESALE'S INQUIRIES INVITED—PRICE LIST AVAILABLE.

- BUY WITH PRIDE THE PRODUCTS BUILT BY THE INDUSTRY'S LEADER — **FAIRCHILD**


Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds.  
California Residents — Add 6% Sales Tax  
Send a 24c Stamp (postage) for a FREE 1977 Catalog.

**JAMES**  
NOW OPEN SATURDAYS

1021 HOWARD STREET  
SAN CARLOS, CA 94070  
PHONE ORDERS — (415) 592-8097



# EDI

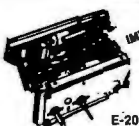

**4-RANGE DIGITAL READOUT INTERVAL TIMER KIT**

• 4 time functions: 1.99 Sec., 1.99 Sec., 1.99 Min., 1.99 Min. • 1/2" High Noise Tube Readouts • For farmhouse use in both processing & enlarging processes • As a timer for sport & contest events (stop watch) • Provides timed 120V AC outlet and S.P. NO contact to trigger buzzer alarm or visual signals • Full Wiring Instructions included — No Cabinet Or Case Available For Timer.

**100.00 VALUE** • Accurate to 1/10 of 1% • LED for Visual Timing **SPECIAL 19.99**

## 100 1/4-WATT 5 & 10% RESISTORS

Each package will include no more than five of any one value. Values of resistors are as follows:

10, 27, 51, 100, 330, 470, 1K, 1.2K, 1.5K, 2.2K, 2.7K, 3.3K, 4.7K, 5.6K, 6.2K, 10K, 12K, 22K, 33K, 68K, 82K, 100K, 120K, 220K, 330K & 1 Meg.



**Special 1.49**

## PANASONIC CD-4 DEMODULATOR

Now, have true four channel sound! A fully assembled demodulator ready to demodulate a CD-4 disc. From the phono cartridge input to the output for the four power amps. Use with any RIAA equalized magnetic cartridge or a semiconductor cartridge.

Easy to install with pictorial applications for various amps. Size: 6-1/8" x 5-1/8" x 1-3/8". Shipping Wt. 6 1/2-Lbs.

**Special Purchase! \$100.00 Value**

## PANASONIC MODEL 450C-II

**CD-4 SEMICONDUCTOR TYPE STEREO CARTRIDGE**

• Special Diamond Stylus Tip • Stylus Pressure Range 1.5 to 2.5 gr.

**Special! \$59.88 Value**



**Special 29.88**



**24-KEY DESK CALCULATOR KEYBOARD**

• Touch-tone type contacts • Complete on circuit board • Frame holds keys and 4 slide switches • 7.5/8" x 3.11/8" x 1.3/4" Highest point = 1.1/4" Lowest point = 1.1/8" • Shipping Wt. 1 lb.

**1.99**

## SPERRY-RAND UNIVAC

**KEYPUNCH KEYBOARD ASSEMBLY**

A fantastic assembly filled with quality component parts. The ideal training keyboard... a super bargain on a complete "as-is" assembly. Size: 13" x 9 1/4" x 4 1/4". Shipping Wt. 10-Lbs.



**24.88**

## PKG/10 1/2-VOLT HOBBY MOTORS

- High Torque Type, Small In Size
- Ideal For Hobbytest, Experiments, Etc.

**X-11 .99**

## 8-TRACK TAPE PLAYER CHASSIS



Complete mechanical chassis tape player with preamp, AC motor, large flywheel. A truly deluxe unit made for famous manufacturer. Needs 13-14V power supply for preamp plus balancing circuit for output.

**CC-105 6.88**



**PRECISION 1-RPM TIMING MOTOR**

• Timing Motor For Clocks, Displays, Etc. • Shipping Wt. 1/2-Lb.

**1.99**

**G-400 .59 3/1.50**

## SPERRY 9-DIGIT SP-425-09 PLANAR PLASMA DISPLAY



Features: Character height: 0.25 inch • Brightness: 70 foot lamberts • Viewing distance: 15 feet.

**.99**



Type	EDI #	Price
IN-4003	E226	Pkg. of 10 .89/Pkg.
IN-207	E226	Pkg. of 10 .89/Pkg.
TTL-7440C	E226	.17 ea.
GE-C103B		29 ea. 10/2.50
ML-741C8	E216	OP Amp. Mini Dip .49 ea.
ML-747CP	E216	Dual 741 .59 ea.
LM-565	E213	Phase Locked Loop 1.29 ea. 3/3.80
LM-309K	E215	5V - 1A - Regulator .99 ea.
TTL-7447	E217	Universal Driver .89 ea.
2SB473	E237	HEP-442/GA018, ECG-131, SK-3052, Power Transistor .88 ea.

**Send for free catalog - satisfaction guaranteed**  
**Min. Order \$3.00 - Allow For Postage**  
**Ill. Residents Add 5% Sales Tax**  
**Prices good thru January 1, 1977 or while stocks last.**  
**Notice: Some items may be of limited quantities and subject to prior sale.**

## ELECTRONIC DISTRIBUTORS, INC.

DEPT. PE 1-4900 ELSTON  
 CHICAGO, ILL. 60630  
 Tel: 312 283-4800

**Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.**

## INTEGRATED CIRCUITS

7400TTL	SN74175N	.90	LM320T-5	1.60	CM08	CD4528	1.50
SN7400N	SN74181N	1.25	LM320T-15	1.60	CC4001	CD4583	4.50
SN7402N	SN74284N	6.00	LM320T-15	1.60	CD4002	CD4091	3.00
SN7410N	SN74285N	6.00	LM330N	1.50	CD4003	CD4092	3.00
SN7414N	SN74286N	1.85	LM330N	1.50	CD4007	7400A	.33
SN7416N	74AL00 TTL	.34	LM340T-5	1.60	CD4008	7410A	.28
SN7417N	SN74181N	1.25	LM340T-15	1.70	CD4011	7412A	.28
SN7420N	SN74182N	.34	LM340T-15	1.70	CD4012	7413A	.28
SN7421N	SN74183N	.39	LM340T-15	1.70	CD4013	7414A	.28
SN7422N	SN74184N	.39	LM340T-15	1.70	CD4014	7415A	.28
SN7423N	SN74185N	.39	LM340T-15	1.70	CD4015	7416A	.28
SN7561N	SN74323N	.39	LM340T-15	1.70	CD4153	7554A	.28
SN756							

# 4K LOW POWER RAM BOARD KIT

THE WHOLE WORKS

Imsai and Altair 8080 plug in compatible. Uses low power static 21L02—1 500 ns. RAM's, which are included. Fully buffered, drastically reduced power consumption, on board regulated, all sockets and parts included. Premium quality plated thru PC Board.

## \$89.95

8 Digit LED  
"METRIC MASTER"

### \$19.95

"RAPID MAN — 12"

### \$29.95

## \$1,000,000 CALCULATOR PURCHASE!

We bought the entire stock of a major manufacturer. New, guaranteed units.

Five functions PLUS complete Metric Conversion functions. Rechargeable batteries. Small, hand held size. With AC charger.

12 Digit — Desk Top Style. Sturdy design. With memory and four complete functions. Big, bright display.

**ALARM CLOCK KIT SIX DIGIT LED**  
Thousands of hobbyists have bought and built our original clock kit and were completely satisfied. But we have received many requests for an alarm clock kit with the same value and quality that you have come to expect from S.D. So, here it is! THE KIT INCLUDES:

- 1 Mostek 50252 Alarm Clock Chip
- 6 Hewlett Packard .30 in. common cathode readouts
- 15 NPN Driver Transistors
- 2 Switches for time set
- 2 Slide Switches for alarm set and enable
- 1 Filter Cap
- 4 IN4002 Rectifiers
- 1 IN914 Diode
- 1 .01 Disc Cap
- 15 Resistors
- 1 Speaker for alarm
- 1 LED lamp for PM indicator

### \$9.95

PCB — \$3.00  
XFMR — \$1.50

## 60 HZ CRYSTAL TIME BASE — FOR DIGITAL CLOCKS \$5.95

### KIT FEATURES:

- A. 60 hz output with accuracy comparable to a digital watch
  - B. Directly interfaces with all MOS Clock chips
  - C. Super low power consumption (1.5 Ma typ.)
  - D. Uses latest MOS 17 stage divider IC
  - E. Eliminates forever the problem of AC line glitches
  - F. Perfect for cars, boats, campers, or even for portable clocks at ham field days. BUY TWO FOR \$10.00!
  - G. Small size, can be used in existing enclosures.
- KIT INCLUDES CRYSTAL, DIVIDER IC, PC BOARD PLUS ALL OTHER NECESSARY PARTS AND SPECS.

### MOTOROLA RTL IC'S

Brand new, factory prime. Hard to find, but still used in a variety of projects. (See the RTL Cookbook by Howard W. Sams.)

MC724P — 59c	MC780P — 89c	MC791P — 69c
MC725P — 59c	MC785P — 49c	MC792P — 59c
MC764P — 49c	MC787P — 89c	MC799P — 59c
MC767P — 69c	MC788P — 49c	MC970P — 89c
MC771P — 49c	MC789P — 59c	MC9709P — 69c
MC775P — 89c	MC790P — 89c	MC9760P — 69c

### TTL INTEGRATED CIRCUITS

7400 — 19c	7430 — 19c	7476 — 35c	74153 — 75c
7402 — 19c	7432 — 34c	7480 — 49c	74154 — 1.00
74L04 — 19c	7437 — 39c	7483 — 95c	74157 — 75c
74S04 — 44c	7438 — 39c	7485 — 95c	74161 — 95c
7404 — 19c	7440 — 19c	7586 — 45c	74164 — 1.10
7406 — 29c	7447 — 85c	7490 — 65c	74165 — 1.10
7408 — 19c	7448 — 85c	7492 — 75c	74174 — 95c
7410 — 19c	7451 — 19c	7495 — 75c	74181 — 2.50
7411 — 29c	7453 — 19c	7496 — 89c	74191 — 1.25
7413 — 50c	7473 — 39c	74121 — 38c	74192 — 1.25
7420 — 19c	7474 — 35c	74123 — 65c	74193 — 1.00
	7575 — 35c	74141 — 75c	74195 — 69c



### "CUBO" —DIGITAL ALARM CLOCK CUBE A PERFECT GIFT — NOT A KIT!

The CUBO Alarm Clock mfg. by Corvus, division of MOSTEK CORP. Originally sold for \$49.95. We bought out their entire inventory. All new, individually gift boxed. Mini size (2 1/2" cube) with maxi performance.

### FEATURES:

- A. 4 Digit H.P. Bright Display
- B. "Second Hand" LED Activity Indicator
- C. 24 Hour Alarm; 12 hour real time format
- D. 10 Minute Snooze
- E. Auto Display Dimming — Adjusts to Ambient Light
- F. AM/PM Indicator
- G. Power Failure Indicator

Uses Famous Mostek MK50250 MOS LSI IC

### \$14.95

(Add 75c P.&H.)



### 1000 MFD FILTER CAPS

Rated 35 WVDC. Upright style with P. C. leads. Most popular value for hobbyists. Compare at up to \$1.19 each from franchise type electronic parts stores.

S.D. SPECIAL 4 for \$1.

### SLIDE SWITCH ASSORTMENT

Our best seller. Includes miniature and standard sizes, single and multi-position units. All new, first quality, name brand. Try one package and you'll re-order more. SPECIAL — 12/\$1.



### MOTOROLA POWER DARLINGTON

Back in Stock!  
Like MJ3001. NPN 80V, 10A. HFE 6000 TYP. TO—3 case. We include a free 723 C volt reg. with schematic for power supply.  
SPECIAL — \$1.99

### WESTERN DIGITAL UART

No. TR1602B. 40 pin DIP.  
This is a very powerful and popular part.  
NEW — \$6.95 with data  
LIMITED QUANTITY

### FAIRCHILD BIG LED READOUTS

A big .50 inch easy to read character. Now available in either common anode or common cathode. Take your pick. Super low current drain, only 5 MA per segment typical.

YOUR CHOICE: 6 for \$7.50  
FND — 510 Common Anode \$1.50 ea.  
FND — 503 Common Cathode \$1.50 ea.

### MICROPROCESSORS & THINGS

By AMD

8080A	Better than Intel	\$24.00
8008-1	High Speed 8008	12.50
8212	I/O Port	3.50
8224	Clock Generator	4.95
2513	Character Generator	10.00

### RESISTOR ASSORTMENT

1/4 W 5% and 10%. PC leads.  
A good mix of values. 200/\$2.



### 74S200

256 Bit High Speed RAM  
Same as 82S16  
\$3.95

1K PROM BACK IN STOCK!  
82S129. 256X4. Bipolar, 50 NS.  
FAST. WITH SPECS.

### \$3.95

### 8T97B

Hex Tri-State Buffer. Back in stock.  
\$1.25

### UP YOUR COMPUTER! 21L02—1 1K LOW POWER 500 NS STATIC RAM

And so is power. Not only are our RAM's faster than a speeding bullet but they are now very low power. We are pleased to offer prime new 21L02 — 1 low power and super fast RAM's. Allows you to STRETCH your power supply farther and at the same time keep the wait light off.  
8 FOR \$17.50

**SALE ON CUT LEAD SEMICONDUCTORS**  
Leads were cut for PCB insertion. Still very useable. All new, unused. Some House no.  
1N914/1n4148 . . . . . 100/\$2.  
1N4002 1 Amp 100 PIV. . . . . 40/\$1.  
1N4745A 16V 1W Zener. . . . . 20/\$1.  
EN2222 NPN Transistor . . . . . 25/\$1.  
EN2907 PNP Transistor . . . . . 25/\$1.  
2N3904 NPN Driver Xstr . . . . . 25/\$1.  
2N3392 GE Pre-amp Xstr . . . . . 25/\$1.  
C103Y SCR. 800MA 60V . . . . . 10/\$1.

**C&K MINI TOGGLE SWITCH**  
No. 7103 SUB MINI SPDT Center OFF.  
SPECIAL — 99c

### TERMS:

Money Back Guarantee. No COD. Texas Residents add 5% tax. Add 5% of order for postage and handling. Orders under \$10. add 75c. Foreign orders: US Funds ONLY!

**CALL YOUR BANK AMERICARD OR  
MASTER CHARGE ORDER IN ON OUR  
CONTINENTAL UNITED STATES TOLL  
FREE WATTS:**

1-800-527-3460

Texas Residents Call Collect  
214/271-0022

**S. D. SALES**  
P. O. Box 28810-D  
Dallas, Texas 75228

ORDERS OVER \$15. CHOOSE \$1. FREE MERCHANDISE

CIRCLE NO. 64 ON FREE INFORMATION CARD



# LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

## A BETTER LIFE STARTS HERE



### CAN'T SLEEP, RELAX? TRY THIS!

Electronic sound conditioner simulates 4 kinds of soothing sounds of ocean surf and rain. "White sound" helps mask unwanted noise, adds restful, intriguing background sound. Program the solid-state unit to

your own need: 2 surf, 2 rain; or "white sound", proven by medical tests to have analgesic effects. Great for meditation, restlessness, sleeplessness psychology.

(A)-No. 71,997AV... (7½×7×3½") 110V AC .....\$79.95 Ppd.  
(B)-AS ABOVE, BUT "WHITE SOUND" ONLY  
No. 71,980AV... (6" Rd.×3½" Ht) .....\$28.00 Ppd.

### SUPER POWER FOR ANY AM RADIO

New antenna assist turns a tiny transistor into a tiger, has pulled in stations up to 1000' miles away! Just set beside radio (no wires, clips, grounding) and fine-tune Select-A-Tenna's dial to same frequency — "gangbusters"! Great for clearing weak signals in radio depressed areas, off-coast islands, crowded frequency stations. Solid state—uses no electricity, batts., tubes.



Stock No. 72,095AV .....\$15.95 Ppd.  
ULTRA SELECT-A-TENNA  
No. 72,147AV ("OVER 1000 MI.) .....\$22.95 Ppd.

### NASA-CHOSEN FOR APOLLO/SOYUZ

157 mi. out in space, the Astronauts used this super 20×60 binocular (modified) to view Earth! Our biggest, most powerful for distance. Far-off objects come in big, clear & sharp to the edge through big 60mm objective lenses; 173-ft. field of view at 1000 yds. Relative brightness, 9.0. Fully coated optics; 20X spcl design eye lenses. Coated BK-7 Porro prism. Extra long All-American style with fold-down rubber eyecups. Includes case & straps.



No. 1556AV... (9¼×8½; 47.5 oz.) .....\$99.95 Ppd.  
No. 1559AV... (4½×6¼; 19 oz.) .....\$29.95 Ppd.

### PRO ELECTRONIC SOUND CATCHER

Parabolic mike w/ 18½" transparent reflecting shield & 2 I.C.'s in amplifier magnifies signals 100x that of omni-direction mikes. Catch sounds never before heard! Highest signal to noise ratio poss. Earphones, tape recorder output, tripod socket; req. two 9v trans, batt. (not incl).



No. 1649AV... (5½ LB.) .....\$299.00 Ppd.  
LOW COST MODEL: NO EARPHONES, ELECTR. CIRCUIT  
No. 1665AV .....\$149.95 Ppd.  
LOWER SENSITIVITY ECON. MOD. W/O ELECTR.  
No. 80,242AV .....\$89.50 Ppd.

GREAT FOR CHRISTMAS GIFTS!  
A UNIQUE SELECTION OF MEMORABLE  
LONG-LASTING GIFTS FOR ALL AGES.



### 4 1/4" ASTRONOMICAL TELESCOPE

See moon craters, rings of Saturn, double stars. Features fine f/10 mirror\* (verified better than 1/10 wave with a scatter plate interferometer) to insure performance to theoretical limit of resolution. Equatorial mount; rack & pinion focusing; aluminum tube, 6X finder, 25mm F.L. 45X Kellner achromatic eyepiece & Barlow lens to double and triple power to 135X. Incl. FREE Star Chart plus 2 Books. \*Pyrex.®.


No. 85,260AV (SHPG. WT. 42 LB.) .....\$159.50 FOB  
No. 85,261AV (CLOCK OR.; 45 LB.) .....\$199.50 FOB


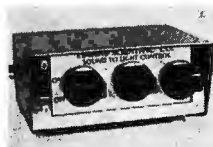
### AN ULTRA-MINIATURE AM RADIO!

It's about the size of a small matchbox—and your ear will light up when you hear it. Pulls in stations with amazing volume and clarity (number depends on locale), yet you can wear it on your key chain, conceal it in pocket or purse! Get news, sports, music wherever you go—listen to the game as you watch it at the stadium. Just insert the earplug (incl) and your directional AM mini marvel plays! Runs ab. 100 hrs. on 2 hearing aid batts (incl). A super gift!

No. 1976AV... (LESS THAN 1¼ OZ.!) .....\$14.95 Ppd.



### SEE MUSIC IN PULSATING COLOR

New 3-Channel Color Organ adds to music listening pleasure, lets you modulate 3 independent strings of colored lamps with intensity of your music to create an audio "light show." They flash, vary in brightness related to music's rhythm, pitch, volume—pulsating lighting performance to music! Fully assembled & priced half that of others, the Edmund Sound To Light Control is a terrific value. Plug in, turn on!

No. 42,309AV... (ASSEMBLED) .....\$17.95 Ppd.  
No. 42,336AV... (UNASSEMBLED) .....\$13.95 Ppd.



### LOW COST PORT. INFRA-RED EYE

For Infra-red crime detection surveillance, security system alignment, I.R. detection, laser checking, nite wildlife study, any work req. I.R. detection & conversion to visible spectrum. Self-cont. scope incl. I.R. light source (90° nite vision), 6032 I.R. converter tube, f/3.5 obj. lens, adjust. triplet eyepiece, auto lighter adapter. 1.6X focuses 10' to inf.; 6.12v DC. Not avail. to CA res. exc. authd. pers. incl. educ.

No. 1683AV... (11 × 14¼ × 3") .....\$299.95 Ppd.  
BINOCULAR STYLE: AS ABOVE, BUT 2.5X  
No. 1685AV... (SUPER BRIGHT I.R. EYE) .....\$329.95 Ppd.



### QUALITY DETECTOR UNDER \$40

New Edmund-developed, fully transistorized BFO unit capable of locating quarter at 18" — powerful 6-trans. oscillator-amplifier circuit. Easily compares to others priced 50% higher! Aluminum pole and housing—not plastic! 6" waterproof search coil (Faraday shielded to elim. outside interference); long 50-hr. battery (9V) life; powerful 2" speaker; 1-knob on-off tune control. Perfect balance; lightweight (2 lbs.). Great buy!

Stock No. 80,222 AV .....\$39.95 Ppd.



### MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN  
**4500 UNUSUAL  
BARGAINS**

Completely new 1977 edition. New items, categories, illustrations. Dozens of electrical and electromagnetics parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.  
300 Edscorp Building, Barrington, N.J. 08007  
Please rush Free Giant Catalog "AV"

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



### COMPLETE & MAIL WITH CHECK OR M.O.

EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

☐ PLEASE SEND GIANT  
FREE CATALOG "AV"

Charge my ☐ American Exp.  
☐ BankAmericard ☐ Master Chg.

Interbank No. \_\_\_\_\_

My Card No. Is \_\_\_\_\_

Card Expiration Date \_\_\_\_\_

**30-DAY MONEY-BACK GUARANTEE.**  
You must be satisfied or return  
any purchase in 30 days for full  
refund.

How Many Stock No. \_\_\_\_\_ Description (609) 547-3488 Price Each \_\_\_\_\_ Total \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

# FREE INFORMATION:

Learning more about a product that's advertised or mentioned in an article in this month's issue is as simple as one, two, three. And absolutely free.

**1** Print or type your name and address on the attached, postage-paid card. Use only one card per person.

**2** Circle the number(s) on the card that correspond to the number(s) at the bottom of the advertisement or article for which you want more information.

(Key numbers for advertised products also appear in the Advertisers' Index.)

**3** Simply mail the postage-paid card.

This address is for our product Free Information Service only. Editorial inquiries should be directed to POPULAR ELECTRONICS, One Park Avenue, New York, N.Y. 10016.

Use only one card per person

**POPULAR ELECTRONICS**

PE11763

Use only one card per person.

**NAME** \_\_\_\_\_

**ADDRESS** \_\_\_\_\_

**CITY** \_\_\_\_\_ **STATE** \_\_\_\_\_ **ZIP** \_\_\_\_\_

(Zip Code must be included to insure delivery.) (Void after Jan. 31, 1977)

Do you construct projects found in our editorial pages? ☐ Yes ☐ No

☐ Please send me 12 issues of Popular Electronics for \$6.99 and bill me.

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105

**POPULAR ELECTRONICS**

PE11762

Use only one card per person.

**NAME** \_\_\_\_\_

**ADDRESS** \_\_\_\_\_

**CITY** \_\_\_\_\_ **STATE** \_\_\_\_\_ **ZIP** \_\_\_\_\_

(Zip Code must be included to insure delivery.) (Void after Jan. 31, 1977)

Do you construct projects found in our editorial pages? ☐ Yes ☐ No

☐ Please send me 12 issues of Popular Electronics for \$6.99 and bill me.

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105

**POPULAR ELECTRONICS**

PE11761

Use only one card per person.

**NAME** \_\_\_\_\_

**ADDRESS** \_\_\_\_\_

**CITY** \_\_\_\_\_ **STATE** \_\_\_\_\_ **ZIP** \_\_\_\_\_

(Zip Code must be included to insure delivery.) (Void after Jan. 31, 1977)

Do you construct projects found in our editorial pages? ☐ Yes ☐ No

☐ Please send me 12 issues of Popular Electronics for \$6.99 and bill me.

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90



# FREE INFORMATION:

First Class  
Permit No. 217  
Clinton, Iowa


## BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

**Popular Electronics**

P.O. Box 2905  
Clinton, Iowa 52732

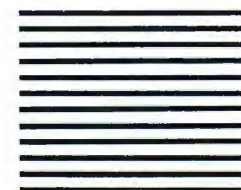

First Class  
Permit No. 217  
Clinton, Iowa

## BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

**Popular Electronics**

P.O. Box 2905  
Clinton, Iowa 52732



First Class  
Permit No. 217  
Clinton, Iowa


## BUSINESS REPLY MAIL

No postage necessary if mailed in the United States

POSTAGE WILL BE PAID BY

**Popular Electronics**

P.O. Box 2905  
Clinton, Iowa 52732

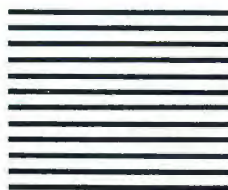

## ALL THE LATEST INFORMATION ON STEREO AND QUADRAPHONIC SYSTEMS AND COMPONENTS WILL BE FOUND IN THE...

### 1977 STEREO DIRECTORY & BUYING GUIDE




Whether you're shopping for your very first stereo or quadraphonic system or trading up components on a sophisticated rig, you'll get happier results if you shop first in the 1977 STEREO DIRECTORY & BUYING GUIDE. It includes more than 1500 products—listed by manufacturer, each with model number, complete specifications, and price:

- 4-Channel Components
- Amplifiers
- Tuners
- Receivers
- Hi-Fi Compacts
- Changers and Turntables
- Speaker Systems
- Phono-Cartridges and Arms
- Cassette, Open-Reel and Cartridge Tape Machines
- Headphones and Microphones
- Raw Tape and Accessories

You can make a pre-store purchasing decision at home. The silent hours you spend with the Directory will assure you many hours of the purest, most perfect listening pleasure. **Only \$1.95!**

*first time ever  
published!*

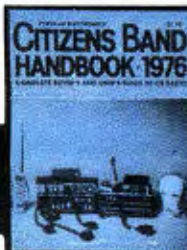

### CITIZENS BAND HANDBOOK

by the editors of POPULAR ELECTRONICS

all the authoritative information you need on CB two-way radios to make an intelligent buying decision for transceivers, antennas and accessories... Here's a partial look at what the experts have packed into one volume:


- Over 500 CB models fully described with technical specs, features, latest prices and photos.
- Lab test evaluations on mobile and base-station transceivers, both AM and SSB, spell out what the rigs can really do.
- Latest FCC Rules and Regulations, discussed in down-to-earth language, so you truly know what you can and cannot do legally.
- Manufacturers' specifications "decoded" to help you read a "spec sheet" with ease.
- All about CB antennas — the true key to "talk power."
- CB language translation chart.
- How emergency CB associations can save your life!
- How phase-lock-loop digital synthesizers work.
- The latest Flash Report on upcoming CB units presented at the first all-CB-manufacturers show.

This packed-with-information Handbook is the Citizens Band publication you've been waiting for! **Only \$1.75!**
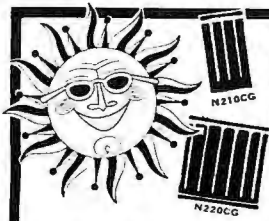
### HERE'S HOW TO ORDER

Mail your order along with your name, address and remittance in the amount of \$2.25 for Stereo Directory (\$1.95 plus 30¢ for postage and handling); \$2.00 for Citizens Band Handbook (\$1.75 plus 25¢ for postage and handling) for each copy ordered. Residents of Calif., Colo., Fla., Ill., Mich., Mo., N.Y. State, D. C. and Texas add applicable sales tax (postage and handling charges non-taxable). Outside U.S.A. copies are \$3.00, postpaid for each publication.

MAIL TO: Consumer Service Division,  
595 Broadway, New York, N.Y. 10012.



## ECONOMIZE WITH Solar Energy Chips

- 10 Times more potent than cad cells in 10 times less space!
- From space projects to hobby!
- Fraction of original cost!
- Rectangular shapes save space!

Cat. No.	Type	Size	MA	MW	Sale	3 for
11E3229	N210CC	2 x 1	50	21	\$1.49	\$3.00
11E3230	N220CC	2 x 1	100	42	1.98	5.00
11E3232	N220CC	2 x 2	100	7	2.49	5.50
11E3231A	N240CC	2 x 4	100	85	3.50	8.00
11E3231B	N240CC	4 x 2	100	85	3.50	8.00

† Two 1 x 2's shingled together; equals 1 volt  
State 1st and 2nd grid choices.

1 oz

## IMAGINE! 7 SWITCHES ON A DIP!

\* Tease Resistant Over-Center Switching Action!

\* Positive Detent For Tactile Feel!

\* Dist. Resistant Construction! Cat. No. 11E2677

\* Low Profile - 0.3" Max. Height Above P.C.

Poly Paks exclusive DIP SWITCHES. Provides highly reliable, low-cost means of manually programming a variety of micro-miniature electrical/electronic circuitry. Device is ruggedly constructed. SPST. High reliability. 7 different circuits on a DIP IC type housing made of ECONOMICAL. Housing of heat-resistant glass-filled nylon material. Fits into 14-pin IC socket, or its phosphor bronze gold-plated connections for PC board use too! Each switch rated at (non-switching) 50 VDC at 100 ma. Meets MIL-stdc spec 3A 2 2 2 2 2 2

\$1.95

A "solid jut" is now back! POLY PAKS is in the SOLAR ENERGY business. We were first in many fields and once again we have "SHONE" them all! These blue energy chips were used by the National Aeronautics Space Agency (NASA) for SPACE & TELEPHONIC COMMUNICATION SATELLITES! Forced to unload due to the economy pinch; factory & POLY PAKS now give you these fifty chips to stimulate all energy-economy-thinking hobbyists. Converts Solar to Electrical Energy!

We are stocking 4 sizes: measured in centimeters 1 x 2, 2 x 2, 2 x 4, 1 x 2 linked together. Silicon "thin plate" forms the basis of the cell. It's a Space Saver! Each cell (chip) generates 0.6 volts, but at different current capabilities. Solder edges for easy "multiple chip building". Each cell has blue-reflective-coated-surface and with transparent protection.

## LARGEST CLOCK PANEL!

- 1.2" HIGH, 4-DIGIT, 7-SEGMENT

Orange, gas discharge! Interfaces directly to AM-PM indicators! Pulsating seconds! hour! Cat. No. 11E3248

We have never seen a digital clock panel with characters so high, orange color so bright. It's by far the finest panel we've sold. The substrate is "sandwiched" between 1/4" thick panels of glass. Each of the printed circuit pins is lettered or numbered to correspond pin-for-pin interfacing with the famous MM5316 clock chip, which WE GIVE FREE! Power requirements 170 volts for anode, 1 1/2 mils per segment. Includes clock tool! Size 4 1/2 x 10 1/2". Makes a nifty looking digital clock for home, office, ham or radio station, lab, etc. Wt. 8 oz.

CHOOSE ANY BARREL KIT LISTED IN THIS MAGAZINE FREE WITH \$25 ORDERS

## "BLASTAWAY" ON 1N4000 RECTIFIER PRICES

Type	PIV	Sale
1N4001	50 for 45c	
1N4002	100 for 55c	
1N4003	200 for 65c	
1N4004	400 for 75c	
1N4005	600 for 85c	
1N4006	800 for 95c	
1N4007	1000 for 1.29	

## FULL EPOXY SILICON BRIDGE RECTIFIERS

WAVE	PIV	2 Amp	6 Amp	10 AMP
100		\$ .69	\$ .89	\$1.49
200		.79	.99	1.69
400		1.19	1.50	2.09
600		1.39	1.75	
800		1.59	1.95	
1000		1.79	2.25	

8 Amp 1/2 x 1 1/2 x 3/16 sq. Code: 2 amp TO-5 case

2250 3 for \$80.


## CITIZENS BAND POWER SUPPLY

- 12 VDC @ 3 AMPS
- REGULATED, CONTINUOUS DUTY
- CONVERTS CB, HAM RIGS TO HOME
- COMPLETELY WIRED

CB'ers ATTENTION! For your CB or Ham rig... 115V to 12VDC converter! Built-in automatic RESET circuit breaker. Powerful 3 amps (8 amp peak) makes it ideal for SSR rigs, too! Attractive walnut like metal modern-design cabinet (5x 4 1/2 x 2 1/4"). B.T. U.S. maker design. Built-in circuit breaker. Front panel has OFF-ON switch and LED light. For 115 VAC 60 cycle. Saves you many \$\$\$ too! Wt. 6 lbs. Cat. No. 11E3452

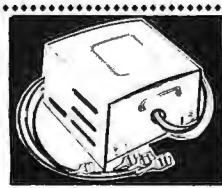
## ECC INDUSTRIAL SPEED CONTROL

Repeat of a sellout! A \$30 item, made by ECC famous for semiconductor, designed and built this speed control for XEROX. Controls home, shop and industrial lighting too. Rating: 1000 watts. A variable speed circuit for controlling many electrical and electronic devices. Easily controls speeds of electric drills, brush type motors, etc. Built with heavy duty aluminum framing. Complete with external 50K pot, for variable speed control, and series resistor. Heavy duty colored wires for 115VAC 60 cycles, and item to be controlled. 10/32 mounting stud. Outperforms our previous sellout. Use with hookup diagram. Use as temperature controller too. Wt. 2 lbs. Cat. No. 11E3392


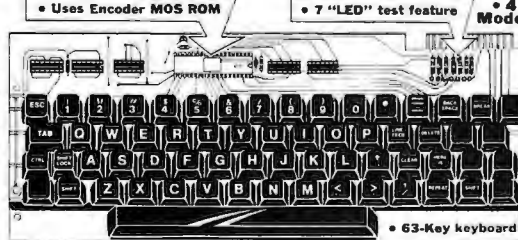
## KEYBOARD & ENCODER KIT

- Double sided PC board
- Outputs — standard ASCII 7 bits plus strobe



• 63-Key keyboard

\$69.95 WIRED KIT

Lowest price Keyboard and Encoder kit we've seen. General purpose ASCII keyboard for data terminal applications. Could be used for TV, RTTY, Code Transmission, Altair and other Mini Computers, etc. Utilizes 2-key rollover MOS memory allowing encoded outputs to be strobed out as each key is depressed. Uses double side pc board. Electronic shift lock, not mechanical on keyboard. Keyswitches, one integral assembly not individual keys. Keyboard: 63 keys (49 encoded keys). 4 mode: normal, shift and control. 3 internal function keys: shift, teach side of board, shift, lock and control. 3 functions: Key Break, Here Is, Repeat. 7 additional functions (can be assigned by user).

Cat. No. 11E3208 Keyboard & Encoder Kit... \$59.95  
Cat. No. 11E3209 Keyboard & Encoder Wired... \$69.95

Electrical specs: voltage requirements plus 5 volts and minus 12 volts, 200mw, negative or positive logic output, jumper selectable, output connector. On the PC board we have A NEW KEYBOARD TEST FEATURE... 7 LEDs! These LEDs display visually the ASCII code for the depressed key. TTL compatible. Kit includes 63 key keyboard, ROM 7 LEDs, resistors, capacitors, TTL IC's and SOCKETS. We include diagram and wiring instructions, ROM code. Wt. 7 lbs. Size overall: 13 x 6 1/2 x 2".


## HONEST ABE PENNY SALE BACK BY POPULAR DEMAND

Type	Sale	2 for	Type	Sale	2 for
SN7400	.22	.43	SN7494	.82	.83
SN7401	.22	.43	SN7495	.86	.87
SN7402	.22	.43	SN7496	.86	.87
SN7403	.22	.43	SN74125	1.29	1.30
SN7404	.22	.43	SN74126	1.29	1.30
SN7405	.22	.43	SN74132	1.95	1.96
SN7406	.22	.43	SN74133	1.95	1.96
SN7407	.22	.43	SN74141	1.12	1.13
SN7408	.22	.43	SN74142	1.69	1.70
SN7409	.22	.43	SN74143	3.25	3.26
SN7410	.22	.43	SN74144	1.12	1.13
SN7411	.22	.43	SN74145	1.12	1.13
SN7412	.22	.43	SN74150	1.12	1.13
SN7413	.22	.43	SN74153	1.53	1.54
SN7414	.22	.43	SN74154	1.09	1.10
SN7415	.22	.43	SN74155	1.59	1.60
SN7416	.22	.43	SN74160	1.59	1.60
SN7417	.22	.43	SN74161	1.80	1.81
SN7418	.22	.43	SN74162	1.79	1.80
SN7419	.22	.43	SN74163	1.79	1.80
SN7420	.22	.43	SN74164	1.79	1.80
SN7491	.22	.43	SN74235	1.79	1.80

TTLs



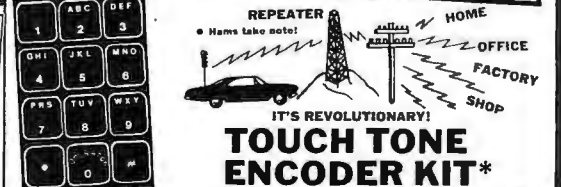ORDER BY CAT. NO. 11E1983 & TYPE NO. AT LEFT



## TOUCH TONE ENCODER KIT\*

1888

1.25M, 2-meter and 6-meter amateur radio operators. If your rig is mobile, connect it easily to a mobile telephone station and contact your home, shop, school, factory. TTE-100 touch tone encoder kit. Kit includes: Chomies touch tone pad, Motorola MC14410 chip, trimpot, resistors, zener, diagram, and G-10 pc board. Electrical specs: 12-16 volts, 5 mils (max), 4 volts PP output. \* Less 1-MC crystal. Cat. No. 11E3385

Cat. No.	Description	Sale	BUY 'EM SEPARATELY
11E3349	Touch Tone Pad	\$4.50	
11E3352	MC14410 Chip	10.50	11E3383 P.C. Board 2.95

## DIGITAL CLOCK



Alarm ON/OFF. Instruction and hookup diagrams. Shpg. wt. 7 ozs.

\$14.95

## Rotron Fans

Now anyone can afford these neat Muffin and Centaur Fans by Rotron. Used extensively for hi-fi eqpt because of low-cost, dependable cooling, as well as flushing computers, power supplies, office equipment, light projectors, transmitters, receivers & more! Weighs only 1-lb. LOW NOISE LEVEL! Humidity & moisture resistant motor. REVERSIBLE AIR FLOW! Impedance protected. Suitable for -40° to +140° F. B115 115 VAC, 3200 rpm, 15 watts, 1.6 amps. Hi-impact, flame retardant polycarbonate propellers in a reinforced phenolic venturi block. Blow away high prices with our Muffin and Centaur fans! Removed from new equipment. Money back guarantee.

Cat. No.	Description	Sale	Shpg. wt.
11E3108	"Muffin" 3-blade	5.00	5 lbs.
11E3109	"Centaur" 2" 5-blade	1.50	1 1/2 lbs.
11E3110	"Centaur" 6-blade	1.50	1 1/2 lbs.

## FAIRCHILD, NATIONAL VOLTAGE REGULATOR PANIC

YOUR CHOICE \$1 • 1-AMP RATING • TO-220 or TO-3 CASES • POSITIVE OR NEGATIVE

3 for	Cat. No.	11E3449 Positive Voltage**	** State voltage and case style when ordering.
\$2.75	Cat. No.	11E3450 Negative Voltage**	

Terms: Add postage. Rated: net 30  
Phone: Wakefield, Mass. (617) 245-3829  
Retail: 16-18 Del Carmine St., Wakefield.  
MINIMUM ORDER — \$6 (Plus Postage)  
POLY PAKS  
P.O. BOX 942E LYNNFIELD, MASS. 01940  
C.O.D.'s MAY BE PHONED



# FREE

IC or FET's WITH  
\$5 & \$10 ORDERS.1  
DATA SHEETS  
WITH MANY ITEMS.

DIODES	TRANSISTORS	TRANSISTORS	TRANSISTORS	LINEAR IC's
1N4001 100V/10mA Diode	2N706 30.24	2N4001 3/51	2N5638 2/51	LM3404-5 1/75
1N4001 100V/1A Rect.	2N718 24	2N4012 3/51	2N5640 2/51	LM3404-6 1/75
1N4154 30V 1N914	2N720 48	2N4122 3/51	2N5640 2/51	LM3404-12 1/75
BR1 50V 1/2 Bridge Rect.	2N722 6/51	2N4124 3/51	2N5640 2/51	LM3404-15 1/75
2N2222A NPN Transistor	2N723 6/51	2N4126 3/51	2N5640 2/51	LM3404-24 1/75
2N2907 PNP Transistor	2N724 6/51	2N4128 3/51	2N5640 2/51	LM3404-30 1/75
2N3055 PNP Amp/10A	2N725 6/51	2N4130 3/51	2N5640 2/51	LM3404-36 1/75
2N3904 NPN Amp/10A	2N726 6/51	2N4132 3/51	2N5640 2/51	LM3404-42 1/75
2N3906 PNP Amp/10A	2N727 6/51	2N4134 3/51	2N5640 2/51	LM3404-48 1/75
CP650 Power FET 1/2Amp	2N728 6/51	2N4136 3/51	2N5640 2/51	LM3404-54 1/75
	2N729 6/51	2N4138 3/51	2N5640 2/51	LM3404-60 1/75
	2N730 6/51	2N4140 3/51	2N5640 2/51	LM3404-66 1/75
	2N731 6/51	2N4142 3/51	2N5640 2/51	LM3404-72 1/75
	2N732 6/51	2N4144 3/51	2N5640 2/51	LM3404-78 1/75
	2N733 6/51	2N4146 3/51	2N5640 2/51	LM3404-84 1/75
	2N734 6/51	2N4148 3/51	2N5640 2/51	LM3404-90 1/75
	2N735 6/51	2N4150 3/51	2N5640 2/51	LM3404-96 1/75
	2N736 6/51	2N4152 3/51	2N5640 2/51	LM3404-102 1/75
	2N737 6/51	2N4154 3/51	2N5640 2/51	LM3404-108 1/75
	2N738 6/51	2N4156 3/51	2N5640 2/51	LM3404-114 1/75
	2N739 6/51	2N4158 3/51	2N5640 2/51	LM3404-120 1/75
	2N740 6/51	2N4160 3/51	2N5640 2/51	LM3404-126 1/75
	2N741 6/51	2N4162 3/51	2N5640 2/51	LM3404-132 1/75
	2N742 6/51	2N4164 3/51	2N5640 2/51	LM3404-138 1/75
	2N743 6/51	2N4166 3/51	2N5640 2/51	LM3404-144 1/75
	2N744 6/51	2N4168 3/51	2N5640 2/51	LM3404-150 1/75
	2N745 6/51	2N4170 3/51	2N5640 2/51	LM3404-156 1/75
	2N746 6/51	2N4172 3/51	2N5640 2/51	LM3404-162 1/75
	2N747 6/51	2N4174 3/51	2N5640 2/51	LM3404-168 1/75
	2N748 6/51	2N4176 3/51	2N5640 2/51	LM3404-174 1/75
	2N749 6/51	2N4178 3/51	2N5640 2/51	LM3404-180 1/75
	2N750 6/51	2N4180 3/51	2N5640 2/51	LM3404-186 1/75
	2N751 6/51	2N4182 3/51	2N5640 2/51	LM3404-192 1/75
	2N752 6/51	2N4184 3/51	2N5640 2/51	LM3404-198 1/75
	2N753 6/51	2N4186 3/51	2N5640 2/51	LM3404-204 1/75
	2N754 6/51	2N4188 3/51	2N5640 2/51	LM3404-210 1/75
	2N755 6/51	2N4190 3/51	2N5640 2/51	LM3404-216 1/75
	2N756 6/51	2N4192 3/51	2N5640 2/51	LM3404-222 1/75
	2N757 6/51	2N4194 3/51	2N5640 2/51	LM3404-228 1/75
	2N758 6/51	2N4196 3/51	2N5640 2/51	LM3404-234 1/75
	2N759 6/51	2N4198 3/51	2N5640 2/51	LM3404-240 1/75
	2N760 6/51	2N4200 3/51	2N5640 2/51	LM3404-246 1/75
	2N761 6/51	2N4202 3/51	2N5640 2/51	LM3404-252 1/75
	2N762 6/51	2N4204 3/51	2N5640 2/51	LM3404-258 1/75
	2N763 6/51	2N4206 3/51	2N5640 2/51	LM3404-264 1/75
	2N764 6/51	2N4208 3/51	2N5640 2/51	LM3404-270 1/75
	2N765 6/51	2N4210 3/51	2N5640 2/51	LM3404-276 1/75
	2N766 6/51	2N4212 3/51	2N5640 2/51	LM3404-282 1/75
	2N767 6/51	2N4214 3/51	2N5640 2/51	LM3404-288 1/75
	2N768 6/51	2N4216 3/51	2N5640 2/51	LM3404-294 1/75
	2N769 6/51	2N4218 3/51	2N5640 2/51	LM3404-300 1/75
	2N770 6/51	2N4220 3/51	2N5640 2/51	LM3404-306 1/75
	2N771 6/51	2N4222 3/51	2N5640 2/51	LM3404-312 1/75
	2N772 6/51	2N4224 3/51	2N5640 2/51	LM3404-318 1/75
	2N773 6/51	2N4226 3/51	2N5640 2/51	LM3404-324 1/75
	2N774 6/51	2N4228 3/51	2N5640 2/51	LM3404-330 1/75
	2N775 6/51	2N4230 3/51	2N5640 2/51	LM3404-336 1/75
	2N776 6/51	2N4232 3/51	2N5640 2/51	LM3404-342 1/75
	2N777 6/51	2N4234 3/51	2N5640 2/51	LM3404-348 1/75
	2N778 6/51	2N4236 3/51	2N5640 2/51	LM3404-354 1/75
	2N779 6/51	2N4238 3/51	2N5640 2/51	LM3404-360 1/75
	2N780 6/51	2N4240 3/51	2N5640 2/51	LM3404-366 1/75
	2N781 6/51	2N4242 3/51	2N5640 2/51	LM3404-372 1/75
	2N782 6/51	2N4244 3/51	2N5640 2/51	LM3404-378 1/75
	2N783 6/51	2N4246 3/51	2N5640 2/51	LM3404-384 1/75
	2N784 6/51	2N4248 3/51	2N5640 2/51	LM3404-390 1/75
	2N785 6/51	2N4250 3/51	2N5640 2/51	LM3404-396 1/75
	2N786 6/51	2N4252 3/51	2N5640 2/51	LM3404-402 1/75
	2N787 6/51	2N4254 3/51	2N5640 2/51	LM3404-408 1/75
	2N788 6/51	2N4256 3/51	2N5640 2/51	LM3404-414 1/75
	2N789 6/51	2N4258 3/51	2N5640 2/51	LM3404-420 1/75
	2N790 6/51	2N4260 3/51	2N5640 2/51	LM3404-426 1/75
	2N791 6/51	2N4262 3/51	2N5640 2/51	LM3404-432 1/75
	2N792 6/51	2N4264 3/51	2N5640 2/51	LM3404-438 1/75
	2N793 6/51	2N4266 3/51	2N5640 2/51	LM3404-444 1/75
	2N794 6/51	2N4268 3/51	2N5640 2/51	LM3404-450 1/75
	2N795 6/51	2N4270 3/51	2N5640 2/51	LM3404-456 1/75
	2N796 6/51	2N4272 3/51	2N5640 2/51	LM3404-462 1/75
	2N797 6/51	2N4274 3/51	2N5640 2/51	LM3404-468 1/75
	2N798 6/51	2N4276 3/51	2N5640 2/51	LM3404-474 1/75
	2N799 6/51	2N4278 3/51	2N5640 2/51	LM3404-480 1/75
	2N800 6/51	2N4280 3/51	2N5640 2/51	LM3404-486 1/75
	2N801 6/51	2N4282 3/51	2N5640 2/51	LM3404-492 1/75
	2N802 6/51	2N4284 3/51	2N5640 2/51	LM3404-498 1/75
	2N803 6/51	2N4286 3/51	2N5640 2/51	LM3404-504 1/75
	2N804 6/51	2N4288 3/51	2N5640 2/51	LM3404-510 1/75
	2N805 6/51	2N4290 3/51	2N5640 2/51	LM3404-516 1/75
	2N806 6/51	2N4292 3/51	2N5640 2/51	LM3404-522 1/75
	2N807 6/51	2N4294 3/51	2N5640 2/51	LM3404-528 1/75
	2N808 6/51	2N4296 3/51	2N5640 2/51	LM3404-534 1/75
	2N809 6/51	2N4298 3/51	2N5640 2/51	LM3404-540 1/75
	2N810 6/51	2N4300 3/51	2N5640 2/51	LM3404-546 1/75
	2N811 6/51	2N4302 3/51	2N5640 2/51	LM3404-552 1/75
	2N812 6/51	2N4304 3/51	2N5640 2/51	LM3404-558 1/75
	2N813 6/51	2N4306 3/51	2N5640 2/51	LM3404-564 1/75
	2N814 6/51	2N4308 3/51	2N5640 2/51	LM3404-570 1/75
	2N815 6/51	2N4310 3/51	2N5640 2/51	LM3404-576 1/75
	2N816 6/51	2N4312 3/51	2N5640 2/51	LM3404-582 1/75
	2N817 6/51	2N4314 3/51	2N5640 2/51	LM3404-588 1/75
	2N818 6/51	2N4316 3/51	2N5640 2/51	LM3404-594 1/75
	2N819 6/51	2N4318 3/51	2N5640 2/51	LM3404-600 1/75
	2N820 6/51	2N4320 3/51	2N5640 2/51	LM3404-606 1/75
	2N821 6/51	2N4322 3/51	2N5640 2/51	LM3404-612 1/75
	2N822 6/51	2N4324 3/51	2N5640 2/51	LM3404-618 1/75
	2N823 6/51	2N4326 3/51	2N5640 2/51	LM3404-624 1/75
	2N824 6/51	2N4328 3/51	2N5640 2/51	LM3404-630 1/75
	2N825 6/51	2N4330 3/51	2N5640 2/51	LM3404-636 1/75
	2N826 6/51	2N4332 3/51	2N5640 2/51	LM3404-642 1/75
	2N827 6/51	2N4334 3/51	2N5640 2/51	LM3404-648 1/75
	2N828 6/51	2N4336 3/51	2N5640 2/51	LM3404-654 1/75
	2N829 6/51	2N4338 3/51	2N5640 2/51	LM3404-660 1/75
	2N830 6/51	2N4340 3/51	2N5640 2/51	LM3404-666 1/75
	2N831 6/51	2N4342 3/51	2N5640 2/51	LM3404-672 1/75
	2N832 6/51	2N4344 3/51	2N5640 2/51	LM3404-678 1/75
	2N833 6/51	2N4346 3/51	2N5640 2/51	LM3404-684 1/75
	2N834 6/51	2N4348 3/51	2N5640 2/51	LM3404-690 1/75
	2N835 6/51	2N4350 3/51	2N5640 2/51	LM3404-696 1/75
	2N836 6/51	2N4352 3/51	2N5640 2/51	LM3404-702 1/75
	2N837 6/51	2N4354 3/51	2N5640 2/51	LM3404-708 1/75
	2N838 6/51	2N4356 3/51	2N5640 2/51	LM3404-714 1/75
	2N839 6/51	2N4358 3/51	2N5640 2/51	LM3404-720 1/75
	2N840 6/51	2N4360 3/51	2N5640 2/51	LM3404-726 1/75
	2N841 6/51	2N4362 3/51	2N5640 2/51	LM3404-732 1/75
	2N842 6/51	2N4364 3/51	2N5640 2/51	LM3404-738 1/75
	2N843 6/51	2N4366 3/51	2N5640 2/51	LM3404-744 1/75
	2N844 6/51	2N4368 3/51	2N5640 2/51	LM3404-750 1/75
	2N845 6/51	2N4370 3/51	2N5640 2/51	LM3404-756 1/75
	2N846 6/51	2N4372 3/51	2N5640 2/51	LM3404-762 1/75
	2N847 6/51	2N4374 3/51	2N5640 2/51	LM3404-768 1/75
	2N848 6/51	2N4376 3/51	2N5640 2/51	LM3404-774 1/75
	2N849 6/51	2N4378 3/51	2N5640 2/51	LM3404-780 1/75
	2N850 6/51	2N4380 3/51	2N5640 2/51	LM3404-786 1/75
	2N851 6/51	2N4382 3/51	2N5640 2/51	LM3404-792 1/75
	2N852 6/51	2N4384 3/51	2N5640 2/51	LM3404-798 1/75
	2N853 6/51	2N4386 3/51	2N5640 2/51	LM3404-804 1/75
	2N854 6/51	2N4388 3/51	2N5640 2/51	LM3404-810 1/75
	2N855 6/51	2N4390 3/51	2N5640 2/51	LM3404-816 1/75
	2N856 6/51	2N4392 3/51	2N5640 2/51	LM3404-822 1/75
	2N857 6/51	2N4394 3/51	2N5640 2/51	LM3404-828 1/75
	2N858 6/51	2N4396 3/51	2N5640 2/51	LM3404-834 1/75
	2N859 6/51	2N4398 3/51	2N5640 2/51	LM3404-840 1/75
	2N860 6/51	2N4400 3/51	2N5640 2/51	LM3404-846 1/75
	2N861 6/51	2N4402 3/51	2N5640 2/51	LM3404-852 1/75
	2N862 6/51	2N4404 3/51	2N5640 2/51	LM3404-858 1/75
	2N863 6/51	2N4406 3/51	2N5640 2/51	LM3404-864 1/75
	2N864 6/51	2N4408 3/51	2N5640 2/51	LM3404-870 1/75
	2N865 6/51	2N4410 3/51	2N5640 2/51	LM3404-876 1/75
	2N866 6/51	2N4412 3/51	2N5640 2/51	LM3404-882 1/75
	2N867 6/51	2N4414 3/51	2N5640 2/51	LM3404-888 1/75
	2N868 6/51	2N4416 3/51	2N5640 2/51	LM3404-894 1/75
	2N869 6/51	2N4418 3/51	2N5640 2/51	LM3404-900 1/75
	2N870 6/51	2N4420 3/51	2N5640 2/51	LM3404-906 1/75
	2N871 6/51	2N4422 3/51	2N5640 2/51	LM3404-912 1/75
	2N872 6/51	2N4424 3/51	2N5640 2/51	LM3404-918 1/75
	2N873 6/51	2N4426 3/51	2N5640 2/51	LM3404-924 1/75
	2N874 6/51	2N4428 3/51	2N5640 2/51	LM3404-930 1/75
	2N875 6/51	2N4430 3/51	2N5640 2/51	LM3404-936 1/75
	2N876 6/51	2N4432 3/51	2N5640 2/51	LM3404-942 1/75
	2N877 6/51	2N4434 3/51	2N5640 2/51	LM3404-948 1/75





## NEW 60/600MHZ PORTABLE COUNTER

- Large 3" 7-digit LED display
- CMOS LSI construction
- Small-ideal for field use
- Portable battery operated
- With NiCd batteries & charger
- Internal crystal time base
- Inputs overload protection
- 1 Hz resolution on low range
- 1 meg input-sensitivity 50 mv
- 50 ohm input-sensitivity 100 mv
- Size: 2 1/2" x 2 7/8" x 1 1/2"
- A 600 HZ FREQUENCY COUNTER THAT CAN GO ANYWHERE... NOT A KIT



ONLY \$299


Dealer Inquiries Invited  
CBS ENTERPRISE P.O. BOX 1356 COCOA BEACH FLA. 32931

LEARN Design Techniques. Electronics Design News-letter, Digital, linear construction projects, design theory and procedures. Annual Subscription \$6.00, sample copy \$1.00. Valley West, Box 2119-B, Sunnyvale, CA 94087.
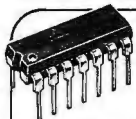
## HOME VIDEO RECORDER

ONLY \$325.00 — FULL COLOR

New Cartrivision Recorder — Top Condition  
Parts, Service, Tape, Programs  
Record Your Favorite T.V. Shows  
Perfect Family Christmas Gift  
**MEDIA ASSOC.,** 1470A N. 4th St., Dept. P.  
San Jose, CA 95112 (408) 294-5450



## Quality Electronic Components

Accelerated Discount Schedule  
Saves You Even More!

2102-1	8080A	LM3909
\$1.99	\$24.95	69¢

## INTEGRATED CIRCUITS — TTL, CMOS, LINEAR & MOS

7400 .21	7473 .30	74174 .98	4001 .23	4073 .23
7401 .21	7474 .30	74175 .98	4002 .23	4075 .23
7402 .21	7475 .30	74176 .79	4006 1.23	4081 .23
7403 .21	7476 .32	74177 .79	4007 .23	4082 .23
7404 .21	7480 .70	74180 .70	4008 .79	4502 .79
7405 .21	7482 .70	74181 2.15	4009 .44	4510 1.14
7406 .25	7483 .70	74182 .79	4010 .44	4511 1.05
7407 .25	7485 .89	74184 2.19	4011 .23	4514 2.80
7408 .21	7486 .28	74185 2.19	4012 .23	4515 2.80
7409 .21	7489 2.19	74188 3.50	4013 .40	4516 1.23
7410 .21	7490 .44	74189 3.50	4014 .96	4518 1.14
7411 .21	7491 .70	74190 2.23	4015 .96	4520 1.14
7412 .21	7492 .44	74191 1.23	4016 .40	4527 1.68
7413 .25	7493 .44	74192 .88	4017 1.05	4528 .88
7414 .89	7494 .70	74193 .88	4018 1.05	4585 1.23
7416 .25	7495 .70	74194 .88	4019 .23	LM309K
7417 .25	7496 .70	74195 .88	4020 1.14	LM324N
7420 .21	74100 1.28	74196 .88	4021 1.14	LM3401-5
7421 .25	74101 .88	74197 .88	4022 .23	LM3401-6
7423 .35	74109 .35	74198 1.49	4023 .23	LM3401-8
7425 .35	74121 .35	74199 1.49	4024 .84	LM3401-12
7426 .25	74122 .44	74201 1.09	4025 .23	LM3401-15
7427 .25	74123 .61	74202 .88	4026 1.68	LM3401-18
7428 .28	74125 .40	74203 .67	4027 .40	LM3401-24
7430 .21	74126 .40	74204 .88	4028 .89	LM3909N
7432 .25	74132 .70	74205 .67	4029 .14	NE531
7433 .30	74141 .88	74206 .67	4030 .23	NE540
7437 .25	74145 .70	75150 1.31	4031 .50	NE555V
7438 .25	74147 1.63	75450 .88	4034 3.50	NE566A
7440 .21	74148 .30	75451 .61	4035 .23	NE568
7441 .88	74150 1.16	75452 .61	4040 1.14	NE561B
7442 .33	74151 .70	75453 .61	4041 .79	NE562B
7443 .63	74153 .65	75454 .61	4042 .79	NE563A
7444 .63	74154 1.03	75455 .61	4043 .79	NE564V
7445 .70	74155 .70	75456 .84	4044 .70	NE567V
7446 .70	74156 .70	75457 .84	4045 .88	uA709CV
7447 .70	74157 .70	75458 1.19	4046 .40	uA710CA
7448 .70	74158 .70	75459 .40	4047 .40	uA711CA
7450 .21	74161 .88	8094 .40	4051 1.26	uA723CA
7453 .21	74162 .88	8095 .67	4052 1.26	uA741CV
7454 .21	74163 .88	8096 .67	4053 1.26	uA747CA
7460 .21	74164 .96	8097 .67	4056 1.58	uA748CV
7470 .30	74166 1.26	8098 .67	4066 .79	MCL458V
7472 .30	74170 2.64	8225 2.19	4071 .23	2102-1... 1.99
	74173 1.42	4000 .23	4072 .23	

## BISHOP GRAPHICS Printed Circuit Drafting

Aids are now available from Dig-Key

## DATA BOOKS

TTL IC's 592 pages	..... \$4.00	Interface IC's 464 pages	..... \$4.00
Linear IC's 957 pages	..... \$5.00	Voit. Regs. 128 pages	..... \$3.00
CMOS IC's 256 pages	..... \$3.00	Linear Appl. 1, 432 pages	..... \$4.00
Transistors 288 pages	..... \$3.00	Linear Appl. 2, 246 pages	..... \$3.00
Memory IC's 592 pages	..... \$3.00	Audio, 196 pages	..... \$3.00

## SILICON TRANSISTORS


MP5018, MP5030, MP5222A, MP5236A, MP5297A, MP5339, MP5393, MP5394, MP5395, MP5356, MP5356S, MP5363A, MP5363B, MP5364, MP5364S, MP5364S, MP5364S, 2N3904, 2N3906, 2N4124, 2N4126, 2N4401, 2N4403, 2N4410, PN4888, 2N5087, 2N5089, PNP229, PNP333, PNP334, PNP337, PNP338, PNP339, 2N5210, 2N5964 .16, \$1.55/10, \$13.60/100 of same part no.

MPF102 .36 \$30.60/C 2N5457 .48 \$41.00/C MP5A13 .28 \$24.00/C 2N3055 .99 \$85.00/C

## AP SUPER STRIP II—Universal Breadboarding

Element with 840 Solderless Plug-In Tie-Points

\$17.00

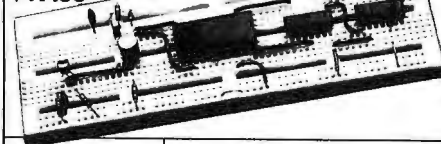

## LED DISPLAYS

LED357 C.C. .375"	\$1.75
LED500 C.C. .500"	\$1.75
LED500 C.C. .500"	\$1.75
LED800 C.C. .800"	\$3.50
LED800 C.C. .800"	\$3.50

## LED LAMPS

NSL5053 T-1 1/4"	18c
NSL5056 T-1 1/4"	18c

## 1/2 WATT ZENER DIODES

1N5226B 3.3v 15 111/C	1N5236B 7.5v 15 111/C
1N5227B 3.6v 15 111/C	1N5237B 8.2v 15 111/C
1N5228B 3.9v 15 111/C	1N5238B 8.7v 15 111/C
1N5229B 4.3v 15 111/C	1N5239B 9.1v 15 111/C
1N5230B 4.7v 15 111/C	1N5240B 10v 15 111/C
1N5231B 5.1v 15 111/C	1N5241B 11v 15 111/C
1N5232B 5.6v 15 111/C	1N5242B 12v 15 111/C
1N5233B 6.0v 15 111/C	1N5243B 13v 15 111/C
1N5234B 6.2v 15 111/C	1N5244B 14v 15 111/C
1N5235B 6.8v 15 111/C	1N5245B 15v 15 111/C

## 12" ALL PURPOSE 1 VOLT P TO P GREEN PHOSPHOR VIDEO DISPLAY

IDEAL UNIT FOR ANY DIGITAL OR GRAPHICS APPLICATION

**\$150** Add \$10 for packing and shipping in continental US

**COMPUTER WAREHOUSE STORE**  
584 Commonwealth Ave. Boston 02215

RESISTOR ASSORTMENT 100/\$1.50, majority 5% 1/8, 1/4, 1/2 watt. No Doubles! New, Uncut. F. Horvath, 299 Schuyler Avenue, Kearny, New Jersey 07032.

**NATIONAL MA1002A**  
DIGITAL CLOCK MODULE

MA1002A Module Only  
**\$10.50**

**A GREAT GIFT IDEA!**

**\$13.95 KIT**

INCLUDES  
MA1002A  
CLOCK MODULE  
SIX SWITCHES  
— and —  
SPECIAL TRANSFORMER

**FEATURES:**

- Bright 4 Digit 0.5" LED Display
- Assembled and Tested Module - You only need connect transformer and switches
- 12 Hour Format with PM Indicator
- 50 or 60 Hz Operation
- Power Failure Indication
- Brightness Control Capability
- Alarm and Snooze Timers
- Compact 3.05"x1.375"

A P PRODUCTS ACE'S		
200K . \$18.95	201K . \$24.95	227... \$59.95
208... \$28.95	212... \$34.95	236... \$79.95
	218... \$46.95	

## WIRE-WRAPPING TOOL

\$5.95

Wraps, Unwraps & Strips 30 ga. Wire

## 1/4 & 1/2 WATT 5% CARBON FILM RESISTORS

5c each in multiples of 5 per value  
\$1.70/500 & \$12.00/1000 of same value  
10 ohm thru 1.0 megohm

## I.C. SOCKETS

8 Pin Solder Tab	.17
14 Pin Solder Tab	.20
16 Pin Solder Tab	.22
18 Pin Solder Tab	.29
24 Pin Solder Tab	.38
28 Pin Solder Tab	.45
40 Pin Solder Tab	.63
8 Pin Wire-Wrap	.26
14 Pin Wire-Wrap	.30
16 Pin Wire-Wrap	.30
18 Pin Wire-Wrap	.40
24 Pin Wire-Wrap	.66
28 Pin Wire-Wrap	.72
40 Pin Wire-Wrap	1.00

## HARDWARE

2-5/16 1/4 Screw	.99/C 7.20/M
2-5/16 1/2 Screw	.99/C 7.65/M
4-40 1/4 Screw	.55/C 3.60/M
4-40 1/2 Screw	.60/C 4.05/M
6-32 1/4 Screw	.65/C 4.40/M
6-32 1/2 Screw	.75/C 4.85/M
8-32 3/8 Screw	.90/C 5.85/M
2-5/16 Hex Nut	.55/C 3.60/M
4-40 Hex Nut	.55/C 3.75/M
6-32 Hex Nut	.60/C 4.00/M
8-32 Hex Nut	.60/C 4.15/M
No. 2 Lockwasher	.85/C 5.75/M
No. 4 Lockwasher	.45/C 3.00/M
No. 6 Lockwasher	.45/C 3.00/M
No. 8 Lockwasher	.45/C 3.00/M

Send for free catalog or mail orders.

"Only Quality Components Sold!"

DON'T FORGET TO APPLY VOLUME DISCOUNT ABOVE

**DIGI-KEY CORPORATION**

P.O. Box 677

Thief River Falls, MN 56701

**SOLID STATE DIGITAL CLOCK CALENDAR ALARM**

- \* Automatic Display of Time & Date.
- \* 6-Digit (hrs-min-sec), 55" High, 7 Segment Planar Gas Discharge Display.
- \* 28/30/31 Day Calendar.
- \* 24 Hr. Alarm w/Snooze (10 min. intervals).
- \* 12 or 24 Hr. Operation (Switch Selected).
- \* 115VAC/220VAC, 50HZ/60HZ (Specify).
- \* Power Failure Indication.
- \* PM Indication (12 Hr. Operation).
- \* Low Profile Black Acrylic Plastic Case with Simulated Rosewood. Fully Assembled, Tested & Guaranteed...\$49.95 Ppd.
- \* In Continental USA, CA Res. add 6% Sales Tax.

**PUNZALAN-ANG ELECTRONICS, 7 Brooks Pl., Pacifica, CA 94044.**

CALCULATOR Information leading to increased versatility of your four-banger. Send \$1.00 to: R. M. W., Box 60006, Sunnyvale, California 94088.

SALE OF GROUND FAULT INTERRUPTER MODULES — Mfrs. closeout on Selected Models. Operates your circuit breaker. While supply lasts. Kabo Electronics, 123 Bacon Street, Natick, Mass. 01760.

MICROCOMPUTER \$100. Uses surplus components. Keyboard, 1K RAM, power supply, LED readouts. Information \$1. NBL-E, Box 1115, Richardson, Texas 75080.

LOGIKLAB 151—MULTIFUNCTION DIGITAL TEST INSTRUMENT. Combines regulated 5 VDC, 1 A power supply with wide range square wave, pulse, and one-shot generator. A basic tool for all experimenters at a low \$79.50. Write for specifications. Integral Electronics Corporation, Box 286, Commack, NY 11725.

NEW! 500 MHz FREQUENCY COUNTER 8-digit built-in TCXO ±2ppm (±.0002%). Complete kit \$249.95. Instruction manual alone \$3.00. Davis Electronics, Dept. C., 636 Sheridan Drive, Tonawanda, NY 14150. (716) 874-5848.

**HOBBY SPECIALS**  
You Test 'Em Save Big Money

POWER PAK	100 asst. (includes Case T03, T066, T0220, T0202)	\$2.99
TRANSISTOR/DIODE PAK	100 asst. (includes Case T05, T039, T018, D07, D041)	\$1.99
I.C. PAK	100 asst. (includes 14 & 16 pin)	\$3.50
RESISTOR PAK	100 asst. (assorted values)	\$1.50
MOS FET	10 asst. (many top nos. Case T072)	\$0.99
SCR PAK	100 asst. (similar to C103 Series) Case T092, VR:10-100V, 1:400MA, IGT: 200MA	\$4.00

Over 100 Bargains for Hobbyists, Schools, Industry  
Call or Write for Free Catalog

**NEW-TONE ELECTRONICS** \$5.00 Minimum Order  
PO BOX 1738A (201) 748-6171 All Orders add \$1.00 postage  
Bloomfield, NJ 07003 N.J. Residents add 5% sales tax

## PLANS AND KITS

**AMAZING ELECTRONIC PRODUCTS**

LASERS SUPER POWERED, RIFLE, PISTOL, POCKET... SEE IN DARK - PYRO-TECHNICAL, DE-BUGGING - UNCRAMBLERS - GIANT TESLA - STUNWAND - TV DISRUPTER - ENERGY PRODUCING, SCIENTIFIC DETECTION, ELECTRIFYING, CHEMICAL, ULTRASONIC, CB, RADIO, AUTO AND MCH DEVICES, HUNDREDS MORE - ALL NEW PLUS INFO UNLIMITED PARTS SERVICE.

**INFORMATION unlimited**  
CATALOG \$1 Box 626 Lord Jeffery PZ. • Amherst, N.H. 03031

FANTASTIC — Solderless breadboard kit with all parts for fascinating experiments with Flasher/Oscillator/Siren chip \$12.95 less battery. Catalog 50 cents (refundable). Satisfaction Guaranteed. Ego, Box 1331-pa, Thousand Oaks, California 91360.

FREE KIT Catalog contains Test and Experimenter's Equipment. Dage Scientific Instruments, Box 1054P, Livermore, CA 94550.

"CBers!" "TREMENDOUS POWER INCREASE!" using NEW higher 46' all-directional CB Antenna!!! Plan \$2. (2/83). Astrobeam-3, 704 Edwards, Visalia, CA 93277.

**TIGER SST SIMPLI-KIT**

**FOR THE DO-IT-YOURSELF**  
**NOW!** a high quality CD Electronic Ignition System in kit form.

Contains all components and solder to build complete Solid-State Electronic CD Ignition System for your car. Assembly requires less than 3 hours.

- Increases MPG 15%
- Increases horsepower 15%
- Eliminates 4 of 5 tune-ups
- Plugs and Points last 50,000 miles
- Instant starting, any weather
- Dual system switch

Fits only 12 volt neg. ground... Only \$21.95 postpaid

**Ti-Star Corporation**  
P.O. Box 1727 Grand Junction, Colorado 81501

## THE KING OF ALTAJ

25.50



### 6-DIGIT ALARM CLOCK

#### THE KING FEATURES:

- 1) 6 digit, 12 hr. 60 cycle or 24 hr. 50 cycle alarm clock.
- 2) Time sharing capability for display of additional information.
- 3) Single 12v. supply and a minimum of interface components.
- 4) AM/FM and automatic power fail-ure indications.
- 5) 10 minute snooze
- 6) Intensity control of LEDs.

Kit No. 70250-1R (Red readouts)  
Kit No. 70250-1G (Green readouts)  
Kit No. 70250-1Y (Yellow readouts)  
Kit No. 70250-2R (DL727 readouts) 5 in. \$29.50

All kits include components, PC Boards, Transformer, case, and construction manual.

## THE KING'S HAREM

### FATIMA 4-DIGIT TEMP. KIT

\$24.95

Features 4 digit temperature display, Fahrenheit or Centigrade, complete CMOS application; uses 7002 4 digit counter.

Kit includes all components, PC Board and instructions for interfacing with THE KING 6-digit alarm clock. Addition Number 1

### DELILA APPLIANCE STARTER \$9.95

(Example) Set your alarm for 7: a.m., set timer for 15 min. At exactly 7 a.m., the appliance will start; at 7:15 your clock alarm will wake you.

Kit includes all components, PC Board and instructions for interfacing with THE KING 6-digit alarm clock. Addition Number 2

### TANYA 60 HZ CRYSTAL TIME BASE

#### ADDITIONAL FEATURES:

- 1) Low Power Consumption
- 2) Directly Interfaces with King MOS Clock Chip.
- 3) 60 Hz output with crystal time base accuracy
- 4) Ideal for Cars, Boats, & Campers.

Kit includes all components, PC Board and instructions for interfacing with THE KING 6-Digit Alarm Clock. Addition Number 3.



**FND 70**  
RED, .25 in. Char.  
15mA per segment.  
Common Cathode.  
\$1.25

**DL727**

One of our best readouts  
5 in. high, 20mA per  
segment. Common anode.  
\$3.75



**FND 800**  
New .5 in. display  
by Fairchild.  
Common Cathode.  
\$1.50  
\$21.50

**DL727**

One of our best readouts  
5 in. high, 20mA per  
segment. Common anode.  
\$3.75



**FND 803**  
New .5 in. display  
by Fairchild.  
Common Cathode.  
\$1.50  
\$21.50

**DL727**

One of our best readouts  
5 in. high, 20mA per  
segment. Common anode.  
\$3.75



**FND 803**  
New .5 in. display  
by Fairchild.  
Common Cathode.  
\$1.50  
\$21.50

**DL727**

One of our best readouts  
5 in. high, 20mA per  
segment. Common anode.  
\$3.75



**FND 803**  
New .5 in. display  
by Fairchild.  
Common Cathode.  
\$1.50  
\$21.50

**DL727**

One of our best readouts  
5 in. high, 20mA per  
segment. Common anode.  
\$3.75



**FND 803**  
New .5 in. display  
by Fairchild.  
Common Cathode.  
\$1.50  
\$21.50


**DL727**

One of our best readouts  
5 in. high, 20mA per  
segment. Common anode.  
\$3.75



## MSI

Wise  
move

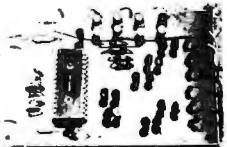


### 4-DIGIT DECADE COUNTER KIT

\$19.95

KIT 018

One chip 4 digit decade counter kit, with both 7 segment and BCD output.

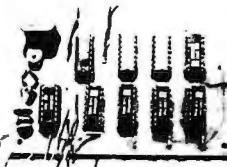1. Chip features internal oscillator for scanning speed.
2. Overflow and count extent outputs.
3. Transfer, reset, count, blanking and true complement control inputs.
4. PC Boards can be cascaded to 8-12-16, etc. digits.
5. Kit includes counter chip, drive circuit for 4 cathode type displays and PC Board. (For read-out boards see FND70-FND303)



### TIME BASES

1 MHz crystal chain time base divider. Outputs: 1MHz-100KHz-10KHz-1KHz-100Hz-10Hz-1Hz-0.1Hz. Accuracy better than .005% with proper adjustment.

Kit 013 complete CMOS with PC board ..... \$15.75

Buffer Circuit for TTL interfacing

Kit 014 Same as Kit 013, but with TTL..... \$13.75

Kit 015 60Hz or 60KHz chain time base using line frequency as reference. Accuracy 0.1-0.05%. Outputs 10Hz-1Hz-0.1Hz. Complete with CMOS shaping circuit and PC Board..... \$8.35

Kit 019 Same as Kit 015, but with TTL and 60Hz only..... \$7.75

Kit 013 60Hz chain time base using line frequency for Kit 020 RPM counter

\*Outputs: 6 sec. = 100th of RPM  
6 sec. = 10th of RPM  
60 sec. = full revolution \$7.75

## MODULAR SCIENTIFIC INSTRUMENTATION

Now you can build some of the most advanced digital electronic instruments with our new series of low-cost modular scientific kits. These kits will expand the range of your electronic applications enormously-and all at a surprisingly low cost.

The heart of the system is our 4-digit Decade Counter (Kit 012) which features a full 4-digit LED readout (you choose the size best suited to your application). Combine this with a 5-volt regulated power supply (Kit 030) and you have the basis of a wide range of sophisticated electronic instruments, including:

A Digital Voltmeter (DVM) .. Kit 012 + Kit 030 + Kit 017  
Frequency Counter..... Kit 012 + Kit 030 + Kit 018  
RPM Counter..... Kit 012 + Kit 030 + Kit 020 + Kit 018

### KIT 018 FREQ. COUNTER

Features FET input front end with trigger circuit for measuring complex waveforms. Measures from 0.1Hz to 10MHz when used with Kit 015 or 018. Measures from .01Hz to 35MHz when used with Kit 013 and 014. \$24.50



### KIT 030 POWER SUPPLY

\*Input voltage: 25V max. \*Output current: 1 amp max.  
\*Load regulation: 50mV \*Output voltage: 5V. \*Line regulation: .01% (requires 8-20V transformer) \$4.55

(Contains all parts except transformer)

### KIT 017 DVM

1.999V as basic, with polarity indication. 1 M ohm input impedance and accuracy to 1% if properly adjusted \$18.50



### KIT 020 RPM COUNTER

Counts from 1 to 100,000 RPM. RPM counter kit contains components and PC board. \$8.95

## MSI CLUB

Send for your membership card to the Modular Scientific Instrumentation Club and receive a big 10% off on future purchases of MSI kits. Send \$3.00 with your name and address. We will promptly send your very own registered membership card. Don't miss out on the savings. Write now.

Memberships valid for one year from date of registration

### TTL BOARDS

MEMOREX computer boards with TTL's Diodes and Transistors, etc.

5 Boards containing 150-250 IC's \$4.50

### GE TRANSISTOR ASSORTMENT

1098 assorted Darling, SCRs, NPN,PNP, etc.

50 for \$1.50  
100 for \$2.50  
300 for \$6.00

### LSI INTEGRATION

MM5318	4-6 digit alarm clock 40 pin dip w/spec.	\$ 4.25
7002	4 digit counter/latch decoder; 7 segment and BCD outputs. 28 pin dip w/spec.	\$12.50
7005	4 digit counter/latch decoder; 7 segment output only. 24 pin dip w/spec.	\$ 9.50
7007	4 digit counter/latch decoder with BCD output only. 16 pin dip w/spec.	\$ 7.00
70250	4-6 digit alarm clock 28 pin dip w/spec.	\$ 5.50
PC Board for 70250	4 digit non-multiplexed radio alarm clock featuring direct drive display output 40 pin dip w/spec.	\$4.50
PC Board for 70380	8 bit parallel CPU.	\$ 3.75
8008	8 bit parallel CPU.	\$19.50
2102	1K static RAM for 8008.	\$ 2.25
MM5203	2K UV erasable PROM.	\$12.25
75481	segment driver.	\$ 0.35
75492	digit driver.	\$ 0.45
7020	6 function calculator chip with direct segment drive. 8 digit.	\$ 2.25

### TTL


7400	-21	7448	-94	74151	-80
7402	-21	7453	-21	74153	-94
7404	-21	7473	-42	74154	-100
7406	-20	7474	-42	74161	-104
7408	-21	7475	-70	74163	-124
7410	-21	7476	-44	74164	-184
7413	-64	7483	-80	74175	-134
7420	-21	7488	250	74176	-144
7427	-29	7490	-74	74181	-280
7430	-21	7492	-80	74192	-130
7437	-44	7493	-80	74193	-130
7438	-38	7495	-80	74195	-84
7440	-21	7496	-80		
7442	-74	74121	-43		
7447	-94	74122	-80		

### CMOS

4000	-24	4018	-149	4037	-450
4001	-24	4019	-59	4040	-159
4002	-24	4020	-159	4041	-89
4008	-149	4021	-149	4042	-79
4007	-24	4022	-119	4043	-80
4008	-115	4023	-24	4048	-59
4009	-59	4024	-99	4049	-59
4010	-55	4025	-24	4049	-59
4011	-24	4027	-59	4050	-59
4012	-24	4028	-99	4055	-99
4013	-59	4029	-139	74C12	-29
4014	-149	4030	-49	74C14	-29
4015	-119	4034	-325	74C107	-129
4016	-59	4035	-139		
4017	-129				
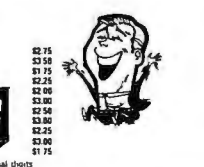
### 4 & 6 DIGIT PC BOARDS

PC Board for 4 digit display FND 800 or 807 \$2.75  
PC Board for 6 digit display FND 800 or 807 \$3.50  
PC Board for 4 digit display MAX series or DL707 \$2.25  
PC Board for 4 digit display FND503 \$2.00  
PC Board for 6 digit display FND503 \$2.50  
PC Board for 4 digit display DL747 \$2.50  
PC Board for 6 digit display DL747 \$3.00  
PC Board for 4 digit display DL727 \$2.50  
PC Board for 6 digit display DL727 \$3.00  
PC Board for 4 digit display FND70 \$2.75



## ALTAJ ELECTRONICS

P.O. BOX 28544, Dallas, Texas 75238

TERMS: Cash or money order. No COD.

Telephone (214) 278-3561





**INTENSIVE 5 week course for Broadcast Engineers.** FCC First Class license. Student rooms at the school. Radio Engineering Inc., 61 N. Pineapple Ave., Sarasota, FL 33577 and 2402 Tidewater Trail, Fredericksburg, VA 22401.

**RADIO BROADCASTING:** Become DJ! Get free tapes - records - equipment. Start own station! Learn How. "Radio!", Box 5516-AK, Walnut Creek, CA 94596.

**FCC EXAMINATIONS.** 532 First, Second, Third Questions-Answers. Proven "topical" study method. \$7.00. "Exams", Box 5516-AK, Walnut Creek, CA 94596.

**LEARN Electronics-Mathematics.** Individualized correspondence lessons. Trial \$2.00: Vinther Institute, Box 9447P, Berkeley, CA 94709.

## TUBES

**RADIO & T.V. Tubes**—36 cents each. Send for free Catalog. Cornell, 4213 University, San Diego, Calif. 92105. **TUBES** receiving, factory boxed, low prices, free price list. Translertonic, Inc., 1365 39th Street, Brooklyn, N.Y. 11218A, Telephone: 212-633-2800.

**TUBES:** "Oldies", Latest. Supplies, components, schematics. Catalog Free (stamp appreciated). Steinmetz, 7519-PE Maplewood, Hammond, Ind. 46324.

## MUSICAL INSTRUMENTS

**UP TO 60% DISCOUNT.** Name brand instruments catalog. Freeport Music, 114 G. Mahan St., W. Babylon, N.Y. 11704. **30% to 60% DISCOUNT!** Any model: Guitar, Amp, Drums. Free Catalog! Warehouse, PE-6, Box 11449, Ft. Worth, Texas 76109.

## BUSINESS OPPORTUNITIES

**I MADE \$40,000.00 Year by Mailorder!** Helped others make money! Free Proof. Torrey, Box 318-NN, Ypsilanti, Michigan 48197.

**FREE CATALOGS.** Repair air conditioning, refrigeration. Tools, supplies, full instructions. Doolin, 2016 Canton, Dallas, Texas 75201.

**MAILORDER MILLIONAIRE** helps beginners make \$500 weekly. Free report reveals secret plan! Executive (1K11), 333 North Michigan, Chicago 60601.

## BULLET ELECTRONICS

P.O. BOX 19442P • DALLAS, TEXAS 75219

**PS-01 POWER SUPPLY KIT**  
IMAGINE! A power supply with a well filtered, regulated output in three voltages. The PS-01A has quality IC regulators, semiconductors and components. The transformer is custom designed and well made. Features 10mv load regulation.  
**YOU GET:**  
Drilled and Plated board  
Complete kit of components  
Heatsinks  
+5V @ 1.5A  
Complete instructions ±15V @ 200mA  
**\$14.95**  
**NOTE:** +5 and ±12VDC supply is available at same price. Order PS-01/B.

**BUILD A COMPLETE CDI IGNITION KIT AT A FRACTION OF THE COST OF OTHER UNITS.** A special buy allows us to sell the complete kit at this low price! Up to 40,000 volts from your present ignition without changing the coil. Simple connections.  
**INCLUDES:** Special toroid transformer  
Drilled and Plated board  
Complete instructions  
All resistors and caps  
All semiconductors  
**\$9.95**  
(Does not include heatsink or case.) For 12V negative ground systems.

**REGULATED 5 VOLT TTL POWER SUPPLY KIT**  
Small (1 1/4" x 1 3/8" x 2 3/8")  
Complete with drilled and plated board  
Includes all components  
The PS-02 is a small, low ripple, regulated, short proof power supply kit that can supply power for 10 to 12 TTL IC's. (350 MA Continuous). \$4.95 or 3/\$12.50

**10 WATT WARBLE ALARM KIT**  
A REAL SCREAMER! Emits a piercing dual tone blast that is impossible to ignore. Great for burglar alarms, signal devices or just a toy. Complete with drilled and plated pc board. Does not include a speaker or power switch. (3-15 volts) \$2.50

**AUDIBLE CONTINUITY TESTER KIT**  
A neat little kit that has a hundred and one uses around the shop and home. You can afford to keep several around at this price!  
**USES:** Code Practice Oscillator  
Continuity Checker  
Transistor, diode or LED checker  
Tone varies with resistance  
Requires 3 to 6 volt batteries (not included)  
**\$1.95**

**HEATSHRINK TUBING ASSORTMENTS**  
A very usable assortment of various 6" pieces of 1/8" to 1/2". 20 pcs. for .59

**TRANSISTORS** (unmarked) 12/\$1.00  
2N2222 12/\$1.00  
2N3904 12/\$1.00  
**SPECIAL MADE SMALL DIAMETER** 50ohm COAX  
Low loss poly-film inner. 1/8" O.D.  
100 ft. roll \$3.99

**SEND A STAMP FOR A FREE CATALOG**

**30% NO C.O.D.** (20% For Alms)  
Add 5% for Postage  
ORDERS UNDER \$10.00 ADD 60¢ HANDLING

**FREE CATALOG**

**GET RICH with Secret Law** that smashes debts and brings you \$500 to \$5 Million cash. Free report! Credit 4K11, 333 North Michigan, Chicago 60601.

## HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Postcard brings facts about this unusual opportunity. Write today! Barta-DK, Box 248, Walnut Creek, CA 94597.

**FREE SECRET BOOK "2042 UNIQUE, Proven Enterprises"** Fabulous "Little Knowns". Work home! Haylings-B, Carlsbad, Calif. 92008.

**HOW TO MAKE \$2,000 WEEKLY** at home using other people's money. Guaranteed. Free Details. Richlieu, Box 25277, Dept. F11, Houston 77005.

**STUFF ENVELOPES,** \$250 per thousand, free supplies, rush stamped, addressed envelope to: M/N Enterprises, Route 1, Box 263E11, Pauls Valley, OK 73075.

## NOVEMBER SPECIALS

TTL	LINEAR	MEMORIES	DISPLAYS
7406 \$ .17	301 \$ .22	1103 \$ .95	DL10A \$1.79
7474 .23	309K .99	1702 8.95	MAN5 1.59
7486 .33	311 .79	2102 1.49	MAN8 1.69
7490 .39	340T-SV .99	5203 8.95	LED's
74107 .29	723 .39	5260 .95	JUMBO CLEAR .13
74123 .59	741 .25	5261 .95	JUMBO ORANGE .15
9602 .59	1414 1.69	F93410 1.39	MV50 10/\$1.00

### RESISTOR KIT

Carbon film - 5%  
1/4 or 1/2 watt  
455 resistors, 48 values  
supplied in a 15 drawer,  
60 compartment storage  
cabinet. Table or wall  
mount. Ready to use



### RESISTOR ASSEMBLY KIT (RISMS)

R	QTY	R	QTY	R	QTY
15	5	680	10	47K	10
33	5	10K	20	68K	10
68	5	15K	10	100K	20
10	10	22K	20	150K	10
15	5	33K	10	270K	10
33	5	47K	20	330K	10
47	10	68K	10	470K	10
68	5	82K	10	600K	10
100	10	10K	20	1.0M	20
150	10	15K	10	1.5M	5
220	10	22K	10	2.2M	5
330	10	33K	10	3.3M	5
470	20	33K	10	4.7M	5

14 WATT 0195 \$24.95 ea.  
12 WATT 0195 \$24.95 ea.

\$20.00 SHIPPING & HANDLING  
SHIPPING VIA UPS OR PARCEL POST

### OTHER AVAILABLE RESISTOR KITS

For additional information write for free catalog.  
100 carbon film resistors ± 5% 1/4 or 1/2 watt  
15 each of 12 values most needed for solid state electronics. 1st quality resistors in a styrene utility box with color code chart. **\$9.95**

1395 carbon film resistors ± 5% 1/4 watt 03255 or 1/2 watt 03505  
105 values with quantities of each determined by typical usage **\$69.00**  
supplied in a 36 drawer, 144 compartment steel cabinet with plastic drawers.

2200 carbon film resistors ± 5% 1/4 watt 04255 or 1/2 watt 04505  
50 resistors per value, 44 values  
supplied in a 15 drawer, 60 compartment steel cabinet with plastic drawers **\$74.95**

2610 carbon film resistors 1/4 watt 05255 or 1/2 watt 05505  
150 values with quantities of each determined by typical usage ± 3% **\$107.00**  
supplied in a 50 drawer, 150 compartment steel cabinet with plastic drawers

400 metal film resistors ± 1% 1/4 watt 11251  
RN 60 temp coeff - 50 PPM/°C  
10 resistors per value, 40 values  
supplied in a 15 drawer, 60 compartment steel cabinet with plastic drawers **\$54.95**

### MEMORIES

1101	256 bit RAM MOS 16 pin	1.39
1103	1024 bit RAM MOS dynamic 18 pin	1.95
1702A	2048 bit PROM static electrically programmable UV erasable 24 pin	10.95
2102	1024 bit RAM static 16 pin	1.95
5203	2048 bit PROM static electrically programmable UV erasable 24 pin	10.95
5260	1024 bit RAM MOS dynamic 16 pin	1.95
5261	1024 bit RAM MOS dynamic 16 pin	1.95
7489	64 bit ROM TTL 16 pin	2.25
82523	256 PROM-SCHOTTKY 16 pin	3.69
F93410	256 bit RAM bi-polar 16 pin	1.95
74187	1024 bit ROM TTL 16 pin	5.75
74200	256 bit RAM tri-state 16 pin	5.45

### SPECIAL DEVICES

372	AF-IF Strip Detector DIP	2.93
546	AM Radio Receiver Subsystem DIP	.75
1310	FM Stereo Demodulator DIP	2.90
1496	Balanced Modulator-Demodulator	.99
1800	Stereo multiplexer DIP	2.48
ULN208	FM Gain Block 34db (typ) mDIP	1.18
ULN209	FM Gain Block 48db (typ) mDIP	1.35
2513	Character Generator 64x8x5 DIP-24	10.20
3046	Transistor Array DIP-14	.73

TTL	LINEAR	MEMORIES	DISPLAYS
7400 .13	7451 .17	74153 .89	74153 .89
7401 .16	7453 .17	74154 .120	74154 .120
7402 .13	7454 .17	74155 .97	74155 .97
7403 .15	7460 .35	74156 .97	74156 .97
7404 .16	7464 .35	74157 .99	74157 .99
7405 .19	7465 .35	74158 1.79	74158 1.79
7406 .20	7470 .30	74160 1.23	74160 1.23
7407 .28	7472 .30	74161 .97	74161 .97
7408 .18	7473 .28	74162 1.39	74162 1.39
7409 .19	7474 .28	74163 1.09	74163 1.09
7410 .16	7475 .49	74164 .99	74164 .99
7411 .25	7476 .30	74165 .99	74165 .99
7413 .43	7483 .68	74166 1.25	74166 1.25
7414 .65	7485 .88	74170 2.10	74170 2.10
7416 .35	7486 .40	74173 1.49	74173 1.49
7417 .35	7489 2.25	74174 1.23	74174 1.23
7420 .16	7490 .43	74175 .97	74175 .97
7422 .30	7491 .75	74176 .89	74176 .89
7423 .29	7492 .48	74177 .84	74177 .84
7425 .27	7493 .46	74180 .90	74180 .90
7426 .26	7494 .78	74181 2.45	74181 2.45
7427 .29	7495 .79	74182 .79	74182 .79
7430 .20	7496 .79	74184 1.90	74184 1.90
7432 .23	74100 .98	74185 2.20	74185 2.20
7437 .25	74105 .44	74187 5.75	74187 5.75
7438 .25	74107 .37	74190 1.15	74190 1.15
7440 .15	74121 .30	74191 1.25	74191 1.25
7441 .89	74122 .38	74192 .95	74192 .95
7442 .59	74123 .65	74193 .85	74193 .85
7443 .73	74125 .54	74194 1.25	74194 1.25
7444 .73	74126 .58	74195 .74	74195 .74
7445 .73	74132 .89	74196 1.25	74196 1.25
7446 .81	74141 1.04	74197 .73	74197 .73
7447 .79	74145 1.04	74198 1.73	74198 1.73
7448 .79	74150 .97	74199 1.69	74199 1.69
7450 .17	74151 .79	74200 5.45	74200 5.45

LINEAR	MEMORIES	DISPLAYS	DISCRETE LED'S
301 .29	324 1.52	560 3.39	ME4 \$ .29
302 .53	340K 1.69	565 1.18	MV50 .12
304 .80	370 1.20	566 1.95	NSL100 .12
305 .71	372 2.93	567 1.95	NSL102 .12
307 .26	373 2.42	709 .26	
308 .89	376 .68	710 .35	
309K 1.35	380 1.30	711 .26	
310 1.87	380-8 1.25	739 1.07	
311 .95	380-1 1.75	741 .32	
319 1.13	381 1.75	747 .71	
320T 1.39	382 1.75	748 .35	
320K 1.39	540 2.95	75491 .71	
322 1.70	554-1 1.19	75492 .80	

DISCRETE LED'S	CLOCK CHIPS
MAN1 \$1.95	CT5002 1.95
MAN2 1.95	CT5005 2.49
MAN3A 1.95	MM5725 1.98
MAN5 2.25	MM5736 2.95
MAN6 2.49	MM5738 3.95
MAN7 1.49	MM5739 3.95
MAN8 2.25	CT7001 5.95
DL10A 2.19	
FD500 1.89	
NS711 1.39	

THESE DISCOUNTS APPLY TO TOTAL OF ORDER - SPECIALS INCLUDED

**10% OFF ON ORDERS OVER \$25**  
**15% OFF ON ORDERS OVER \$100**

LARGE QUANTITY PRICING AVAILABLE ON REQUEST  
PLEASE SPECIFY ITEM AND QUANTITY

**OPTO ISOLATORS**  
MCD2 Opto isolator diode 1.09  
MCT2 Opto isolator transistor .70

**FREE CATALOG AVAILABLE ON REQUEST INCLUDES**  
RESISTORS ±1% & ±5%, TANTALUM CAPACITORS,  
POWER SUPPLY KITS, CLOCK KITS, TOOLS, RESIS-  
TOR & CAPACITOR KITS & MISCELLANEOUS DEVI-  
CES

**CLOCK CHIPS**  
CT5002 1.95  
CT5005 2.49  
MM5725 1.98  
MM5736 2.95  
MM5738 3.95  
MM5739 3.95

### FREE CATALOG AVAILABLE ON REQUEST

Satisfaction guaranteed. Shipment will be made postage prepaid within 3 days from receipt of order. Payment may be made with personal check, charge card (include number and exp. date), or money order. Phone Orders - BoA and M/C card or C.O.D.

Add \$1.00 to cover shipping and handling if order is less than \$10.00.  
California residents add sales tax. Include shipping expense for orders shipped out of U.S. and Canada approx. 10% of order.

**INTERNATIONAL ELECTRONICS UNLIMITED**  
P.O. BOX 3036-P MONTEREY, CA. 93940 USA  
PHONE (408) 659-3171



7400N TTL			
SN7400N	.16	SN7400N	.25
SN7401N	.21	SN7401N	.22
SN7402N	.21	SN7402N	.22
SN7403N	.16	SN7403N	.22
SN7404N	.16	SN7404N	.22
SN7405N	.24	SN7405N	.32
SN7406N	.20	SN7406N	.30
SN7407N	.20	SN7407N	.32
SN7408N	.25	SN7408N	.50
SN7409N	.18	SN7409N	.50
SN7410N	.30	SN7410N	.70
SN7411N	.30	SN7411N	.89
SN7412N	.33	SN7412N	.89
SN7413N	.35	SN7413N	.89
SN7414N	.35	SN7414N	.89
SN7415N	.35	SN7415N	.89
SN7416N	.35	SN7416N	.89
SN7417N	.35	SN7417N	.89
SN7418N	.35	SN7418N	.89
SN7419N	.35	SN7419N	.89
SN7420N	.35	SN7420N	.89
SN7421N	.35	SN7421N	.89
SN7422N	.35	SN7422N	.89
SN7423N	.35	SN7423N	.89
SN7424N	.35	SN7424N	.89
SN7425N	.35	SN7425N	.89
SN7426N	.35	SN7426N	.89
SN7427N	.35	SN7427N	.89
SN7428N	.35	SN7428N	.89
SN7429N	.35	SN7429N	.89
SN7430N	.35	SN7430N	.89
SN7431N	.35	SN7431N	.89
SN7432N	.35	SN7432N	.89
SN7433N	.35	SN7433N	.89
SN7434N	.35	SN7434N	.89
SN7435N	.35	SN7435N	.89
SN7436N	.35	SN7436N	.89
SN7437N	.35	SN7437N	.89
SN7438N	.35	SN7438N	.89
SN7439N	.35	SN7439N	.89
SN7440N	.35	SN7440N	.89
SN7441N	.35	SN7441N	.89
SN7442N	.35	SN7442N	.89
SN7443N	.35	SN7443N	.89
SN7444N	.35	SN7444N	.89
SN7445N	.35	SN7445N	.89
SN7446N	.35	SN7446N	.89
SN7447N	.35	SN7447N	.89
SN7448N	.35	SN7448N	.89
SN7449N	.35	SN7449N	.89
SN7450N	.35	SN7450N	.89
SN7451N	.35	SN7451N	.89
SN7452N	.35	SN7452N	.89
SN7453N	.35	SN7453N	.89
SN7454N	.35	SN7454N	.89

## CONSUMER ELECTRONICS

### PONG

### SUPER PONG

SINGLE GAME \$55.00  
4 GAMES IN ONE \$79.95

GAMES INCLUDED IN SUPER PONG ARE:

- PONG
- CATCH
- SUPER PONG
- HANDBALL

FEATURES OF PONG AND SUPER PONG

- Incremental speed on volleys increases excitement.
- Playing field adjusts to any size screen.
- Game appears in color or in black & white, depending on television set.
- Unmistakable "PONG" sound accompanies each volley.
- Digital scoring flashes on the screen between each point.
- 2 player challenge or Solitaire.
- Hooks up simply to any model television set, the screen actually becomes the playing field.
- English and other languages can be used to make any member of the family a Pong champion.
- Battery operated by 4 size "D" flashlight batteries included with the Unit.

AC Adaptor (Eliminates Batteries) **\$9.95**

### PONG

FOR YOUR HOME TV

## DISCRETE LEDs

**125" dia.**

XC209 Red 10/\$1  
XC209 Green 4/\$1  
XC209 Yellow 7/\$1  
XC209 Orange 4/\$1

**150" dia.**

XC111 Red 10/\$1  
XC111 Green 4/\$1  
XC111 Yellow 7/\$1  
XC111 Orange 4/\$1

**190" dia.**

XC111 Red 10/\$1  
XC111 Green 4/\$1  
XC111 Yellow 7/\$1  
XC111 Orange 4/\$1

**.200" dia.**

XC222 Red 10/\$1  
XC222 Green 4/\$1  
XC222 Yellow 7/\$1  
XC222 Orange 4/\$1  
SSL-22RT 4/\$1

**.185" dia.**

XC526 Red 10/\$1  
XC526 Green 4/\$1  
XC526 Yellow 7/\$1  
XC526 Orange 4/\$1  
XC526 Clear 4/\$1

**.200" dia.**

XC556 Red 10/\$1  
XC556 Green 7/\$1  
XC556 Yellow 7/\$1  
XC556 Orange 7/\$1  
XC556 Clear 7/\$1

**.085" dia.**

MV50 .085" dia. Micro red LED 6/\$1

## DISPLAY LEDs

**CMOS**

CD4000	.25	CD4001	.25
CD4002	.25	CD4003	.25
CD4006	2.50	CD4007	.25
CD4009	.59	CD4010	.59
CD4011	.59	CD4012	.59
CD4013	.47	CD4014	.47
CD4015	.56	CD4016	.56
CD4017	1.35	CD4018	.56
CD4019	.55	CD4020	1.49
CD4021	1.25	CD4022	1.25
CD4023	.25	CD4024	1.50
CD4025	.25	CD4026	1.50
CD4027	.89	CD4028	1.65
CD4029	2.80	CD4030	.65

**LINEAR**

LM3004	.80	LM3005	.80
LM3006	.80	LM3007	.80
LM3008	.80	LM3009	.80
LM3418	.80	LM3419	.80

## CRYSTALS

THESE FREQUENCIES ONLY

Part #	Frequency	Case/Style	Price
CV1A	1.000 MHz	HC33/U	\$5.95
CV2A	2.000 MHz	HC33/U	\$5.95
CV3A	4.000 MHz	HC18/U	\$4.95
CV7A	5.000 MHz	HC18/U	\$4.95
CV12A	10.000 MHz	HC18/U	\$4.95
CV14A	14.31818 MHz	HC18/U	\$4.95
CV19A	18.000 MHz	HC18/U	\$4.95
CV22A	20.000 MHz	HC18/U	\$4.95
CV30B	30.000 MHz	HC18/U	\$4.95

### CLOCK CHIPS — CALCULATOR CHIPS

MMS309	6 Digit, BCD Outputs, Reset PIN.	\$9.95
MMS311	8 Digit, BCD Outputs, 12 or 24 Hour	4.95
MMS312	4 Digit, BCD Outputs, 1 PPS Output	4.95
MMS314	8 Digit, 12 or 24 Hour, 50 or 60 Hz	4.95
MMS316	4 Digit, Alarm, 1 PPS Output	6.95
MMS318	Video Clock Chip, For Use With MMS641	9.95
CT7001	4 Digit, Calendar, Alarm, 12 or 24 Hour	9.95


### CALCULATOR CHIPS

MMS725	6 Digit, Four Function, Less Decimal	\$2.95
MMS731	8 Digit, 5 Function, $\pm$ , $\pi$ , $\sqrt{\phantom{x}}$ , $\%$	2.95
MMS739	8 Digit, 4 Function, Floating Decimal	2.95
CT5030	12 Digit, 4 Function and $\pi$	7.95

### MISC. MOS

MMS320	TV Camera Sync. Generator	\$19.95
MMS330	4 1/2 Digit DVM Chip	9.95
MMS359	60 Hz Timebase Circuit From 3.58 MHz	3.95
MMS641	Video Generator for MMS318	18.00
MC1408-L7	7 Bit Digital to Analog Converter	10.95
MMS607	4 Decade Counter with Latches	10.95
LD101/LD111	3 1/2 Digit DVM Chip Set	25.00
SS900	100 MHz $\rightarrow$ 10 Counter For Prescalers	13.95


## IMK 3 1/2 DIGIT DVM KIT



This 0-2 VDC, .05 per cent digital voltmeter features the Motorola 3 1/2 digit DVM chip set. It has a 4" LED display and operates from a single +5V power supply. The unit is completed with an injection molded black plastic case complete with Bezel. An optional power supply is available which fits into the same case as the 0-2V DVM allowing 117 VAC operation.

**A. 0-2V DVM with Case \$49.95**  
**B. 5V Power Supply \$14.95**

## VECTOR WIRING PENCIL



Vector Wiring Pencil P173 consists of a hand held featherweight (under one ounce) tool which is used to guide and wrap insulated wire, feed off a self-contained replaceable bobbin, into components installed on pre-punched P- Pattern Vectorboards. Connections between the wrapped wire and component leads pads or terminals are made by soldering. Complete with 250 FT of red wire.

**\$7.95**

### REPLACEMENT WIRE — BOBBINS FOR WIRING PENCIL

W36-3-A-Pkg 3	250 ft. 36 AWG GREEN	\$1.95
W36-3-B-Pkg 3	250 ft. 36 AWG RED	\$1.95
W36-3-C-Pkg 3	250 ft. 36 AWG CLEAR	\$1.95
W36-3-D-Pkg 3	250 ft. 36 AWG BLUE	\$1.95

### 1/16 VECTOR BOARD

0.1" Hole Spacing

Part No	P-Pattern	W	L	Price	2-Up
PHENDIC	64P44 D22XXP	4.50	6.50	1.72	1.54
	169P44 D22XXP	4.50	17.00	3.69	3.31
EPOXY GLASS	64P44 D62	4.50	6.50	2.07	1.86
	169P44 D62	4.50	8.50	2.56	2.31
	169P44 D62	4.50	17.00	5.04	4.53
	169P44 D62	4.50	17.00	8.23	8.26
EPOXY GLASS COPPER CLAD	169P44 D62C1	4.50	17.00	6.80	6.12

### HEAT SINKS

205-CB	Beryllium Copper Heat Sink with Black Finish for TO-5	.25
291-36H	Aluminum Heat Sink for TO-220 Transistors & Regulators	.25
680-75A	Black Anodized Aluminum Heat Sink for TO-3	1.60

### NIBBLING TOOL — DIAGONAL CUTTER



This nibbling tool is perfect for cutting out complex shapes from sheet metal, plastic, and other materials. It features a 1/8" wide, 1/4" deep cutting edge and a 1/4" wide, 1/4" deep cutting edge. It is made of high speed steel and is hardened to HRC 62.

**Light Blue Handle \$8.50 ea.**

### 63 KEY KEYBOARD



This keyboard features 63 un-coded SPST keys, unattached to any kind of P.C.B. & a very solid molded plastic 13 x 4 base suits most applications.

**\$19.95**

### JOYSTICK



These joysticks feature four potentiometers, that vary resistance proportional to the angle of the stick. Sturdy metal construction with plastic components only at the movable joint. Perfect for electronic games and instrumentation.

**\*5K Pots \$6.95**  
**\*100K Pots \$7.95**

## MICROPROCESSOR COMPONENTS

### 8080 SUPPORT DEVICES

8080A	8212	8 BIT INPUT/OUTPUT PORT FOR 8080	\$ 5.95	8080	
\$34.95	8216	NON INTERRUPT BI-DIRECTIONAL BUS DRIVER	7.95	\$24.95	
	8224	CLOCK GENERATOR AND DRIVER FOR 8080	12.95		
	8228	SYSTEM CONTROLLER AND BUS DRIVER FOR 8080	12.95		

### CPU'S

8008	8 BIT CPU	\$19.95	1101	256 x 1	Static	\$ 2.25
8080	Super 8008	24.95	1103	1024 x 1	Dynamic	2 for 1.00
8080A	Super 8080A	34.95	2101	256 x 1	Static	5.95
			2102	1024 x 1	Static	1.75
			2107	4096 x 1	Dynamic	9.95
			2111	256 x 4	Static	6.95
			7010	1024 x 1	Static	29.95
			7489	16 x 4	Static	2.49
			8101	256 x 4	Static	6.95
			8111	256 x 4	Static	6.95
			8599	16 x 4	Static	3.49
			91102	1024 x 1	Static	2.25
			74200	256 x 1	Static	6.95
			93421	256 x 1	Static	2.95
			MM5262	2K x 1	Dynamic	.99

### UART'S

AY-5-1013	30K Baud	\$5.95
2513	Char. Gen	\$ 9.95
2516	Char. Gen	10.95
74LS387	1024-Bit Programmable	1.95

### ROM'S

1702A	2048	FAMOS	\$13.95
5203	2048	FAMOS	1.495
82523	32 x 8	Open C	5.00
82523	32 x 8	Tri-state	5.00
74LS287	1024	Static	7.95
3601	256 x 4	Fast	3.95

### BIPOLAR PROM SPECIAL

6300-1 (70 NS)	256 x 4 OPEN COLLECTOR BIPOLAR PROM (EQUIVALENT TO 82S126)	\$2.95
6301-1 (70 NS)	256 x 4 TRI STATE BIPOLAR PROM (EQUIVALENT TO 82S129)	\$2.95

## Continental Specialties

### Proto Board 100 \$19.95



Proto Board 100 is a low cost, big 10 IC capacity prototyping board. It features a 100 pin DIP socket, 100 pin DIP connector, and 100 pin DIP header. It is made of high quality materials and is easy to use.

### THE MINI-BREADBOARD BUDGET KIT \$29.95



The Mini-Breadboard Budget Kit is a complete kit for prototyping 100 pin DIP ICs. It includes 100 pin DIP sockets, 100 pin DIP connectors, and 100 pin DIP headers. It is made of high quality materials and is easy to use.

### Proto Board 100 \$39.95



Proto Board 100 is a low cost, big 10 IC capacity prototyping board. It features a 100 pin DIP socket, 100 pin DIP connector, and 100 pin DIP header. It is made of high quality materials and is easy to use.

### Proto Board 100 \$59.95



Proto Board 100 is a low cost, big 10 IC capacity prototyping board. It features a 100 pin DIP socket, 100 pin DIP connector, and 100 pin DIP header. It is made of high quality materials and is easy to use.

### DIGITAL WATCHES

#### Ladies Watch

- 6 Function
- Bracelet Styling
- 1 Year Guarantee
- Model 900
- Specify Gold or Chrome

**\$69.95**

#### EXELAR Mens Watch

- 5 Function
- Quartz Crystal
- Black Leather Band
- Manufacturer Guarantee
- Specify Gold or Chrome

**\$29.95**

### DIGITAL QUARTZ CAR CLOCK



Complete kit for mounting bracket of the injection molded case including the three conductor power cord and all components including the MMS314 clock chip. Features quartz accuracy of .01%, six digit, .35" high LED display. Works on any 12 volt system — motorcycles, boats, vans, motorhomes, autos, and trucks.

**Kit: \$29.95 Assembled: \$39.95**

### DIGITAL CLOCK KIT — 3 1/2 INCH DIGITS



This clock features big 3 1/2" high digits for viewing in offices, auditoriums, etc. Each digit is formed by 31 bright 0.2 LEDs. The clock operates from 117 VAC, has either 12 or 24 hr operation. The 6 digit version is 27" x 3 1/2" x 1 1/2", and the 4 digit is 18" x 3 1/2" x 1 1/2". Kits come complete with all components, case and transformer. Specify 12 or 24 Hr. When Ordering.


**4 DIGIT KIT \$49.95 4 DIGIT ASSEMBLED \$59.95**  
**6 DIGIT KIT \$69.95 6 DIGIT ASSEMBLED \$79.95**

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds.  
 California Residents — Add 8% Sales Tax — Data Sheets 25¢ each  
 Send a 24c Stamp (postage) for a FREE 1977 Catalog

## JAMES

1021 HOWARD AVE., SAN CARLOS, CA. 94070  
 PHONE ORDERS WELCOME — (415) 592-8097

## CB RADIO



### NEW IDI ICB-630

23-Channel Synthesized CB Transceiver

SIZE: 6 1/2" (W) x 2" (H) x 8 1/2" (D)  
 POWER INPUT: 5 Watts/12-Volt Max.  
 POWER OUTPUT: 4 Watts RMS

**\$99.95**

### MOBILE CB ANTENNA \$24.95

**BASE LOAD - FIBERGLASS WHIP KA-2401**  
 Mounts on Hood or Trunk Lid

### AMTEX 8 TRACK AM/FM STEREO \$69.95



FEATURES:

- 8 track stereo player
- AM/FM mpx radio
- Advanced IC construction
- Dial on door and slide-bar switch type
- Compact — only 1-25/32" (45mm) high, 4-13/16" (122mm) deep, 6-11/16" (170mm) wide and 5 position adjustable shaft distance.
- Complete in-dash type design.
- Easily adjustable antenna trimmer for best performance

### KRACO CAR SPEAKERS \$14.95

**Flush Mount 10 Oz. Mag./8 ohm Model SST-101F**

### 5 FUNCTION ELECTRONIC CALCULATOR \$8.95

**RAODFIN MODEL 8P**




FEATURES:

- 6 Digit Display
- 5 Functions consists of addition, subtraction, multiplication, division, percentage, with constant on all functions, with full floating decimal point.
- Power source is 1 piece 9V DC Battery 60GP. Jack for AC adapter.
- Black superfine grained finish plastic cabinet

### 5 FUNCTION ELECTRONIC CALCULATOR \$19.95

**WALLET-NOTEBOOK AND POCKET CHECKBOOK RAODFIN MODEL 1710**



FEATURES:

- 6 Digit Display
- 5 Functions consists of addition, subtraction, multiplication, division, percentage, with constant on all functions, with full floating decimal point.
- Power source is 6 AAA cells 9 V DC
- Wallet is 2 tone brown, cabinet is black plastic


### DIGITAL ALARM CLOCK \$17.95

**Novus**

This 4 digit Novus Alarm Clock is a very reliable and smartly styled unit. It provides such features as an alarm settable to any minute of the day, a 7 minutes snooze alarm, a power failure indicator, and even an A.M., P.M. indicator.

**NOT A KIT**

### JE700 CLOCK \$17.95




The JE700 is a low cost digital clock, but is a very high quality unit. The unit features a simulated walnut case with dimensions of 6 1/2" x 7 1/2" x 1 1/2". It utilizes a MAN72 high brightness readout, and the MMS314 clock chip.

### KIT - ALL COMPONENTS & CASE \$34.95

**WIRED & ASSEMBLED \$39.95**


### JE803 PROBE \$9.95 Per Kit



The Logic Probe is a unit which is for the most part indispensable in trouble shooting logic families TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a ICAPI 10 mA max. It uses a MAN3 readout to indicate any of the following states by these symbols: (H) - 1 (LOW) - 0 (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result.

**printed circuit board**

### T-L 5V 1A Supply \$9.95 Per Kit

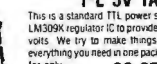

This is a standard TTL power supply using the well known LM309K regulator IC to provide a solid 1 AMP of current at 5 volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only

### ± 5 VOLT POWER SUPPLY \$39.95



Completely Assembled

- +5 Volts @ 6 Amps Regulated Output
- 5 Volts @ 6 Amps Regulated Input
- 6.3 Volts @ 5 Amps Unregulated Output
- Length 8 1/2" x Width 6 1/2" x Height 4"

**Limited Supply**



## BOOKS AND MAGAZINES

FREE book prophet Elijah coming before Christ. Wonderful bible evidence. Megiddo Mission, Dept. 64, 481 Thurston Rd., Rochester, N.Y. 14619.

POPULAR ELECTRONICS INDEXES For 1975 now available. Prepared in cooperation with the Editors of "P/E," this index contains hundreds of references to product tests, construction projects, circuit tips and theory and is an essential companion to your magazine collection. 1975 Edition, \$1.50 per copy. 1972, 1973 and 1974 editions \$1.50 each, or \$5.50 for the set of four (1972 thru 1975). Add \$.25 per order for postage and handling. INDEX, Box 2228, Falls Church, Va. 22042.

FREE CATALOG. Aviation and Space Books. Aero Publishers, 329PE West Aviation, Fallbrook, California 92028.

THE AUDIO AMATEUR—A quarterly publication for the serious audio constructor. Free prospectus. The Audio Amateur, Box 176Z, Peterborough, N.H. 03458.

CRIMEFIGHTERS! SHOPLIFTING! LOCKPICKING! DE-BUGGING! All 3 books for only \$5.00. Don-Q, 548-PE, Seattle, Washington 98111.

DC REGULATED SUPPLIES — \$2.00. OPERATIONAL AMPLIFIERS — \$2.00. Design, build, use, and troubleshoot through understanding. An engineer authors. Technical Publications Department, Jaquish Enterprises, Box 875, Troy, NY 12181.

BACK ISSUE MAGAZINES. 1890 to 1976. Free list. Send stamped envelope to Everybody's Bookshelf, Dept. PE, 317 West 6th, Los Angeles, CA 90014.

MICROCOMPUTER Hobbyists - Dictionary of Microcomputer Terminology. Hundreds of definitions. For beginners and experienced. \$2.00. Own Products, Box 16116, Irvine, CA 92713.

SOFTWARE BREAKTHROUGH — Basic Software Library: over 500 pages. Business, Recreational, Engineering, etc. programs — plus Basic reference. Christmas special — \$39.95 (\$2 handling) or send \$1 for information. Software, Box 2096, Ashland, VA 23005.

FREE! Consumer Service Division Catalog. Includes a wide variety of products associated with the special interests of readers of Ziff-Davis magazines — PSYCHOLOGY TODAY, POPULAR PHOTOGRAPHY, STEREO REVIEW, POPULAR ELECTRONICS, BOATING, FLYING, CAR & DRIVER, CYCLE, SKIING. Send for YOUR free catalog today. Consumer Service Div.: 595 Broadway, Dept. CL, N.Y., NY 10012.

### TMS 4030 JL 4096-BIT DYNAMIC RAM

These keyboards were manufactured for use on Texas Instrument's line of Silent 700 series data terminals. They are fully encoded with TTL large scale integrated circuits (T.I. TMS 5000 in 40 pin socket). Additional IC's provide a parallel 7 bit, without parity, code plus a strobe signal indicating "valid" data and six other independent outputs for those special keys which are not encoded. Internal circuitry provides for two key rollover and de-bounce. Output is on standard 10 pin double readout connector for data and power input. And 8 pin double readout connector for six special switch functions.

KB-6. Clare/Pender 720627-1 New - tested \$39.95  
T.I. Part number 959327-1 Used - tested \$29.95  
A 56 key ASCII encoded alphanumeric keyboard with six extra switch closures to ground marked HERE IS, PAPER ADV., BREAK, REPEAT, TAPE, TAPE.

### SLIDE SWITCH ASSORTMENT

standard and miniature  
40 for \$5.00

NE 3 NEEDLE  
100 — \$3.95  
100 — \$4.95

SWITCHCRAFT Micro 220  
100 — \$3.95  
100 — \$4.95

SPEEDY BEND  
100 — \$3.95  
100 — \$4.95

AC adapter \$3.00 ea.  
INPUT: 115 VAC, 60 Hz, 100 mA  
OUTPUT: 5 VDC, 100 mA  
10 for \$22.95

Kynar solid state  
plated wire wrap wire  
30 AWG Blue Or Yellow  
1000 ft spool \$3.95  
26 AWG Red Or Blue  
1000 ft spool \$12.50

LM301AH  
100 for \$39.95

PC Mount CLOCK POWER TRANSFORMER  
PRIMARY 117 VOLT 18 VA  
OUTPUT: 5 VDC, 100 mA  
10 for \$15.00 100 for \$49.95

### SN74S201 256 BIT RAM

with 3 state output.  
Plug in replacement for SN74 200 & SN74S200.  
\$3.95 ea. 10 for \$25.00

2N5449 50v 800 mA  
6/\$1.00 100 for 9.95

### HEAT SHRINKABLE TUBING Ass't. 2.95

25' 6" LENGTHS  
various sizes & colors.

### BISMUTH ALLOY.

Melts in boiling water  
4 oz. ingot \$3.95  
1 lb. \$9.95  
Fun to play with

### ACOUSTIC COUPLER

This coupler was manufactured by Novation, Inc. Tarzana, California for use in Texas Instrument's model 725 Electronic Data Terminal. It is compatible with 8ell 103 and 113 data sets or equivalent. The coupler operates asynchronously to a maximum speed of 450 baud in the full-or-half-duplex mode coupled to a standard telephone handset. Transmit freq. is 1270Hz for mark and 1070Hz for space. Receive frequency is 2225Hz for mark and 2025Hz for space. Unit required  $\pm 12$  VOLTS and + 5 VOLTS for operation. Complete with schematic & all pertinent information, fully reconditioned, calibrated, and guaranteed \$47.50

### DISCRETE LEDS

MVSD RED  
200" dia.  
RED  
125" dia.  
100 for \$13.95

### KEYBOARD ASSORTMENT

CALCULATOR & COMPUTER  
5 for \$9.95

### PRINTED CIRCUIT BOARD G-10

1 1/2" thick, unetched copper clad 1 oz. 2 sides  
Size 1 10 100  
3x6" .50 2.50 19.95  
4x12" 1.00 5.00 39.95  
8x8" 1.50 9.95 59.75  
Guaranteed. \$1.95 each. 10 for \$15.00

### PITTMAN 12 VDC MOTOR

runs on as low as 2 volts  
rated 12 volts 250' mA, 2.8 inch of torque at 5000 RPM.  
Size 1 1/2" DIA X 2" long  
with 0.118 inch shaft. New  
Guaranteed. \$1.95 each. 10 for \$15.00

### TMS 4030 JL 4096-BIT DYNAMIC RAM

Low Power 400 mW \$9.95  
with data and 22 Pin SOCKET  
removed from sockets 8 FOR \$64.95  
Tested and guaranteed

### ELECTRONIC PARTS

4400 MITCHELLDALE B-2  
HOUSTON, TEXAS 77092

CIRCLE NO. 3 ON FREE INFORMATION CARD

### "ELECTRONIC NOISE"

— \$4.95 book provides introduction to electronic noise theory; includes low noise preamplifier schematics! Details — free catalog — LHC, Box 453, Littleton, MA 01460.

### REAL ESTATE

BIG...FREE...CATALOG! 256 pages! Over 2,600 top values coast to coast! UNITED FARM AGENCY, 612-EP, West 47th, Kansas City, MO 64112.

### MAGNETS

MAGNETS. All types. Specials-20 disc. or 10 bar, or 2 stick or 8 assorted magnets. \$1.00. Magnets, Box 192-H Randallstown, Maryland 21133.

### PERSONALS

MAKE FRIENDS WORLDWIDE through international correspondence. Illustrated brochure free. Hermes-Verlag, Box 110660/2, D-1000 Berlin 11, Germany.

# EDLIE'S BARGAIN BONANZA

## ONLY HIGHEST QUALITY PRODUCTS



□ (HP017) COPPER CLAD BOARDS!  
Copper on one side, 1/16" thick. Excellent quality for either production or experimental work.  
6"x17 1/2" \$1.19 ea. 3/\$2.99

□ Copper on both sides. 1/16" thick. Size 12"x18".  
(HP018) \$1.99 ea. 3/\$4.99

□ (HP134) 8 ROTARY SWITCHES  
Some multiple gang. \$1.00

□ (HP128) 13 MINIATURE ELECTROLYTIC CAPACITORS \$1.00  
Axial & upright, popular values.

□ (HP144) TRANSISTOR REPAIR KIT \$1.19  
Various parts used to repair transistorized devices.

□ (HP336) TO-3 TRANSISTOR SOCKETS 12 for \$1.00

□ 9 V. BUZZER FOR ALARMS 99c ea. 6 for \$5

□ (HP164) 4 ROLLS OF WIRE \$1.00  
Approx 25 ft. per roll, 20-28ga.

□ (HP140) TAPE RECORDER SPARE PARTS KIT \$2.95  
Parts for repairing most tape recorders: capacitors, meter, pilot lamp, jacks, and MUCH MORE.

□ (HP167) 10 MINIATURE POTENTIOMETERS \$1.00

□ (HP182) 2 MISC. METERS \$1.00  
Miniature.

□ (HP156) 60 DISC CAPACITORS \$1.00  
Asst. from .0001 to .1, most 600v, 25U, NPO, N750, etc.

## SURPLUS TUBES

All guaranteed for 1 full year.

ANY 3 FOR \$1.49  
Acquired from U.S. Defense depots or removed from equipment (new and used). These are laboratory tested and guaranteed for one full year! Most are of such standard makes as RCA, GE, etc.

3A3	6AQ7	6CG7	6T8
3BN6	6AT6	6CM7	6W4
3DG4	6AU6	6DE4	8SN7
3KT6	6AV6	6DR7	10EW7
3Q4	6AX4	6DW4	12AE7
3S4	6AX5	6EB8	12AL5
48C5	6AY3	6EM7	12AU7
48N6	6BA6	6GF7	12AV6
48V8	6BG6	6GH8	12BH7
5B6	6BJ8	6K6	18FW6
6AF4	6BQ6	6K11	25L6
6AG5	6BZ6	6LB6	35EH5
6AL5	6CB6	6SN7	36AM3

□ FLAT WIRE RIBBON CABLE  
Useful for IC connection  
4 Conductor 25 ft \$1.00

□ (HP155) TUBE BONANZA! \$1.00  
20 asst. popular tubes, untested.

□ (HP142) 50 PRECISION RESISTORS \$1.00  
All 1%, 1/2w and 1w. low and high ohmages.

□ (HP150) POWER TRANSFORMER  
Primary 117 volts. Sec. 1-11.1 volts; Sec.2 17.7 volts; Sec.3 15.9 volts; Sec.4 27.7 volts. Each winding approx. 750 mils. Size 2 1/4" H x 2" D x 3 1/2" mounting centers. \$1.95

□ (HP175) 70 1/2w CARBON RESISTORS \$1.00  
Asst. values. Some 5%.

□ (HP154) 150 CUT LEAD RESISTORS \$1.00  
Carbon, all leads long enough for soldering.

□ (HP149) 20 POLYSTYRENE TOP GRADE CAPACITORS \$1.00

□ (HP132) 20 DUAL POTS \$1.00

24V. C.T. FILAMENT TRANSFORMER 1/2A. WITH 150V. TAP.  
□ (HP202) 99c ea 6 for \$4.99

**MONEY BACK GUARANTEE**  
Terms: Minimum order \$5.00. Include postage. Either full payment with order or 20% deposit, balance C.O.D.

**BONUS FREE CAPACITOR KIT**  
With Every \$5 Purchase

**WRITE FOR FREE 1976 VALUE PACKED CATALOG**  
Listing thousands of components, tubes, transistors, IC's, kits, test equipment.

## THIS MONTH'S SPECIALS!

□ 7400	18c	□ 7446	80c
□ 7401	18c	□ 7447	80c
□ 7402	22c	□ 7448	80c
□ 7403	23c	□ 7473	49c
□ 7404	23c	□ 7474	49c
□ 7405	23c	□ 7475	85c
□ 7406	23c	□ 747	53c
□ 7410	23c	□ 7490	79c
□ 7411	27c	□ 7492	79c
□ 7413	40c	□ 7493	69c
□ 7420	23c	□ 7495	79c
□ 7430	23c	□ 74121	57c
□ 7440	30c	□ 74122	57c
□ 7442	\$1.12	□ 74123	67c

**LINEARS**  
□ LM309K 5v 1a. reg. \$1.15  
□ 555 Timer 75c  
□ 556 Dual 555 \$1.00  
□ 556 Function gen. \$1.75  
□ 557 Tone decoder \$1.95  
□ 741 comp. op amp 39c  
□ 2513 Char. gen. \$5.95  
□ 8038 volt cont osc \$4.25

**CLOCK CHIPS WITH DATA**  
□ (MM5314) 6 dig clock \$4.95  
□ C77001 Alarm & Date \$5.95

**LED'S**  
□ (HP223) 10 Asst LEDS \$1.00  
□ (HP242) 5 Jumbo Green LEDS \$1.00  
□ (HP242) 5 Med Yellow LEDS \$1.00  
□ (HP001) 5 Jumbo Red LEDS \$1.00  
□ (HP011) 5 Med Red LEDS \$1.00  
□ (HP012) 5 Mini Red LEDS \$1.00  
□ (HP293) DL707 (equiv.) 7 seg red LED, .3" char., comm anode \$1.50  
□ (HP006) DL 704 (equiv.) same as DL707 except comm cath \$1.50  
□ (HP007) DL747 7 seg red LED, .6" char., comm anode \$2.25  
□ (HP013) MAN 5 (equiv.) 7 seg green LED, .27 char., comm. anode \$1.49

**IC BREADBOARDS & TERMINALS**  
Boards have .042 holes. Made of 1/16" polyester glass.  
□ (BB663) 3"x4" \$1.16  
□ (BB664) 3"x6" \$1.34  
□ (BB665) 4"x6" \$1.65  
□ (BB666) 4"x8" \$2.12

Push-in terminals  
□ (HP6601-20) pkg 20/90c  
□ (HP6601-100) pkg 100/\$2.98

Push-in flanged pins  
□ (BB6602-20) pkg 20/90c  
□ (BB6602-100) pkg 100/\$2.98

Push-in flea clips  
□ (BB6603-20) pkg 20/90c  
□ (BB6603-100) pkg 100/\$2.98

□ (B008) 14 pin DIP sockets 3 for \$1  
□ (HP1104) IC REMOVAL AND INSERTION TOOL \$4.95  
"Pul-n-seric" extracts and inserts ICS without damage.

**REED RELAYS**  
□ (HP203) SPST, 12V, 1000 ohms coil. Price 79c  
Prices are subject to change without notice.




# Olson®

**Parts and Accessories**  
SPECIALIZING IN ELECTRONICS FOR 35 YEARS

Your BANKAMERICA welcome here

master charge THE MITSUBISHI CARD

## Under-Dash LOCK MOUNT

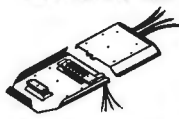

AU-344  
**229**  
Reg. \$6

Locks player in place. Slides in & out. 6 x 13/16 x 7". 6 or 12 VDC. Shipping weight 2 lbs.

## Standard Dial DESK PHONE



PH-117  
**799**  
Reg. \$13

Factory reconditioned. Comes with base, dial & coil. Less bell. Styles may vary. Wt. 8 lbs.

## 1000 Ohms/Volt Multimeter/Tester



TE-184  
**599**  
Reg. \$11

Color-coded scales, AC and DC Volts: 0-10-250-1000. DC Current: 0-100 mA. 2 1/2 x 3 1/2 x 1". Styles may vary. Wt. 3 lbs.

## Olson "X-Air" 2-Way Speaker System



SP-241  
**899**  
Reg. \$15

• Ideal for Home & RV's  
5" woofer. 55-18,000 Hz. 10 watts. 8 ohms. Walnut vinyl finish. 7 1/4 x 9 3/4 x 4 1/2". 4 lbs.

## TELEDYNE Deluxe Stereo Amplifier

AM-479

**\$49**



Reg. \$89

"Phase Power" 4-Channel Synthesizer. Large VU Meters. 20-36K Hz. Response. 18 1/4 x 4 3/4 x 1 1/4". 117 VAC. 15 lbs.

## Cassette Tape



Quality blank Cassette tapes from Olson. 1/2 lb.

TA-879, Pkg. of 3, 60 min. **1.99**

TA-929, Pkg. of 3, 90 min. **1.29**

## 8-Track Tape



Famous manufacturer's high quality, low-priced tapes. 1/2 lb.

TA-854, 40 Min. **1.49**

TA-855, 80 Min. **1.79**

## Auto Stereo 8-Track Tape Player



AU-428  
**1999**  
Reg. \$24

Player mounts easily under dash. Slide controls. 7 1/2 x 5 1/2 x 2 1/2". 12 VDC. neg. grd. Styles may vary. 4 lbs.

## Police Converter Kit

Model EC-2900. Use KB-380 AM radio & tune in the 152-174 MHz band for police, etc. 2 lbs.

**799**  
Reg. \$13

## Pencil-Tip Soldering Iron

TL-448 **199**  
Reg. \$3.29



## Rembrant Personal Security

XM-482


**\$3**



Reg. \$4

• Compact Size  
Pushbutton for piercing, police-like siren. Solid state. w/case. 1 lb. XM-483, Heavy Duty, Reg. \$9...\$5 XM-484, Professional, Reg. \$11 \$8

## CB Mobile "Power Mike"

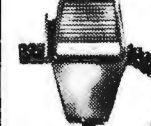

**1299**  
Reg. \$19

MK-130  
Features push-to-talk switch. Max sen. -42 dB. Case, mtg. clip & batt. incl. Styles may vary. Wt. 2 lbs.

### PARTS & COMPONENTS

8 Track Tape Deck Chassis  
4 Digit Mechanical Counter  
5 Digit Mechanical Counter  
2 watt Solid-State Phono Amp.  
5 Digit 117 volt AC Counter  
12 Hour Timer, 117 V. AC  
6 Digit 117 V. AC Counter  
L.E.D. Pkg. of 5 Small Red 2V. 5 MA  
L.E.D. Pkg. of 5 Large Green 2 V. 5 MA  
L.E.D. Pkg. of 5 Small Green 2 V. 5 MA  
L.E.D. Pkg. of 5 Large Yellow 2V. 5 MA  
L.E.D. Pkg. of 5 Small Yellow 2 V. 5 MA  
L.E.D. Pkg. of 5 Large Orange 2 V. 5 MA  
L.E.D. Pkg. of 5 Large Clear 2 V. 5 MA  
7 Seg. L.E.D. Readout. 3" Com. K Reel  
LM-309K 5 V. IC Regulator T0-3  
3 Amp. 50 PIV Diodes Pkg. of 2  
3 Amp. 400 PIV Diodes Pkg. of 2  
1 Amp. 200 PIV 50 Piece Kit  
P Channel FET 2N5460  
18 Amp. 200 PIV Diode IN3493R  
Medium Power Transistor 25B474  
Cadmium Photo Cells. 500 Ohm. Pkg. 2  
N Channel FET 2N3819  
40 Watt NPN Transistor, Pkg. of 4  
709 IC Hi-Gain OP-Amp  
PC Board Kit — Make Your Own  
PC Wire Kit, 150 Ft.  
Magnet Wire, 28 Ga. 375 Ft.  
4PDT Plug-In Relay, 117 V. AC Coil  
16 Step Relay, 110 Ohm Coil, 450 Ohm Reset  
SPDT 5A. Plug-In Relay 117 V. AC  
DPST Power Relay 25A. Cont. 117 V. Coil  
Heavy Duty Solenoid, 117 V. AC  
Miniature Solenoid, 1/2" Trav. 117 V. AC  
Reed Switch with Mag. Pkg. 10  
SPDT Key Switch 3A. Contacts

REG. SALE  
RA-383 17.00 11.99  
XM-367 1.49 .59  
XM-543 3.00 1.29  
AM-529 16.00 11.00  
XM-533 2.00 .99  
SW-777 4.00 1.79  
XM-481 2.29 1.39  
PL-234 1.19 .60  
PL-235 1.19 .60  
PL-236 1.19 .60  
PL-237 1.19 .60  
PL-238 1.19 .60  
PL-249 1.19 .60  
PL-274 1.19 .60  
XM-414 2.00 1.29  
TR-511 1.60 1.19  
OI-055 .70 .59  
OI-056 1.20 .79  
DI-051 1.69 .69  
TR-430 1.19 .59  
DI-054 1.49 .59  
TR-147 3.79 1.29  
TR-512 .90 .59  
TR-429 1.00 .49  
TR-440 1.29 .59  
RE-131 1.49 .69  
XM-393 6.59 3.99  
WW-575 1.89 .99  
WR-281 .89 .69  
SW-543 2.69 1.79  
SW-842 5.79 3.79  
SW-417 1.19 .79  
SW-646 2.69 1.69  
SW-839 1.79 .79  
SW-840 2.00 .89  
SW-632 2.69 .79  
SW-808 1.20 .79

### PARTS & COMPONENTS

1/4 RPM Timing Motor, 117 V. AC  
1 RPM Timing Motor, 117 V. AC  
8 RPM Reversible Motor, 117 V. AC  
Tubular Capacitor Kit, 100 Pcs.  
Ceramic Capacitor Kit, 100 Pcs.  
100 Ceramic Capacitors, values clearly marked  
50 Asst. Electrolytic Capacitors, Axial/Radial  
100 Asst. Carbon Resistors, 1/4-1/2 Watt Sizes  
5 Asst. SCR's, 15 V. and Up, 100 MA to 1.6 AMP  
500 MW Zener Diodes, 4.3-6.3-9.1-12 & 15 Volts  
3 Unijunction Transistors, 40 V. 375 MW. 4 ON/S  
L.E.D. Pkg. of 5 Red, 2 Volt - 5 MA  
Ultra-Mini L.E.D. Pkg. of 5 Red, 2 V. 5 MA  
TI Calculator Key Board, 20 Keys  
3 1/2 Digit Liquid Crystal Display  
Oarlinton Amp. Transistor Kit, 6 Transistors  
Photo Transistor, 5 Pieces - Epoxy Type  
6 Amp. Full Wave Bridge Rectifier 50 PIV  
6 Amp. Full Wave Bridge Rectifier 400 PIV  
PNP Transistor Assortment Pkg. of 10  
NPN Transistor Assortment Pkg. of 10  
7-Segment L.E.D. Display .3 In. Green  
7-Segment L.E.D. Display .3 In. Red  
7-Segment L.E.D. Display .3 In. Yellow  
Micro Type Switch Kit, 7 Assorted  
Knob Kit, 25 Pcs. Assorted  
Hobby Motor Kit, 3-6 V. DC, Pkg. 5

REG. SALE  
MO-277 .49 .30  
MO-289 .49 .30  
MO-393 2.50 .99  
CC-229 2.00 1.29  
CC-211 1.49 1.19  
CC-210 1.29 .80  
CD-407 5.00 2.00  
RR-077 1.79 1.00  
TR-298 1.79 1.00  
DI-052 1.00 .50  
TR-441 1.29 .50  
PL-233 1.19 .60  
PL-289 1.29 .70  
XM-523 5.00 1.60  
XM-371 10.00 3.00  
TR-507 2.00 1.50  
TR-502 1.00 .60  
DI-057 1.20 .80  
DI-058 1.90 1.00  
TR-445 1.00 .60  
TR-446 1.00 .60  
XM-341 2.69 1.00  
XM-370 2.00 1.00  
XM-342 2.49 1.00  
SW-430 1.89 1.49  
KN-030 1.00 .69  
MO-333 .59 .49

### TOOLS — SPECIAL AND PRACTICAL

Wire Wrap Tool, 30 Ga Wire on .025 Post  
IC Insertion/Extraction Tool  
IC Plug-In Test Adapter  
12 Volt DC Soldering Iron, Pencil Tip  
Tuner/Contact Cleaner, 6 Oz. Can  
Dymo Label Maker. Uses 1/4 In. Tape  
Double Face Foam Tape 1/4 x 52 In.

REG. SALE  
TL-845 2.60 2.00  
TL-846 1.25 1.00  
TE-396 2.60 2.00  
TL-793 4.00 3.00  
TL-459 1.49 .80  
TL-752 1.89 .90  
TA-903 1.00 .80

### RECORDING TAPE AND ACCESSORIES

8 Track, 40 Min. Blank Tape  
10 In. Reel 3600 Ft. 1 Mil Mylar Tape  
8 Track Head Demagnetizer, 12 Volt DC

REG. SALE  
TA-907 .69 .50  
TA-608 2.99 2.00  
HF-160 3.00 1.30

OLSON ELECTRONICS, 250 S. FORGE ST.  
DEPT. IR, AKRON, OHIO 44327

FREE CATALOG

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_  
☐ SEND OLSON CATALOG ☐ FREE PA CATALOG  
☐ SHIP THE FOLLOWING

HOW MANY	STOCK NUMBER	DESCRIPTION	PRICE EACH	TOTAL

ENCLOSE POSTAGE AND SALES TAX

**INSTALLATION**  
AVAILABLE FOR  
CB-AUTO STEREO  
SECURITY ALL OLSON  
STORES COAST-TO-COAST

**FREE PA CATALOG**

**REPAIR SERVICE**  
AVAILABLE IN ALL OLSON STORES.



## The BIGGEST "BRIGHTEST" BESTEST 6 Digit LED Alarm Clock & Elapsed Timer Kit

available at this value anywhere

\$17.95 Complete

- 6-Fairchild .50" LED Displays
- 0-60 Min. Elapsed Timer
- 12 Hr. 60 cycle oper.
- AC or DC oper.
- 5375AB Nat. Clock Chip
- "Freeze" Feature on any Mode
- 24 Hr. Alarm w/snooze
- Field Tested over 6 months

The kit contains P.C. Boards, Xformer, and EVERY Part Required for the Clock and all options except Cabinet or Crystal Time Base for D.C. Oper. If desired, see below.

### AC/DC - ALARM Clock Kit - 12/24 Hr.

\$7.50 quantities of 1-5 \$6.50 quantities of 6 & up

- Your choice of Display Colors - Red, Green, Blue, Amber
- Displays Hrs. & Min. - Switch to Min. & Secs. on Command.
- AM/PM Indication
- Field Tested for 6 months

The kit will include a 5316 National Clock Chip, 4 Fluorescent Display tubes, all electronic components, switches, controls & complete instructions, specs, etc. for clock and all optional Features. Other parts required or if desired are as follows:

- PC Board, Drilled & Silk Screened for Clock & all options ..... \$3.00
- Xformer (for AC oper.) — \$1.00 App. (SCR output) timer kit — \$2.00
- Speaker Alarm Kit — \$2.00 Count Down (turn-off) timer kit — \$2.00

## HOBB-Y-TRONIX, INC.

Box 511, Edison, N.J. 08817

Orders must include Check - No COD's. Add \$1.00 handling for orders under \$25.00. N.J. residents - add 5% tax.

## 6 Digit LED Stop-Watch Kit

Split Time

\$26.95

Taylor Time

### FEATURES:

- Simple construction needing only the parts listed below
- Small enough for hand held case
- Needs only 3-AA cell batteries

### KIT INCLUDES:

- Latest Technology Intersil Mos Chip # 7205
- 3.2768 MHz Crystal
- 2 mini slide & 3 MOM. PB Switches
- 3 pairs (6 digits) Double Digit LED Displays
- Variable Trimmer Cap.

P.C. BOARD for above ..... \$3.95

## Clock Kit Accessories

60 Hz Crystal Time Base Kit ..... \$4.95 complete  
Includes P.C. Board, Crystal, 17 Stage Divider IC and all camps.

Wooden Case - Walnut gr. incl. Filter ..... \$4.00 each  
Dimension - 6 5/16" W x 2 9/16" H x 3 7/16" D (3/4" Material)

Plexiglass Case (Ch. - Bl., White, Blue, & Smoke) ..... \$3.00 each  
Dimensions - 5 13/16" W x 2 1/4" H x 5 3/8" D (3/4" Material)

Individual Filters - Red, Smoke, Blue, Amber and Green ..... \$.60 each

## Blinky/Flasher/Timing Kit

\$2.50 each 5 for \$10.00

### Kit includes:

P.C. Board, 555 Timer, all components and a connector for a 9V Battery

## ELECTRONIC COMPONENTS — A small SAMPLING

21102-1 Low Power 500NS 1k Ram	\$1.95 ea.
LM309K - 5 Volt Regulator - Raytheon	79¢
LM340T Series Regs. - 5, 6, 12, 15 & 24 V (pos.)	99¢
LM741 Op. Amp. 14 Pin Dip Pkg.	4 for 99¢
2N3055 NPN Transistor TO-3 Pkg.	59¢
2N4904 PNP (complement to 2N3055)	69¢
25 Amp - 200 Volt Full Wave Bridge	\$1.49
10 Pk - 220 Power Tab Xistors, NPN & PNP Asst.	\$1.49
15 Pk - LED's Assorted Sizes and Colors	\$1.49
Bi-Polar LED - Red/Green	\$1.00
14, 16, & 18 Pin IC Sockets	10 for \$1.59

CIRCLE NO. 40 ON FREE INFORMATION CARD

INTEL 8080 CPU	\$24.50
2518-HEX 32 BIT SR	\$6.00
2102-1 1024 BIT RAM	\$1.80
5280-4K DYNAMIC RAM	\$12.50
5202A UV PROM	\$12.50
MM5203 UV PROM	\$12.50
1702A UV PROM	\$12.50
5204-4K PROM	\$24.95
MINIATURE MULTI-TURN TRIM POTS	
100, 500, 2K, 5K, 10K, 100K, 200K	\$1.75 each
MULTI-TURN TRIM POTS Similar to Bourns	\$3.00
3010 style 3/16" x 5/8" x 1-1/4": 50, 100, 1K, 10K, 50K ohms	\$1.50 ea.
LIGHT ACTIVATED SCR's	3/\$4.00
TO-18, 200V 1A.	\$1.75

### TRANSISTOR SPECIALS

2N3585 NPN Si TO-66	\$ .95
2N3772 NPN Si TO-3	\$1.60
2N4908 PNP Si TO-3	\$1.00
2N6055 NPN Si TO-3 Darlington	\$1.30
2N5088 PNP Si TO-92	4/\$1.00
2N4899 NPN Si TO-66	\$ .60
2N4004 PNP GE TO-5	5/\$1.00
2N3919 NPN Si TO-3 RF	\$1.50
MP54 13 NPN Si TO-92	3/\$1.00
2N3767 NPN Si TO-66	\$ .70
2N2222 NPN Si TO-18	5/\$1.00
2N3055 NPN Si TO-3	\$ .80
2N3904 NPN Si TO-92	5/\$1.00
2N3906 PNP Si TO-92	5/\$1.00
2N5295 NPN Si TO-220	\$ .50
2N6109 NPN Si TO-220	\$ .55
2N3638 PNP Si TO-5	5/\$1.00
2N6517 NPN TO-92 Si	3/\$1.00

### CMOS (DIODE CLAMPED)

74C02 - .25	4016 - .50	4035 - 1.75
74C10 - .25	4017 - 1.30	4042 - 1.60
4001 - .25	4018 - 1.40	4047 - 2.60
4002 - .25	4019 - .60	4049 - .70
4005 - 1.60	4022 - 1.20	4050 - .70
4007 - .25	4023 - .25	4055 - 1.20
4009 - .50	4024 - 1.25	4066 - 1.20
4010 - .60	4025 - .25	4071 - .30
4011 - .25	4027 - .65	4077 - .30
4012 - .25	4028 - 1.50	4081 - .35
4013 - .50	4029 - 1.75	4076 - 1.20
4015 - 1.40	4030 - .90	

### LED READOUTS

FND 500-5" C.C.	\$1.95
HP 7740-3" C.C.	\$1.40
MAN-7-3" C.A.	\$1.25
NS 33-3 dig. array	\$1.35
DL 747	\$2.75

Send 25¢ for our catalog featuring Transistors and Rectifiers  
145 Hampshire St., Cambridge, Mass.

Terms: FOB Cambridge, Mass.  
Send Check or Money Order.  
Include Postage. Minimum Order \$5.00, COD's \$20.00

### PRINTED CIRCUIT BOARD

4-1/2" x 6-1/2" SINGLE SIDED EPOXY BOARD 1/16" thick, unetched  
\$3.50 ea. 5/\$2.20  
VECTOR BOARD 1" SPACING  
4.5" x 6" SHEET ..... \$1.25

### 4 WATT IR LASER DIODE \$7.95

2N 3820 P FET	\$ .45
2N 5457 N FET	\$ .45
2N 4891 UJT	\$ .45
TIS 43 UJT	\$ .35
ER 900 TRIGGER DIODES	4/\$1.00
2N 6028 PROG. UJT	\$ .85

VERIPAX PC BOARD  
This board is a 1/16" single sided paper epoxy board, 4 1/2" x 6 1/2" DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16, or LSI DIP IC's with bussing for power supply connector. \$4.00

MV 5691 YELLOW-GREEN	
BIPOLAR LED	\$1.25
MT-2 PHOTO TRANS	\$ .60
RED, YELLOW, GREEN OR	
AMBER LARGE LED's	ea. \$ .20
14 PIN DIP SOCKETS	\$ .25
16 PIN DIP SOCKETS	\$ .28
MOLEX PINS	100/\$1.00
8 PIN MINI DIP SOCKETS	\$ .25
10 WATT ZENERS 3.9, 4.7, 5.6, 8.2, 12, 15, 18, 22, 100, 150 or 200V	ea. \$ .60
1 WATT ZENERS 4.7, 5.6, 10, 12, 15, 18 OR 22V	ea. \$ .25

### Silicon Power Rectifiers

PRV	1A	3A	12A	50A	125A
100	.06	.14	.30	.80	3.70
200	.07	.20	.35	1.15	4.25
400	.09	.25	.50	1.40	6.50
600	11	.30	.70	1.80	8.50
800	15	.35	.90	2.30	10.50
1000	20	.45	1.10	2.75	12.50

### SILICON SOLAR CELLS

2 1/4" diameter  
5V at 500 ma. .... \$5.00 ea., 6/\$27.50

### REGULATED MODULAR POWER SUPPLIES

+15 VDC AT 100ma	\$27.95
115VAC INPUT	
5VDC AT 1A, 115VAC INPUT	\$24.95
12 VDC AT 5 AMP	\$24.95
IN 4148 (IN914)	15/\$1.00

### TANTALUM CAPACITORS

22UF 35V \$1.00	6.8UF 35V \$1.00
47UF 35V \$1.00	22UF 35V \$ .40
68UF 35V \$1.00	33UF 35V \$ .40
1UF 35V \$1.00	30UF 6V \$1.00
3.3UF 35V \$1.00	100UF 35V \$ .50
4.7UF 35V \$1.00	150UF 15V \$ .40
M7001 ALARM CLOCK CHIP	\$6.00

### NATIONAL MOS DEVICES

MM1402 - 1.75	MM5057 - 2.25
MM1403 - 1.75	MM5058 - 2.75
MM1404 - 1.75	MM5060 - 2.75
MM5013 - 2.50	MM5061 - 2.50
MM5016 - 2.50	MM5555 - 4.75
MM5017 - 2.70	MM5556 - 4.75
MM5055 - 2.25	MM5210 - 1.95
MM5056 - 2.25	

### TTL IC SERIES

74L00 - .25	7441 - .85	74126 - .60
7400 - .18	7442 - .55	74150 - 1.00
7401 - .18	7445 - .75	74151 - .80
7402 - .18	7446 - .80	74153 - .79
7403 - .22	7447 - .69	74154 - 1.05
7404 - .22	7448 - .77	74155 - 1.00
7405 - .22	7472 - .40	74157 - .75
7406 - .35	7473 - .40	74161 - 1.00
7407 - .33	7474 - .40	74164 - 1.05
7408 - .25	7475 - .50	74165 - 1.05
7409 - .25	7476 - .40	74173 - .95
7410 - .18	7480 - .48	74174 - 1.20
7411 - .25	7483 - .80	74175 - .95
7412 - .40	7485 - .88	74177 - 1.00
7413 - .46	7486 - .45	74180 - 1.00
7414 - 1.00	7489 - 2.00	74181 - 2.40
7415 - .33	7490 - .48	74190 - 1.15
7416 - .33	7491 - .75	74191 - 1.10
7420 - .18	7492 - .49	74192 - .80
7425 - .30	7493 - .49	74193 - .90
7426 - .35	7494 - .80	74194 - 1.25
7427 - .28	7495 - .80	74195 - .75
7430 - .18	7496 - .73	74196 - 1.10
7432 - .30	74107 - .40	75324 - 1.75
7437 - .30	74121 - .39	75491 - .60
7438 - .30	74123 - .75	75492 - .60
7440 - .18	74125 - .60	

### MINIATURE DIP SWITCHES

CTS-206-4 Four SPST switches in one minidip package.	\$1.50
CTS-206-8 Eight SPST switches in a 16 pin DIP package.	\$2.55

AY-51013-A30K ser./par., par./ser., universal UART. .... \$6.95

### ALCO MINIATURE TOGGLE SWITCHES

ALCO 106 SPDT	\$1.20
MTA 206 DPDT	\$1.70

### Full Wave Bridges

PRV	2A	6A	25A
200	.95	1.25	2.00
400	1.15	1.50	3.00
600	1.35	1.75	4.00

### SANKEN AUDIO POWER AMPS

Si 1010 G 10 WATTS	\$ 6.90
Si 1020 G 20 WATTS	\$13.95
Si 1050 G 50 WATTS	\$24.95

CCD 110 LINEAR 256 XI BIT SELF SCANNING CHARGED COUPLED DEVICE ..... \$99.00

CCD 201 - 100 x 100 CHARGE COUPLED DEVICE ..... \$135.00

### LINEAR CIRCUITS

LM 309K 5V 1A REGULATOR	\$1.15
7529 - 40 + 40V REGULATOR	\$ .50
301/748 Hi Per. Op. Amp.	\$ .31
320T 5, 12, 15, OR 24V	
NEGATIVE REG.	\$1.50
709C - Op. Amp.	\$ .31
741A or 741C OP AMP.	\$ .31
710 COMPARATOR	\$ .35
CA 3047 Hi Per. Op. Amp.	\$ .95
340T 5, 6, 8, 12, 15, 18, 24V POS	
REG. TO 200	\$1.50
101 OPER. AMP. HI PERFORM.	\$ .75
LM 308 OPER. Amp., Low Power	\$ .95
747 - DUAL 741	\$ .85
556 - DUAL TIMER	\$1.00
537 - PRECISION OP. AMP.	\$1.70
LM 3900 - QUAD OP. AMP.	\$ .49
LM 324 - QUAD 741	\$1.50
560 - PHASE LOCK LOOP	\$2.00
561 - PHASE LOCK LOOP	\$2.00
565 - PHASE LOCK LOOP	\$1.25
566 FUNCTION GEN.	\$1.65
567 - TONE DECODER	\$1.50
LM 1310N FM STEREO DEMOD.	\$2.75
8038 IC VOLTAGE CONT. OSC.	\$3.90
LM 370 - AGC SQUELCH AMP.	\$1.15
555 - 2us - 2 HR. TIMER	\$ .45
553 QUAD TIMER	\$2.50
FCD 810 OPTO-ISOLATOR	\$ .80
1458 DUAL OP. AMP.	\$ .50
LM 380 - 2W AUDIO AMP.	\$ .95
LM 377 - 2W Stereo Audio Amp.	\$2.50
LM 381 - STEREO PREAMP.	\$1.50
LM 382 - DUAL AUDIO PREAMP	\$1.50
LM 311 - HI PER. COMPARATOR	\$ .90
LM 319 - Dual Hi Speed Comp.	\$1.25
LM 339 - QUAD COMPARATOR	\$1.50

### TRIACS SCR'S

PRV	1A	10A	25A	1.5A	6A	35A
100	.40	.70	1.30	.40	.50	1.20
200	.70	1.10	1.75	.60	.70	1.60
400	1.10	1.60	2.60	1.00	1.20	2.40
600	1.70	2.30	3.60			

## SOLID STATE SALES

P.O. BOX 74A  
SOMERVILLE, MASS. 02143 TEL. (617) 547-4005

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

# PLANNING TO MOVE?

Let us know 8 weeks in advance so that you won't miss a single issue of **POPULAR ELECTRONICS**.

Attach old label where indicated and print new address in space provided. Also include your mailing label whenever you write concerning your subscription. It helps us serve you promptly.

Write to: P.O. Box 2772, Boulder, CO 80323, giving the following information:

- ☐ Change address only ☐ Extend my subscription
- ENTER NEW SUBSCRIPTION**
- ☐ 1 year \$9.98 ☐ Payment enclosed  
Allow 30-60 days for delivery. (1 extra BONUS issue)
- ☐ Bill me later

NEW ADDRESS HERE 0190

Name \_\_\_\_\_ please print

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Additional postage per year For Canada add \$3 For countries outside U.S. and Canada, add \$5—cash in U.S. currency only

AFFIX OLD LABEL

If you have no label handy, print OLD address here.

Name \_\_\_\_\_ please print

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_


**2102L1**  
A COOL  
MEMORY  
**\$1.95**  
450 ns guaranteed,  
full temp range.

**GODBOUT**  
BILL GODBOUT ELECTRONICS  
BOX 2355, OAKLAND AIRPORT, CA 94614

TERMS: Add 50¢ handling to orders under \$10. Cal res add tax. No COD; to place BankAmericard® or Mastercharge® orders, call (415) 562-0636, 24 hours.

**LIMITED QTY.  
SPECIALS**

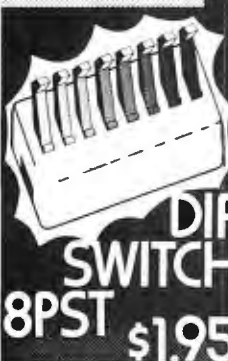9601 prec. one shot...3/\$1.00  
74B40 fast 7440...7/\$1.00  
MM5262 2K dynamic RAM...\$1.25  
FPQ3725 Quad PNP transistor array, type 2N3725, in DIP.  
FOUR quad arrays.....\$1.00



**DIP SWITCH**  
**8PST \$1.95**

**Musicians! Build a Phase Shifter \$39.95**

One of our most popular music kits: this premium phaser offers extremely low distortion and noise. With contour, speed, and level controls. Includes PC board, sockets for ICs, regulator for stable operation, pots, all components, and data. Less connectors, case, two 9V batteries. Postpaid in USA. See our flyer for other kits.

**Resistor Asst. No 1 is back: still \$3.95**

500 or more quarter-watt resistors, with a good mix of values. ALSO AVAILABLE: Resistor Asst. #2: over 300 half-watt resistors, leads cut & formed for PC insertion. \$1.95

**SEND FOR FREE FLYER!**

CIRCLE NO 35 ON FREE INFORMATION CARD

**TO220  
HEAT  
SINKS  
4/\$1**



**For  
faster  
service**

**USE  
ZIP  
CODE**

**on  
all  
mail**

## CB SPECIALS—R.F. DRIVERS—R.F. POWER OUTPUTS—FETS

2SC481	1.85	2SC767	15.75	2SC866	5.85	2SC1449	1.60	40081	1.50
2SC482	1.75	2SC773	.85	2SC013	1.50	2SC475	1.50	40082	3.00
2SC495	1.10	2SC774	1.75	2SC1014	1.50	2SC1678	5.50	2SC608	4.85
2SC502	3.75	2SC775	2.75	2SC1017	1.50	2SC1679	4.75	SK3046	2.15
2SC517	4.75	2SC776	3.00	2SC1018	1.50	2SC1728	2.15	SK3047	2.15
2SC614	3.80	2SC777	4.75	2SC1173	1.25	2SC1760	2.15	SJ2095	3.50
2SC615	3.90	2SC778	3.25	2SC1226A	1.25	2SC1816	5.50	SK3048	3.25
2SC616	4.15	2SC797	2.50	2SC1237	4.50	2SC1908	.70	SK3054	1.25
2SC617	4.25	2SC798	3.10	2SC1237	3.50	2SC1957	1.50		
2SC699	4.75	2SC781	3.00	2SC1243	1.50	2SF8	3.00	2SK19	1.75
2SC710	.70	2SC789	1.00	2SC1306	4.75	HEP-S 3001	3.25	2SK30	1.00
2SC711	.70	2SC796	3.15	2SC1306-1	4.90	2SD235	1.00	2SK33	1.20
2SC735	.70	2SC799	4.25	2SC1307	5.75	MRFB004	3.00		
2SC756	3.00	2SC802	3.75	2SC1307-1	6.00	4004	3.00	3SK40	2.75
2SC765	9.50	2SC803	4.00	2SC1377	5.50	4005	3.00	3SK45	2.75
2SC766	10.15	2SC839	.85	2SC1449	1.30	40080	1.25	3SK49	2.75

## JAPANESE TRANSISTORS

2SA512	.60	2SB187	.60	2SC458	.70	2SC815	.75	2SC1569	1.25
2SA316	.75	2SB235	1.75	2SC460	.70	2SC828	.75	2SC1756	1.25
2SA473	.75	2SB303	.65	2SC478	.80	2SC829	.75		
2SA483	1.95	2SB324	1.00	2SC491	2.50	2SC830	1.60	2SD30	.95
2SA489	.80	2SB337	2.10	2SC497	1.60	2SC839	.85	2SD45	2.00
2SA490	.70	2SB367	1.60	2SC515	.80	2SC945	.65	2SD45	.75
2SA505	.70	2SB370	.65	2SC535	.75	2SC1010	.80	2SD68	.90
2SA564	.50	2SB405	.85	2SC536	.65	2SC1012	.80	2SD72	1.00
2SA628	.65	2SB407	1.65	2SC537	.70	2SC1051	2.50	2SD88	1.50
2SA643	.85	2SB415	.85	2SC563	1.50	2SC1061	1.65	2SD151	2.25
2SA647	2.75	2SB461	1.25	2SC605	2.00	2SC1079	3.75	2SD170	2.00
2SA673	.85	2SB463	1.65	2SC620	.80	2SC1096	1.25	2SD180	2.75
2SA679	3.75	2SB471	1.75	2SC627	1.75	2SC1098	1.15	2SD201	1.95
2SA682	.85	2SB474	1.50	2SC642	3.50	2SC1115	2.75	2SD218	4.75
2SA699	1.30	2SB476	1.25	2SC643	3.75	2SC1168	.70	2SD300	2.50
2SA699A	1.75	2SB481	2.10	2SC644	.70	2SC1170	4.00	2SD313	1.10
2SA705	.55	2SB492	1.25	2SC681	2.50	2SC1172B	4.25	2SD315	.75
2SA815	.85	2SB495	.95	2SC684	2.10	2SC1209	.55	2SD318	.95
2SA816	.85	2SB507	.90	2SC687	2.50	2SC1213	.75	2SD341	.95
		2SB511	.70	2SC696	2.35	2SC1226	1.20	2SD350	3.25
2SB22	.65			2SC712	.70	2SC1243	.85	2SD352	.80
2SB54	.70	2SC206	1.00	2SC713	.70	2SC1293	.85	2SD380	.90
2SB56	.70	2SC240	1.10	2SC732	.70	2SC1308	4.75	2SD389	.75
2SB77	.70	2SC261	.65	2SC733	.70	2SC1347	.80	2SD390	.75
2SB128	2.25	2SC291	.65	2SC739	.70	2SC1383	.75	2SD437	5.50
2SB135	.95	2SC320	2.00	2SC715	1.75	2SC1409	1.25		
2SB152	4.50	2SC352	.75	2SC762	1.90	2SC1410	1.25	C106B1	.50
2SB173	.55	2SC353	.75	2SC783	1.00	2SC1447	1.25		
2SB175	.55	2SC371	.70	2SC784	.70	2SC1448	1.25	MPS-U31	4.00
2SB178	1.00	2SC372	.70	2SC785	1.00	2SC1507	1.25	MPS-80001	.25
2SB186	.60	2SC394	.70	2SC793	2.50	2SC1509	1.25		

## POWER-TRANSISTORS HIGH-VOLT. TV. TYPE

BU204	1300V	3.90	BU207	1300V	5.40	2SC1172B	1100V	4.25
BU205	1500V	4.70	BU208	1500V	6.25	2SC308	1100V	4.95
BU206	1700V	5.90	2SC1170	1100V	4.00	2SC1325	1100V	4.95

## OEM SPECIALS

1N270	.10	2N960	.55	2N2219A	.30	2N2913	.75	2N3740	1.00	2N4401	.20
1N914	.10	2N962	.40	2N2221	.25	2N2914	1.20	2N3771	1.75	2N4402	.20
		2N967	.50	2N2221A	.30	2N2916A	3.65	2N3772	1.90	2N4403	.20
2N173	1.75	2N1136	1.35	2N2222	.25	2N3019	.50	2N3773	3.00	2N4409	.20
2N178	.90	2N1142	2.25	2N2222A	.30	2N3053	.30	2N3819	.30	2N4410	.25
2N327A	1.15	2N1302	.25	2N2270	.40	2N3054	.70	2N3823	.70	2N4416	.75
2N334	1.20	2N1305	.30	2N2322	1.00	2N3055	.75	2N3856	.20	2N4441	.85
2N336	.90	2N1377	.75	2N2323	1.00	2N3227	1.00	2N3866	.85	2N4442	.90
2N338A	1.05	2N1420	.20	2N2324	1.35	2N3247	3.40	2N3903	.20	2N4443	1.20
2N398B	.90	2N1483	.95	2N2325	2.00	2N3250	.50	2N3904	.20	2N4852	.55
2N404	.30	2N1540	.90	2N2326	2.85	2N3375	6.50	2N3905	.20	2N5061	.30
2N443	1.75	2N1543	2.70	2N2327	3.80	2N3393	.20	2N3906	.25	2N5064	.50
2N456	1.10	2N1544	.80	2N2328	4.20	2N3394	.17	2N3925	3.75	2N5130	.20
2N501A	3.00	2N1549	1.25	2N2329	4.75	2N3414	.17	2N3954	3.50	2N5133	.15
2N508A	.45	2N1551	2.50	2N2368	.25	2N3415	.18	2N3954A	3.75	2N5138	.15
2N555	.45	2N1552	3.25	2N2369	.25	2N3416	.19	2N3955	2.25	2N5198	3.75
2N652A	.85	2N1554	1.25	2N2484	.32	2N3417	.20	2N3957	1.25	2N5294	.50
2N677C	6.00	2N557	.15	2N2712	.18	2N3442	1.85	2N3958	1.20	2N5296	.50
2N706	.25	2N1560	2.80	2N2894	.40	2N3553	1.50	2N4037	.60	2N5306	.20
2N706B	.40	2N1605	.35	2N2903	3.30	2N3563	.20	2N4093	.85	2N5354	.20
2N711	.50	2N1613	.30	2N2904	.25	2N3565	.20	2N4124	.20	2N5369	.20
2N711B	.60	2N1711	.30	2N2904A	.30	2N3638	.20	2N4126	.20	2N5400	.40
2N718	.25	2N1907	4.10	2N2905	.25	2N3642	.20	2N4141	.20	2N5401	.50
2N718A	.30	2N2060	1.85	2N2905A	.30	2N3643	.15	2N4142	.20	2N5457	.35
2N720A	.50	2N2102	.40	2N2906	.25	2N3645	.15	2N4143	.20	C103Y	.25
2N918	.35	2N2218	.25	2N2906A	.30	2N3646	.14	2N4220A	.45	C103D	.40
2N930	.25	2N2218A	.30	2N2907	.25	2N3730	1.50	2N4234	.95	C106B1	.50
2N956	.30	2N2219	.25	2N2907A	.30	2N3731	2.75	2N4400	.20	C106D1	.75

### SILICON UNIJUNCTIONS


2N2646	.50	2N2160	.65
2N2647	.60	2N4870	.50
2N6027	.55	2N4871	.50
2N6028	.70	2N4891	.50
D5E37	.25	2N4892	.50
		2N4893	.50
		2N4894	.50
		MU10	.40

### INTEGRATED CIRC.

UA703C	.40
709C OP. AMP.	.25
741C OP. AMP.	.25
7400	.15
TA 7061P	3.00
TA 7205P	10.00
UPC 1001h2	6.00
NE 555	1.25

### RECTIFIERS

	10	100
1N4001	.60	5.00
1N4002	.70	6.00
1N4003	.80	7.00
1N4004	.90	8.00
1N4005	1.00	9.00
1N4006	1.10	10.00
1N4007	1.20	11.00

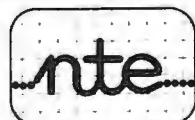

**New-Tone Electronics**

P.O. Box 1738 A

Bloomfield, N.J. 07003

Phone: (201) 748-6171, 2, 3

**ALL PARTS GUARANTEED AND TESTED ON PREMISES.**

N.J. residents add 5% sales tax. Minimum order \$5.00. All orders add \$1.00 postage. Dealers write or phone for discount prices.

CIRCLE NO. 51 ON FREE INFORMATION CARD



# SILICON GENERAL LINEAR IC's

Silicon General's complete line of linear IC's is now easily available to you from Ancrona. These original parts have been manufactured and tested by Silicon General to meet rigid industrial and military quality standards. Nearly all are directly interchangeable with National, Fairchild, T.I., RCA, Signetics and other manufacturers' devices. Of course, all of Silicon

General's proprietary devices are available, including the new SG1524/3524 Regulating Pulse Width Modulator, the IC that has made switching regulator design both practical and economical. Order these premium quality IC's by phone or mail from our Los Angeles office, or pick up the parts you need at one of Ancrona's over-the-counter sales outlets listed below.

## REGULATORS

POSITIVE ADJUSTABLE				REGULATING PULSE WIDTH MODULATORS				POSITIVE SPOT POWER				NEGATIVE SPOT POWER			
1-24	25up	100up		1-24	25up	100up		1-24	25up	100up		1-24	25up	100up	
SG100T	6.00	5.55	4.65	SG1524J	20.00	15.55	13.50	SG109T	12.50	10.00	8.00	SG120-05K	12.50	10.00	8.00
SG200T	6.00	4.80	4.00	SG2524J	16.45	12.85	10.75	SG109K	13.50	11.00	9.00	SG120-06T	1.80	1.40	1.10
SG300T	2.70	2.15	1.80	SG3524J	10.15	8.10	6.75	SG209T	10.75	8.55	7.20	SG120-08K	2.25	1.90	1.50
SG300N	2.30	1.85	1.52	★ DUAL TRACKING ★				SG209K	12.75	10.20	8.55	SG120-12K	2.25	1.90	1.50
SG105T	2.30	1.85	1.52	SG1501AT	10.15	8.10	6.75	SG309T	1.80	1.40	1.10	SG120-15K	2.25	1.90	1.50
SG205N	6.00	4.80	3.20	SG2501AT	11.65	9.30	7.75	SG309K	2.25	1.90	1.50	SG120-18K	2.25	1.90	1.50
SG305T	4.20	2.15	1.75	SG3501AT	8.65	6.90	5.75	SG123K	49.20	39.00	32.45	SG120-24K	1.80	1.40	1.10
SG305AT	1.45	1.15	.96	SG2501AJ	10.15	8.10	6.75	SG223K	25.00	19.55	16.55	SG120-25K	1.80	1.40	1.10
SG305M	2.00	1.60	1.33	SG3501AJ	5.95	4.75	3.95	SG323K	9.00	7.20	6.00	SG120-26K	1.80	1.40	1.10
SG305N	1.45	1.15	.96	SG3501AJ	7.45	5.95	4.95	SG7805T	11.50	9.75	7.50	SG120-27K	1.80	1.40	1.10
SG305M	1.20	.95	.80	SG3501AN	5.90	4.70	3.90	SG7805CT	1.80	1.40	1.10	SG120-28K	1.80	1.40	1.10
SG723T	3.15	2.55	2.10	SG1568T	6.40	5.50	4.45	SG7805K	13.00	10.50	8.50	SG120-29K	1.80	1.40	1.10
SG723J	5.25	4.15	3.48	SG1568J	6.70	5.30	4.55	SG7805CK	2.25	1.90	1.50	SG120-30K	1.80	1.40	1.10
SG723CJ	2.50	1.97	1.65	SG1468T	2.90	2.35	1.90	SG7806T	11.50	9.75	7.50	SG120-31K	1.80	1.40	1.10
SG723CT	1.25	.98	.83	SG1468N	2.90	2.35	1.90	SG7806CT	1.80	1.40	1.10	SG120-32K	1.80	1.40	1.10
SG723CN	1.08	.90	.75	SG1468J	3.50	2.90	2.35	SG7806K	13.00	10.50	8.50	SG120-33K	1.80	1.40	1.10
NEGATIVE ADJUSTABLE				SG4501T	2.95	2.35	1.95	SG7806CK	2.25	1.90	1.50	SG120-34K	1.80	1.40	1.10
SG104T	12.00	9.50	8.00	SG4501N	2.95	2.35	1.95	SG7808T	11.50	9.75	7.50	SG120-35K	1.80	1.40	1.10
SG204T	9.85	7.70	6.55	SG4501J	4.45	3.55	2.95	SG7808CT	1.80	1.40	1.10	SG120-36K	1.80	1.40	1.10
SG304T	3.25	2.58	2.15	★ ADJUSTABLE DUAL TRACKING ★				SG7808K	13.00	10.50	8.50	SG120-37K	1.80	1.40	1.10
SG1511T	4.05	3.00	2.65	SG1502J	11.65	9.30	7.75	SG7808CK	2.25	1.90	1.50	SG120-38K	1.80	1.40	1.10
SG1511J	6.50	4.95	3.90	SG2502J	10.15	8.10	6.75	SG7812T	11.50	9.75	7.50	SG120-39K	1.80	1.40	1.10
SG3511T	3.85	2.75	2.35	SG2502N	8.65	6.90	5.75	SG7812CT	1.80	1.40	1.10	SG120-40K	1.80	1.40	1.10
SG3511J	5.95	4.00	3.40	SG3502J	7.45	5.95	4.95	SG7812K	13.00	10.50	8.50	SG120-41K	1.80	1.40	1.10
								SG7812CK	2.25	1.90	1.50	SG120-42K	1.80	1.40	1.10

## OP AMPLIFIERS

GENERAL PURPOSE COMPENSATED				GENERAL PURPOSE UNCOMPENSATED				HIGH PERFORMANCE				MICROPOWER PROGRAMMABLE			
1-24	25up	100up		1-24	25up	100up		1-24	25up	100up		1-24	25up	100up	
SG107T	6.00	4.75	4.05	SG101AT	5.00	3.95	3.35	SG747J	7.70	6.10	5.10	SG308AM	5.00	3.95	3.35
SG107J	12.00	9.95	8.35	SG201AT	8.25	6.55	5.50	SG747CJ	4.00	3.20	2.65	SG4250CT	12.00	10.50	8.75
SG207T	4.50	3.60	3.00	SG201AJ	3.50	2.78	2.32	SG747CN	2.40	1.90	1.60	SG4250CM	4.50	3.60	3.00
SG207J	7.20	5.75	4.80	SG201AN	1.95	1.55	1.30	SG747CT	3.00	2.35	2.00	VOLTAGE FOLLOWERS			
SG207M	3.50	2.78	2.15	SG201AM	2.25	1.78	1.52	SG1458T	1.95	1.55	1.30	SG110T	7.50	6.00	5.00
SG207N	3.00	2.38	2.00	SG301AT	.95	.78	.65	SG1458M	1.72	1.35	1.15	SG110J	19.10	15.30	12.75
SG307T	.90	.72	.60	SG301AJ	1.25	.98	.83	SG1558T	5.50	4.40	3.65	SG210T	6.85	5.45	4.55
SG307J	1.80	1.43	1.20	SG301AN	.95	.78	.65	SG108T	9.85	7.80	6.55	SG210J	15.75	12.60	10.50
SG307M	.80	.64	.53	SG301AM	.90	.72	.60	SG108J	12.60	10.20	8.55	SG310T	4.00	3.20	2.65
SG307N	.90	.72	.60	SG748T	2.50	1.95	1.70	SG108AJ	16.40	12.58	10.65	SG310J	5.50	4.40	3.68
SG1436T	4.65	3.75	3.40	SG748C	.90	.72	.60	SG208T	8.50	6.80	5.70	SG310M	2.00	1.56	1.34
SG1436CT	2.60	2.50	1.85	SG748CN	.95	.75	.63	SG208J	10.60	8.40	7.05	★ HIGH SLEW RATE ★			
SG1456T	3.40	2.70	2.20	SG748CT	.97	.78	.65	SG208AJ	11.75	9.40	7.85	SG741ST	5.05	4.00	3.35
SG1456CT	2.85	2.35	1.90	DUAL COMPENSATED				SG308T	1.50	1.20	1.00	SG741SCT	2.00	1.60	1.38
SG1536T	27.00	22.50	18.00	SG747T	5.70	4.50	3.80	SG308AJ	6.00	4.80	4.00	SG741SCM	1.80	1.50	1.20
SG1556T	12.25	11.00	10.15					SG3250T	12.00	9.50	8.00	QUAD			

## INTERFACE IC's

SENSE AMPS				QUAD COMPARATORS				DUAL PERIPHERAL DRIVERS				MEMORY DRIVERS			
1-24	25up	100up		1-24	25up	100up		1-24	25up	100up		1-24	25up	100up	
SG7520J	2.50	2.10	1.80	SG211T	6.35	5.05	4.20	SG55450BJ	2.95	2.30	2.00	SG75461T	1.60	1.40	1.20
SG7520N	2.05	1.75	1.58	SG211J	12.55	10.20	8.50	SG75450BJ	1.40	1.25	.95	SG75461M	1.40	1.25	1.05
SG7521J	2.00	1.67	1.44	SG211M	5.50	4.50	3.65	SG75450BN	1.20	1.05	.95	SG75462T	2.85	2.15	1.90
SG7521N	1.60	1.34	1.16	SG311T	2.50	1.98	1.68	SG75451BT	2.95	2.30	2.00	SG75462M	1.40	1.25	1.05
SG7522J	2.50	2.10	1.80	SG311M	5.50	4.40	3.65	SG75451BT	1.40	1.25	1.05	SG75463T	2.85	2.15	1.90
SG7522N	2.05	1.75	1.58	SG139J	10.50	8.40	7.00	SG75451BM	1.20	1.05	.95	SG75463M	1.40	1.25	1.05
SG7523J	2.00	1.67	1.44	SG239AJ	18.40	14.80	12.15	SG75452BT	1.40	1.25	1.05	SG75464T	2.85	2.15	1.90
SG7523N	1.60	1.34	1.16	SG239J	8.40	6.65	5.60	SG75452BM	1.20	1.05	.95	SG75464M	1.40	1.25	1.05
SG7524J	2.50	2.10	1.80	SG239AJ	14.80	11.60	9.90	SG75453BT	2.95	2.30	2.00	BUS TRANSCEIVER			
SG7524N	2.05	1.75	1.58	SG239AN	6.50	5.15	4.32	SG75453BT	1.40	1.25	1.05	SG75532J	7.80	6.20	5.25
SG7525J	2.00	1.67	1.44	SG239AN	11.00	8.70	7.30	SG75453BM	1.20	1.05	.95	SG75532M	6.65	5.25	4.40
SG7525N	1.60	1.34	1.16	SG339J	2.50	1.98	1.67	SG75460J	2.85	2.15	1.90	SG75532J	6.65	5.25	4.40
SG7526J	2.50	2.10	1.80	SG339M	2.25	1.78	1.50	SG75460J	1.60	1.40	1.20	TIMERS			
SG7526N	2.05	1.75	1.58	SG339AJ	5.00	3.95	3.35	SG75460N	1.20	1.05	.95	SG555T	13.00	10.48	8.70
SG7529J	2.00	1.67	1.44	SG339AN	4.50	3.55	3.00	SG55461T	2.85	2.15	1.90	SG555Y	15.00	12.00	10.00

## TRANSISTOR ARRAYS

1-24	25up	100up	
SG3045J	4.50	3.65	3.00
SG3046N	1.30	1.05	.86
SG3146J	4.60	3.65	3.05
SG3146N	1.60	1.25	1.05
SG3821N	1.80	1.40	1.20
SG3821J	2.70	2.15	1.80
SG3822T	1.80	1.30	1.00
SG3822N	1.60	1.30	1.00
SG3822J	2.70	2.15	1.80
SG3823N	1.75	1.40	1.20

## OTHER LINEARS

WIDEBAND AMPLIFIERS				MULTIPLIERS				MODULATORS			
1-24	25up	100up		1-24	25up	100up		1-24	25up	100up	
SG733T	7.45	5.95	4.95	SG1595J	8.20	7.00	6.15	SG1496J	1.60	1.25	1.05
SG733J	8.25	6.60	5.50	SG1495J	5.05	3.45	2.55	SG1496T	1.60	1.25	1.05
SG733CJ	2.20	1.75	1.45	SG1495N	2.25	1.90	1.55				
SG733CN	2.00	1.60	1.35								
SG733CT	2.10	1.70	1.40								
SG1401T	4.00	3.20	2.65								
SG1401J	4.45	3.60	3.00								
SG2401T	3.25	2.60	2.15								

Send \$1.00 for Short Form Catalog

Package Designation

D - (Same as J Pkg.)  
M - Mini-Dip

J - Ceramic Dual-in-line  
N - Molded Dual-in-line Pkg.

K - TO-3 Power Pkg.  
T - TO-5 (Multilead)

F - Flat Pk.  
Y - Mini-Ceramic Dip

**Order your Silicon General linear IC's by phone or mail from Ancrona**

**or visit our Ancrona Stores**

**AUTHORIZED DISTRIBUTOR**  
**ANCRONA CORP.**

Prices effective through November 30, 1976.  
Minimum order \$10.00. Add \$1.00 to cover postage and handling.

NOVEMBER 1976

## ADVERTISERS INDEX

READER SERVICE No.	ADVERTISER	PAGE NUMBER
1	A P Products Incorporated	111
2	A V R Electronics	104
3	Ace Electronics Parts	128
31	Acoustic Fiber Sound Systems, Inc.	11
6	Adva Electronics	120
6	Advanced Microcomputer Products	124
7	Altaj Electronics	123
8	Ancrona Corp.	132
80	Ancrona Corp.	120
9	Aries, Inc.	133
10	Associated Electronics	91
11	Avanti Research & Development, Inc.	105
15	B & K Precision products of Dynascan	10
12	Boman Industries	39
13	Browning Laboratories, Inc.	109
16	Bullet Electronics	125
	Burstein-Applebee	109
	CREI Capitol Radio Engineering Institute	60, 61, 62, 63
	Circuit Design, Inc.	108
	Cleveland Institute of Electronics	70, 71, 72, 73
14	Cobra Product of Dynascan	SECOND COVER
17	Continental Specialties Corporation	7
18	Continental Specialties Corporation	88
19	Crown	16
20	Delta Electronics Co.	114
21	Delta Products, Inc.	95
22	Digi-Key Corporation	122
	Dixie Hi-Fidelity Wholesalers	104
23	EICO	85
24	Edlie Electronics, Inc.	128
25	Edmund Scientific Co.	116
26	Edmund Scientific Co.	134
27	Electronic Book Club	8
28	Electronic Distributors, Inc.	114
29	Eltron	121
30	Empire Scientific Corp.	6
32	47th Street Photo	111
34	Fluke	77
35	Godbout Electronics, Bill	131
36	Grantham School of Engineering	102
37	Greenlee Tool Co.	91
38	Hal Communications Corp.	88
39	Handic USA Inc.	76
5	Heath Company	98, 99, 100, 101
40	Hobb-y-tronix	130
41	Hufco	30
	IMS Associates, Inc.	1, 121
42	Illinois Audio	109
43	International Electronics Unlimited	125
44	JS&A National Sales Group	5
45	James	113
46	James	126, 127
33	Johnson Co., E. F.	2
47	Lafayette Radio Electronics	9
48	McIntosh Laboratory, Inc.	30
49	MTS	26, 27
	NRI Schools	12, 13, 14, 15
50	National Camera Supply	103
	National Technical Schools	80, 81, 82, 83
51	New-Tone Electronics	131
52	Non-Linear Systems	103
81	OK Machine & Tool Corporation	38
53	Olson Electronics	129
54	Optoelectronics, Inc.	112
55	PAIA Electronics	107
56	Pickering & Co.	THIRD COVER
57	Poly Paks	119
58	Poly Paks	121
59	PolyMorphic Systems	107
60	Prentice Hall	31
	Processor Technology Co.	108
61	Quest Electronics	114
	Radio Shack	40
62	SAE	69
63	SBE, Inc.	33
64	S.D. Sales Co.	115
65	Sansui Electronics Corp.	29
66	Schober Organ Corp., The	107
67	Senore	96, 97
	Solid State Sales	130
69	Southwest Technical Products Corporation	17
70	Stereo Corp. of America	111
71	Technics by Panasonic	19
72	Telex Communications, Inc.	93
73	U. S. Pioneer Electronics	50, 51
74	Ungar	46
4	United Audio Products, Inc.	FOURTH COVER
75	Vernitron Corporation	20
76	Wawasee Electronics	92
77	Weatheralert	18
78	Yamaha International Corporation	21
CLASSIFIED ADVERTISING		
112, 114, 120, 122, 124, 125, 128, 133		

## HOME ENTERTAINMENT FILMS

START A NEW HOBBY... COLLECT SUPER 8 MAGNETIC SOUND FILMS. Runs the gamut from "Where Jesus Walked" (Biblical Judea and Galilee) to "Bye-Bye Birdie" with Ann-Margaret and Dick Van Dyck; "Queen Boxer" (Judy Lee—Karate) — each 400' Super 8 Color Magnetic Sound — only \$46.95 PPD (limited offer — you save \$3.75 each). "Member of the Wedding" (Ethel Waters); "Christmas Carol" (Alistair Sims); "Dirigible" (A Frank Capra Feature) — each 400' B&W Magnetic Sound Film, \$36.95 (save \$3.75 each). Or, make selection from Columbia Pictures or Castle catalogs, \$0.50 each; or Sportlite order form, \$0.25 (coins, stamps, no checks, pls). SPORT-LITE, Elect-11, Box 24-500, Speedway, IN 46224.

## INVENTIONS WANTED

INVENTORS: Manufacturers Need New Products. Free "Recommended Procedure," by a creative fee-based invention service company. Washington Inventors Service, 422-T Washington Building, Washington, D. C. 20005.

## INVENTORS

### RECOGNITION...FINANCIAL REWARD...OR CREDIT FOR "INVENTING IT FIRST" MAY BE YOURS!

If you have an idea for a new product, or a way to make an old product better, contact us, "the idea people." We'll develop your idea, introduce it to industry, negotiate for cash sale or royalty licensing. Write now without cost or obligation for free information. Fees are charged only for contracted services. So send for your FREE "Inventor's Kit." It has important Marketing Information, a special "Invention Record Form" and a Directory of 500 Corporations Seeking New Products.

**RAYMOND LEE ORGANIZATION**  
230 Park Avenue North, New York, NY 10017  
At no cost or obligation, please rush my FREE "Inventor's Kit No. A-112".

Name  Please Print

Address

City  State  Zip

## RUBBER STAMPS

RUBBER ADDRESS STAMPS. Free Catalog. 45 type styles. Jackson's, Dept. K, Brownsville Rd., Mt. Vernon, Ill. 62864.

## DO-IT-YOURSELF

MODULAR TELEPHONES now available. Sets and components, compatible with Western Electric concept. Catalog 50 cents. Box 1654W, Costa Mesa, California 92626.

## HYPNOTISM

SLEEP learning. Hypnotic method. 92% effective. Details free. ASR Foundation, Box 23429EG, Fort Lauderdale, Florida 33307.

FREE Hypnotism. Self-Hypnosis. Sleep Learning Catalog! Drawer H400, Ruidoso, New Mexico 88345.

AMAZING self-hypnosis record releases fantastic mental power. Instant results! Free trial. Write: Forum (AA11), 333 North Michigan, Chicago 60601.

## MISCELLANEOUS

WINEMAKERS: Free illustrated catalog yeasts, equipment. Semplex, Box 12276P, Minneapolis, Minn. 55412.

## FREE! CONSUMER SERVICE DIVISION CATALOG

Includes a wide variety of products associated with the special interests of readers of Ziff-Davis magazines—Psychology Today, Popular Photography, Stereo Review, Popular Electronics, Boating, Flying, Car and Driver, Cycle, Skiing.

Send for your free catalog today.  
Consumer Service Div., 595 Broadway, N.Y. N.Y. 10012

ARIES brought you the first calculator kit, and the first digital clock kit... and now brings you three of the most innovative electronic kits ever made. The System 300 Electronic Music Synthesizer kit is the most advanced in the world today, regardless of price. The AR-781 is a space-age beauty for any decor. And the wholly solid state AR-830 does the work of a \$400.00 tape memory unit.




WARNING... if you're interested in a music synthesizer, don't make a move until you see our catalog first. It's more like a handbook than a catalog, with hundreds of in-depth photographs and descriptions to explain electronic music principles, and to show equipment to do the job. ARIES now offers a complete complement of modules, keyboards, and cases, matched to the most rigorous professional standards. Starter systems priced as low as \$395.00.

A clear, ruby-red cylinder shows off all six digits of this modern calendar clock. Easy-to-read numbers show the hours, minutes, and seconds, as well as the month and day every ten seconds. Red LED 7-segment numerals are 0.33" high, in a sturdy cylinder 2-1/2" in diameter and 4-3/4" long, with finished hardwood ends. Time and calendar are controlled by 60 Hz line frequency, with a 12-month movement. Separate time and calendar adjustments. Includes all the components, PC boards, housing, and instructions. Shipping weight 2 lbs. AR-781 Clock Kit ..... \$34.50



Add finger-touch operation to your old-fashioned dial telephone with an ARIES AR-830 Automatic Digital Telephone Dialer. This has the same layout and convenience as Ma Bell, plus other features she doesn't offer yet. For instance... AR-830 always remembers the last number you dialed, in case the line was busy and you want to try again later. Not only that, but the Dialer's memory can store as many as ten of your favorite numbers for one-touch dialing. AR-830 uses standard dialing and muting contacts; consult local tariffs before connecting. Sh. wt. 2 lbs. AR-830 Dialer Kit ..... \$69.50

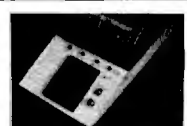

## ARIES INC.

119 Foster Street  
Peabody, Mass., 01960  
(617) 532-0450

CIRCLE NO. 9 ON FREE INFORMATION CARD

POPULAR ELECTRONICS INDEX for 1975 now available. Prepared in cooperation with the Editors of "P/E," this index contains hundreds of references to product tests, construction projects, circuit tips and theory and is an essential companion to your magazine collection.

1975 Edition, \$1.50 per copy. 1972, 73, and 74 editions also still available at \$1.50 each, or \$5.50 for the set of four (1972, thru 1975). Add \$.25 per order for postage and handling.

INDEX, Box 2228, Falls Church, Va., 22042

## Popular Electronics

ANNUAL INDEX  
..... 1975



# LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

## A BETTER LIFE STARTS HERE

### WORLD'S SMALLEST RECHARGEABLE CALCULATOR!

Small but mighty! 8-digit, 4-function electronic calculator does everything big ones do—even has automatic % key... for only \$19.95. Take it anywhere. Fits in your pocket— $\frac{1}{2}$  size of cigarette pack.  $\frac{3}{4}$  oz. dynamo features floating decimal, constant key, lead zero depression, more! Includes plug-in rechargeable Ni-Cad battery pack.  $2 \times 3\frac{1}{2} \times \frac{9}{16}$ " with plenty of room for most fingers. Another Edmund first with advanced technology.

Stock No. 1945AV .....\$19.95 Ppd.



### SAVE 50%! 8 X 20 MONOCULAR

Fantastic bargain! Top quality Spy Scope, a \$30 value, now offered at \$14.95! Our special purchase saves you 50% and you get 100% coated optics; 393 ft. field of view. Only 2 oz.—stores in pocket, purse, glove compartment. Fits in your palm—peer into hard-to-see places without letting subject know you're spying. Great for birders and race fans; incl. neck strap, leatherette  $3\frac{1}{2} \times 1\frac{1}{2} \times 2$ " case. Beautiful brushed metal finish. Buy two—one for a gift!



### KNOW YOUR ALPHA FROM THETA!

For greater relaxation, concentration, monitor your Alpha/Theta brainwaves w. audible or visible signal on Biosone II. Has 3 feedback modes, outputs to monitor logic signal, filter sel. feedback, broad sensitivity control; other professional feats. of \$200-up units. Easily operated 4-lb. portable has total brainwave monitoring capability! 2 9v tr. batteries.

No. 1668 ( $9\frac{1}{2} \times 5\frac{1}{2} \times 4\frac{1}{4}$ ") .....\$149.95 Ppd.

LOW COST STARTERS' UNIT (PORTABLE)

No. 71,809 AV ( $4\frac{1}{2} \times 2\frac{3}{4} \times 4\frac{1}{4}$ ") .....\$55.00 Ppd.



### FUEL MISER RECLAIMS HEAT

Save your 40% wasted heat to warm a basement, garage or rec room at no extra cost! Instead of going "up the chimney" it goes where you want it. Remove part of furnace exhaust pipe, slip Heat Exchanger in. At 125 fan automat. forces clean air through unit which heats to over 200°F., can be ducted to 20 ft. from unit. 110v AC. Inst.

No. 19, 194AV (5/8" DIA.) Shpg. 17 lb. ....\$121.00 FOB

No. 19, 195AV (6" DIA.) Shpg. 17 lb. ....\$121.00 FOB

No. 19, 198AV (7" DIA.) Shpg. 17 lb. ....\$121.00 FOB



GREAT FOR CHRISTMAS GIFTS!  
A UNIQUE SELECTION OF MEMORABLE,  
LONG-LASTING GIFTS FOR ALL AGES.

### NEW! THE UNIQUE EDMUND



### 4 1/4" NEWTONIAN RICHEST FIELD REFLECTOR TELESCOPE

Clearer, brightest, most spectacular wide angle views of moon, stars, comets, galaxies ever — and portable! See heavenly wonders! Sets up in seconds (precollimated, ready to use). Pop the eyepiece in, focus — and zing!  $3\frac{1}{2}$ " field of view gives you more stars in a single view than any other type scope! Bright, crisp, finely resolved images. For sky gazing and earth gazing! Take it anywhere (only 17", 10 lb.), easily use it over your shoulder, (has adjustable carrying strap), in your lap, on a tripod; rotate the spherical base on its own mount for use on a table, car hood. Top quality optical system features  $4\frac{1}{4}$ " f/4 parabolic primary mirror ( $\frac{1}{8}$  wave, 17" F.L.); std. 28mm Kellner eyepiece (15X). No other telescope like it. Great Christmas gift — it's even bright red!

No. 2001AV .....\$129.95 Ppd.  
Spec. Introductory Price! Goes to \$149.95 Dec. 25, 1976



### WORLD'S SMALLEST HI-FI ( $6\frac{5}{8} \times 4\frac{1}{2} \times 6"$ )

Now, the gorgeous sound of true hi-fi w/ a receiver & sep. 8-ohm speaker ( $6\frac{5}{8} \times 11 \times 6"$ ) small enough, and priced low enough, to go in your bedroom, den, kitchen, office, shop! Great for doctors, dentists. Its wide-range rich sound compares favorably to any stereo at its price, but it's not—it's a monophonic FM radio into which you can plug a cassette, etc. (record, play back!) Hi-fi system has Baxandall type controls (ab. 12 dB boost or cut @ 100 Hz & 10 KHz). Beautiful!

No. 72,262AV ... (120V AC) .....\$127.50 Ppd.



### 18 HOURS' WEATHER AT A GLANCE

Glance at our Weather Wizard and know what to expect for the next 8-18 hrs. Be up to 80-85% accurate (better than most pro's)! Based on wind—no charts, dials—no computations! Program WW for your location once, then forecasting is automatic. Roofmounted windvane sends pulses to indoor control unit programmed w/75 yrs. data; interprets on 3 panel lights (Unsettled; Fair; Change). Who needs TV! Incl. vane, support, 60 ft. of cable,  $5 \times 4\frac{1}{2} \times 3\frac{1}{2}$ " control unit, instruc.

No. 72,200AV (110V, 60 CYCLES) .....\$99.95 Ppd.



### HANDY VERSATILE METAL DETECTOR

Not only ideal for searching out treasure, metal or mineral (its pitch tells you which), this hand-held (8 oz.; 12 1/4" long) high quality 2 oscillator BFO unit is great on security searches! And a real bloodhound at locating hidden pipes, other metal at home or work. Self-contained! 6" oval search coil and compact size let you get where ordinary detectors won't; has extension handle. It may make you rich, can save lives (concealed weapons, letter bombs) and work!

No. 72,255AV (9V BATT. NOT INCL) .....\$39.95 Ppd.



### MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN 4500 UNUSUAL BARGAINS

Completely new 1977 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.  
300 Edscorp Building, Barrington, N.J. 08007  
Please rush Free Giant Catalog "AV"

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_



### COMPLETE & MAIL WITH CHECK OR M.O.

EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

☐ PLEASE SEND GIANT FREE CATALOG "AV"

Charge my ☐ American Exp. ☐ BankAmericard ☐ Master Chg.

Interbank No. \_\_\_\_\_

My Card No. Is \_\_\_\_\_

Card Expiration Date \_\_\_\_\_

30-DAY MONEY-BACK GUARANTEE.  
You must be satisfied or return any purchase in 30 days for full refund.

How Many Stock No. \_\_\_\_\_

Description (609) 547-3480 Price Each Total

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

# What's rare earth doing in Pickering's new OA-7's? Making the greatest sound in the slenderest headphones...That's What!



An important technological advance makes possible a headphone with superb listening characteristics and a particularly high degree of comfort.

The innovation is the use of rare earth elements in the compound of the permanent magnet of each earpiece...besides having superior magnetic properties, these magnets are also of much smaller size (and lighter weight), while still achieving an improved response over conventional permanent magnets.

The foam cushioned headband is exceptionally comfortable, and the earpiece yokes incorporate a unique pivoting system that enables the earpiece to fit snugly against the ear.

This is Open Audio headphone design and engineering at its best!



*"for those who can hear the difference"*

For further information write to: Pickering & Co., Inc., Dept. PE, 101 Sunnyside Blvd., Plainview, N.Y. 11803

CIRCLE NO. 56 ON FREE INFORMATION CARD



The new Dual CS721 is the ultimate expression of the principles that determine the performance of tonearms and drive systems. Its straight-line, tubular tonearm pivots horizontally and vertically within a true, four-point gimbal, thus maintaining dynamic balance in all planes.

Another Dual innovation—Vertical Tonearm Control—contributes in yet another way to fine tracking performance. A vernier height adjustment over

# The new Dual CS721 represents everything Dual has learned about turntables.

an 8mm range parallels the tonearm to the record with any cartridge. This eliminates the added mass

of cartridge spacers otherwise needed to achieve precise vertical tracking angle. In all,

there are seven tonearm settings and adjustments — from stylus overhang to cueing height and descent speed — all serving to optimize tracking performance with any cartridge.

The direct-drive system of the CS721 is of comparable precision. The electronically-controlled, DC, brushless motor is the smoothest and quietest ever made. A major contribution to this end result is an exclusive Dual feature: two stacked coil layers, each consisting of eight coreless bifilar-wound coils, that overlap to achieve a gapless rotating magnetic field. This eliminates the successive magnetic pulses typical of all other motor designs.

Although the CS721 is Dual's most expensive model, it is hardly the most expensive turntable available today. When you make comparisons, as we believe you should, you may well consider the CS721 considerably underpriced.

**Dual**


**United Audio Products**

120 So. Columbus Ave., Mt. Vernon, N.Y. 10553  
Exclusive U.S. Distribution Agency for Dual

Straight-line tubular tonearm provides maximum torsional rigidity and lowest effective mass. With the same effective tonearm length and tangential tracking error, any other shape must either sacrifice rigidity or increase mass.

**The Dual CS721.** Single-play direct-drive turntable with fully automatic start and stop, plus continuous repeat. Features include: 10% electronic pitch control, illuminated strobe, dynamically-balanced 12" platter, anti-skating separately calibrated for conical, elliptical and "long-contact" styli. Less than \$400, including base and cover.

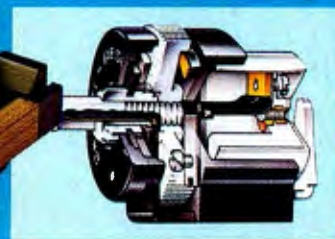**Dual CS704.** Similar, except semi-automatic. Mechanical sensor locates lead-in groove of 12" and 7" records; tonearm lifts and motor shuts off at end of play. Less than \$310, including base and cover.



Counterbalance contains two mechanical filters, tuned to absorb energy in resonance-frequency ranges of tonearm/cartridge system and chassis to avoid feedback.

Other Dual turntables: Fully automatic, single-play/multi-play: 1225, less than \$140; 1226, less than \$170; 1228, less than \$200; 1249, less than \$280. Semi-automatic, single-play Duals: 502, less than \$160; 510, less than \$200.